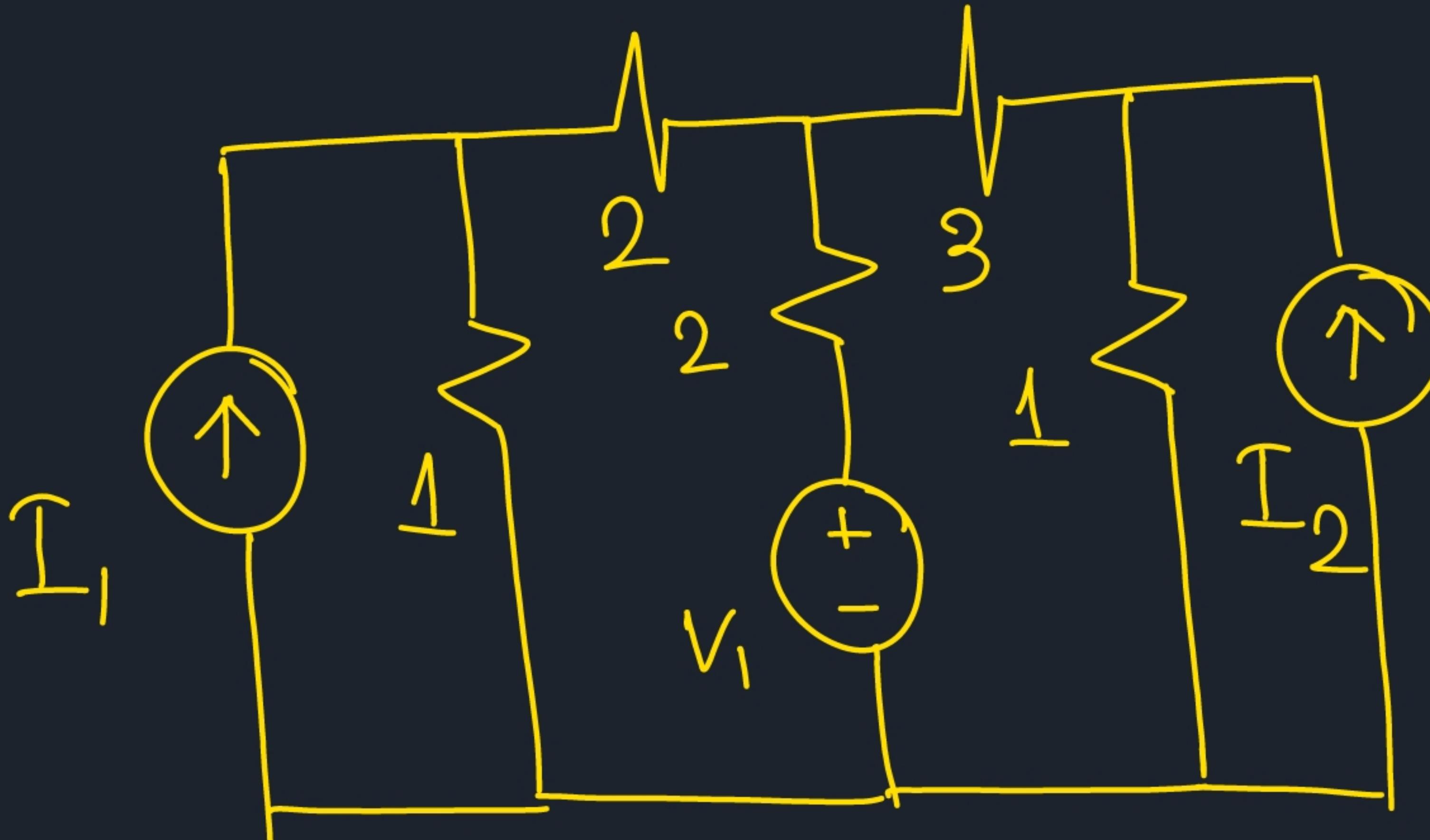




SUPERPOSITION :-



$$\begin{bmatrix} 5 & -2 \\ -2 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} I_1 - V_1 \\ -I_2 + V_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & -1 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5 & -2 \\ -2 & 6 \end{bmatrix}^{-1} \begin{bmatrix} 1 & 0 & -1 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \frac{3}{13} & -\frac{1}{13} & -\frac{2}{13} \\ \frac{1}{13} & -\frac{5}{26} & \frac{3}{26} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \end{bmatrix}$$


$$i_1 = \left(\frac{3}{13}\right) I_1 - \left(\frac{1}{13}\right) I_2 - \left(\frac{2}{13}\right) V_1$$

$$i_2 = \left(\frac{1}{13}\right) I_1 - \left(\frac{5}{26}\right) I_2 + \left(\frac{3}{26}\right) V_1$$

$$\begin{aligned} I_{2\Omega} &= i_1 - i_2 \\ &= \left(\frac{2}{13}\right) I_1 + \left(\frac{3}{26}\right) I_2 \\ &\quad - \left(\frac{7}{26}\right) V_1 \end{aligned}$$


$$= I_{2\Omega}' + I_{2\Omega}'' + I_{2\Omega}'''$$

 Problem:-

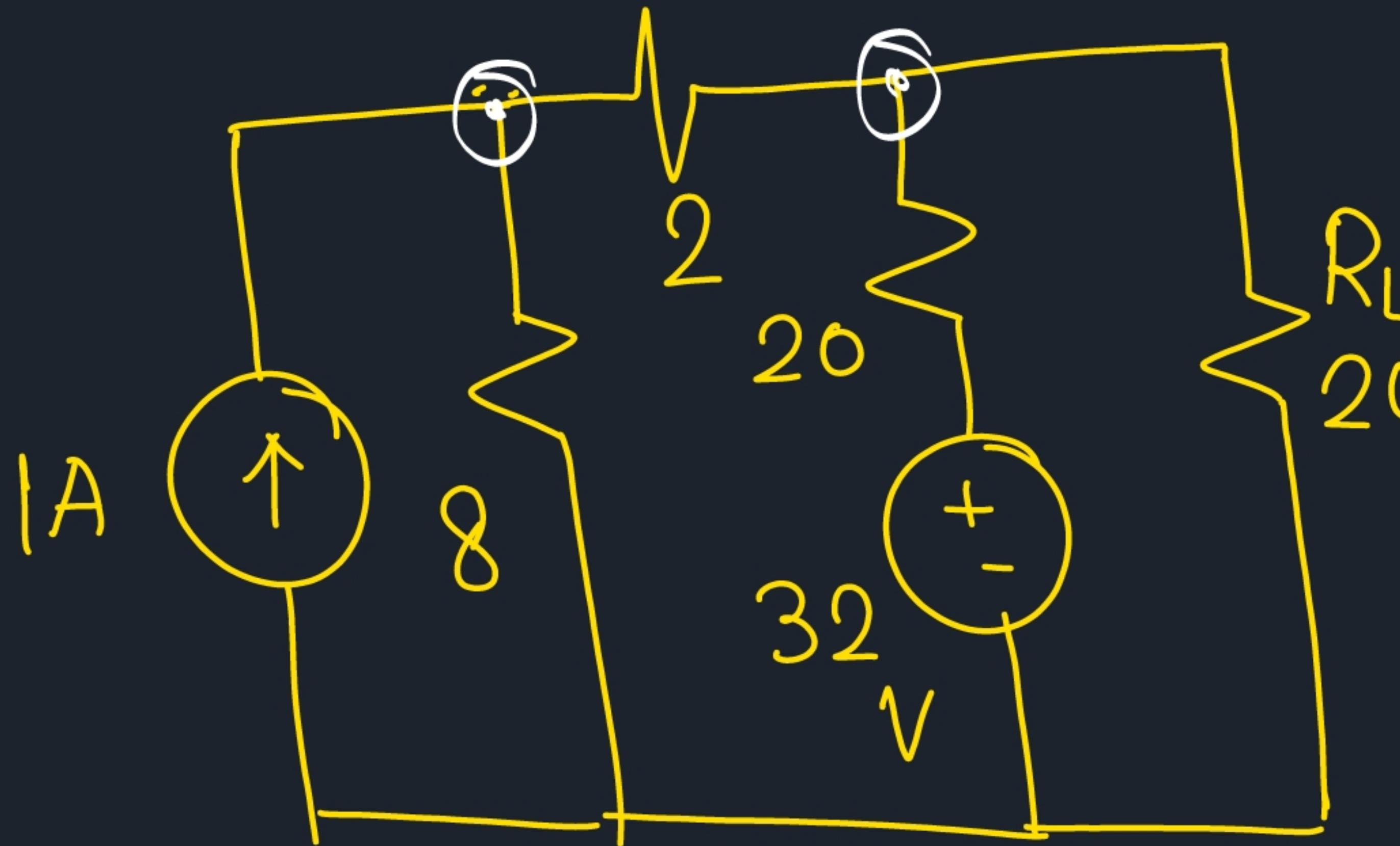


$$I_L' = \left(1 \times \frac{8}{8+12} \right) \times \frac{1}{2}$$

$$I_L'' = \left(\frac{32}{20+10||20} \right) \times \frac{10}{10+20}$$

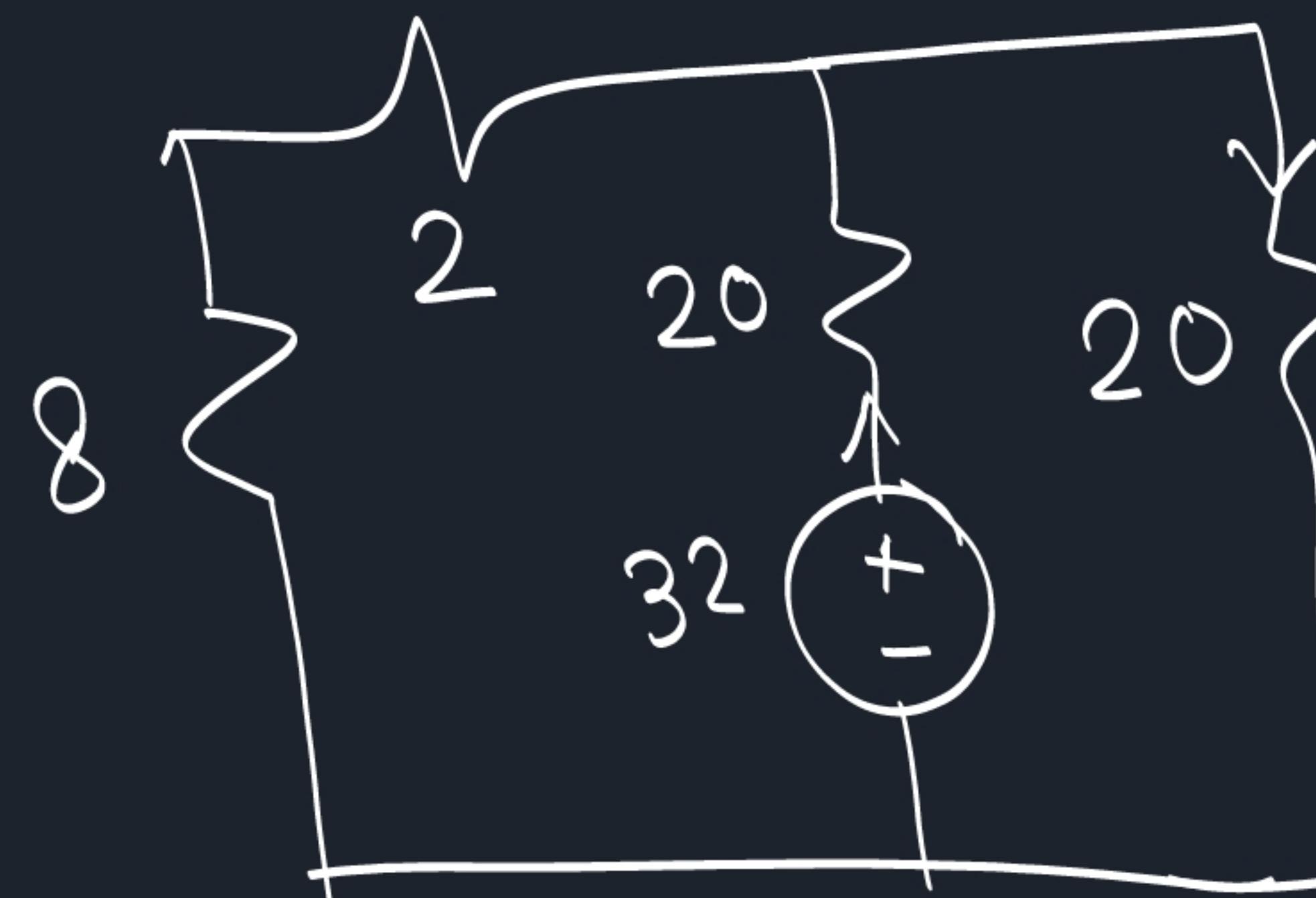


$$I_L = I_L' + I_L''$$

$$= 0.6 \text{ Amps.}$$

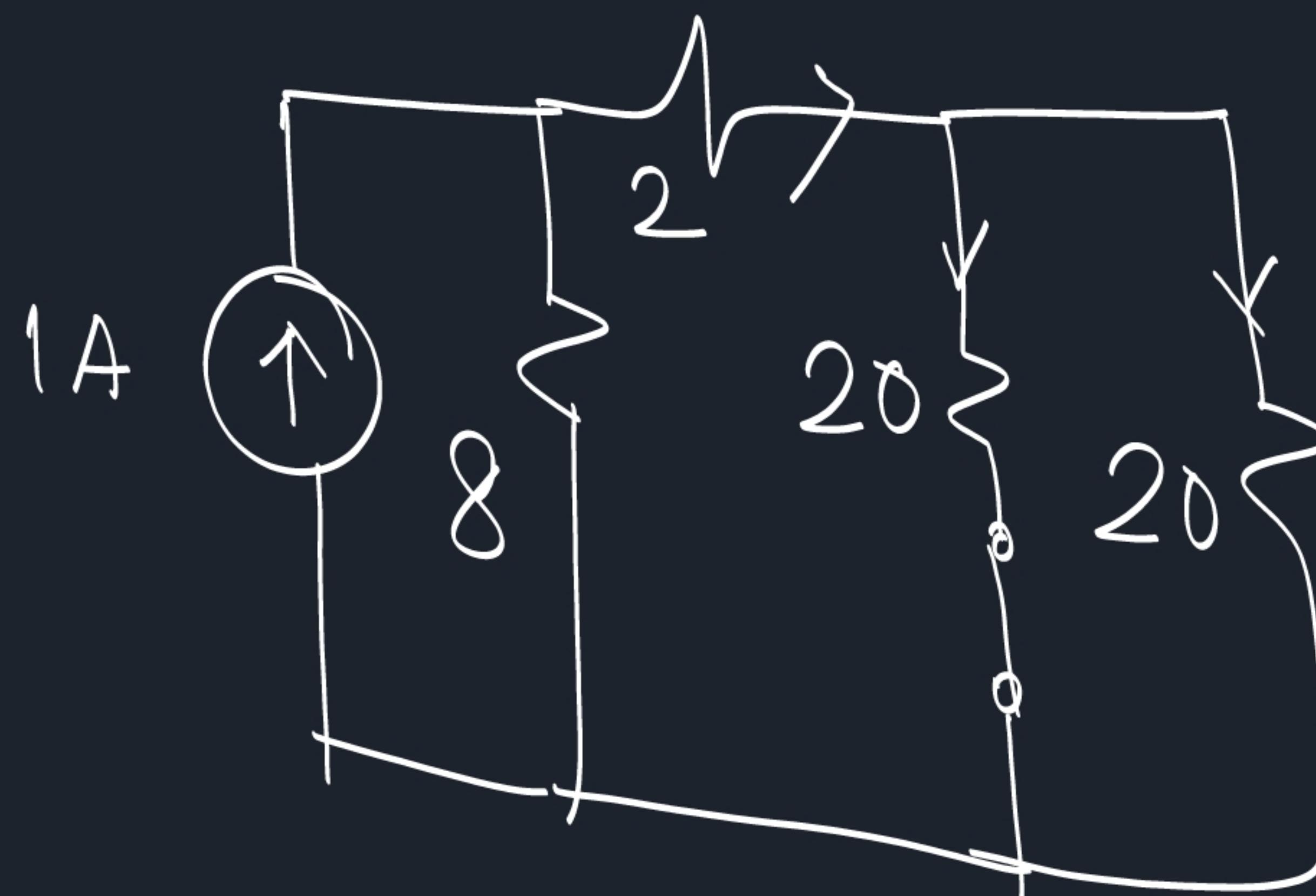

Problem:-



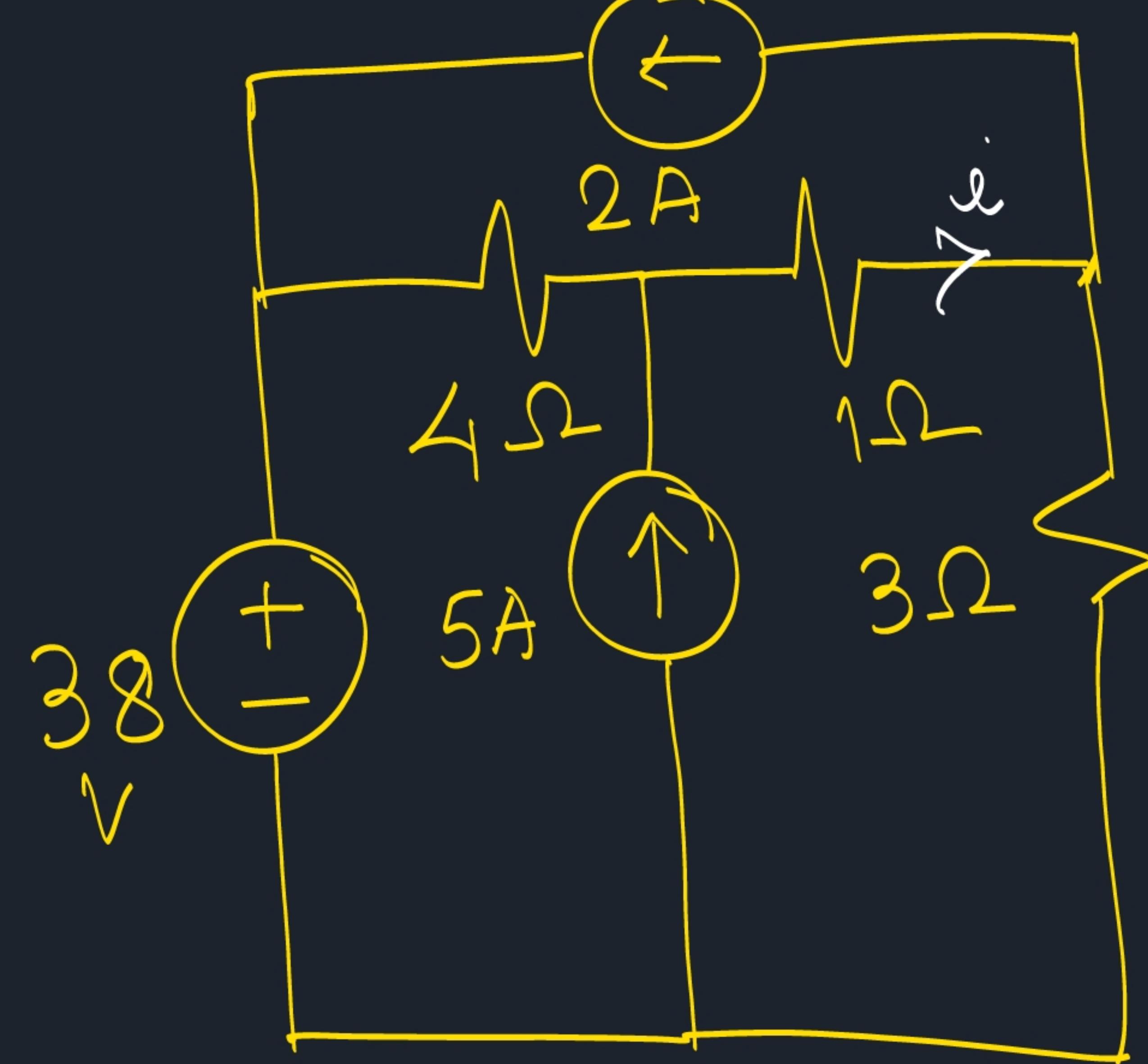


find i using
Superposition.


$$i_1 = \frac{38}{8} A$$

$$i_2 = 5 \times \frac{4}{8} = \frac{20}{8} A$$
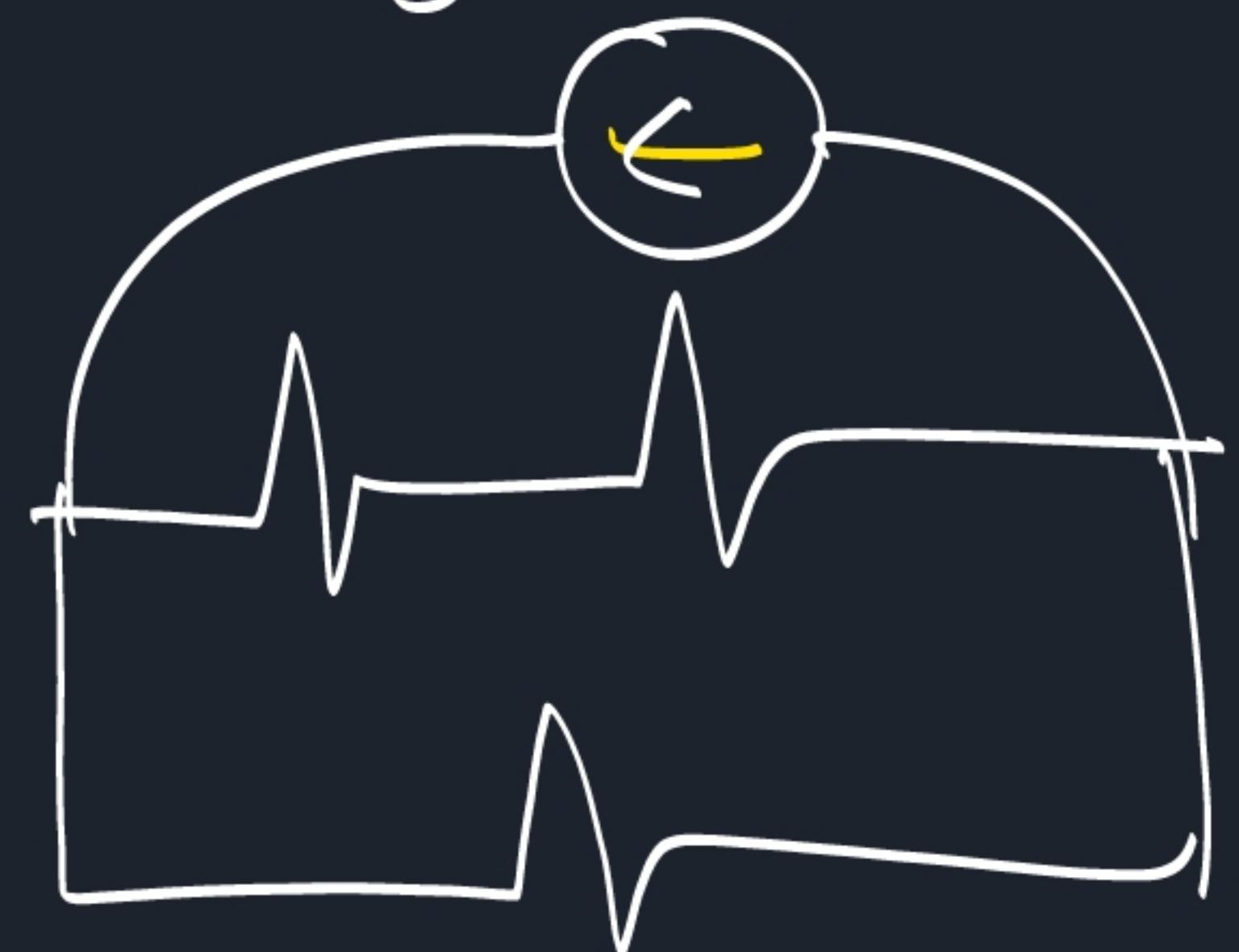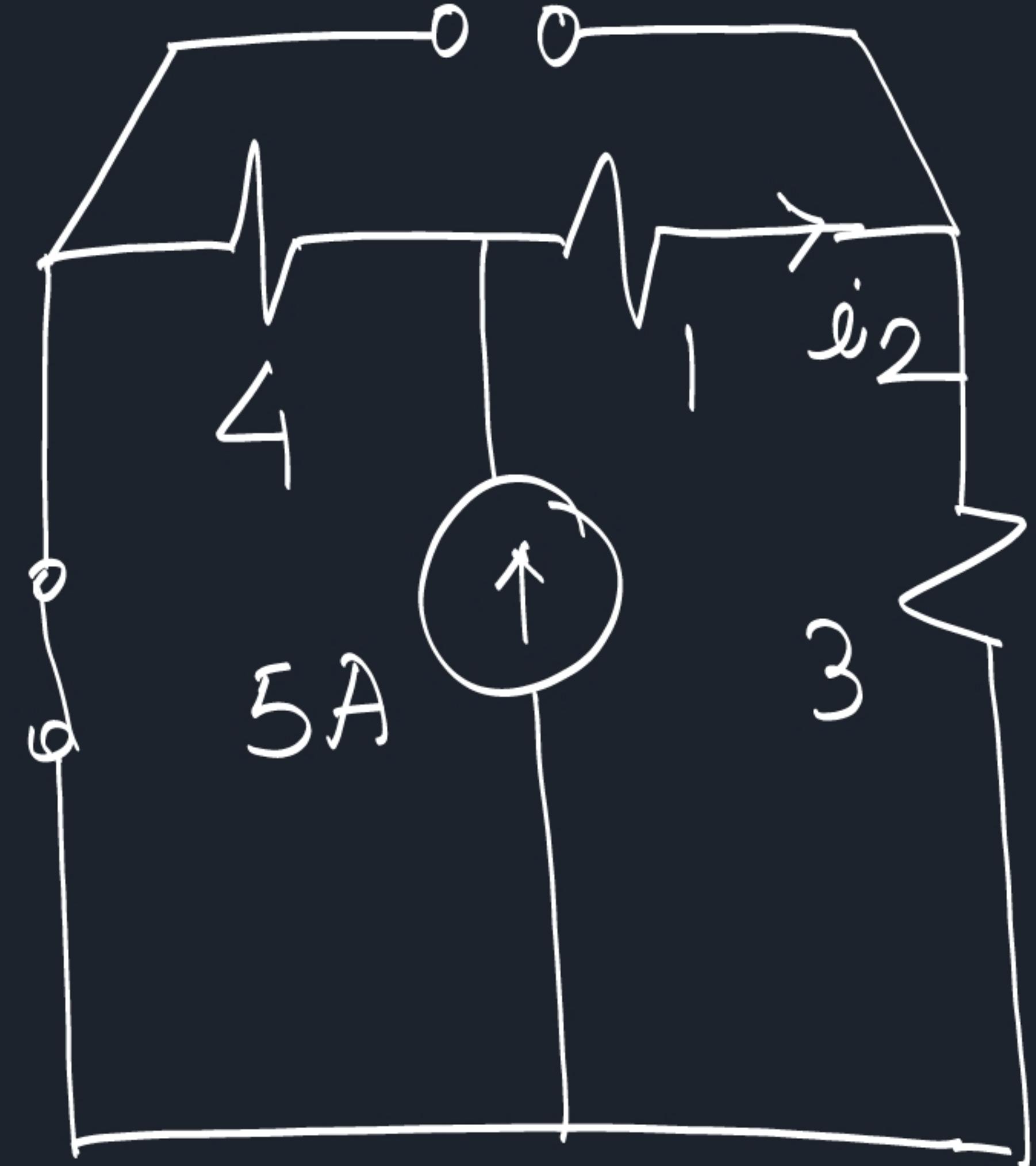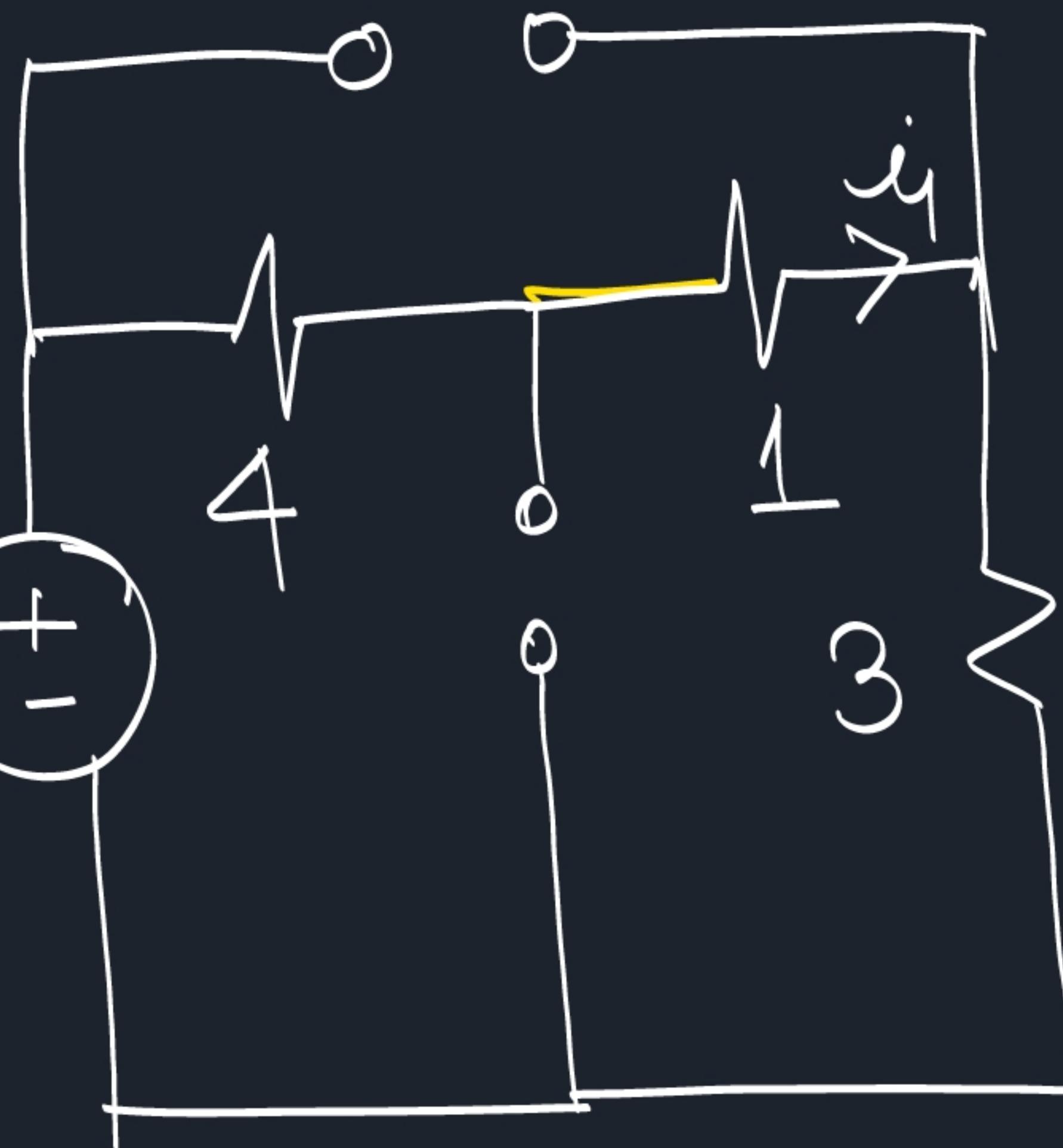
$$i_3 = 2 \times \frac{3}{8} = \frac{6}{8}$$



 Problem:-

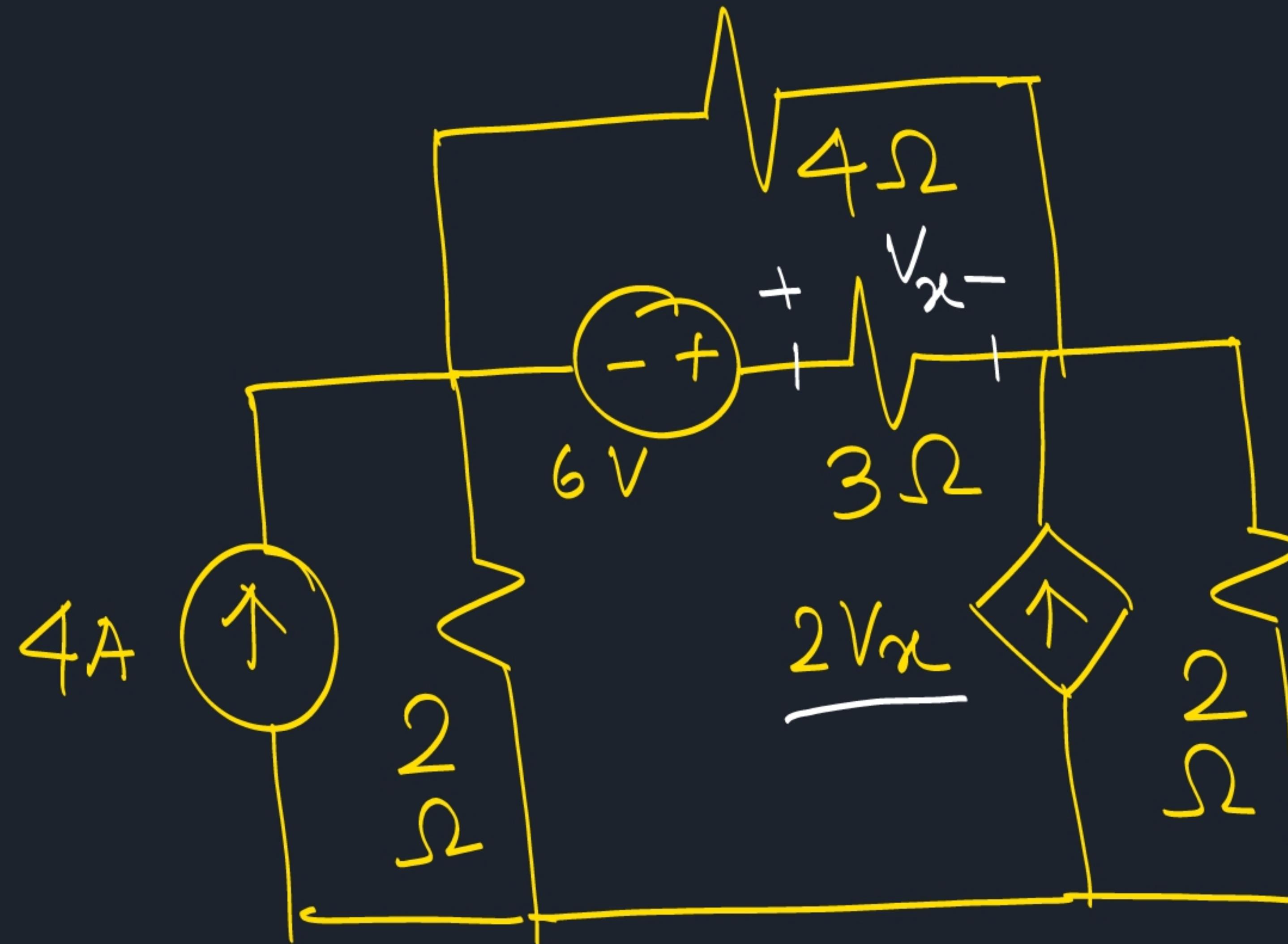




Find V_x Using Superposition.

$$V_x = 3xi$$

$$8 - 4i_1 - 4V_{x1} - V_{x1} = 0$$

$$V_{x1} = ?$$
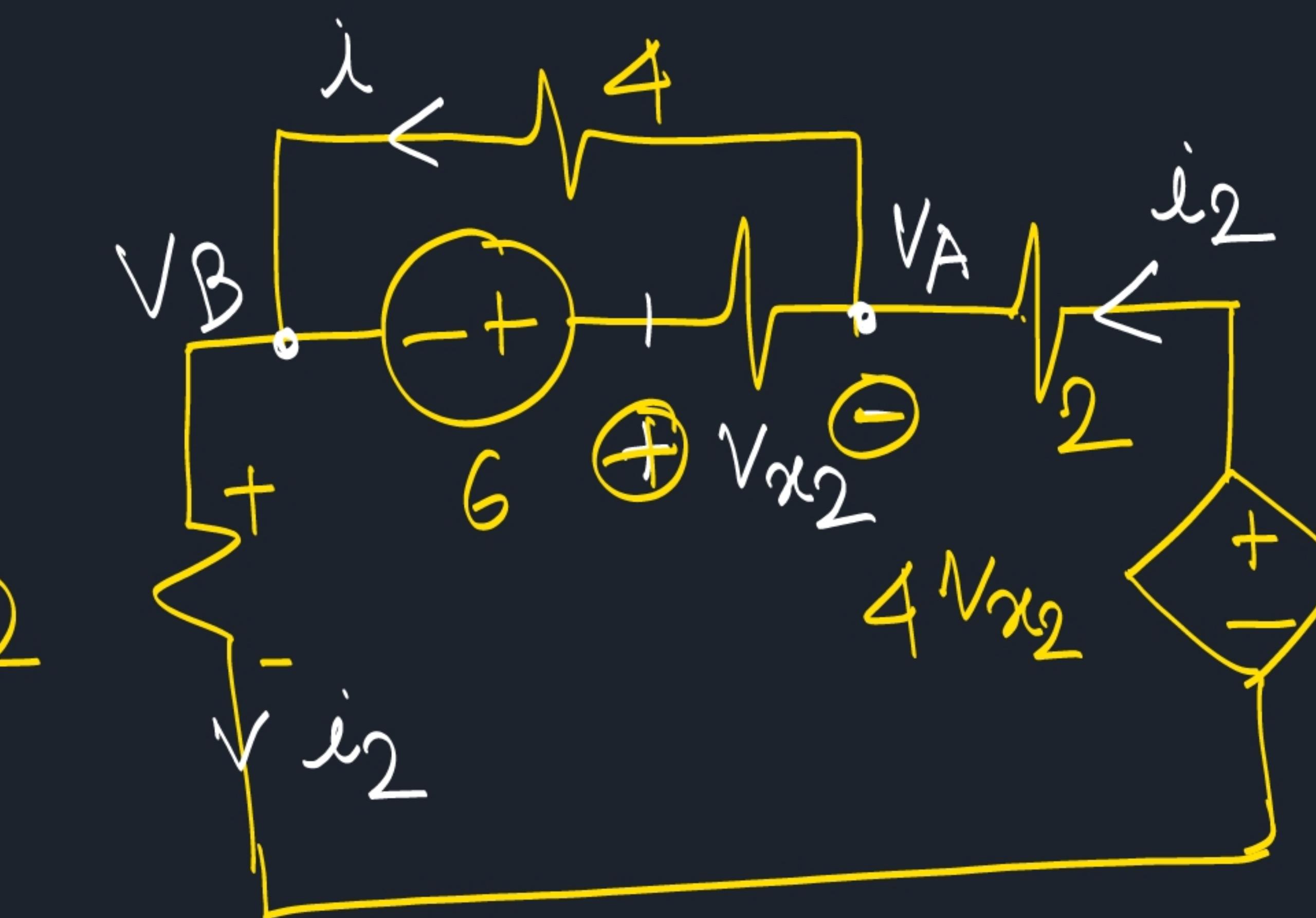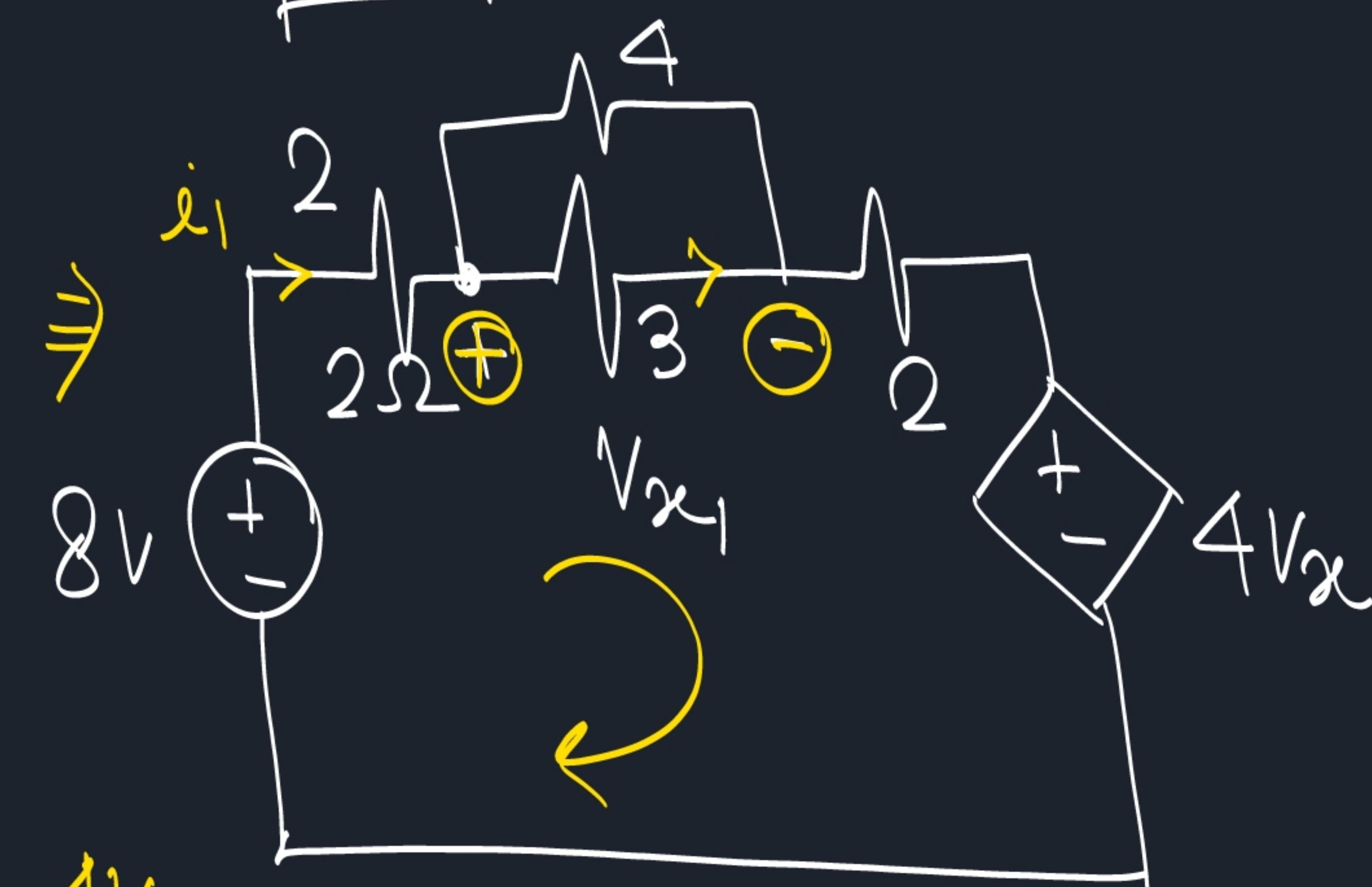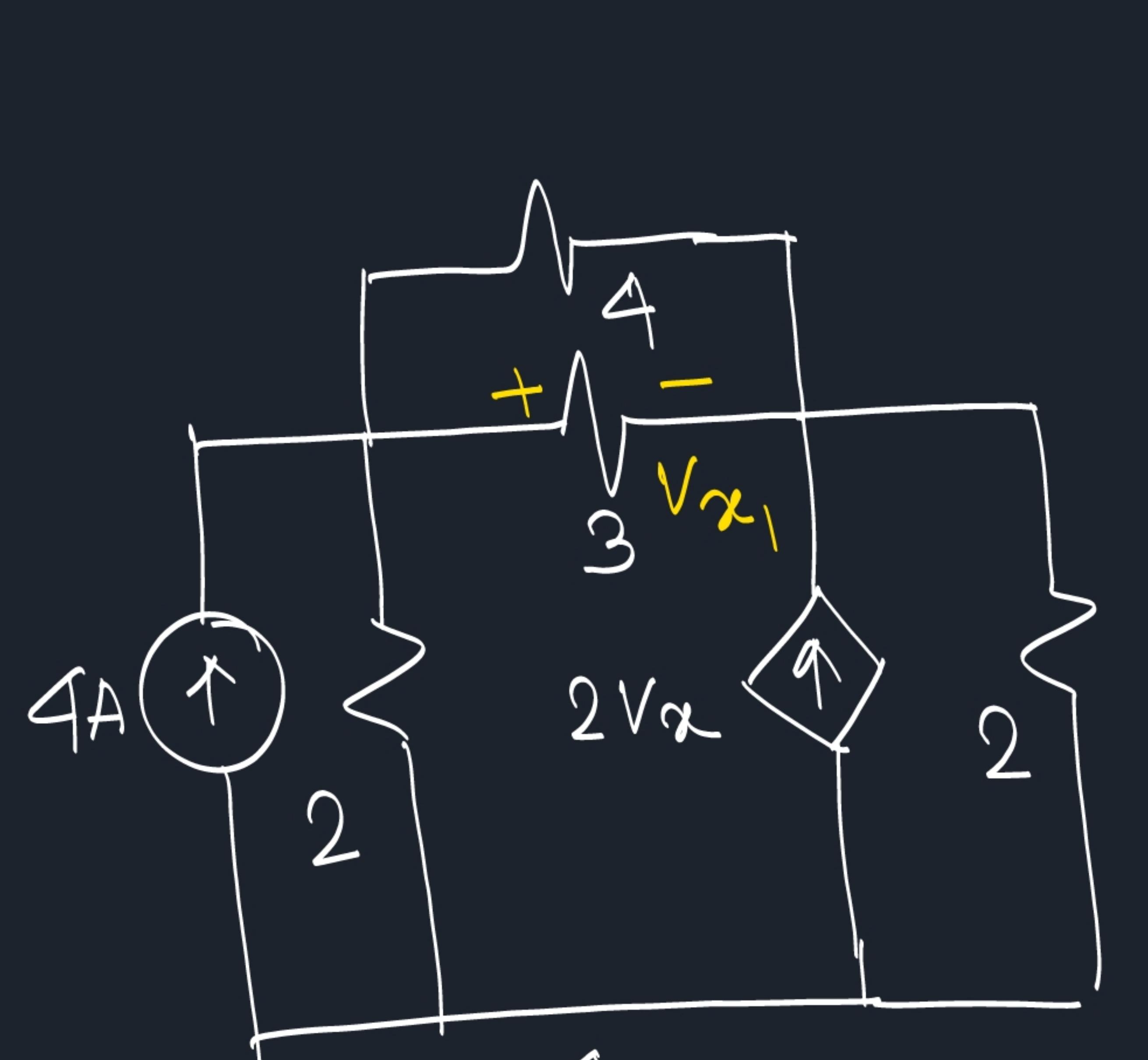
$$i_1 \times \frac{4}{7} \times 3 = V_{x1}$$



$$4V_{x2} - 4i_2 + V_{x2} - 6 = 0$$





$$i_2 = \frac{V_A - V_B}{4} = \frac{6 - V_{x2}}{4}$$

$$i_2 = \left(\frac{6 - V_{x2}}{4} + \frac{V_x}{3} \right)$$

2.727 V is the $\underline{V_x}$



THEVENIN'S THEOREM:-

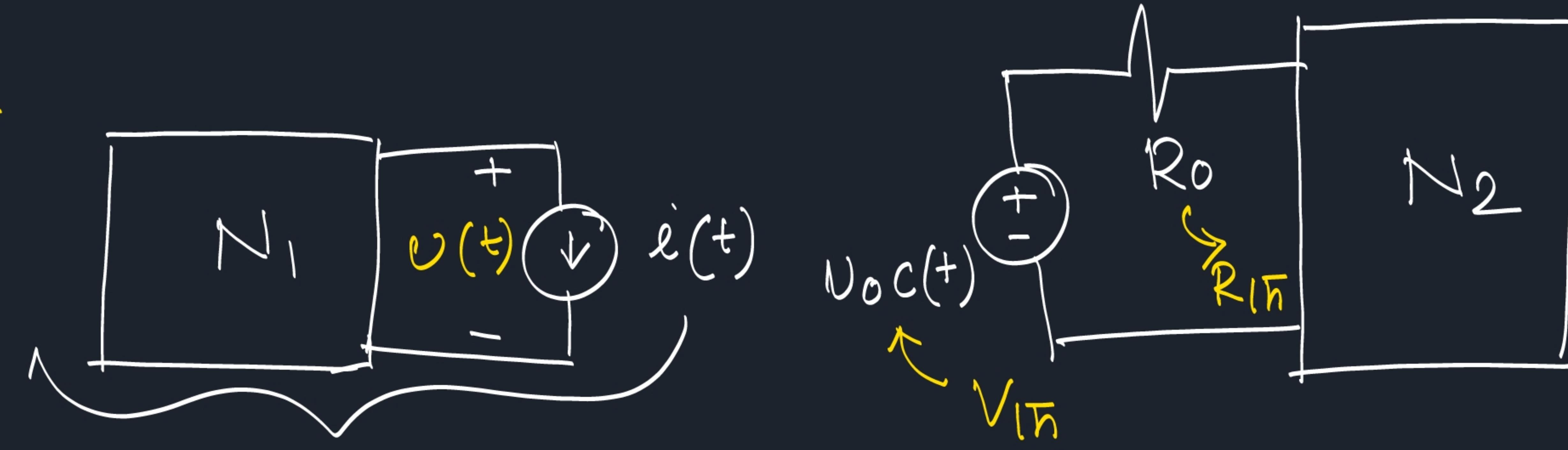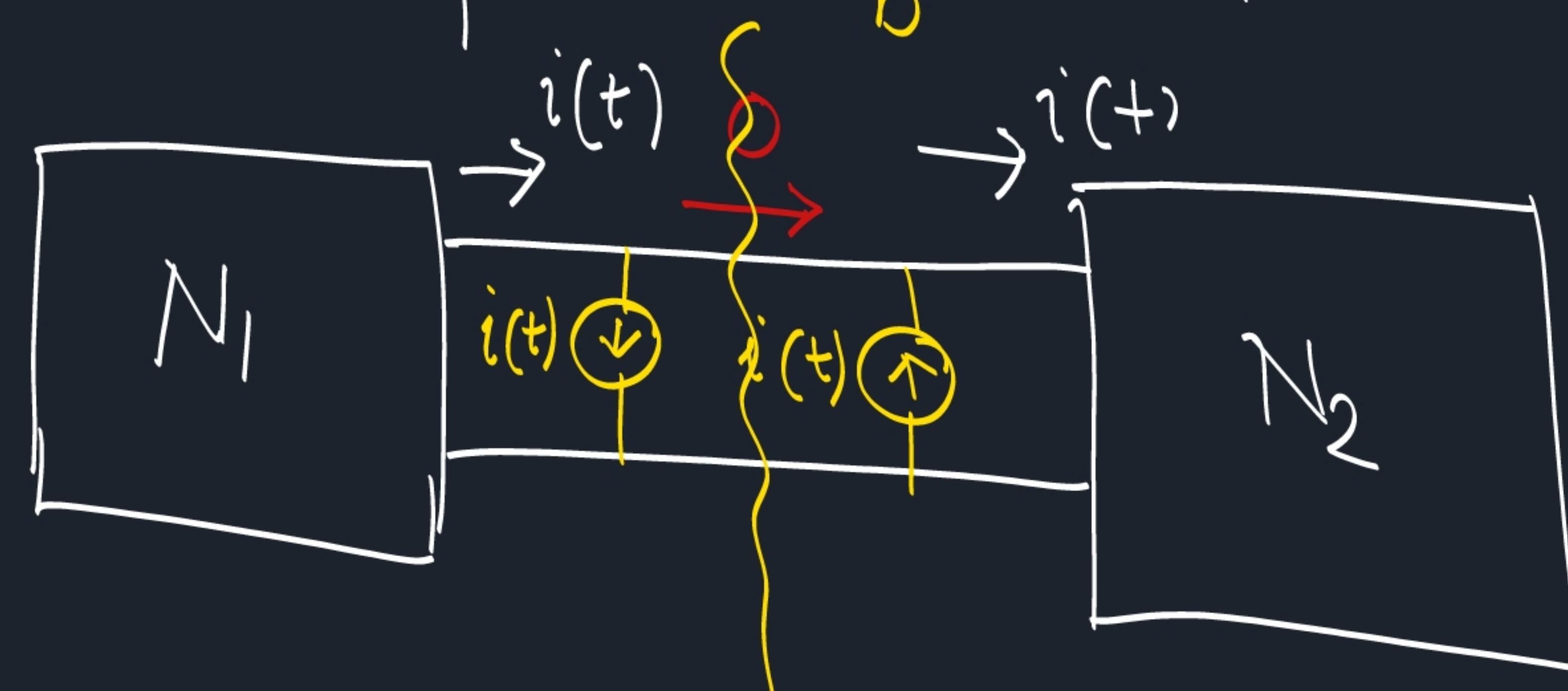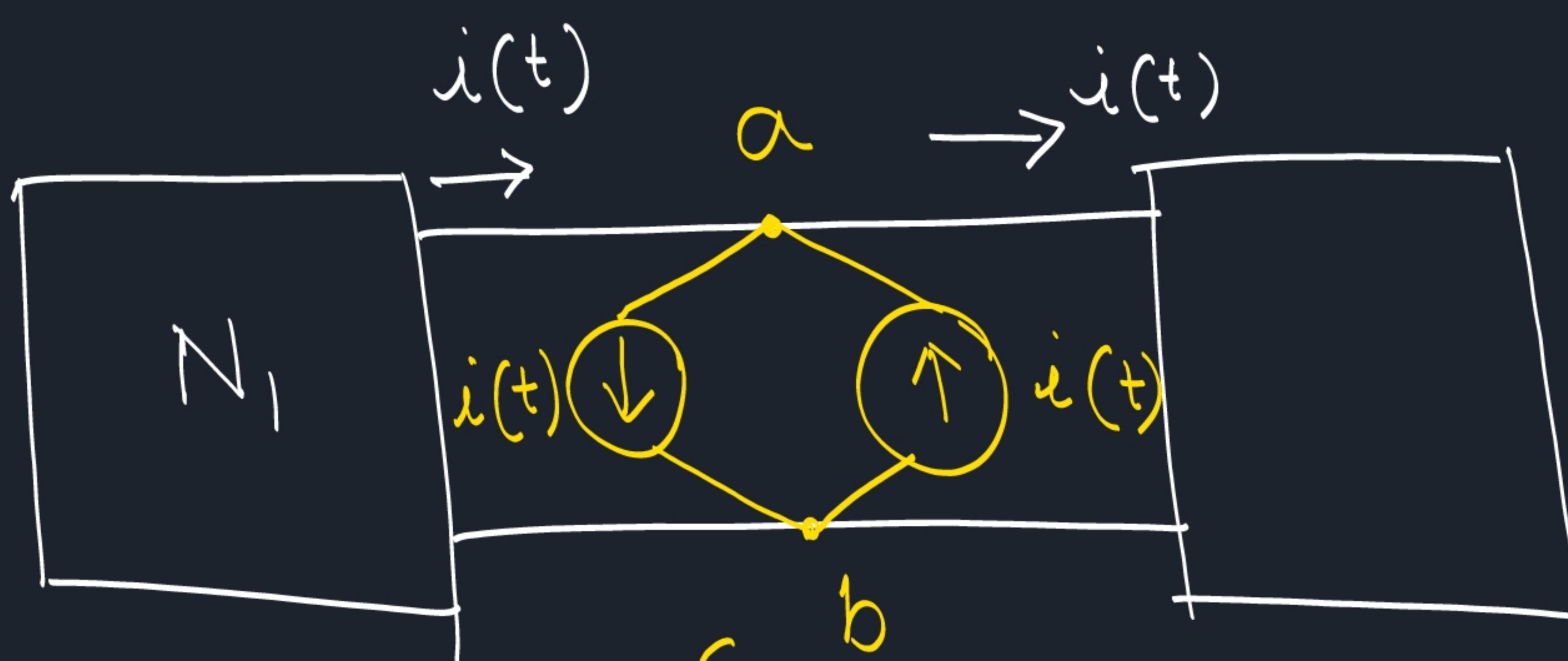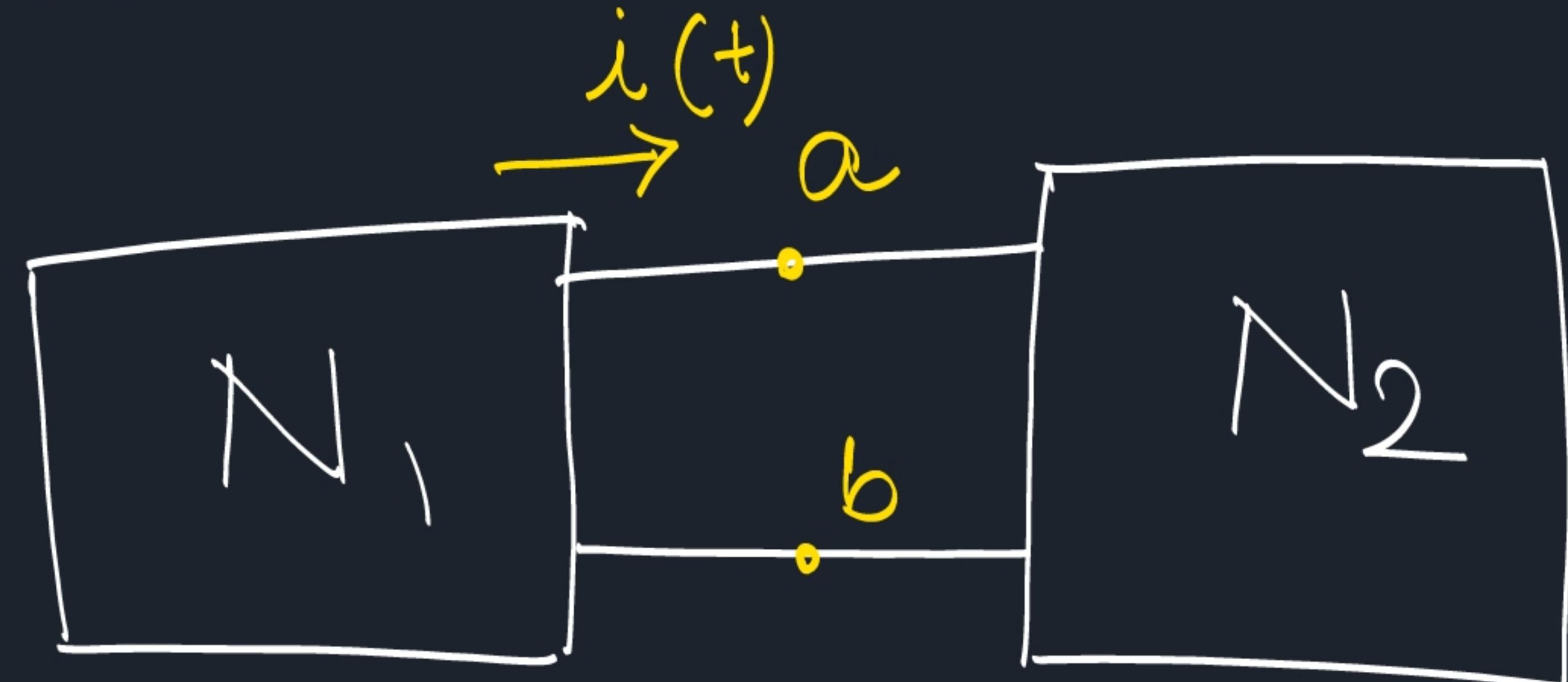


$$V(t) = \sum_{i=1}^n a_i V_{si} + \sum_{j=1}^m b_j I_{sj} + a_0 i(t)$$


when $i(t) = 0$ $\rightarrow V_{oc}(t) = V_{th}(t)$

$$V(t) = V_{oc}(t) + a_0 i(t)$$

$$a_0 = \frac{V(t)}{i(t)} = -R_o$$

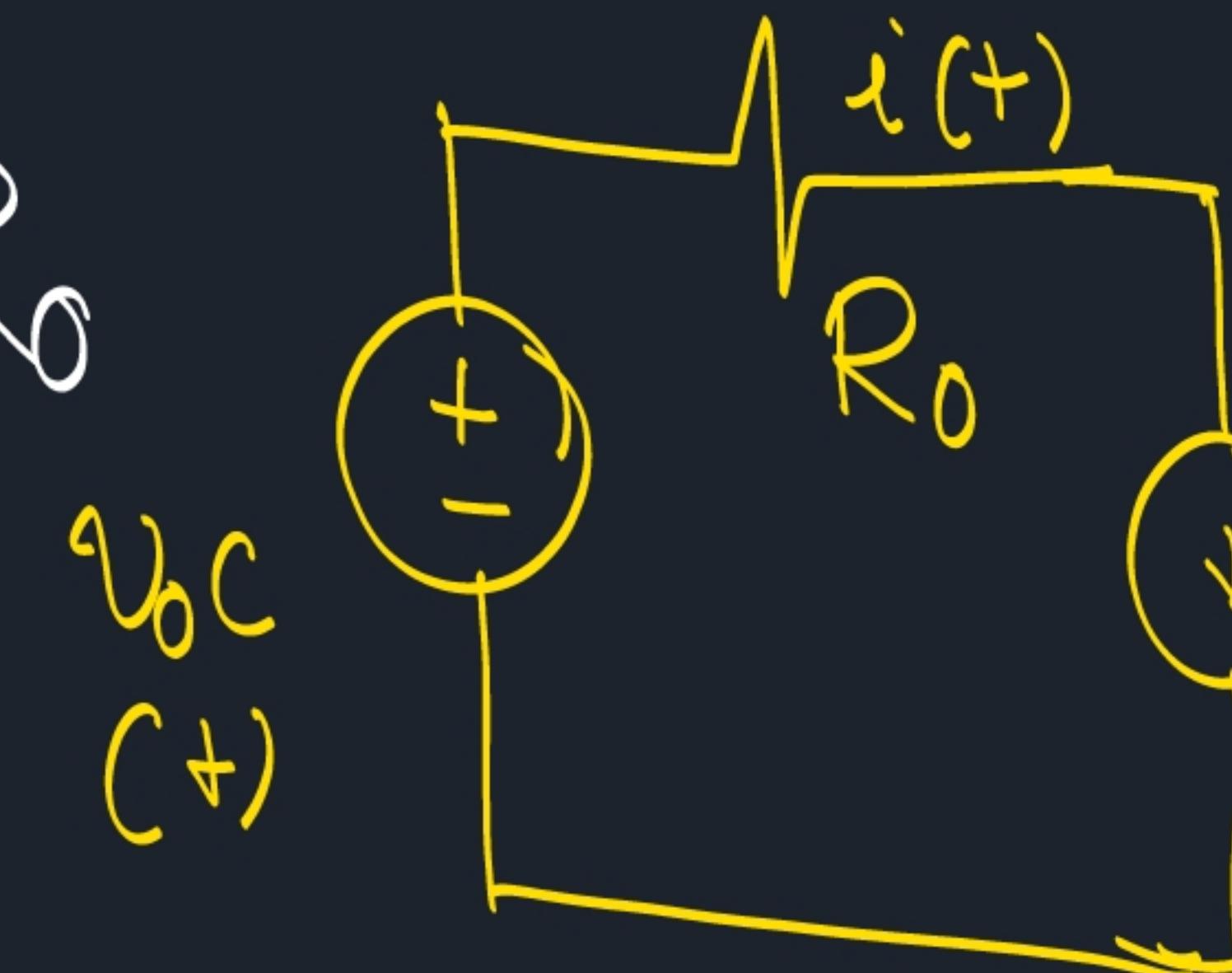


$$V(t) = V_{oc}(t) - R_o i(t)$$

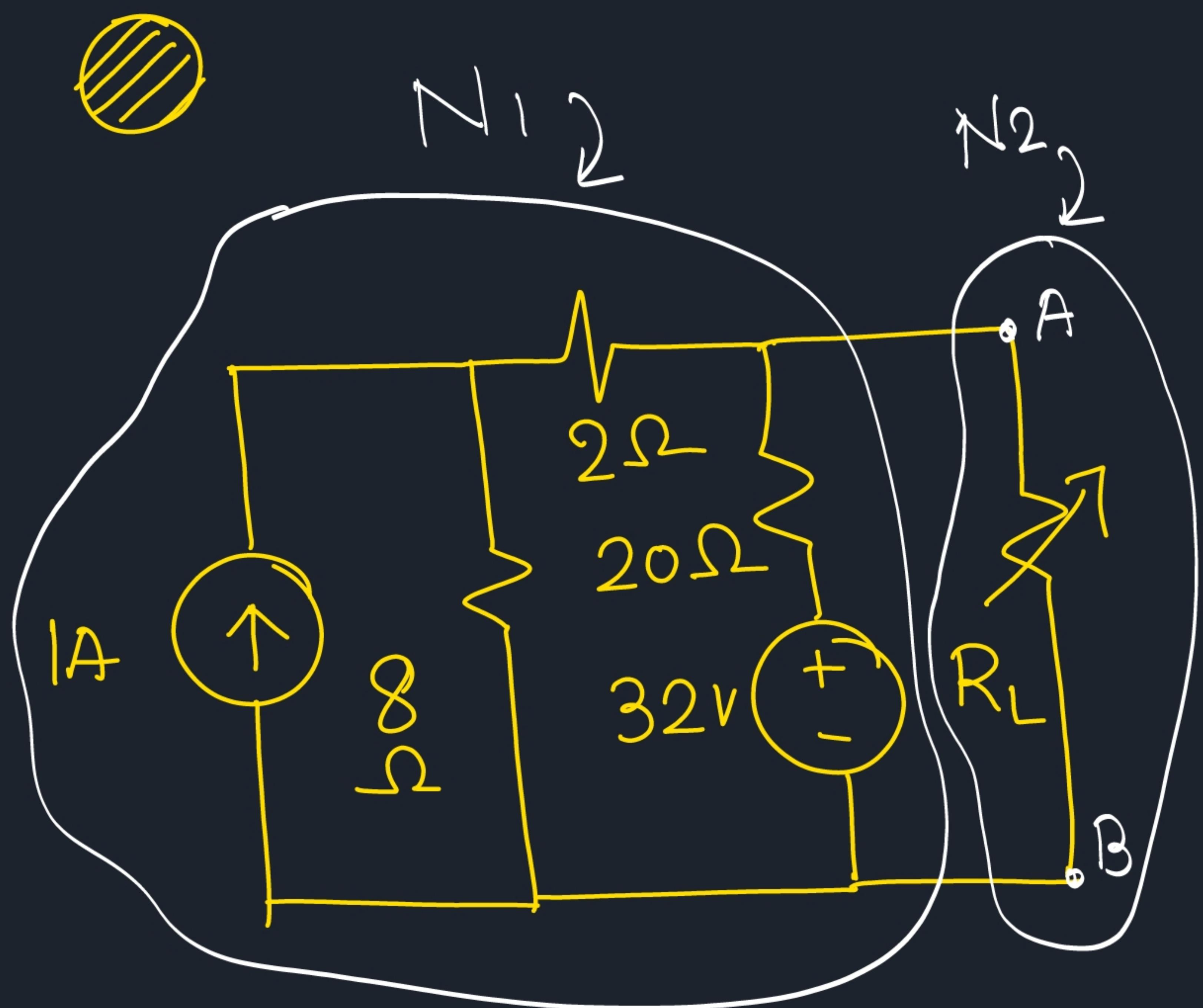

Objective


$$V_{Th} = ?$$
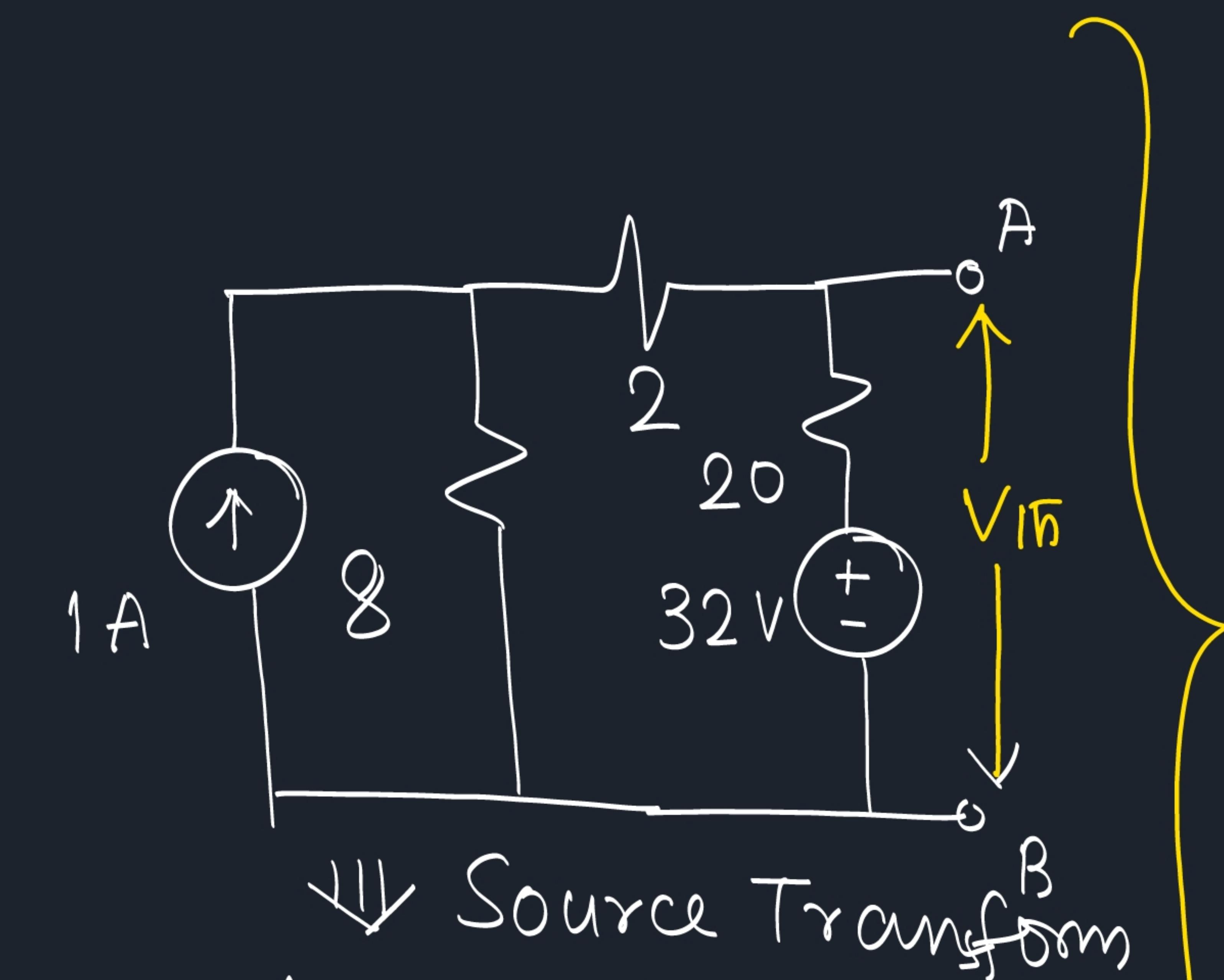
$$R_{Th} = ?$$


$$i = \frac{8 - 32}{10 + 20}$$

$$V_{Th} = 20i + 32$$

$$= \underline{\underline{16V}}$$

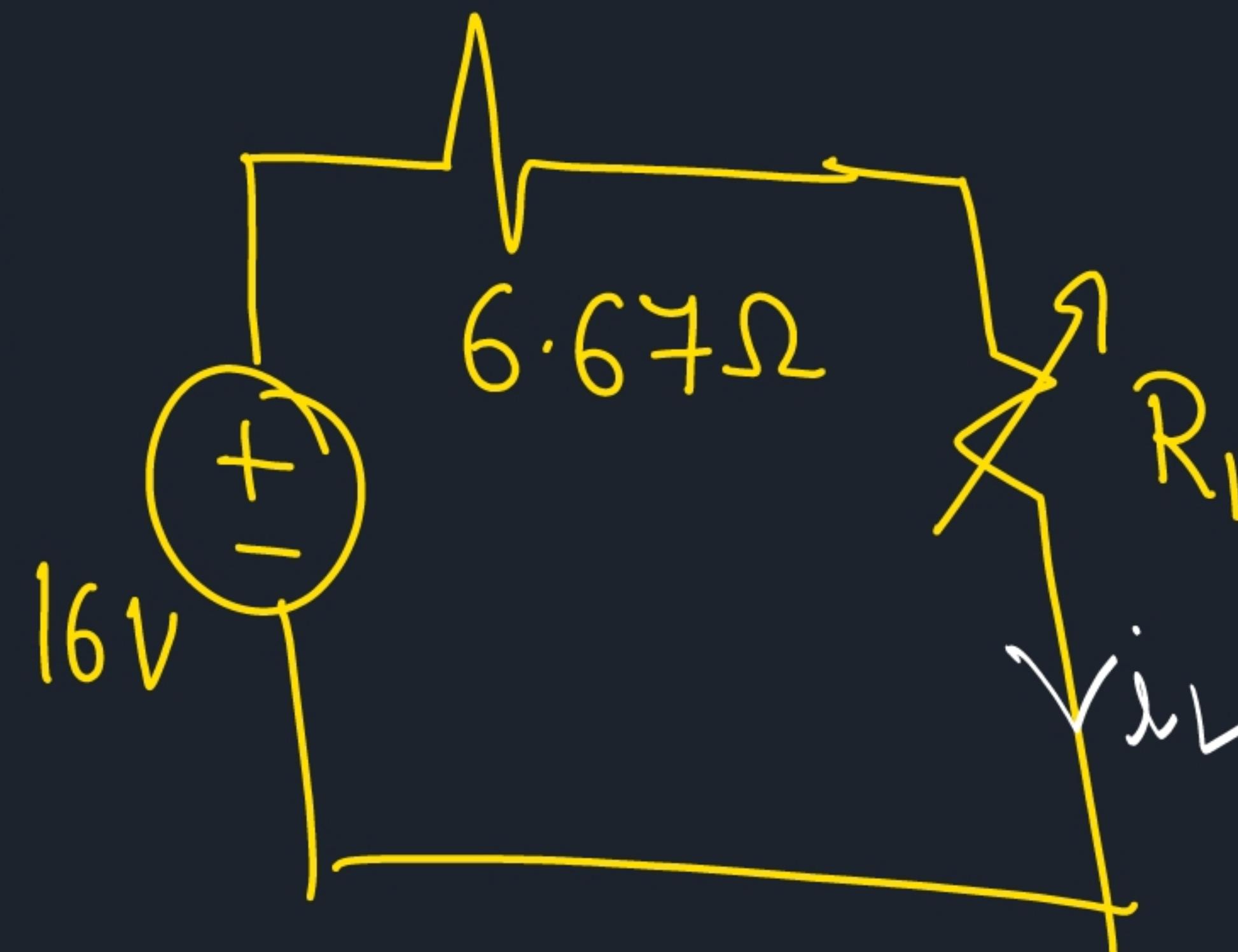


$$R_{Th} = (8+2) \parallel 20$$


$$= 10 \parallel 20 = \frac{10 \times 20}{10 + 20}$$

$$= 6.67 \Omega$$


$$i_L = \frac{16}{6.67 + R_L}$$

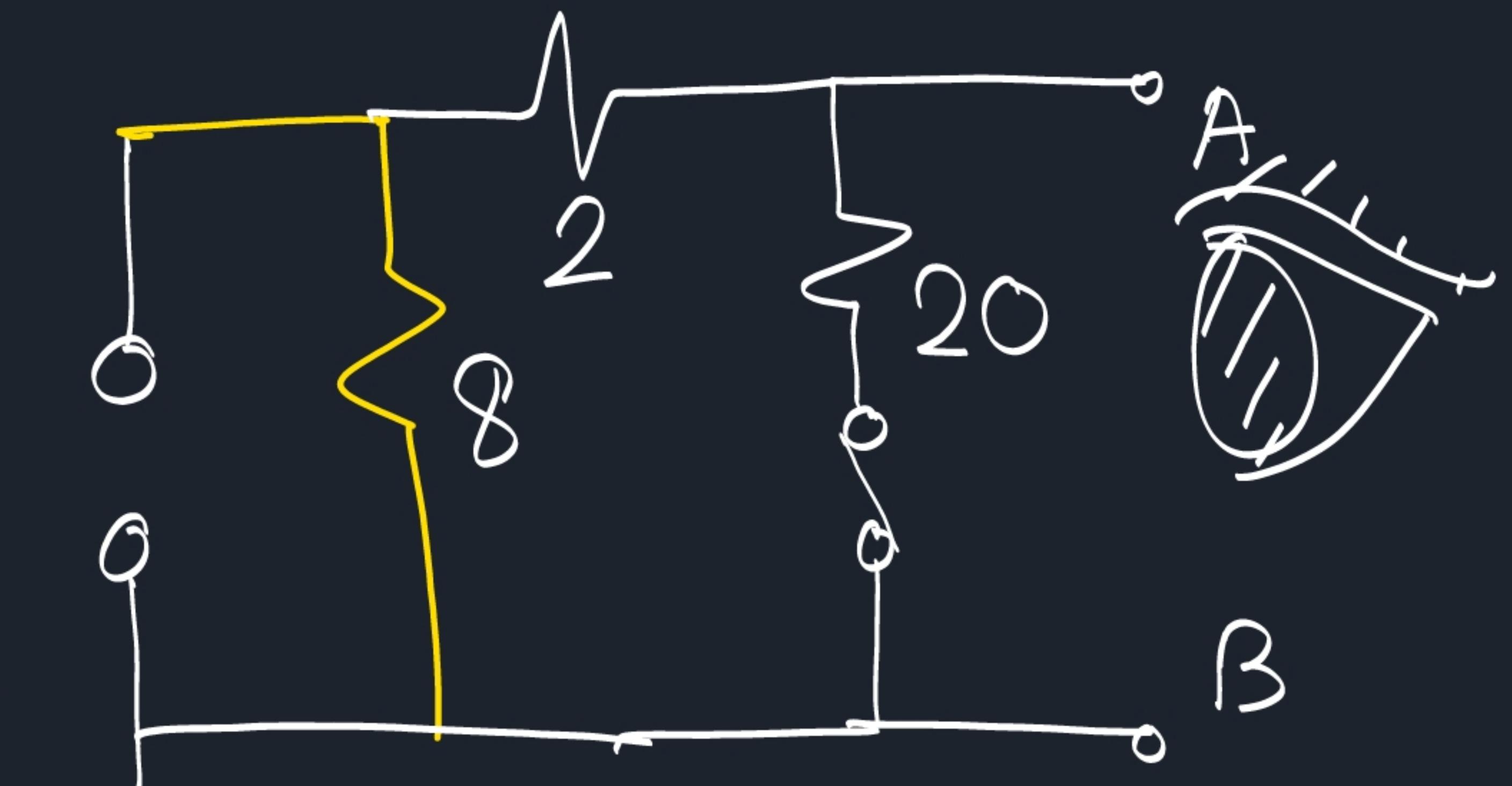





Problem:-

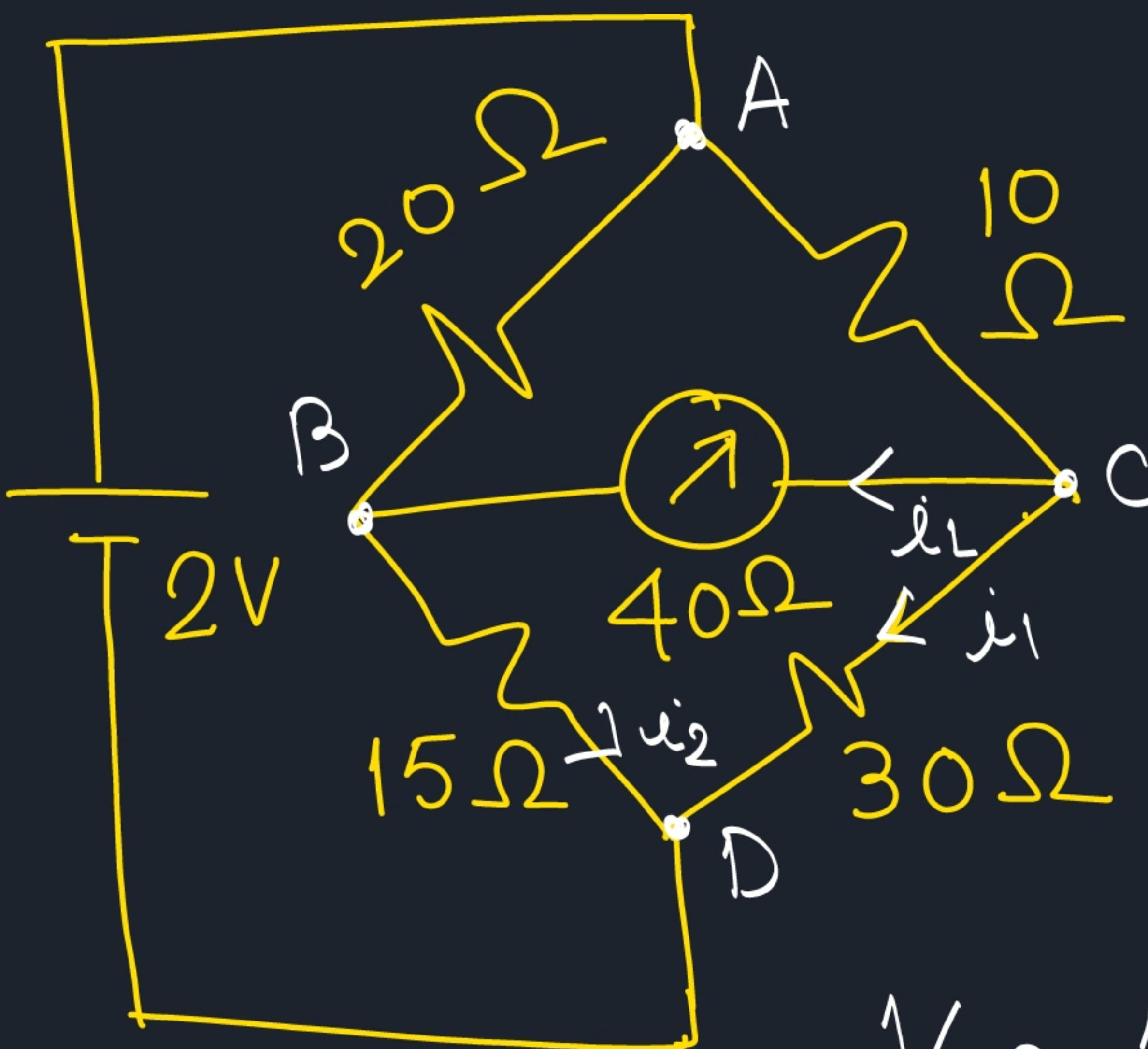

$$i_L = 11.46 \text{ mA}$$

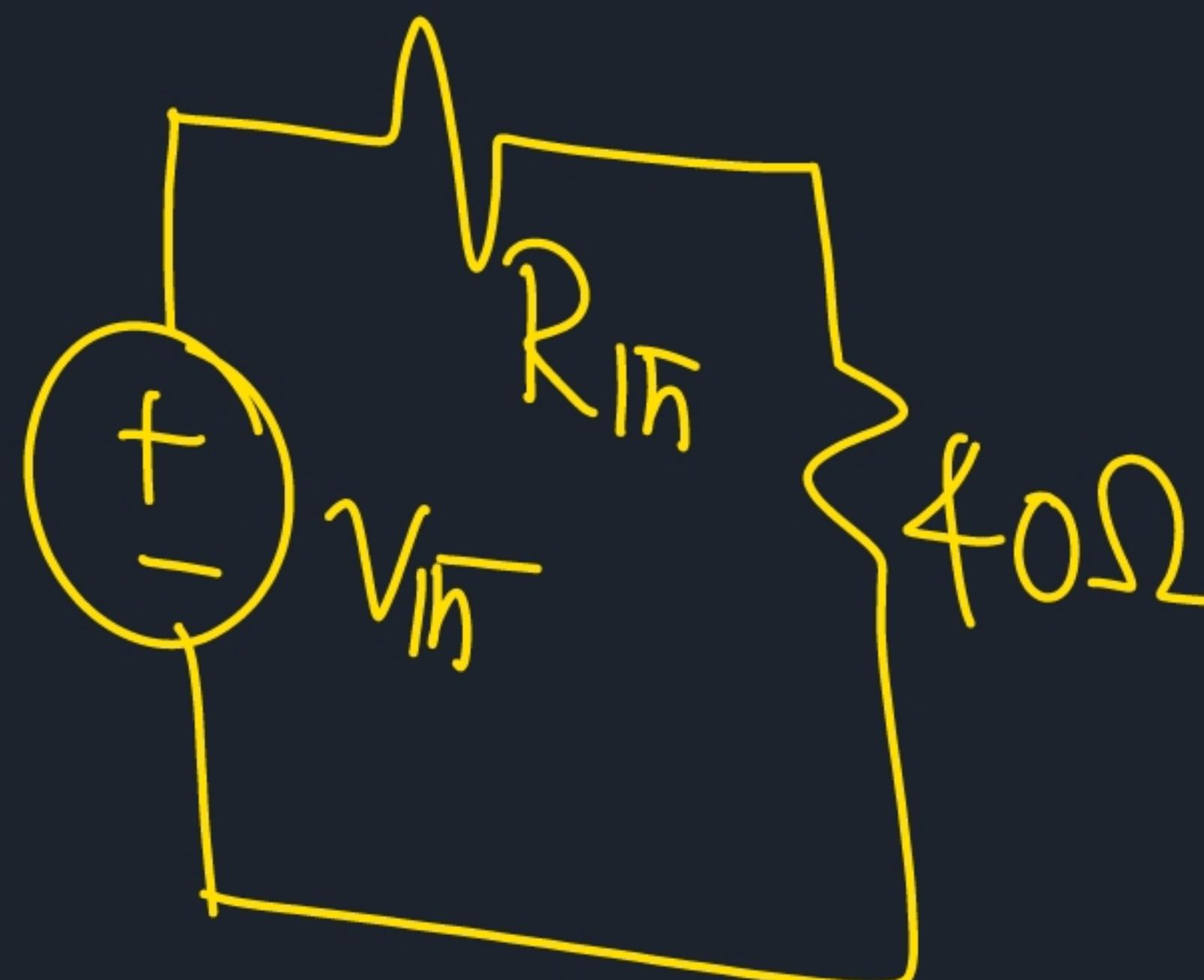
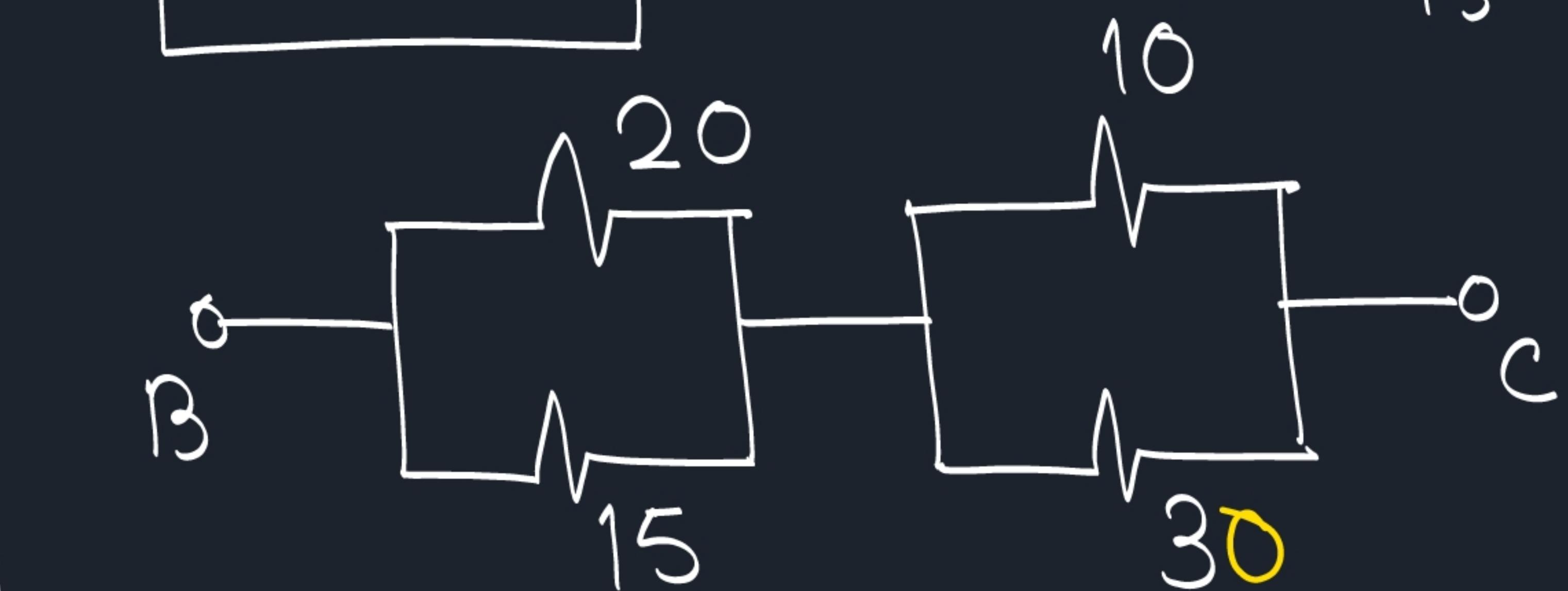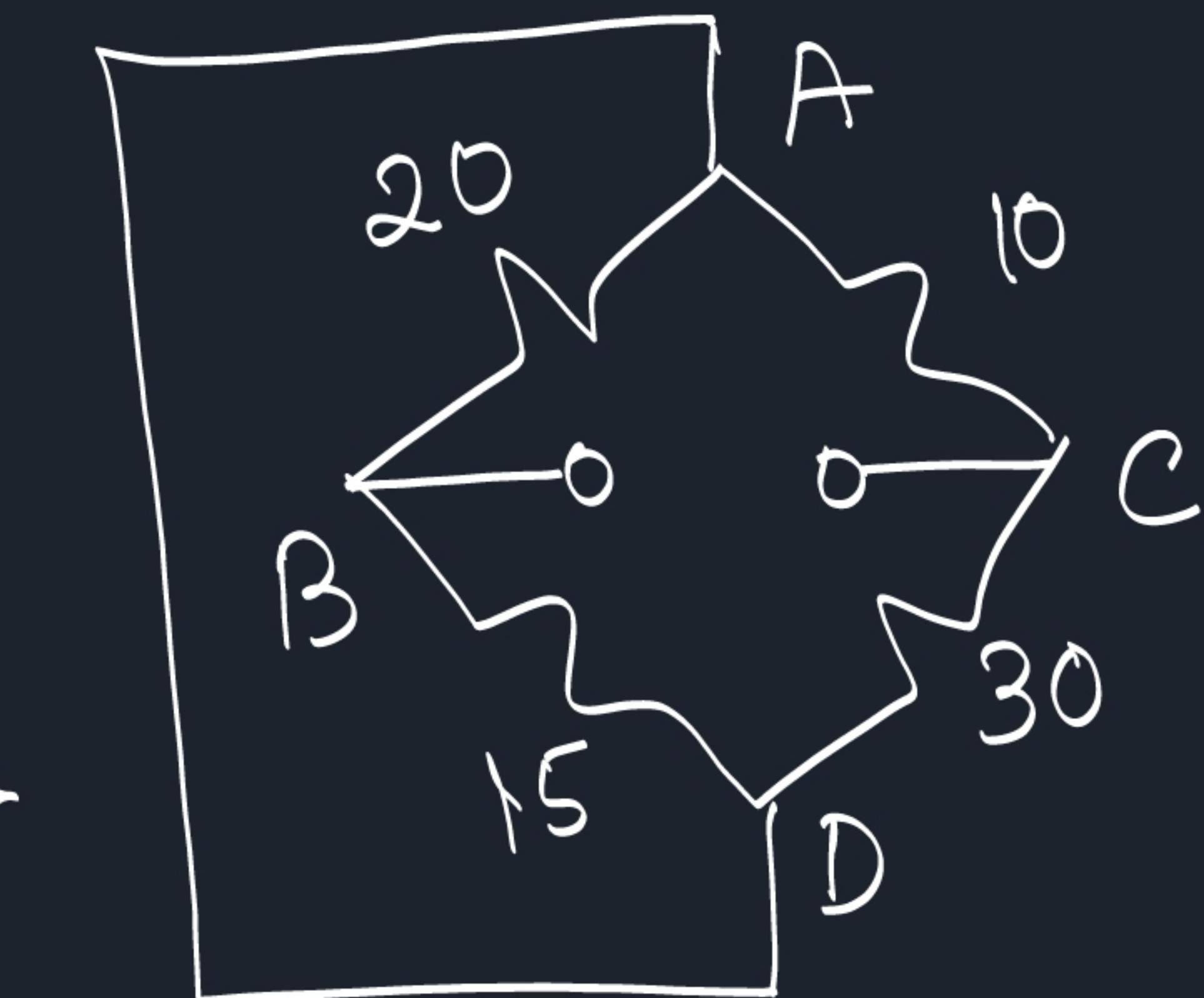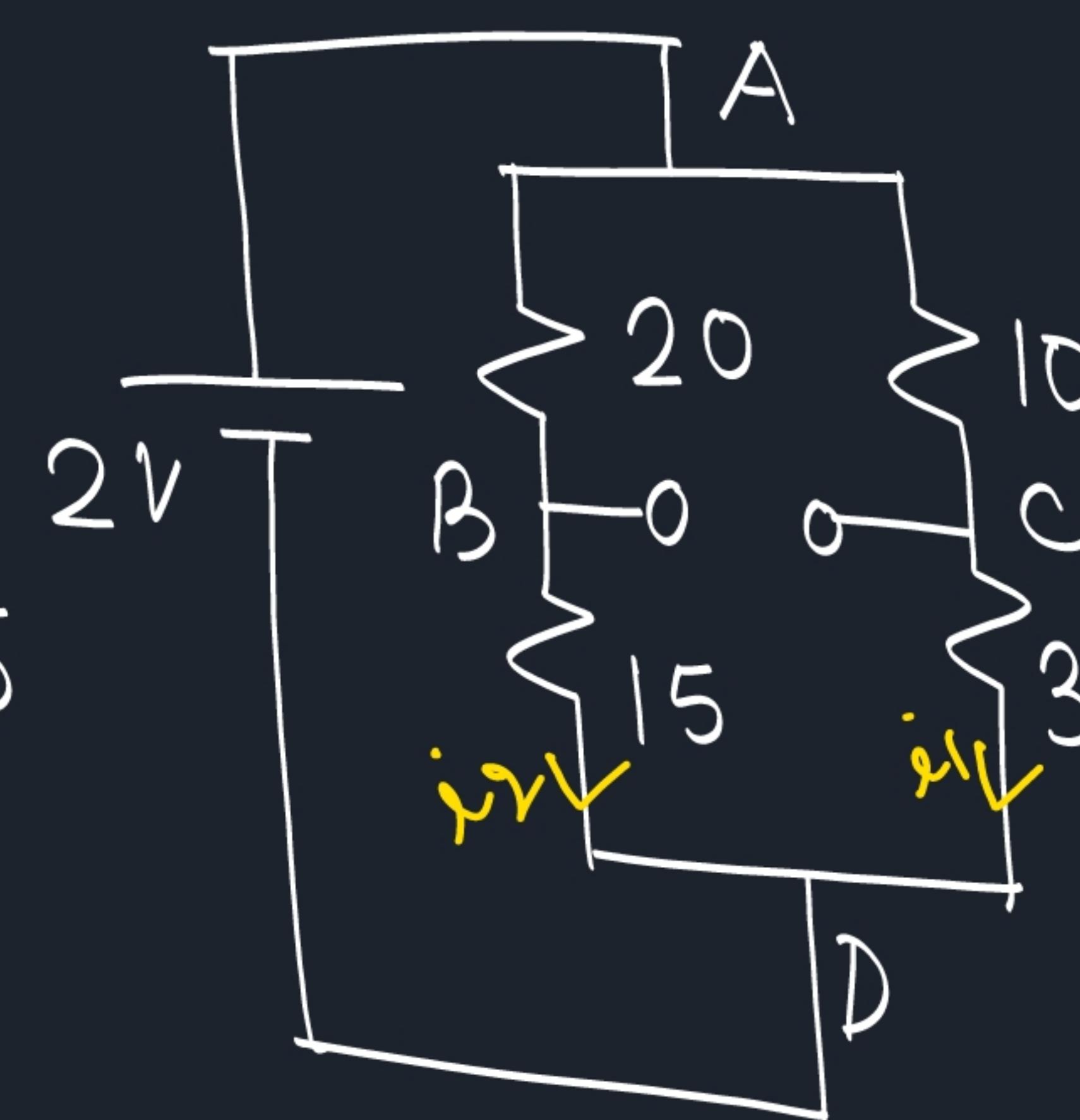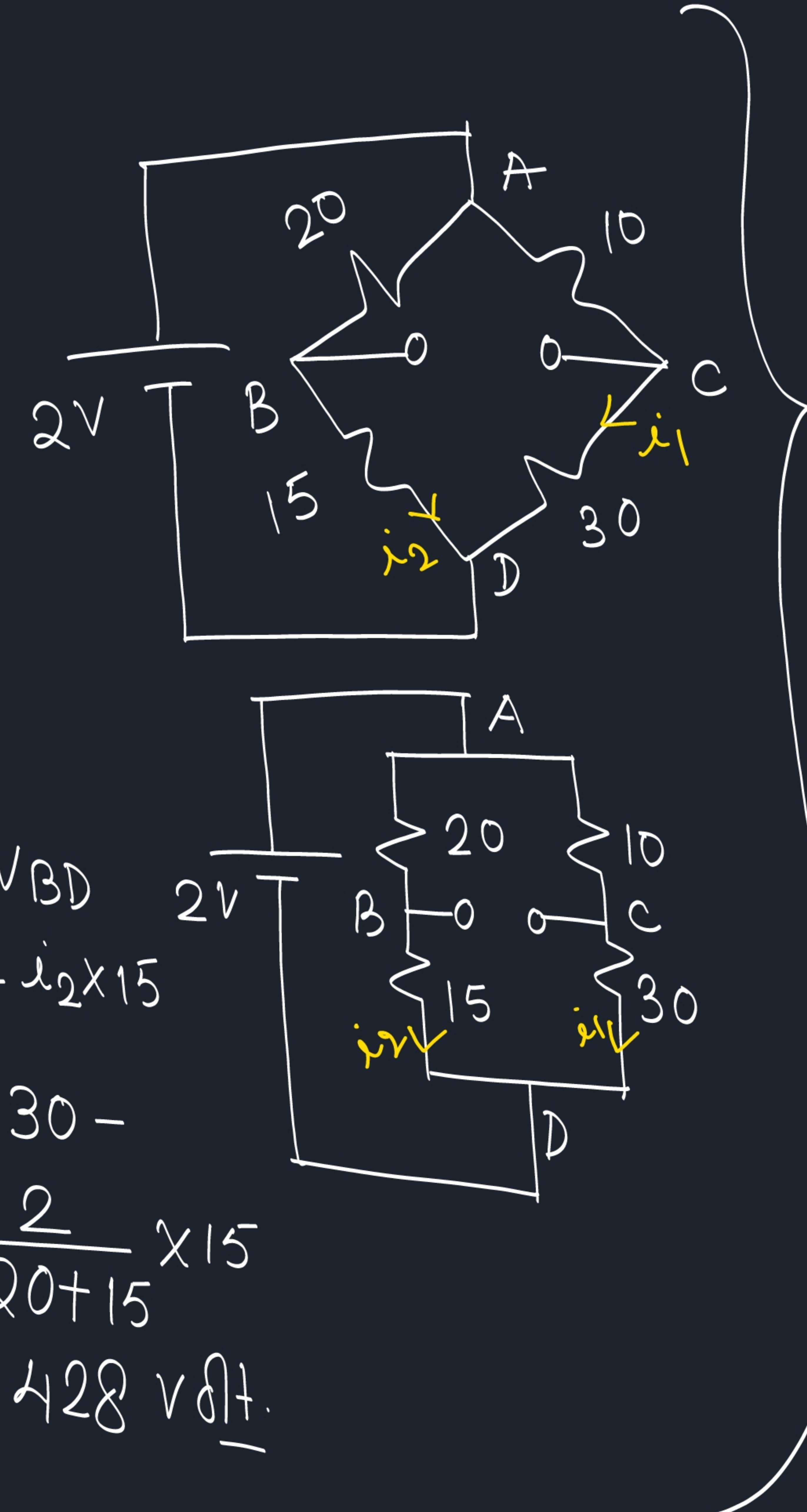
$$\begin{aligned} V_{CB} &= V_{CD} - V_{BD} \\ V_{IH} &= i_1 \times 30 - i_2 \times 15 \\ &= \frac{2}{10+30} \times 30 - \frac{2}{20+15} \times 15 \\ &= 0.6428 \text{ V}_H \end{aligned}$$







$$R_{IH} = ? \quad (20 \parallel 15) + (10 \parallel 30) = 16.071$$

$$i_L = \frac{0.6428}{40 + 16.071} \text{ Amp.}$$

=

8593

NORTONS THEOREM :-

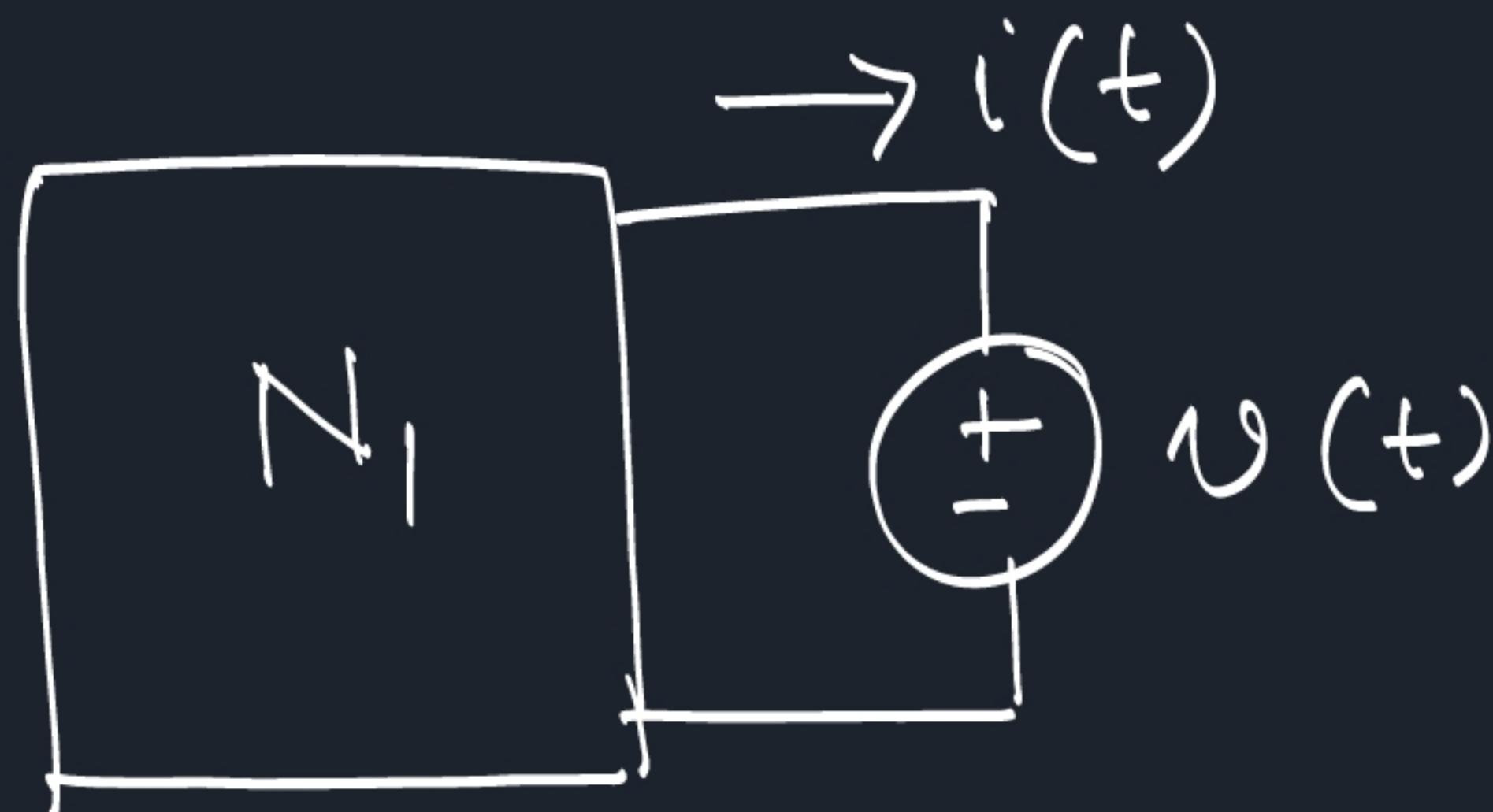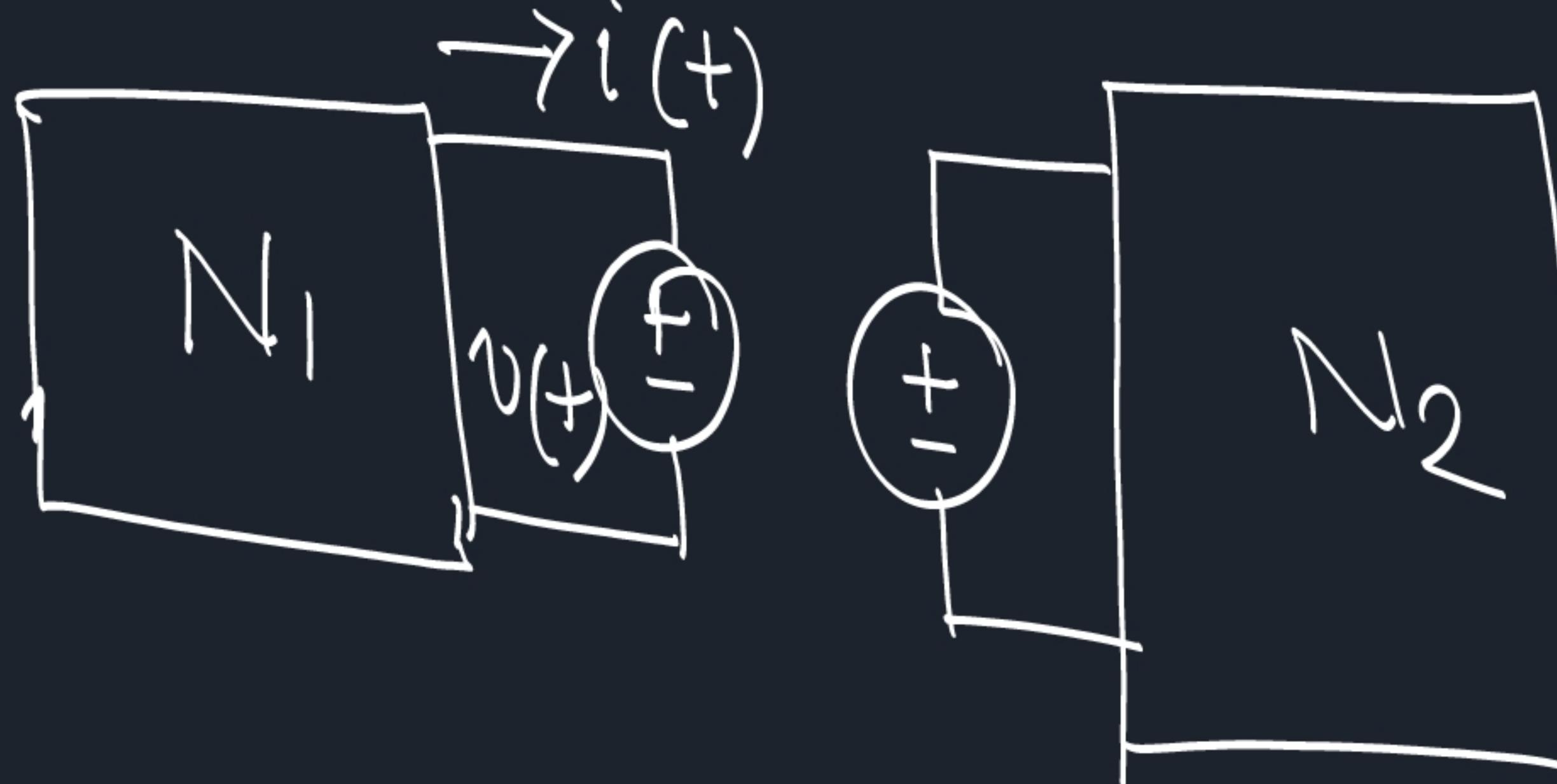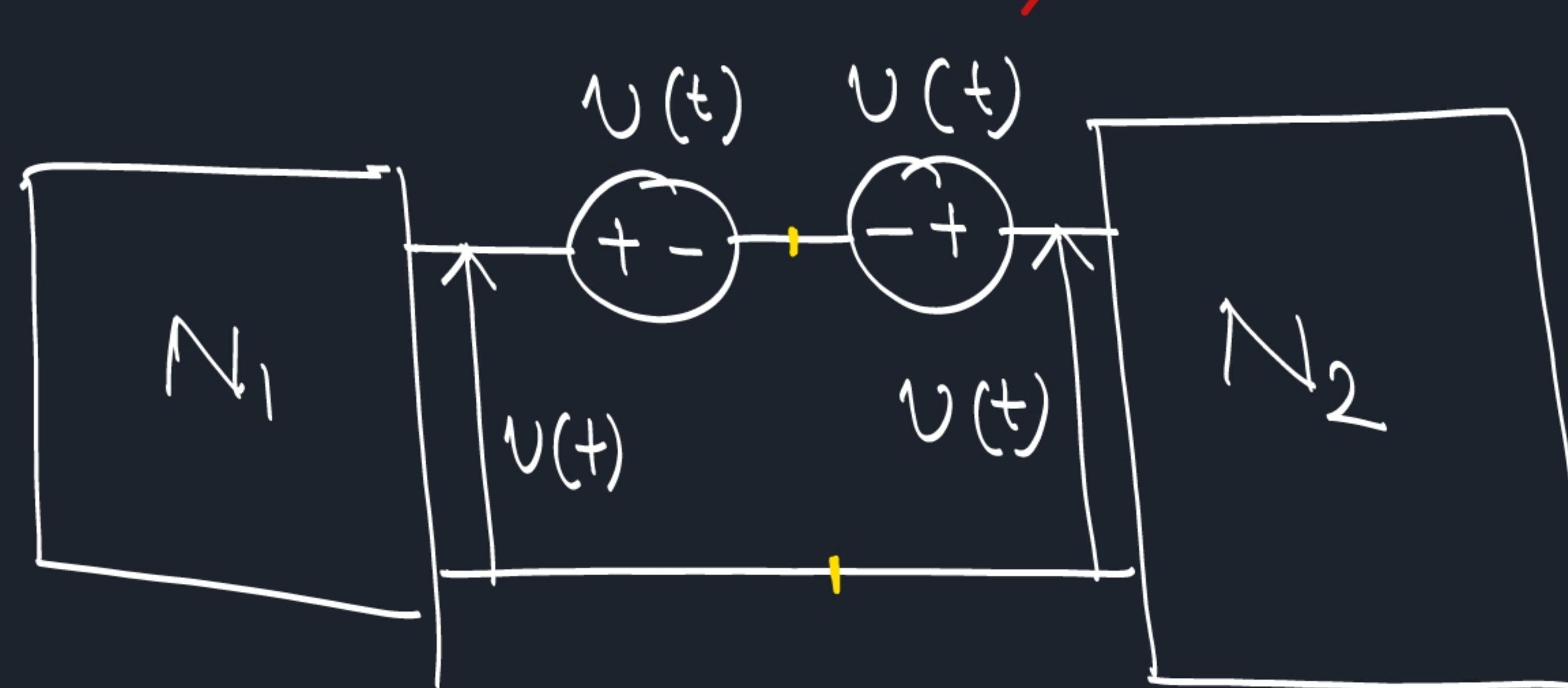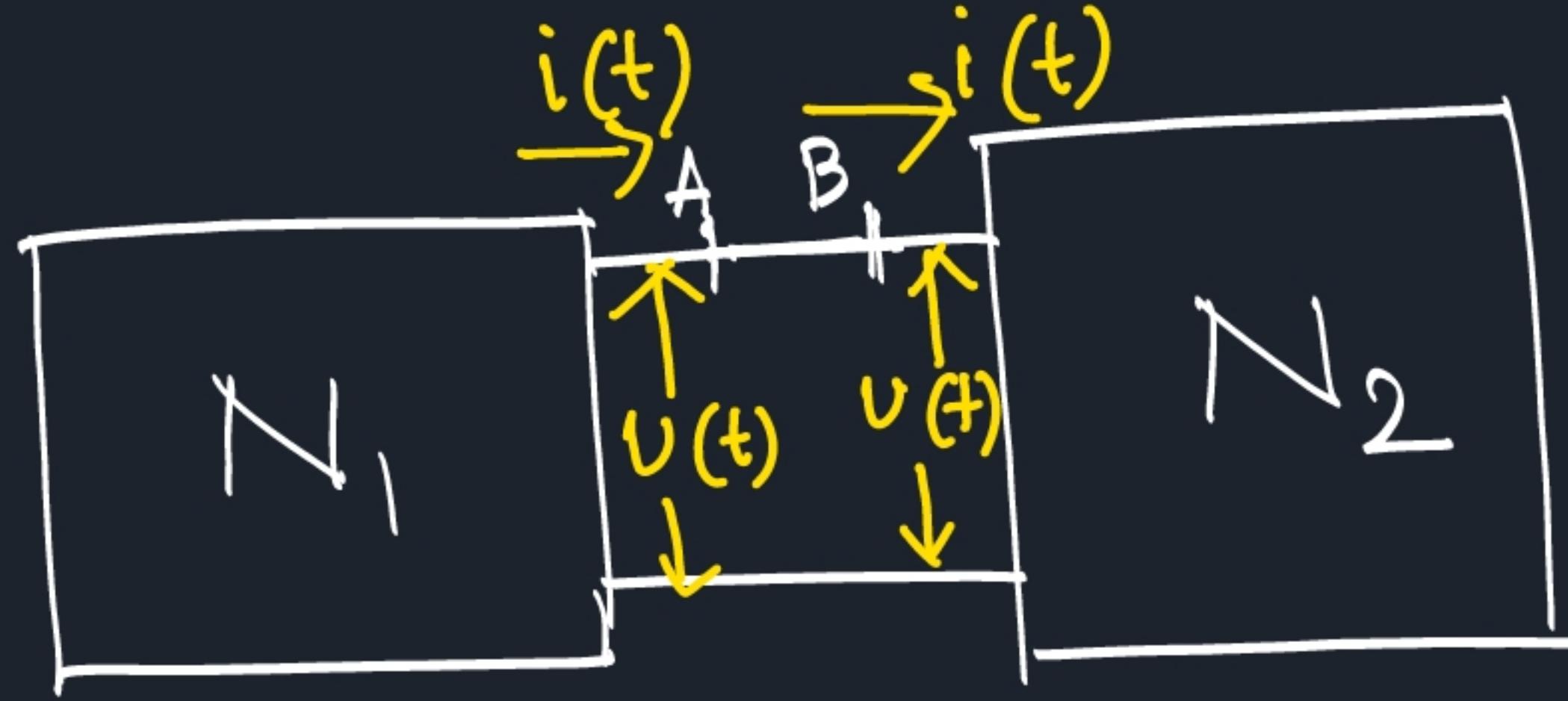


find out $i(+)=?$
m no of indep. Voltage Source
m " " " Current "

$$i(t) = \sum_{i=1}^m c_i v_{si}(t) + \sum_{j=1}^n d_j I_{sj} + C_0 V(t)$$



$$\text{make } V(t) = 0 \quad i(t) = I_N = I_{SC} = \sum_{i=1}^m c_i v_{si}(+) + \sum_{j=1}^n d_j I_{sj}$$

$$C_0 = \frac{i(t)}{V(t)} = -G_{SC} = -G_N$$

$$i(t) = I_{SC} - G_{SC} V(t)$$

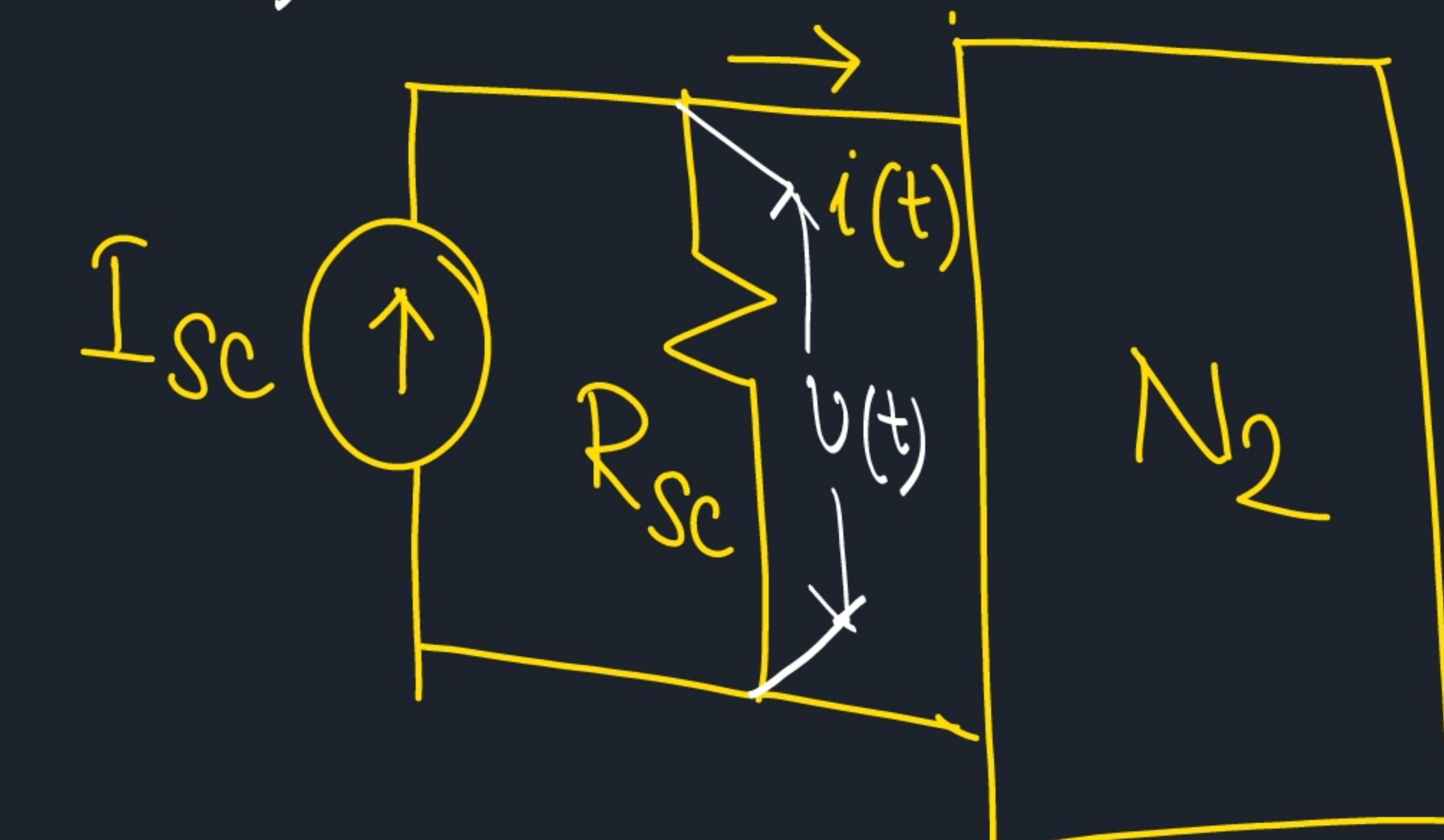

Problem:-

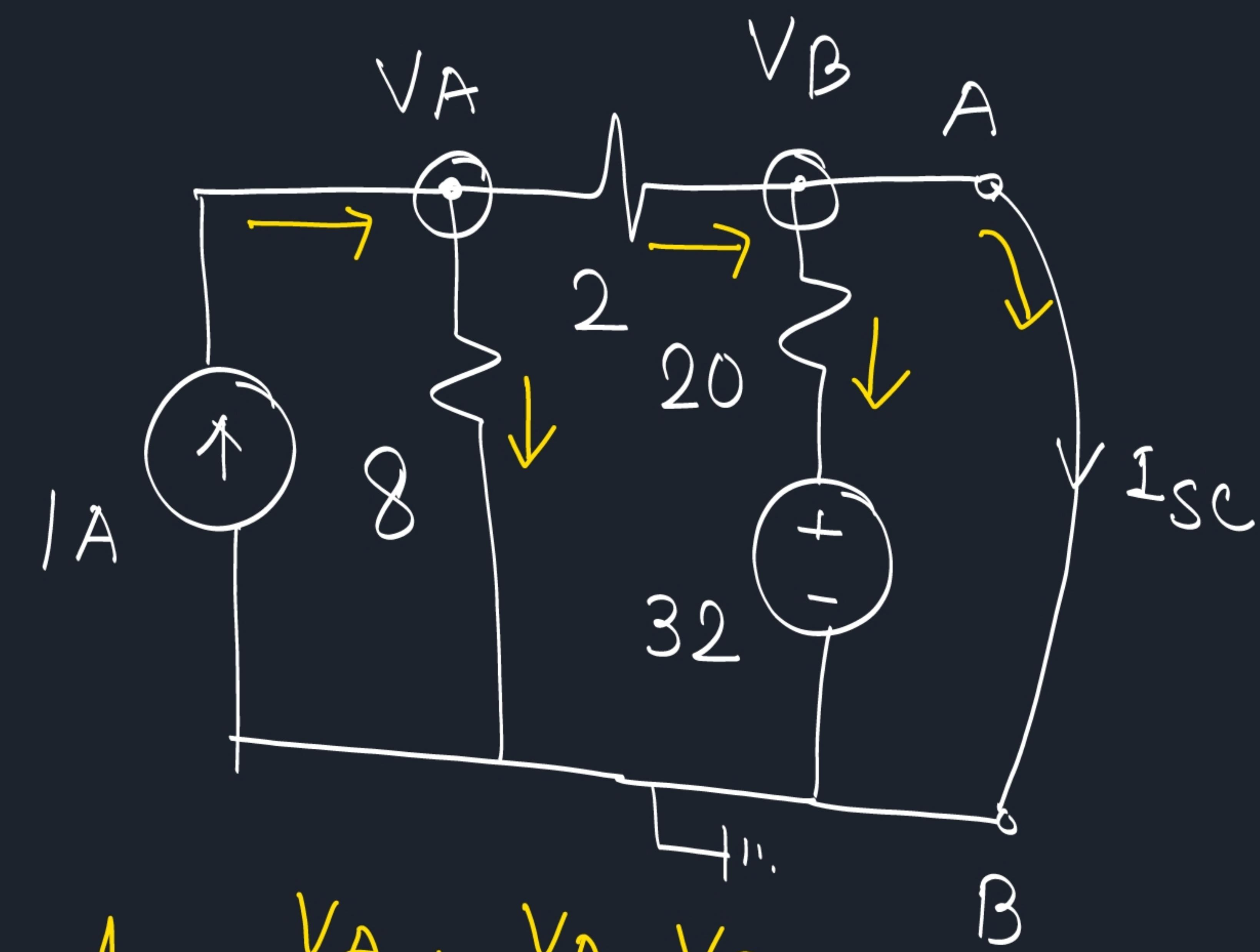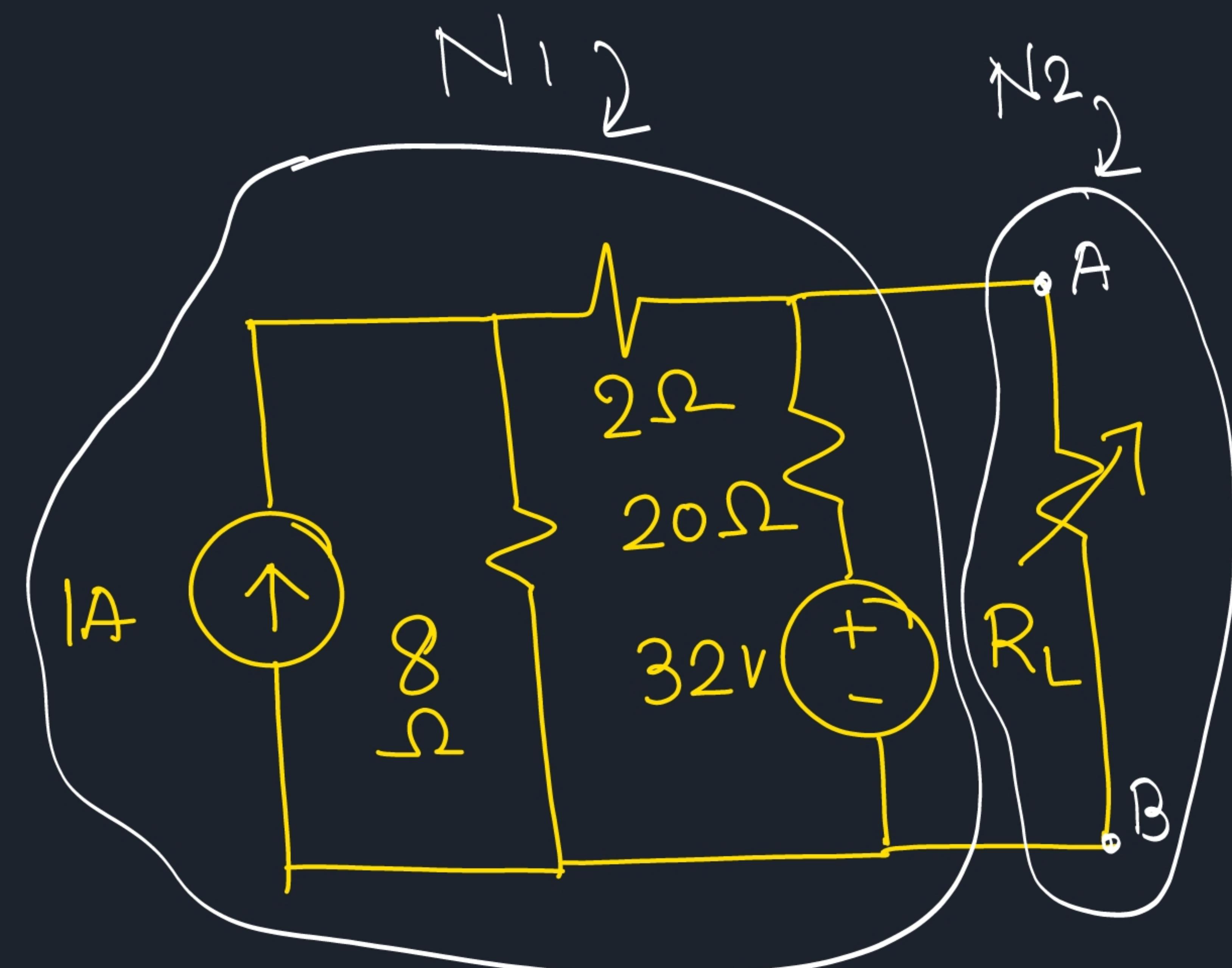





$$I = \frac{V_A}{8} + \frac{V_A - V_B}{2}$$

$$V_B = 0$$


$$\frac{V_A - V_B}{2} = \frac{V_B - 32}{20} + I_N$$

$$\underline{I_N = 2.4 \text{ Amps.}}$$

Problem:-

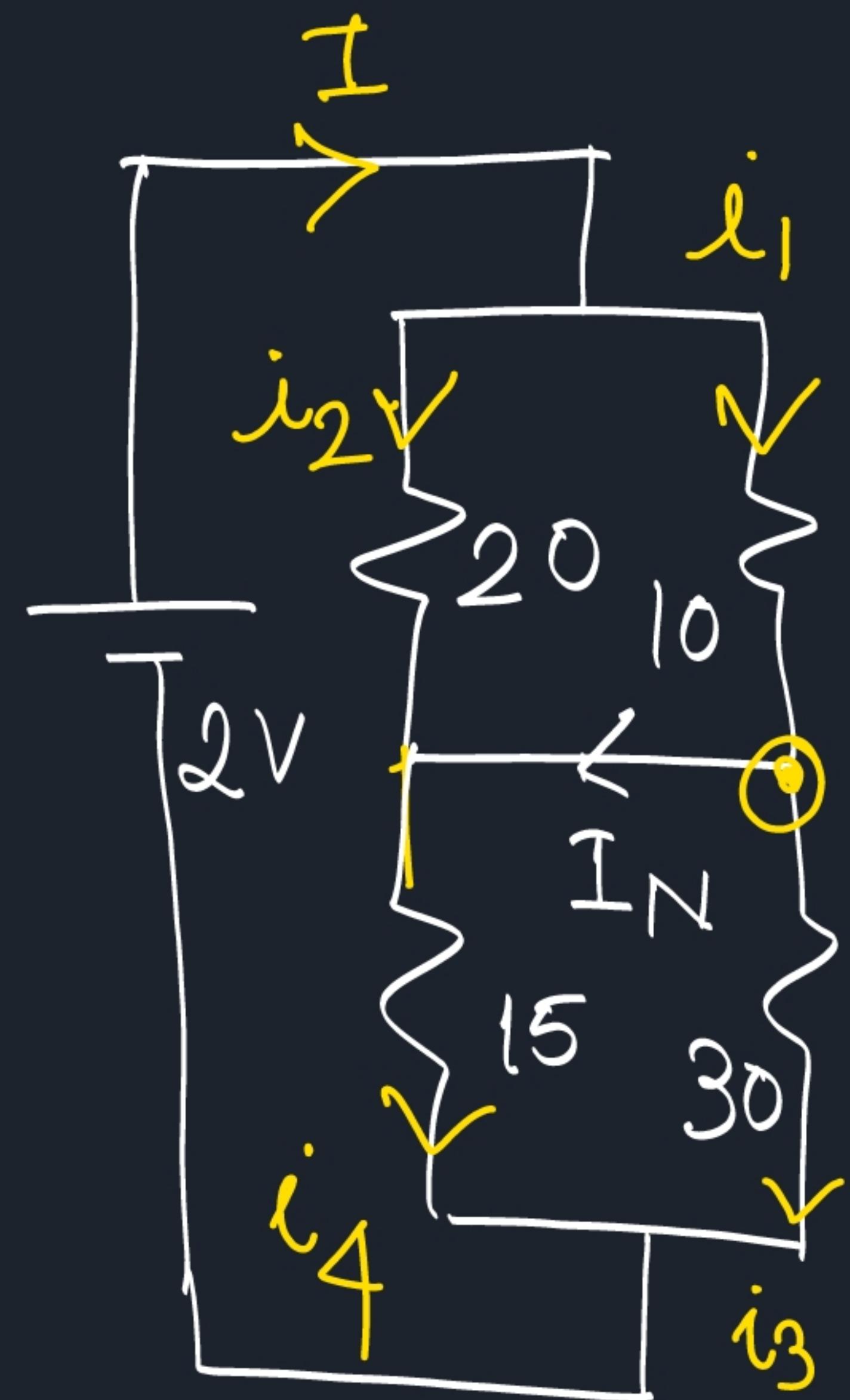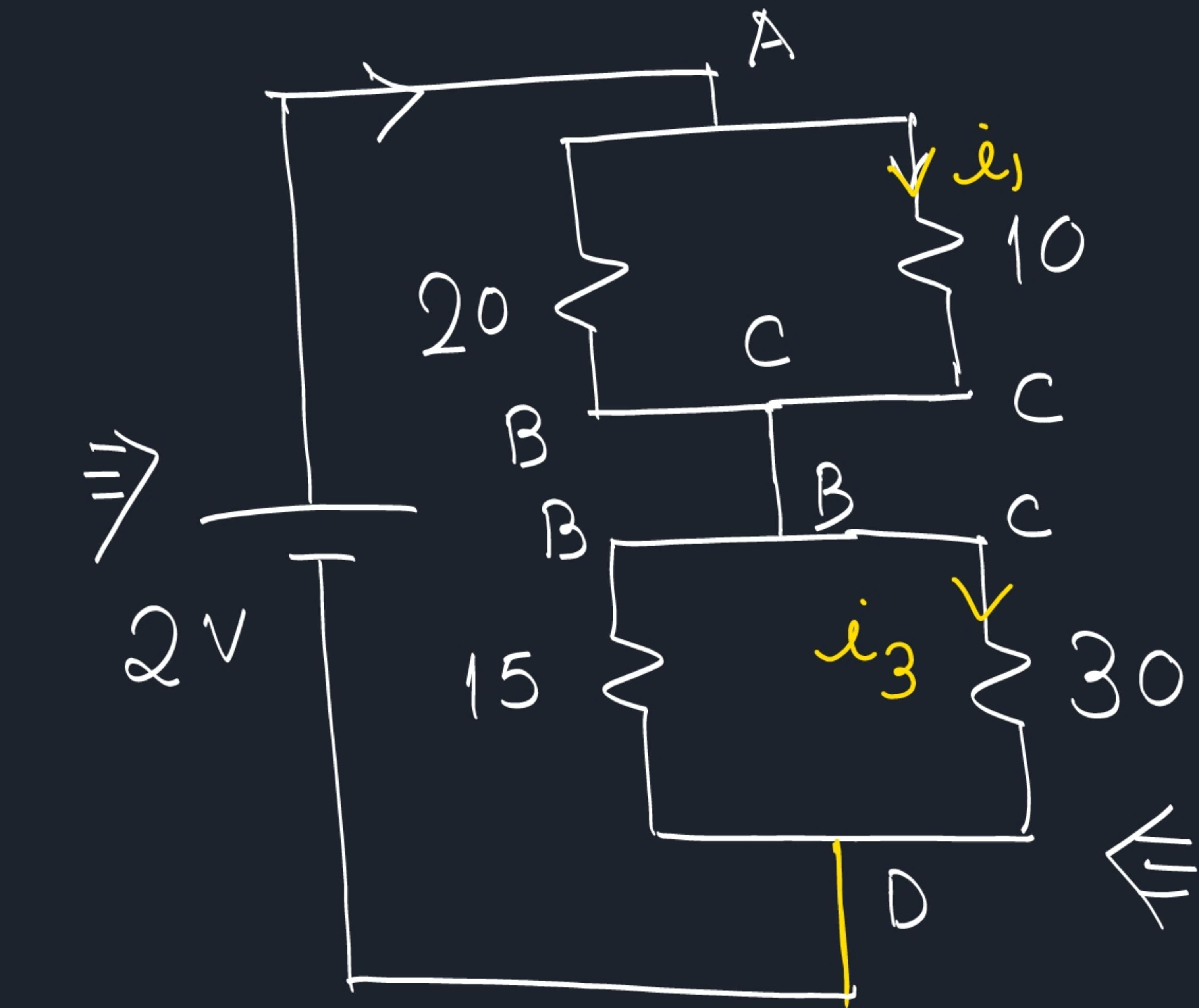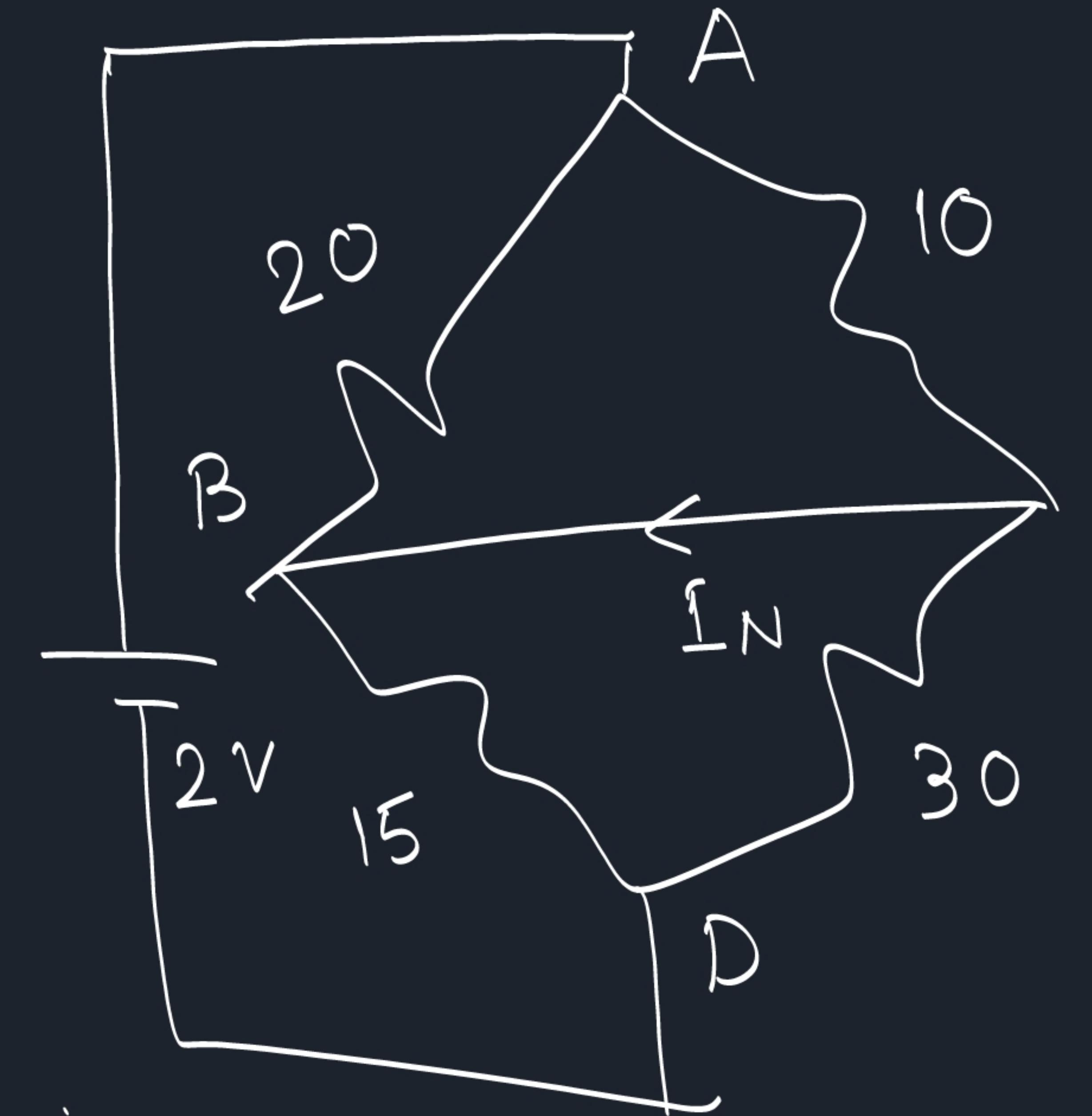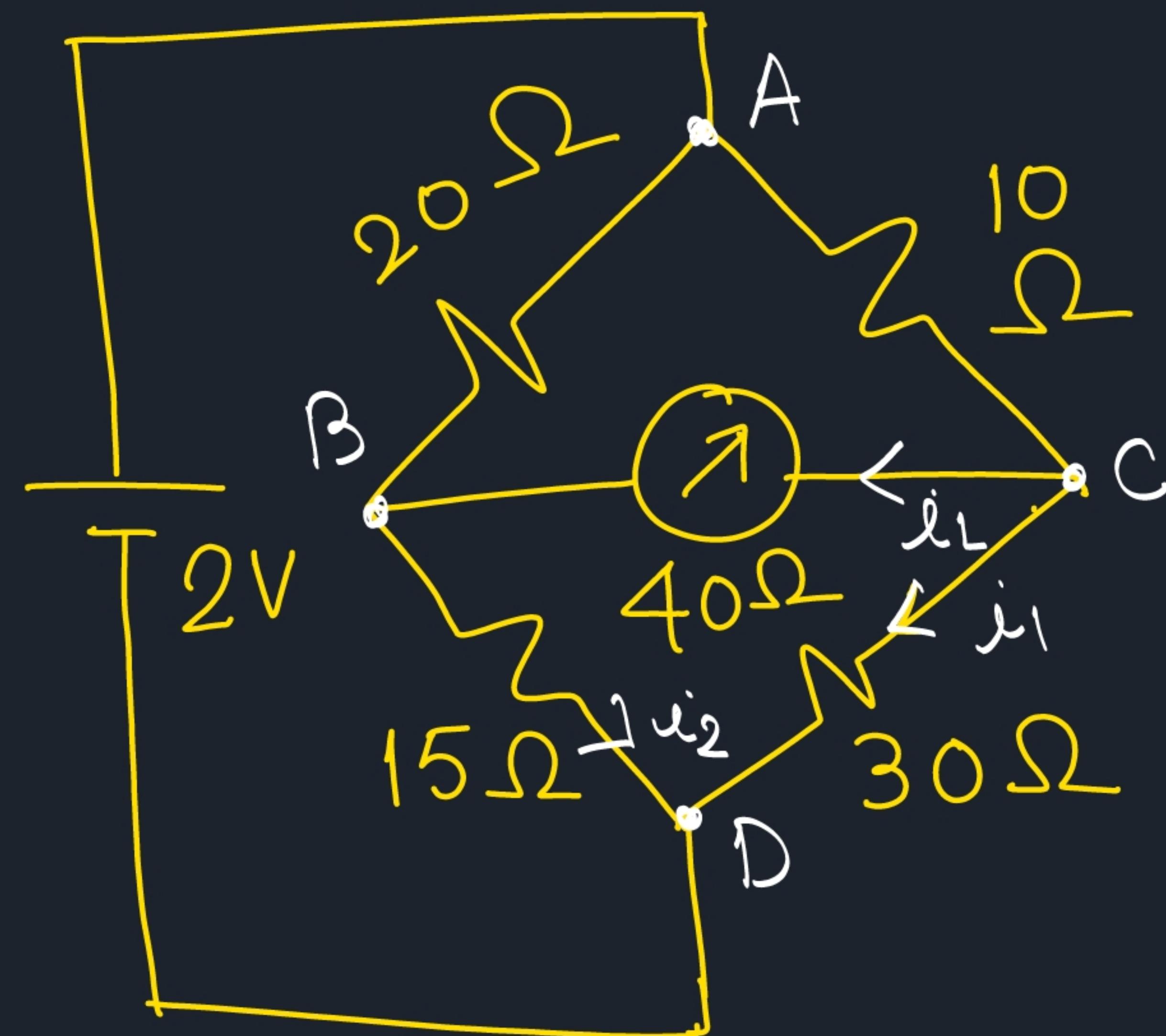


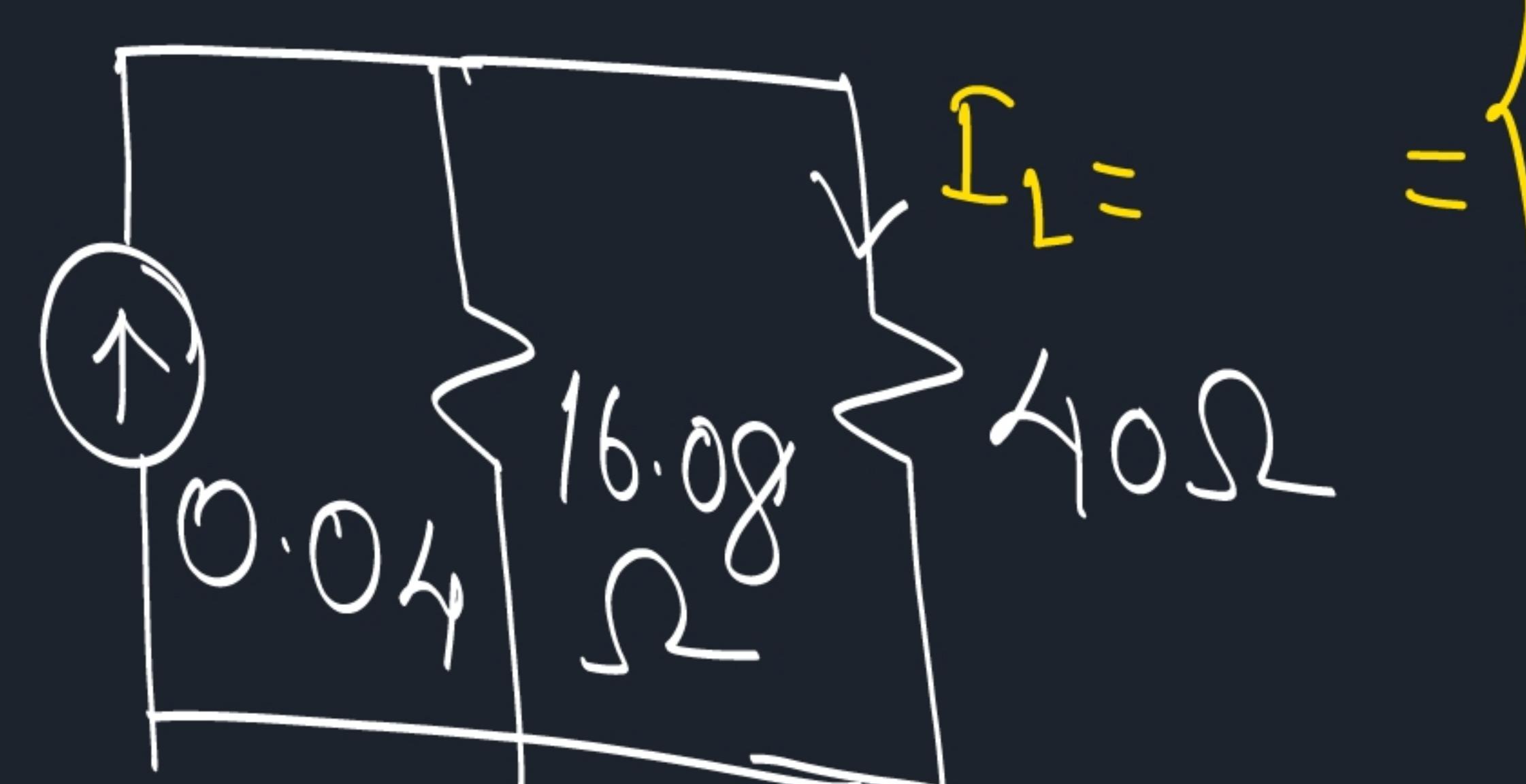
$$R_N = 16.08 \Omega \quad I_N = i_1 - i_3$$



$$I_L = \left\{ I \times \frac{20}{30} - I \times \frac{15}{45} \right\} = 0.04 \text{ Amp.}$$



$$I = \frac{2}{(20 \parallel 10) + (15 \parallel 30)} \text{ Amp} = 0.12 \text{ A}$$


Equivalent Resistance

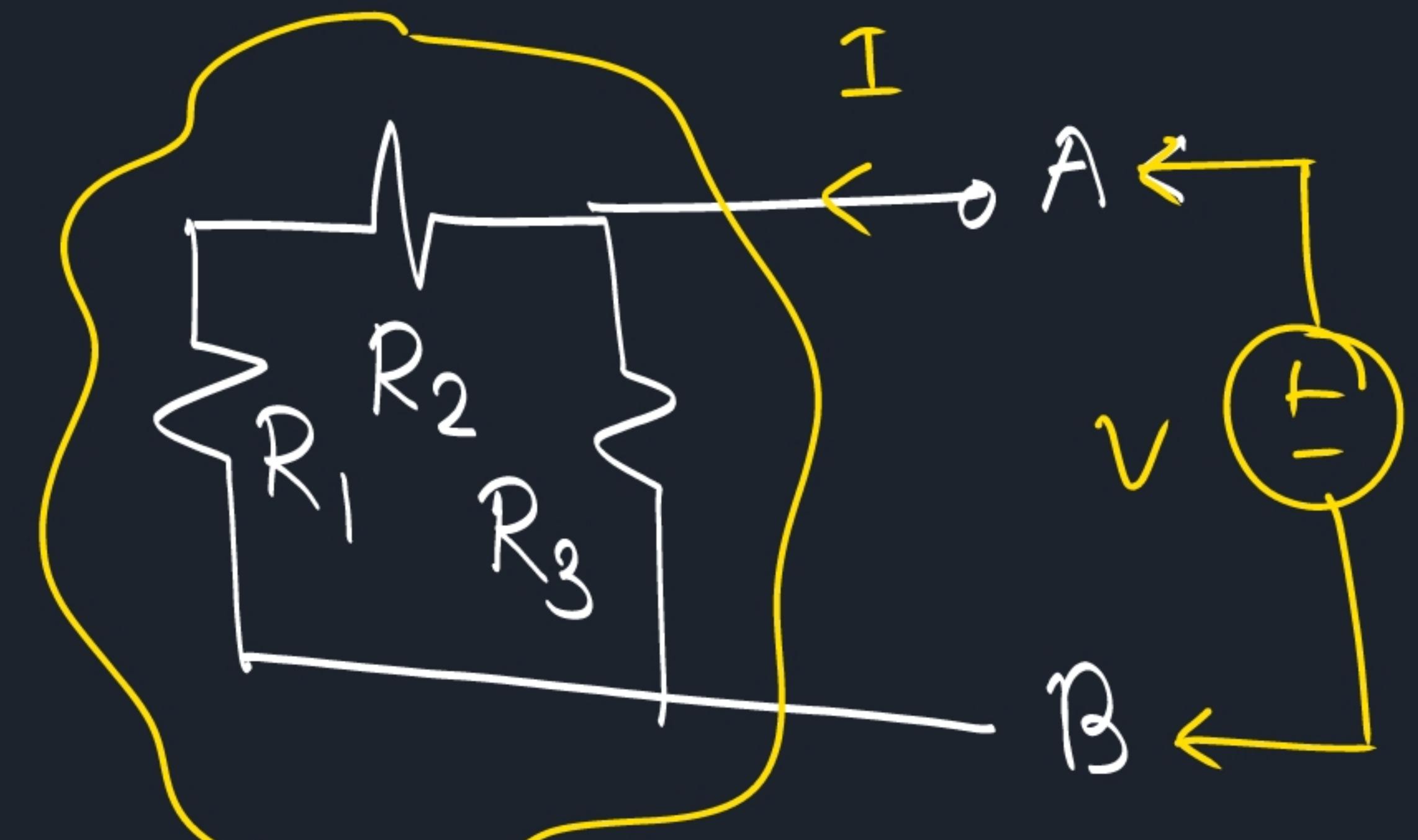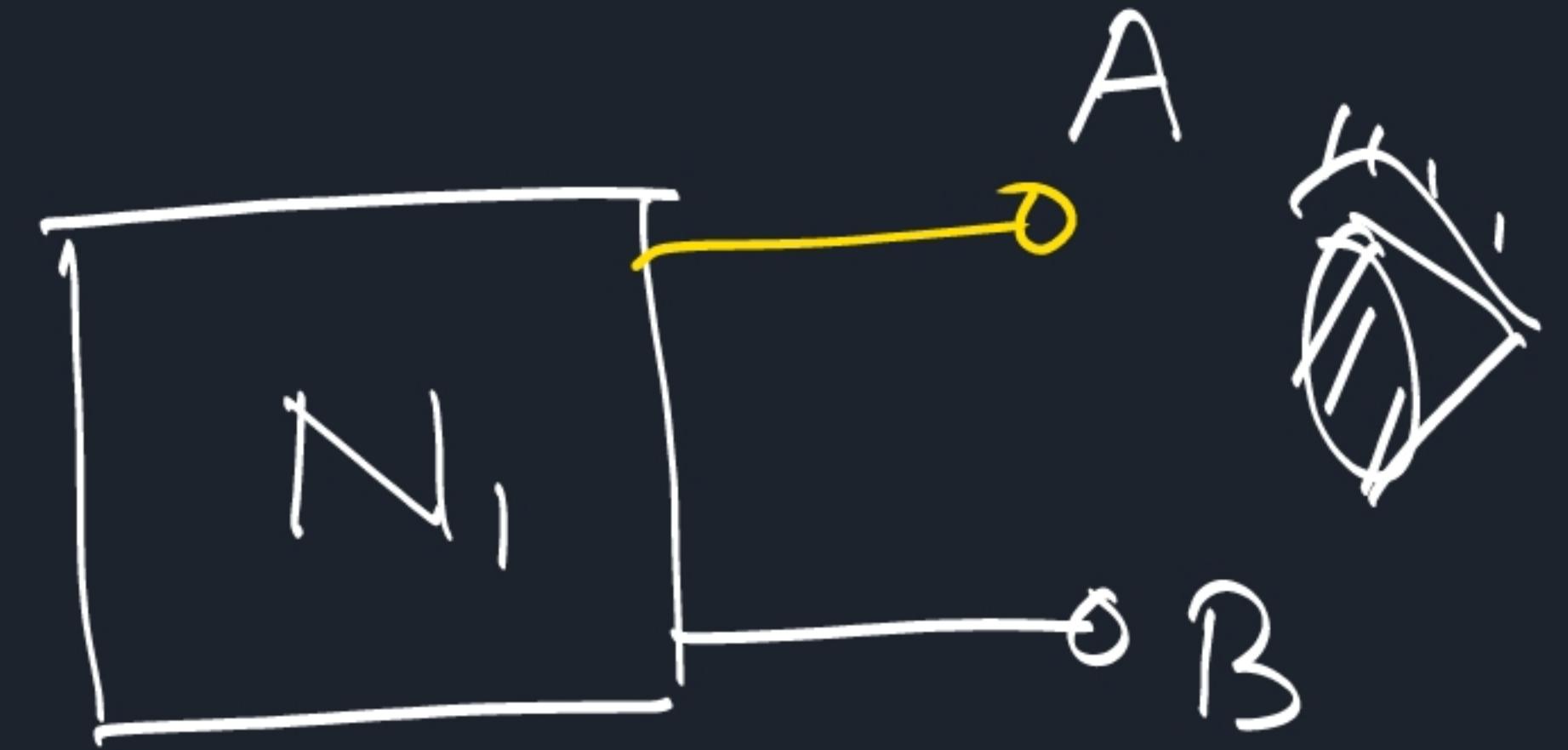

$$I = \frac{V}{R_1 + R_2} + \frac{V}{R_3}$$

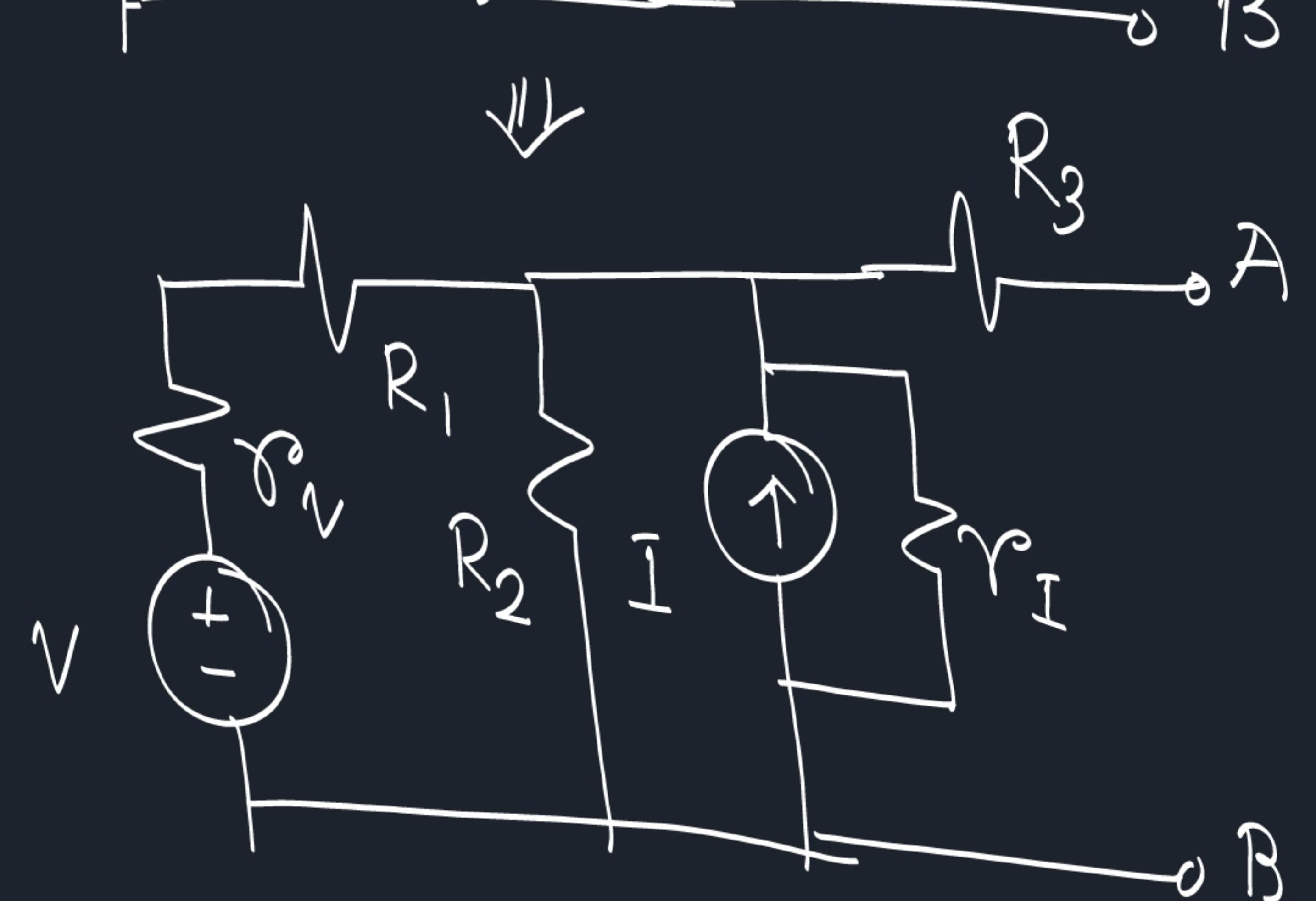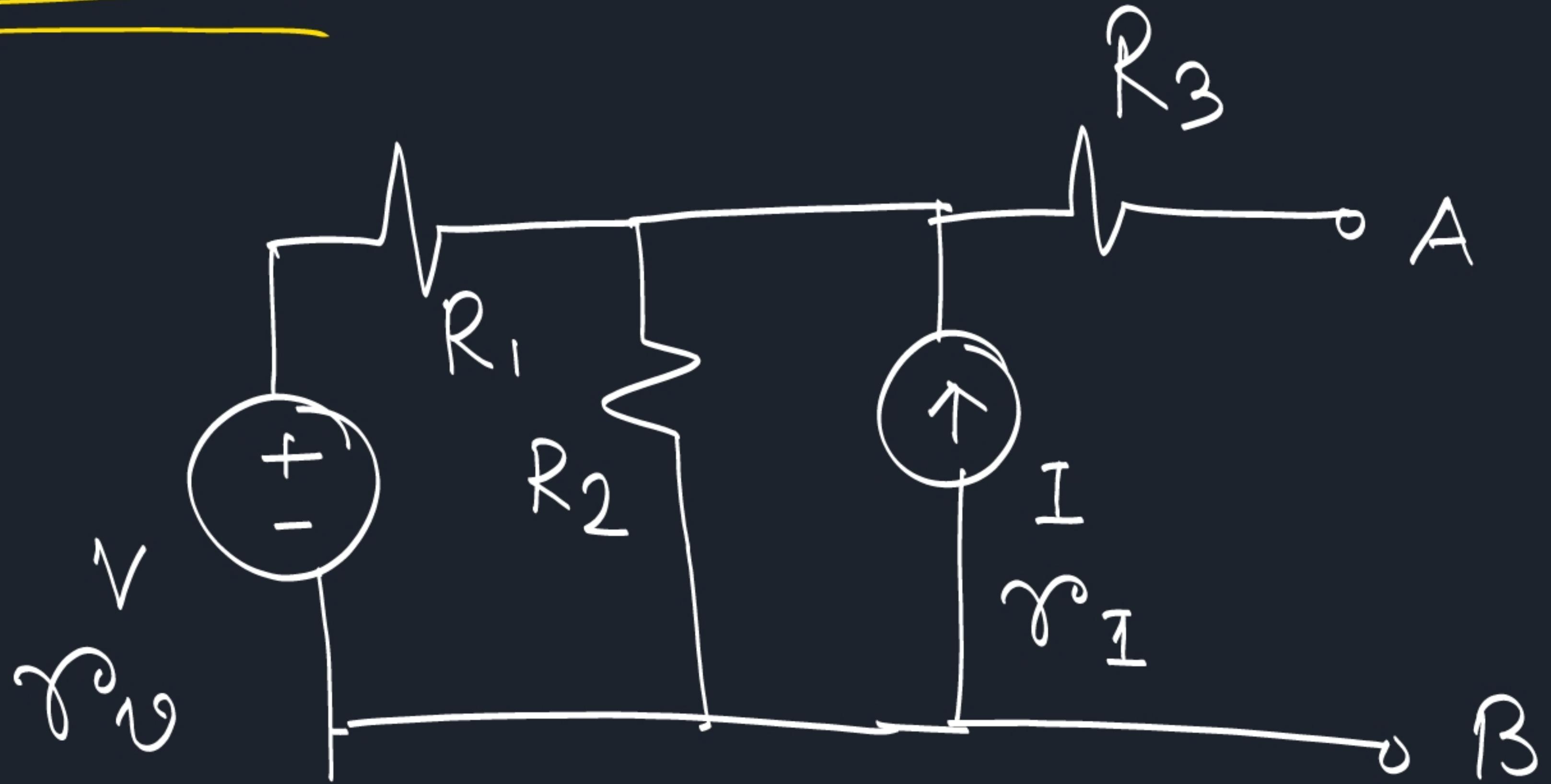
$$\frac{V}{I} = R_{eq} = \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{R_3}}$$



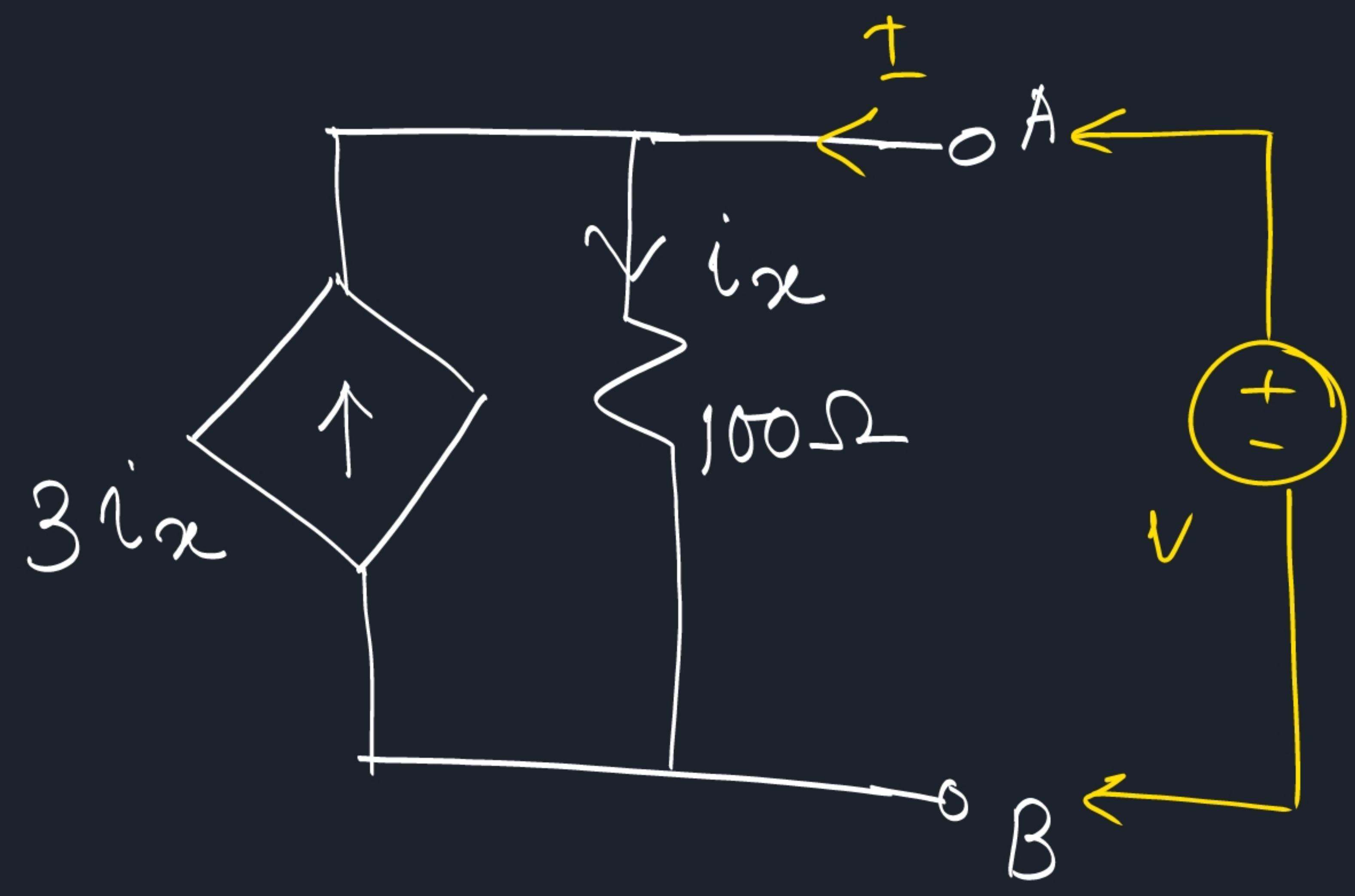

$$\begin{aligned}I &= i_x - 3i_x = -2i_x \\&= -\frac{2V}{100}\end{aligned}$$

$$\frac{V}{I} = -50 \Omega$$

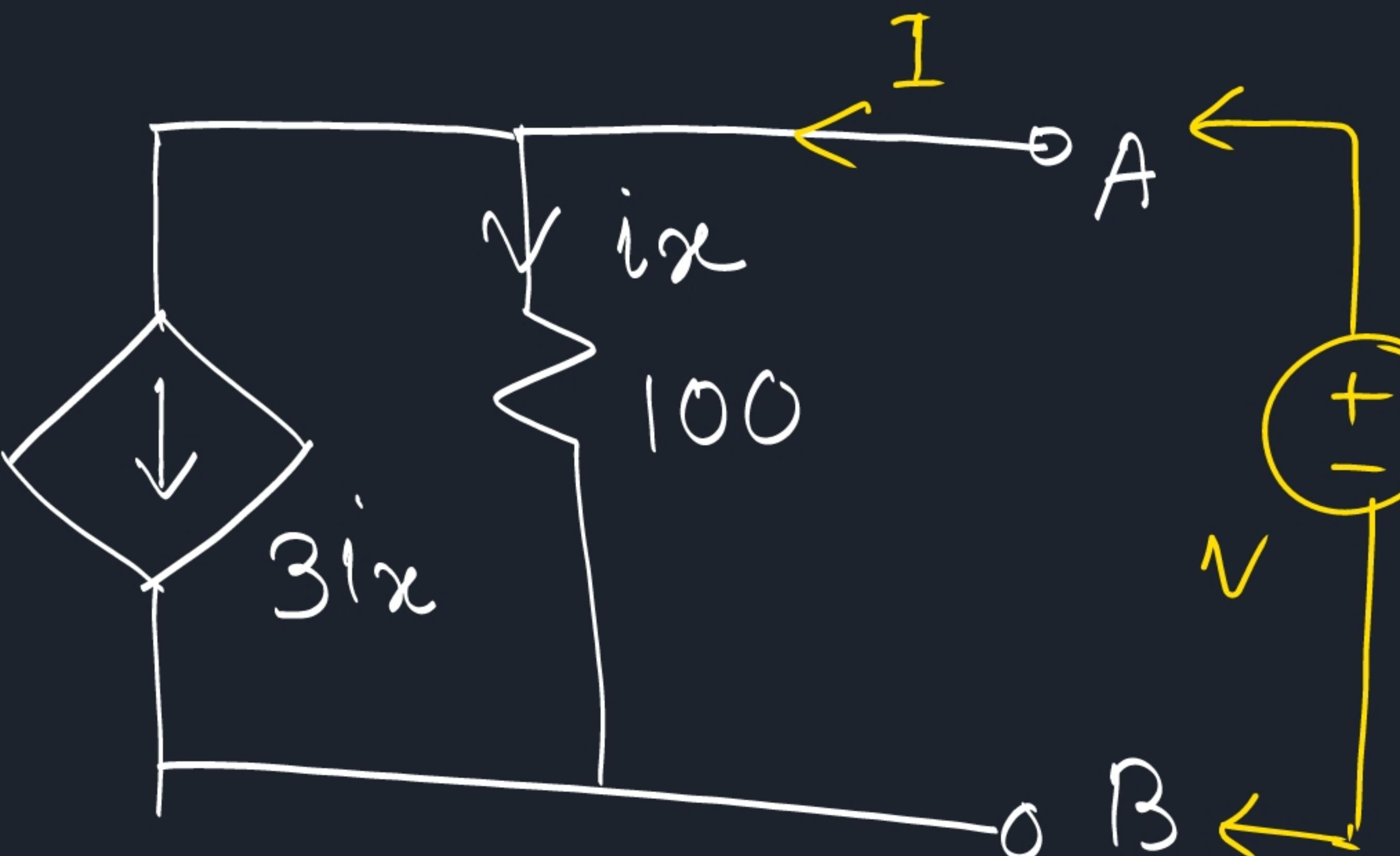


$$I = 3i_x + i_x$$

$$\begin{aligned}&= 4i_x \\&= \frac{4V}{100}\end{aligned}$$

$$\frac{V}{I} = 25 \Omega$$




Problem:-

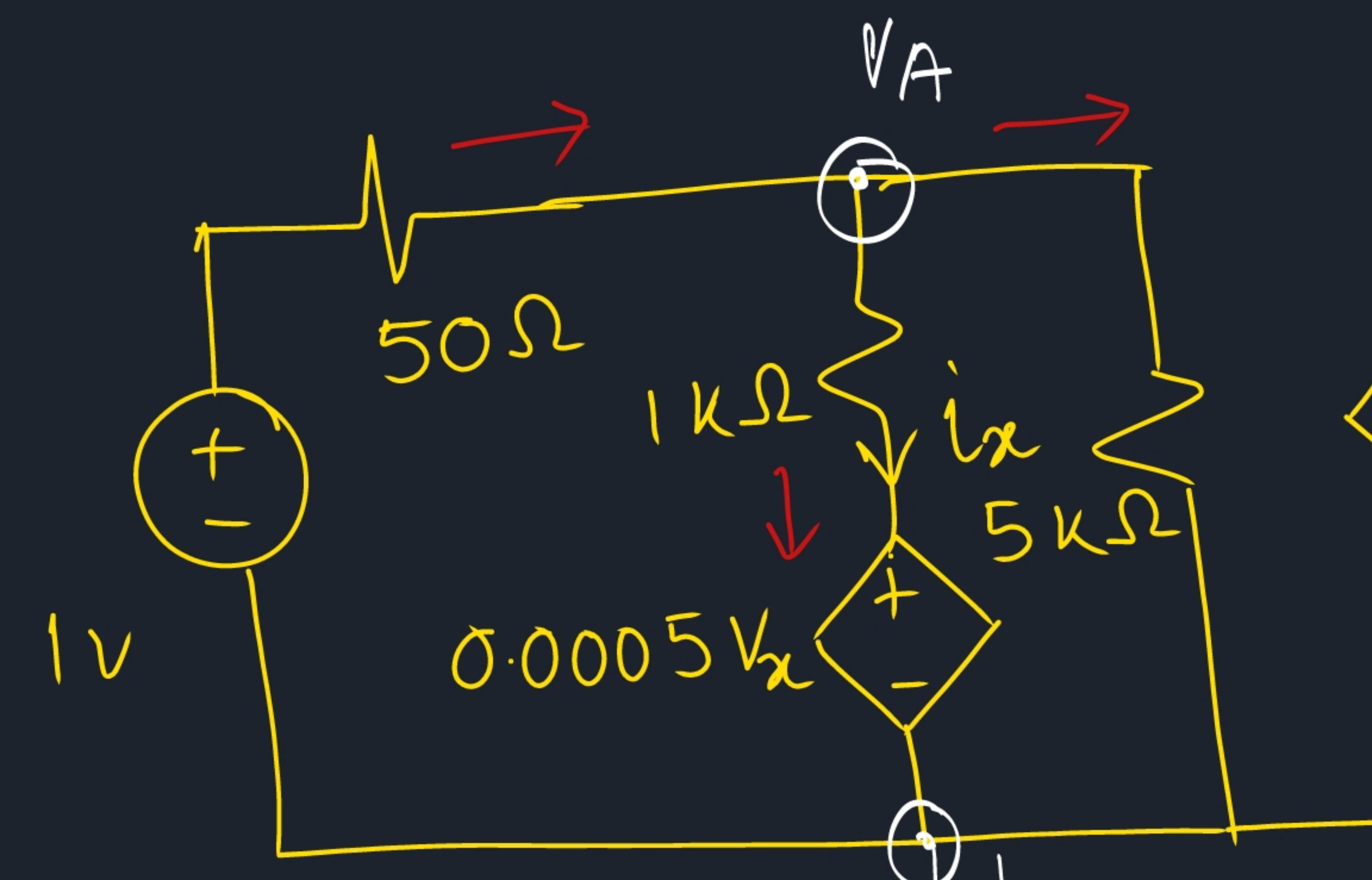

$$V_x = V_{1\text{H}}$$
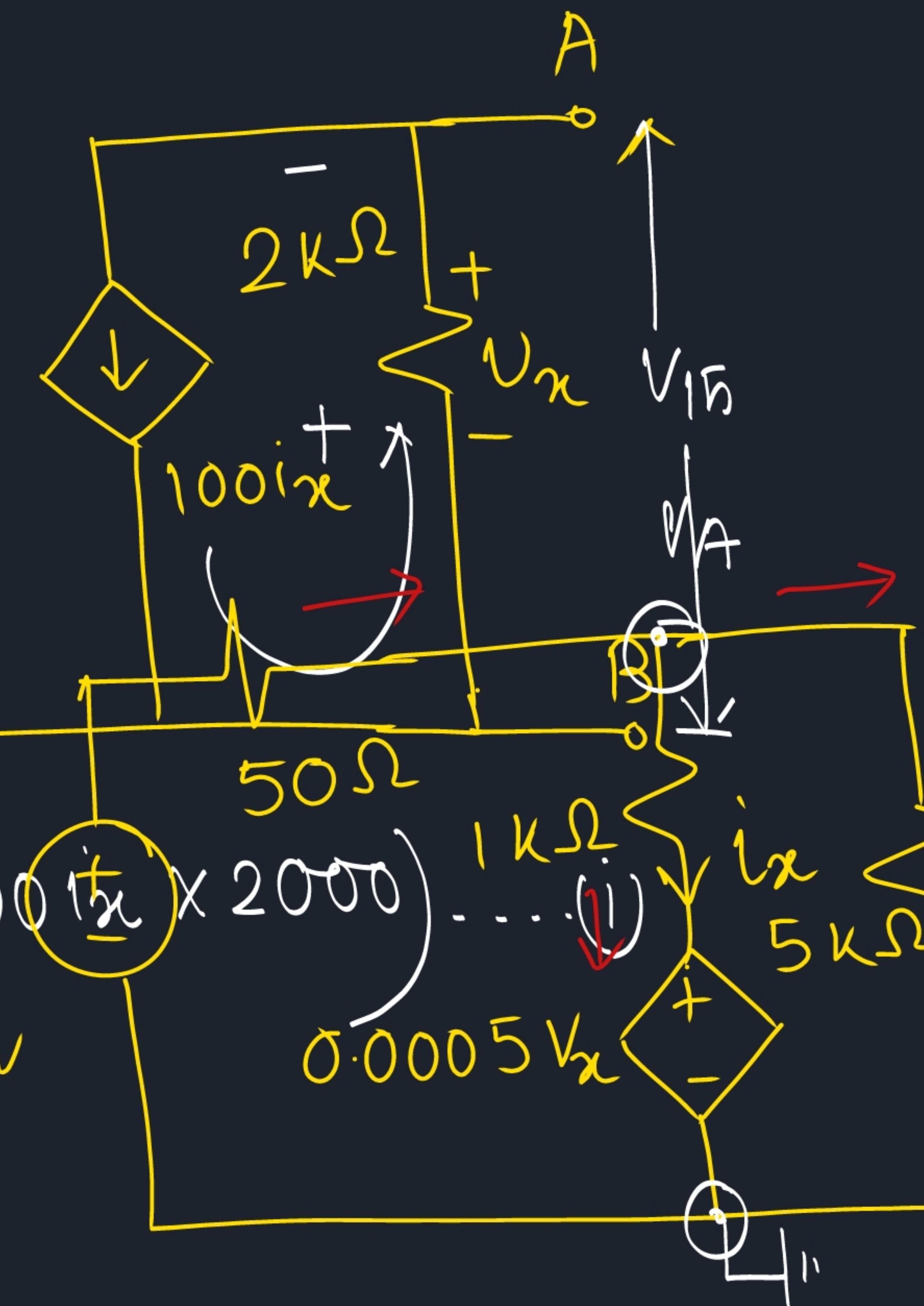
$$V_x = (-100i_x \times 2000) - 0.0005V_x$$





$$\frac{1 - V_A}{50} = \frac{V_A - 0.0005V_x}{1000} + \frac{V_A}{5000}$$

---(ii)

$$i_x = \frac{V_A - 0.0005V_x}{1000}$$
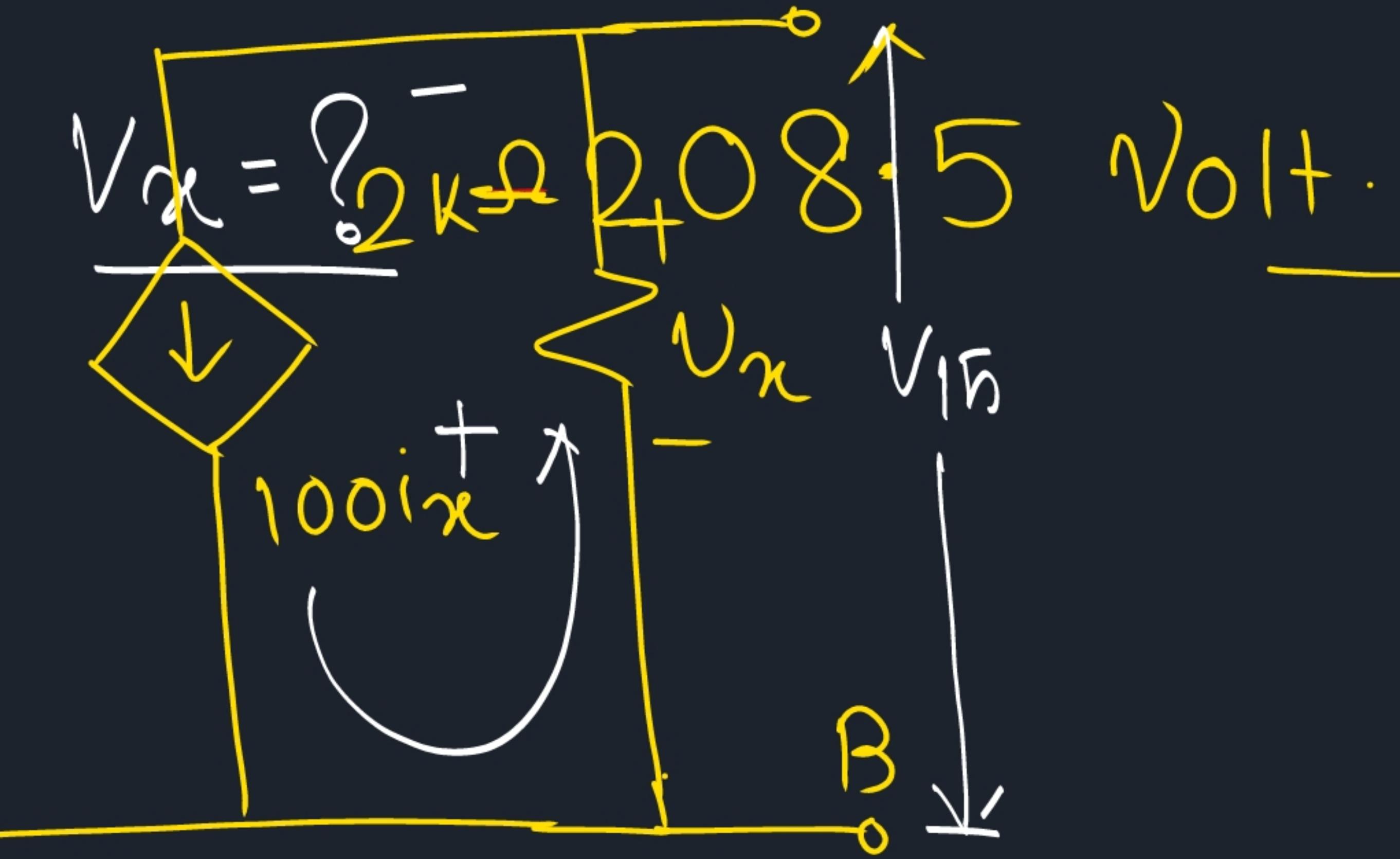
$$\Rightarrow V_A = 1000i_x + 0.0005V_x \quad \dots \text{(iii)}$$



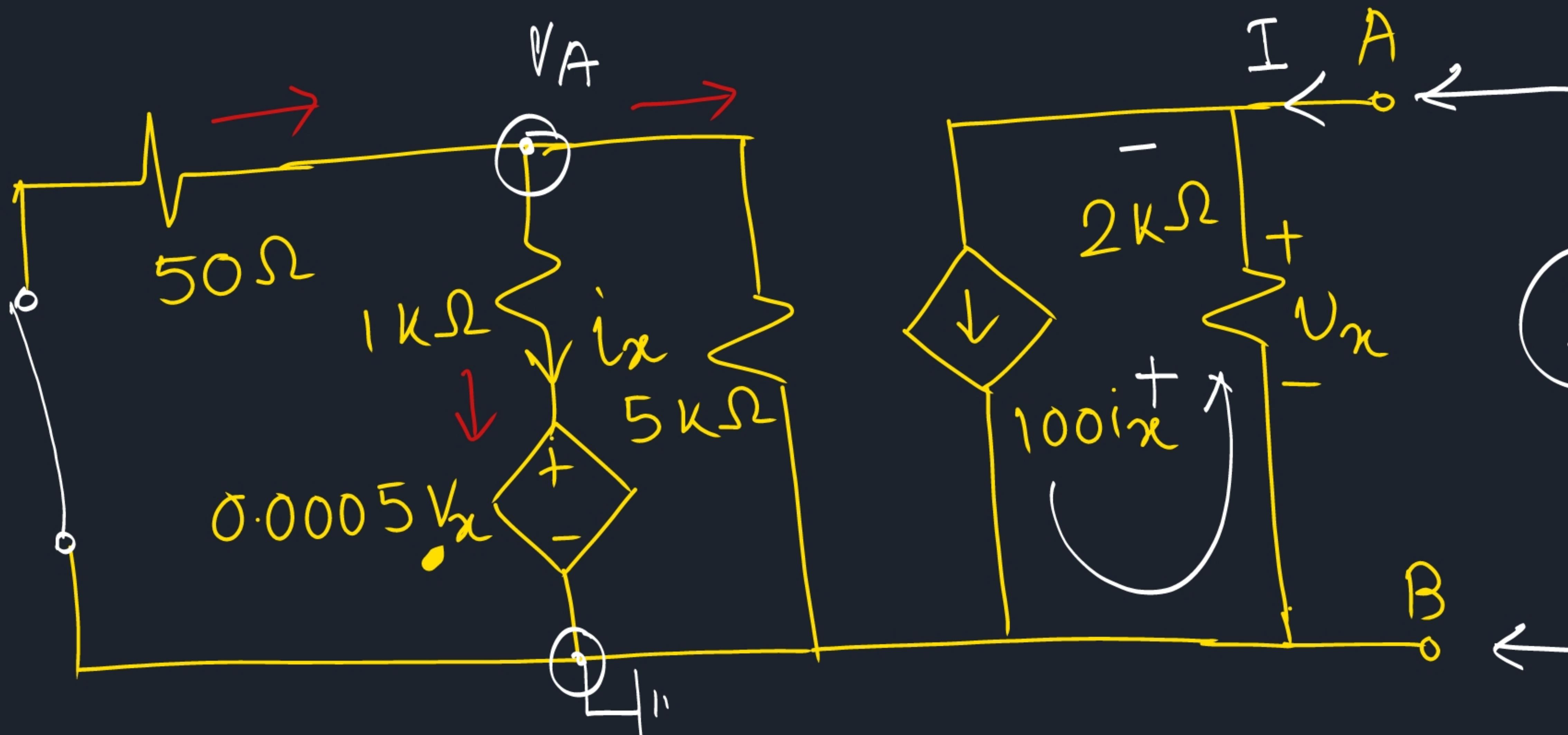

$\frac{V}{I} = R_{th}$ = Internal equiv. Resistance
from A-B terminal

$$V_x = V$$

$$I = \frac{V}{2000} + 100ix \quad \dots \text{(i)}$$

$$\frac{0 - V_A}{50} = \frac{V_A}{5000} + \frac{V_A - 0.0005V}{1000}$$

$$ix = \frac{V_A - 0.0005V}{1000} \quad \dots \text{(ii)}$$



$$\frac{0.0005}{1000} V = V_A \left(\frac{1}{1000} + \frac{1}{5000} + \frac{1}{50} \right) \quad \dots \text{(iii)}$$

$$\boxed{\frac{V}{I} = ?}$$

$2.21 \text{ k}\Omega$

$$\frac{I}{V} = \frac{1}{2000} + 100 \left(\frac{ix}{V} \right)$$

Max. Power Transfer Theorem:-

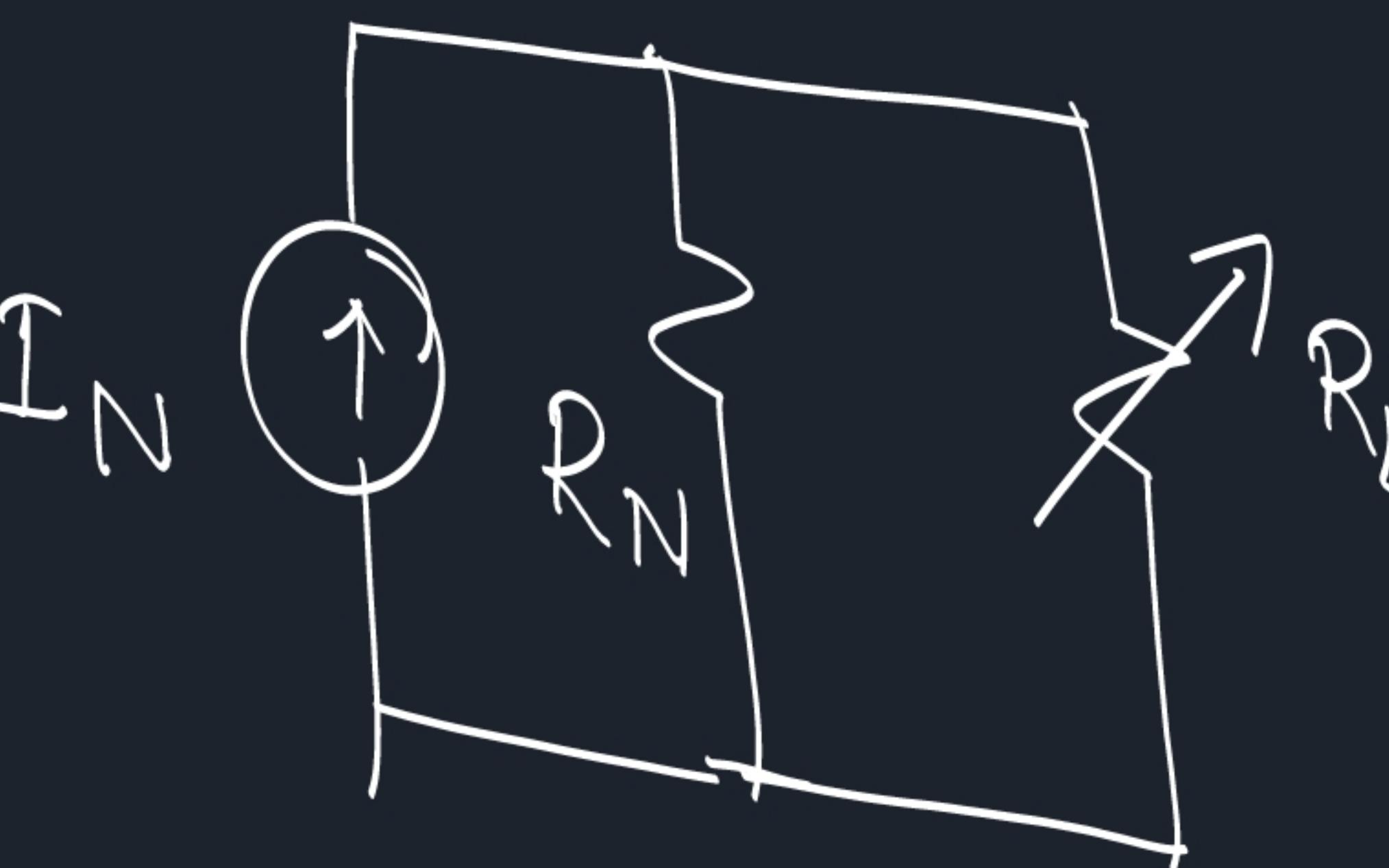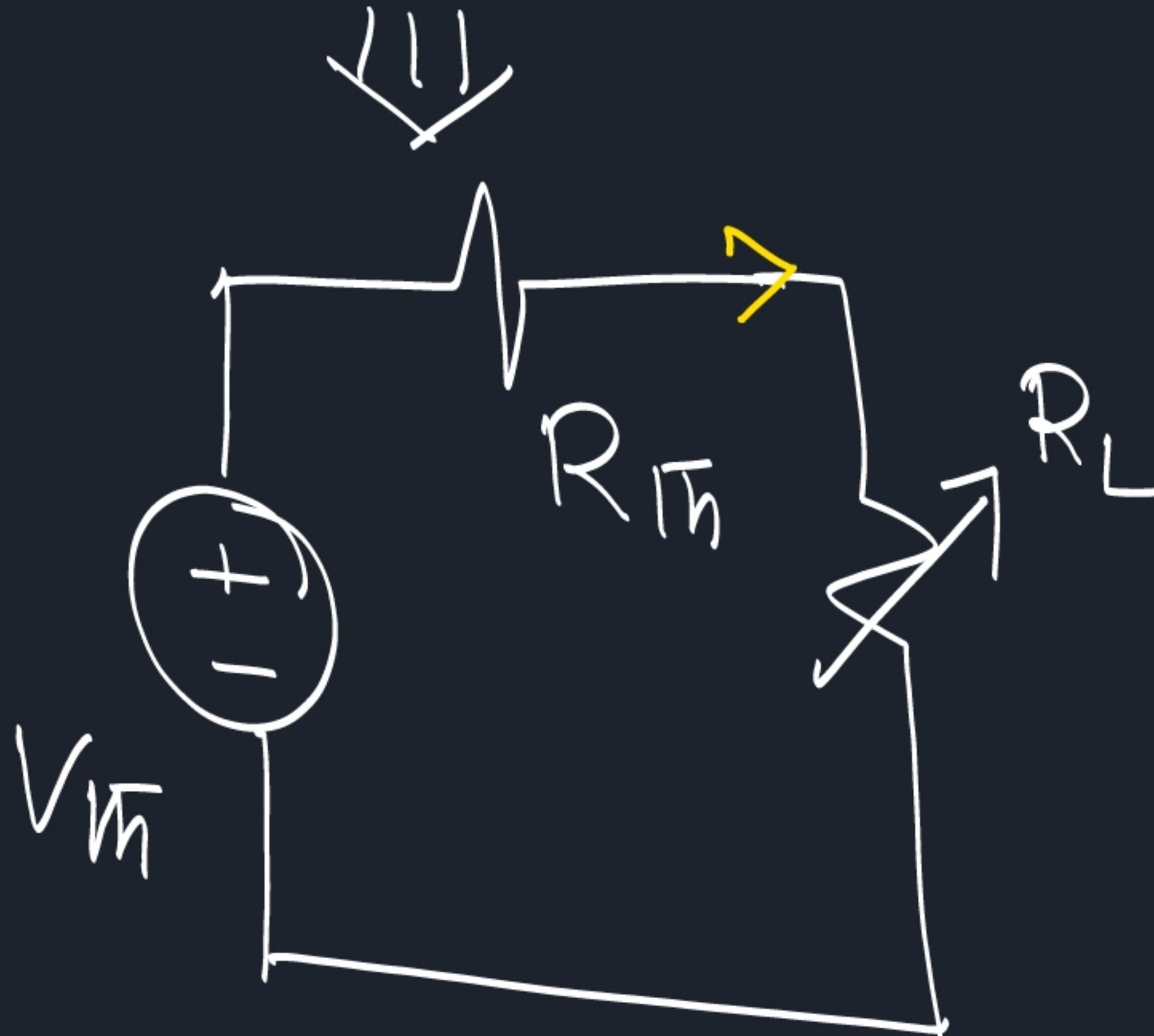



$$I_L = \frac{V_{Th}}{(R_{Th} + R_L)}$$

$$P_L = I_L^2 R_L$$

$$= \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$
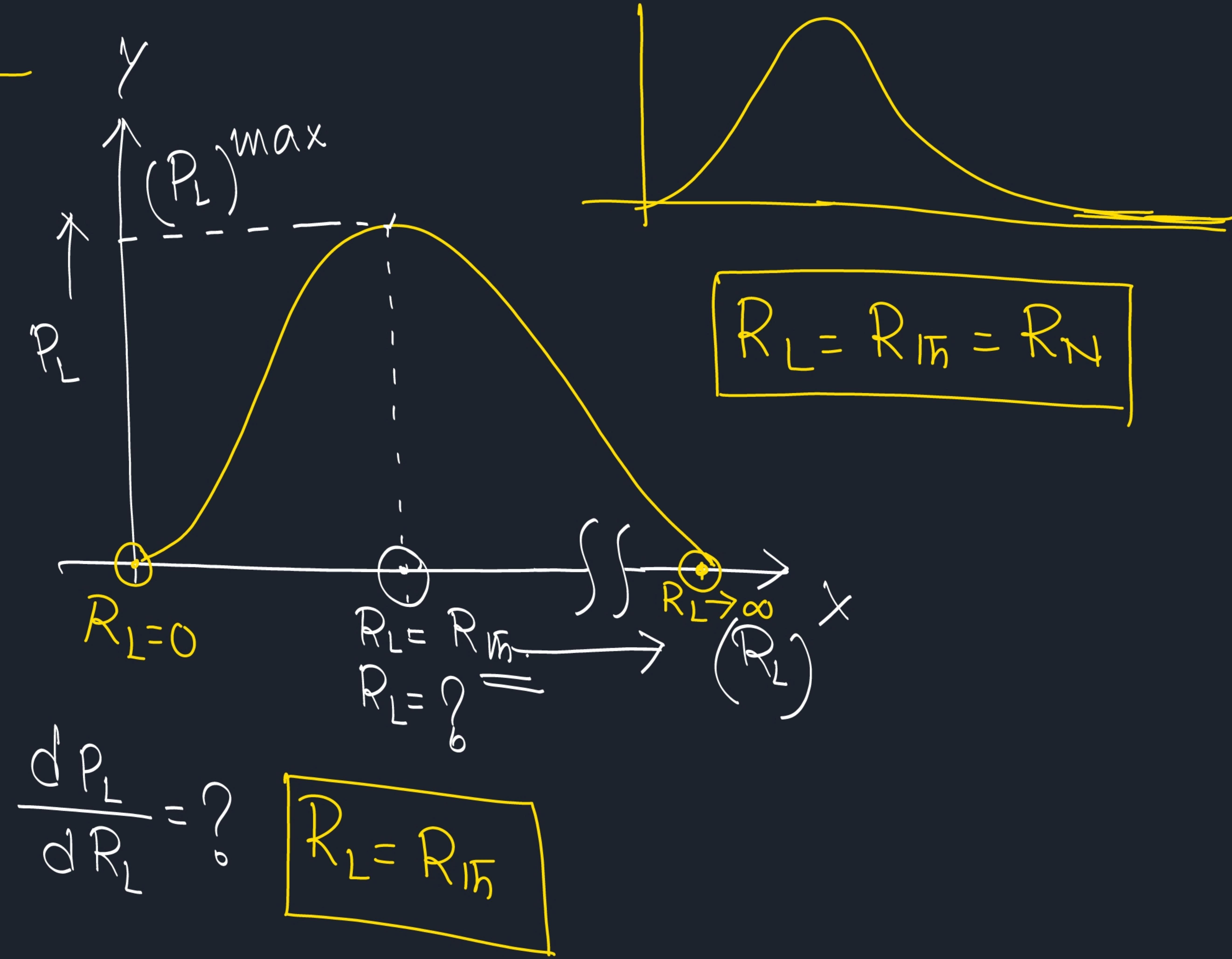
$$(P_L)^{\max} = \frac{V_{Th}^2}{4R_{Th}}$$




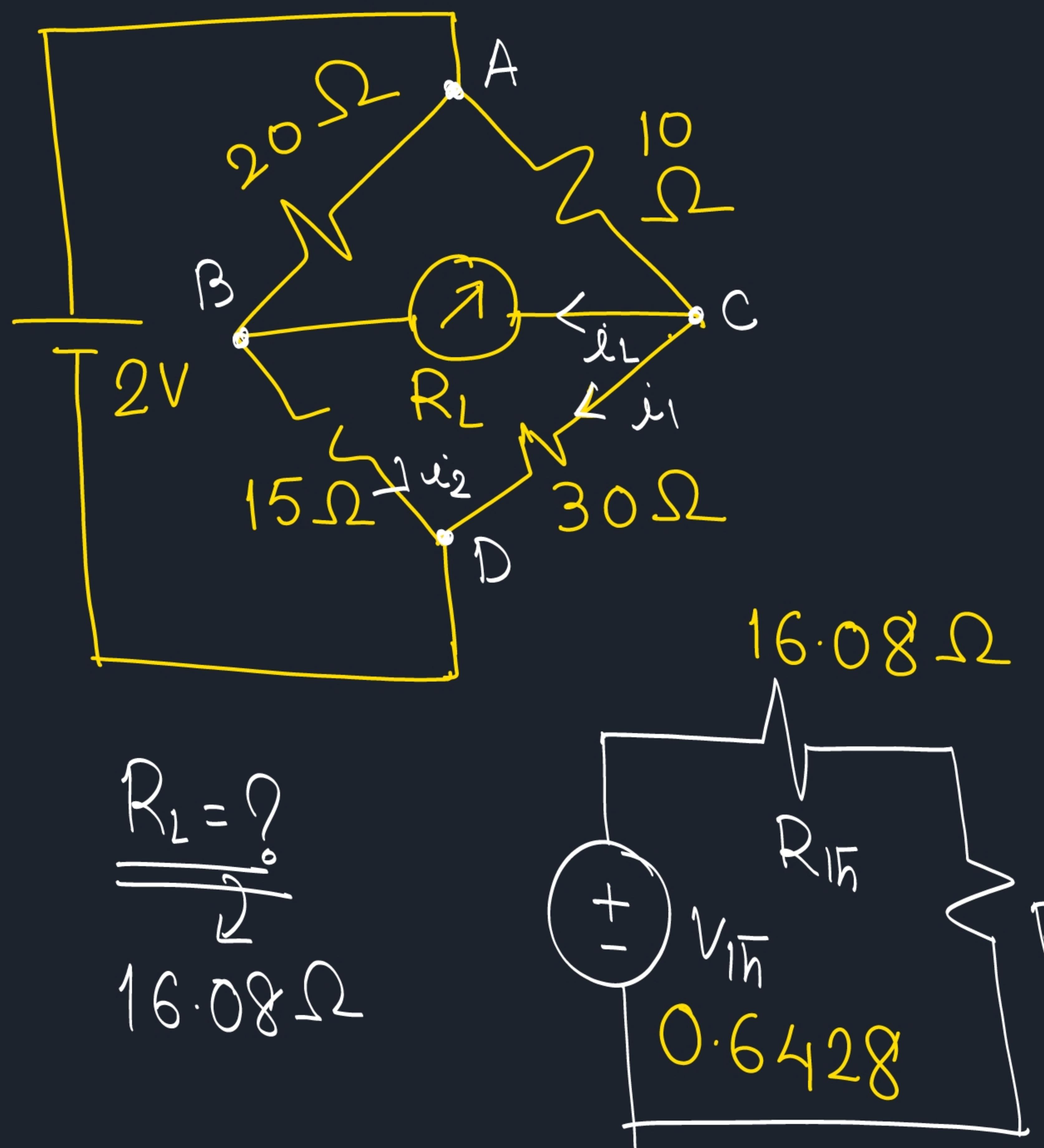

$$\begin{aligned}
 & \frac{(V_{Th})^2}{4R_{15}} \\
 &= \left\{ \frac{0.6428^2}{4 \times 16.08} \right\} \text{ Watt} \\
 &= \underline{6.428 \text{ mW}}
 \end{aligned}$$

Problem:-


$R_L = ?$ for max power transfer. I

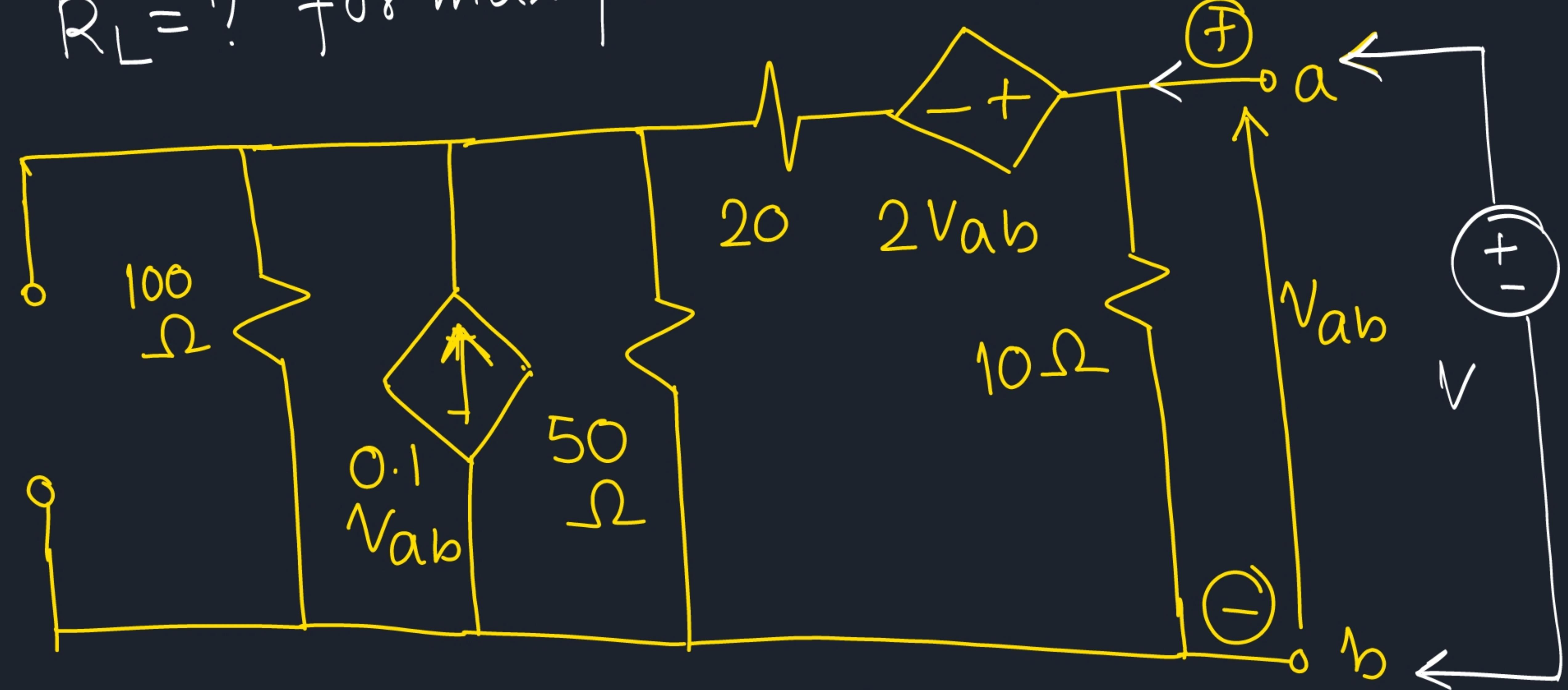


Test Source Method.

$$I = i_1 + i_2 \\ = \frac{V}{10} + \frac{V - 2V - 10/3V}{100/3 + 20}$$
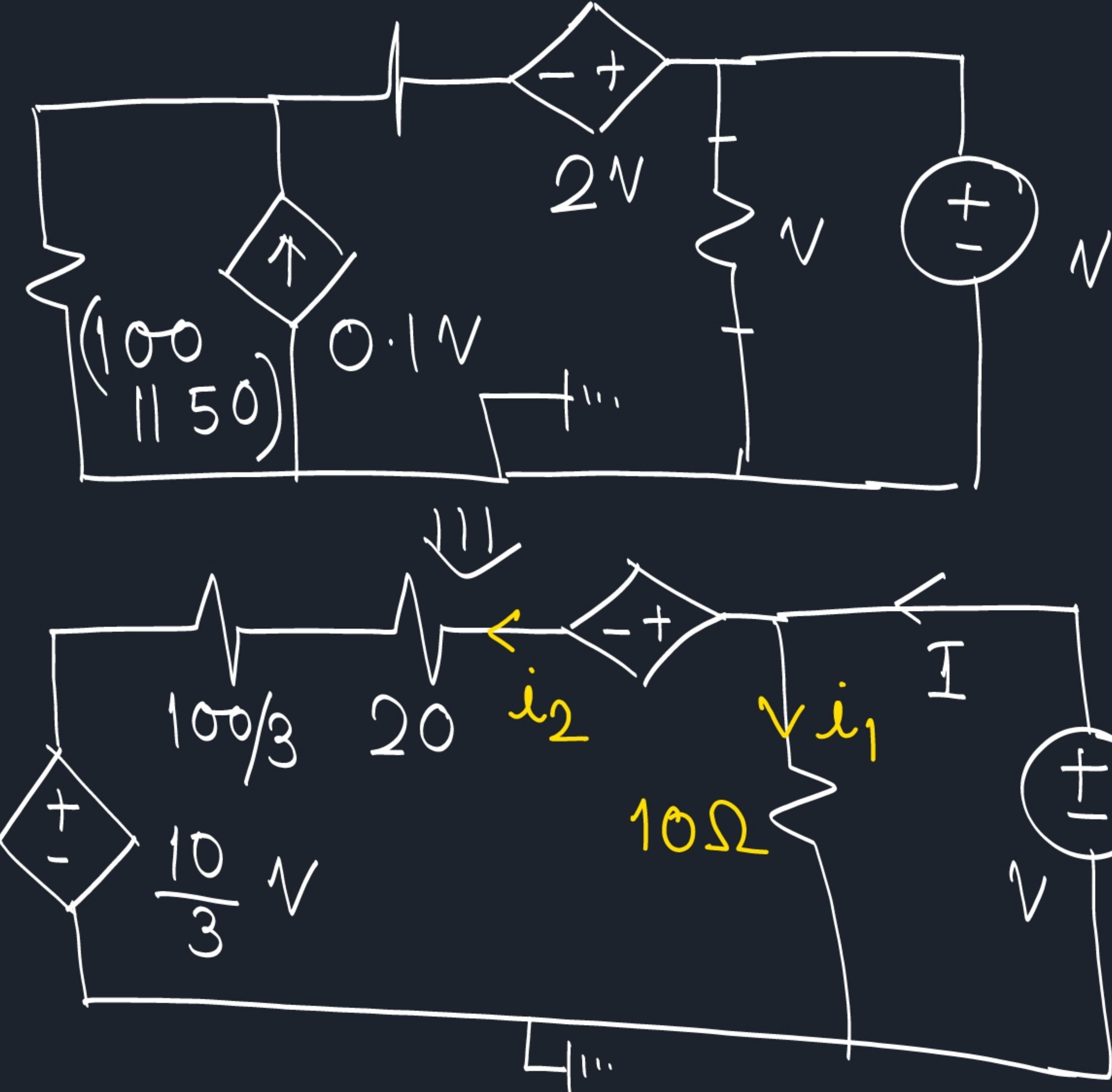
$$\left(\frac{V}{I}\right) = ? \boxed{53.33 \Omega}$$




Problem:-

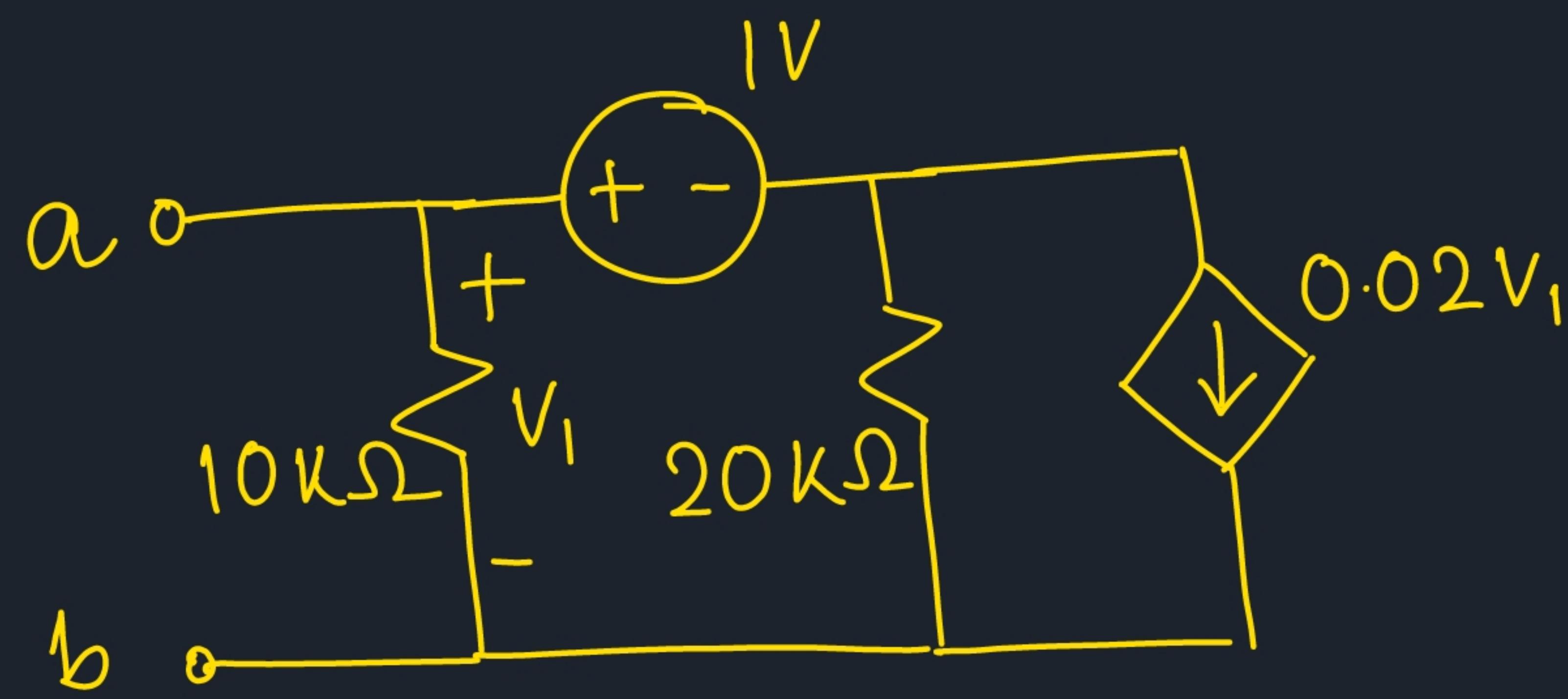

i) Find Power dissipated when
1 kΩ resistance is connected
b/w a-b terminal

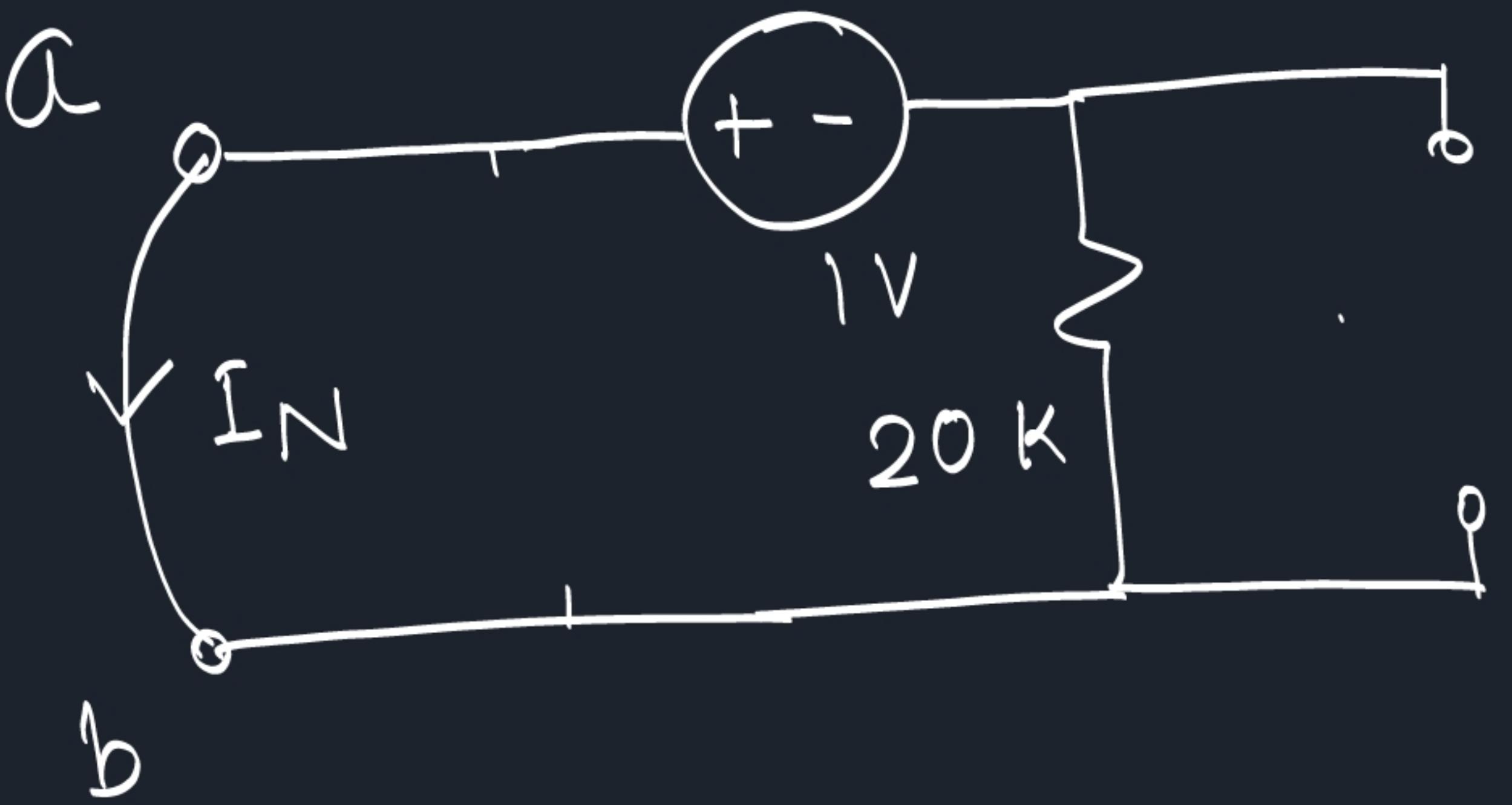ii) Find max power extracted
from the ckt.



$$I_N = \frac{1}{20 \times 10^3} \text{ Amp}$$



$$I = i_1 + i_2 \\ = \frac{V}{10,000} + \frac{V + (0.02 \times 20 \times 10^3)V}{20,000}$$

$$\left(\frac{V}{I}\right) = ?$$

