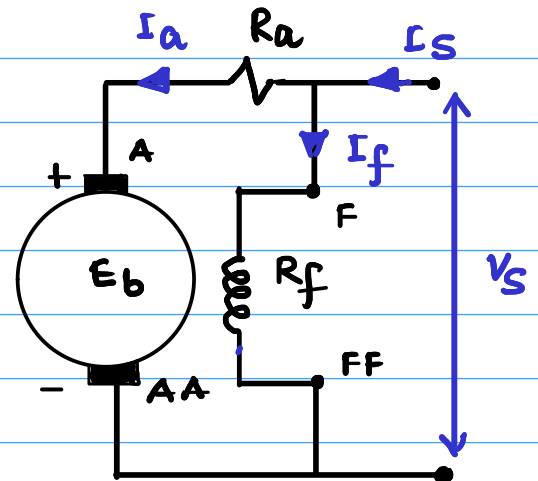


Shunt DC Motor :-

$$V_s = E_b + I_a R_a + 2V_{brush}$$

$$E_b = \frac{\Phi Z N (P)}{60} \left(\frac{P}{A} \right)$$

$$I_s = I_f + I_a$$




Gross Mechanical Power Developed $\Rightarrow P_{gross} = E_b I_a$

Shaft power developed $\Rightarrow P_{shaft} = P_{gross} - P_{mech}$

$$\tau_{gross} = \frac{P_{gross}}{\omega}$$

$$\tau_{shaft} = \frac{P_{shaft}}{\omega}$$
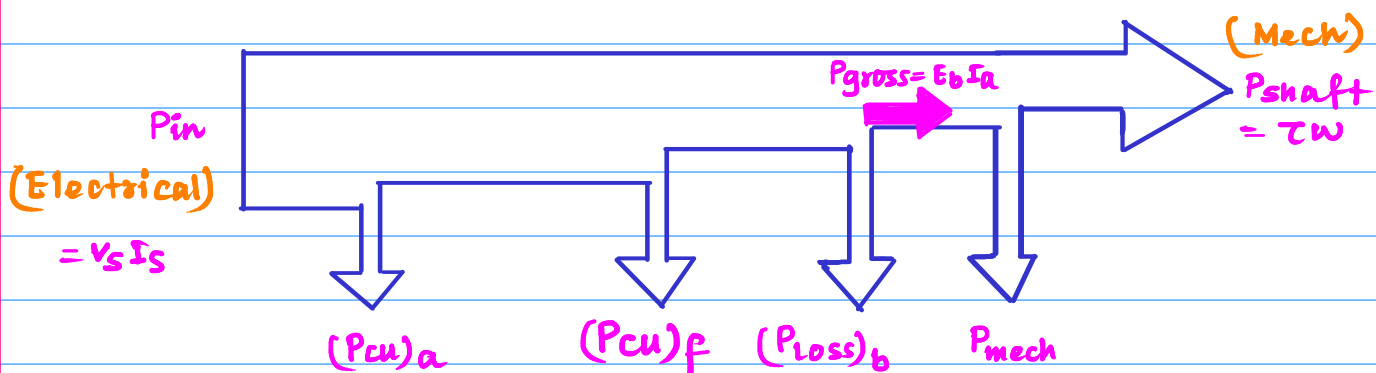
$$\omega = \frac{2\pi N}{60} \text{ rad/sec.}$$




Power flow diagram of DC shunt motor

Efficiency for DC Motor

$$= \frac{P_{out}}{P_{in}} \times 100$$

$$= \frac{P_{out}}{P_{out} + (P_{cu})_a + (P_{loss})_b + (P_{cu})_f + P_{mech}} \times 100 \%$$

Series DC Motor :-

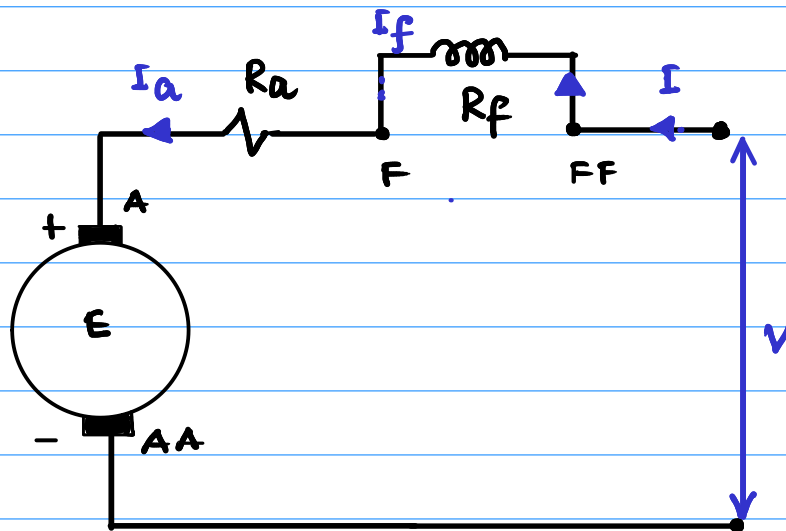

$$V_s = E_b + I_a (R_a + R_f) + 2V_{brush}$$

$$E_b = \frac{\Phi Z N (P)}{60 (A)}$$

$$I_a = I_f = I_s$$

Gross mechanical power generated $P_{\text{gross}} = E_b I_a$

$$(P_{\text{cu}})_a = I_a^2 R_a$$

$$(P_{\text{cu}})_f = I_f^2 R_f = I_a^2 R_f$$

$$\omega = \frac{2\pi N}{60} \text{ rad/sec}$$

$N = \text{Speed in RPM}$

$$(P_{\text{loss}})_b = 2V_{\text{brush}} I_a$$


$P_{\text{mech}} = \text{Friction and windage loss}$

Shaft power developed $\Rightarrow P_{\text{shaft}} = P_{\text{gross}} - P_{\text{mech}}$

$$\tau_{\text{gross}} = \frac{P_{\text{gross}}}{\omega}$$

$$\tau_{\text{shaft}} = \frac{P_{\text{shaft}}}{\omega}$$
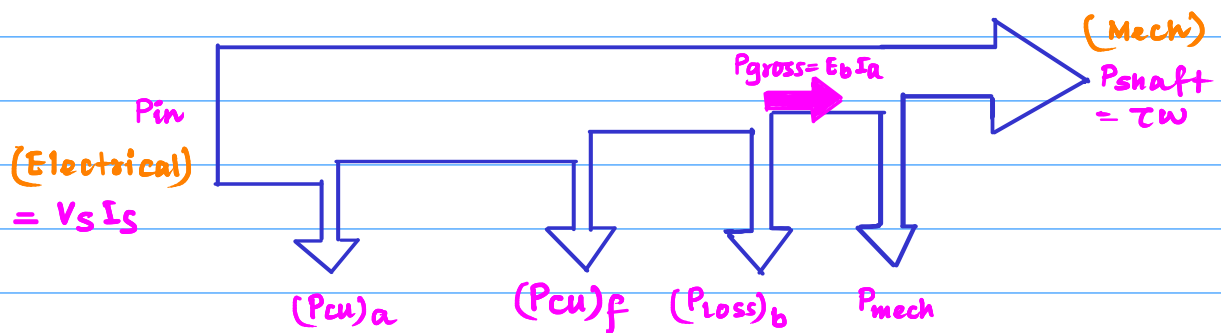
$$\omega = \frac{2\pi N}{60} \text{ rad/sec.}$$



Power flow diagram of DC Series Motor

Efficiency for DC Series Motor

$$= \frac{P_{\text{out}}}{P_{\text{in}}} \times 100$$

$$= \frac{P_{\text{out}} \times 100}{P_{\text{out}} + (P_{\text{cu}})_a + (P_{\text{loss}})_b + P_{\text{mech}} + (P_{\text{cu}})_f} \%$$

Problem:-

4 pole 220 V shunt motor has 540 lap-wound conductors.

Motor rating $\Rightarrow 5.595 \text{ kW}$

$$I_f = 1 \text{ A}$$

$$I_a = 32 \text{ A}$$

$$R_a = 0.09 \Omega$$

$$\phi = 30 \text{ mwb}$$

Calculate speed and torque developed in shaft.

Sol:-

$$E_b = V_t - I_a R_a = ?$$

$$N = ?$$

$$T_{sh} = \frac{P_{shaft}}{\frac{2\pi N}{60}} = ?$$

⊙ Problem :-

A 500 V DC shunt motor takes a current of 5 A at no load.

$$R_a = 0.22 \, \Omega \quad R_f = 250 \, \Omega$$

Find efficiency when taking a current of 100 A.

Soln :-