

 DC M/C :-

1. Fleming's Right Hand Rule }  $\rightarrow$  Induced Emf Dir?

2. " Left Hand Rule }


$$(\vec{E} = l \vec{v} \times \vec{B})$$

Charge: 

$\{ l \cdot \vec{v} \times \vec{B}$

Velocity Magnetic Flux Density

Velocity M.F.D.

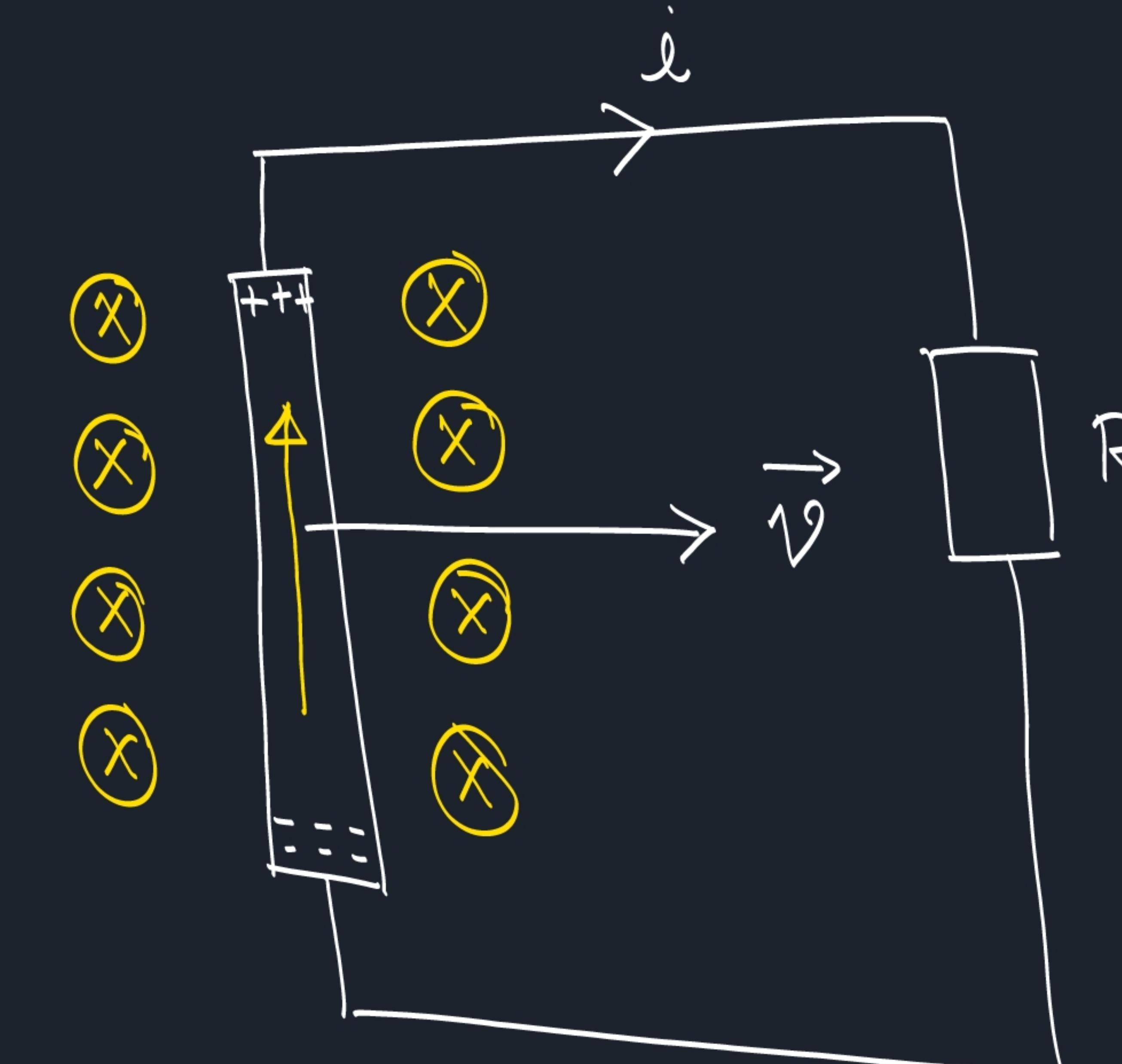

$$i = \frac{Blus \sin\theta}{R}$$


$$\boxed{i = \frac{Blu}{R}}$$

Flemings Left Hand Rule:-


$$d\vec{F} = i d\vec{l} \times \vec{B}$$

$$\underline{\underline{F = i l \times B}}$$

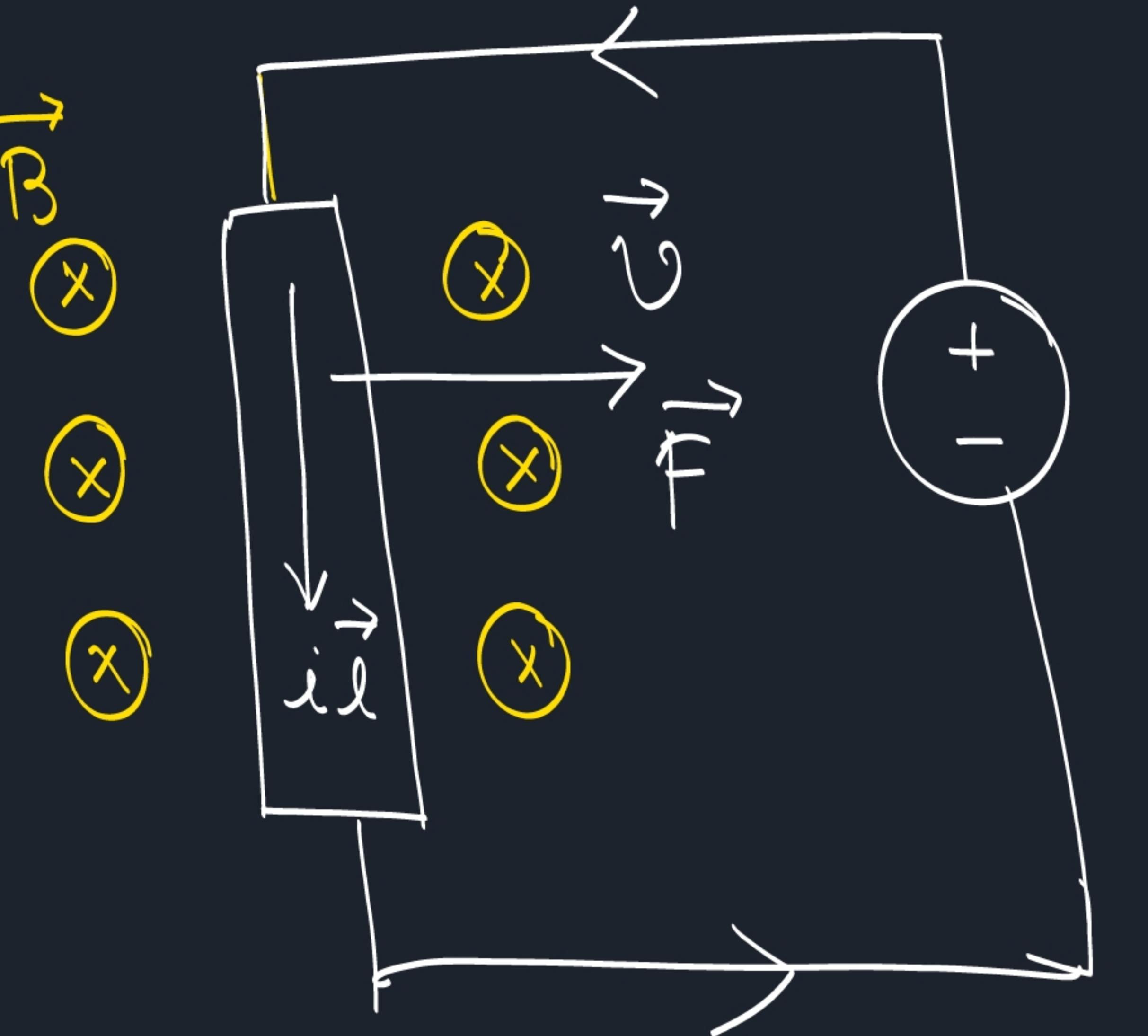Dir<sup>n</sup> of Force on  
Current carrying  
Conductor.



## DC Generator :-

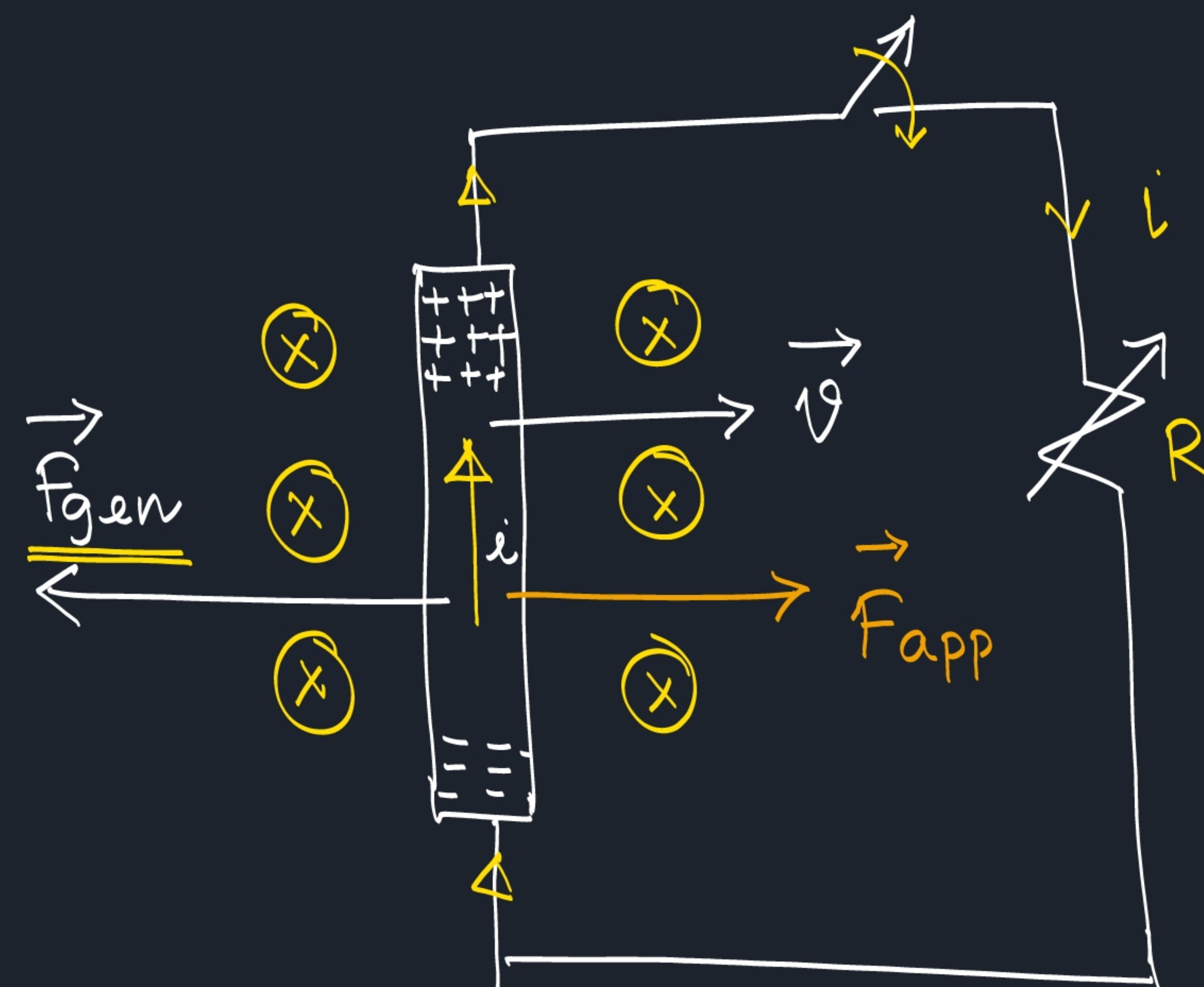

$$(\vec{E} = \lambda \vec{v} \times \vec{B})$$


$$i = \frac{BLV}{R}$$

$$|F_{app}| = |F_{gen}|$$

Must have to have a prime mover.

electromagnetic Torque is in the  
opposite dir. of angular Velocity.

## DC Motor :-

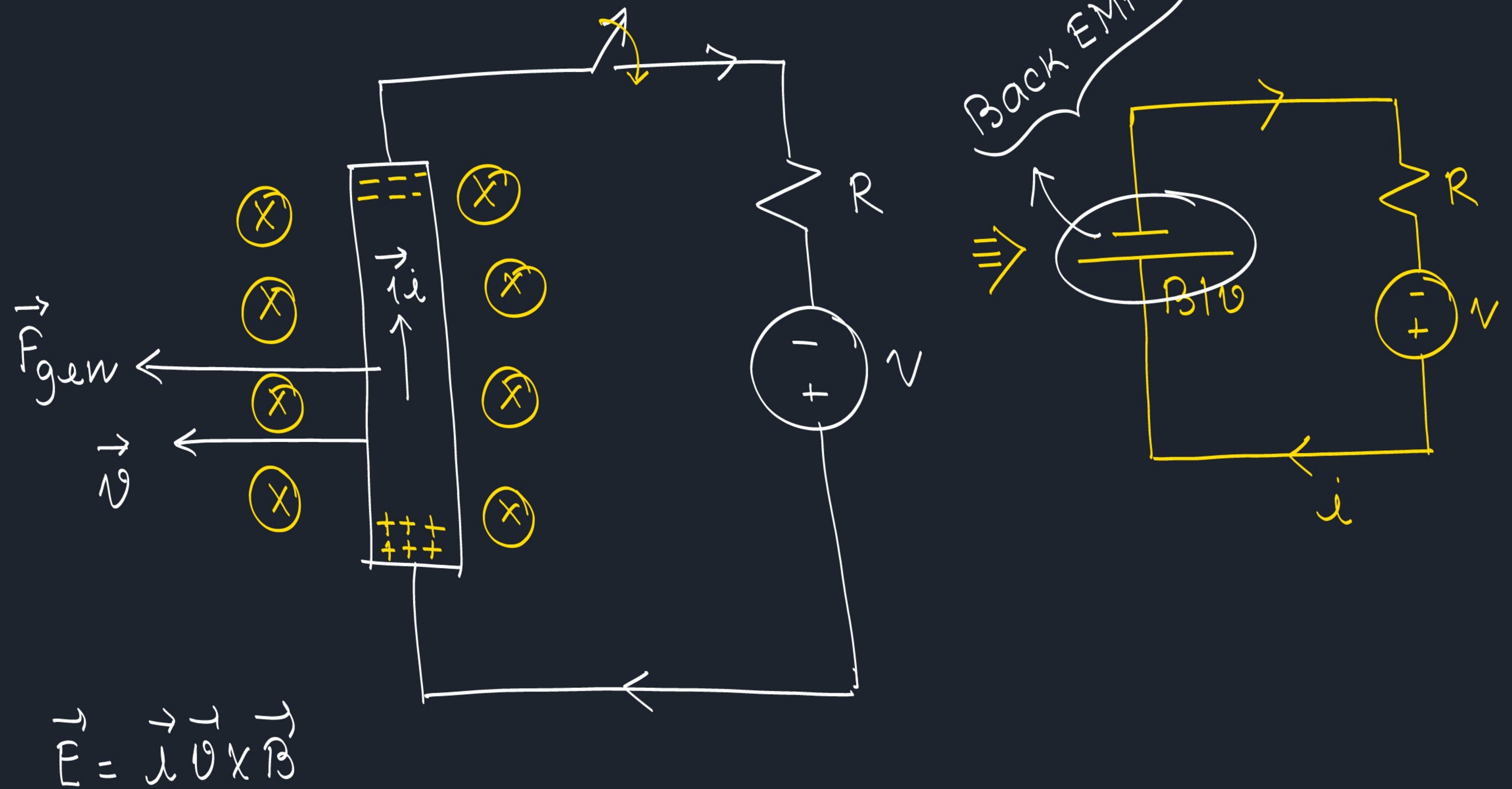

$$i = \frac{V - B1V}{R}$$

  OC Gen:—

Stalōy ·

```
graph TD; A[Rotor (Armature)] --> B[Place Conductors]; A --> C[Keep The Magnets.]; B --> D[Stator]
```

Rotor (Armature)

↓

Place Conductors






↓

Stator

↓

Keep The  
Magnets.
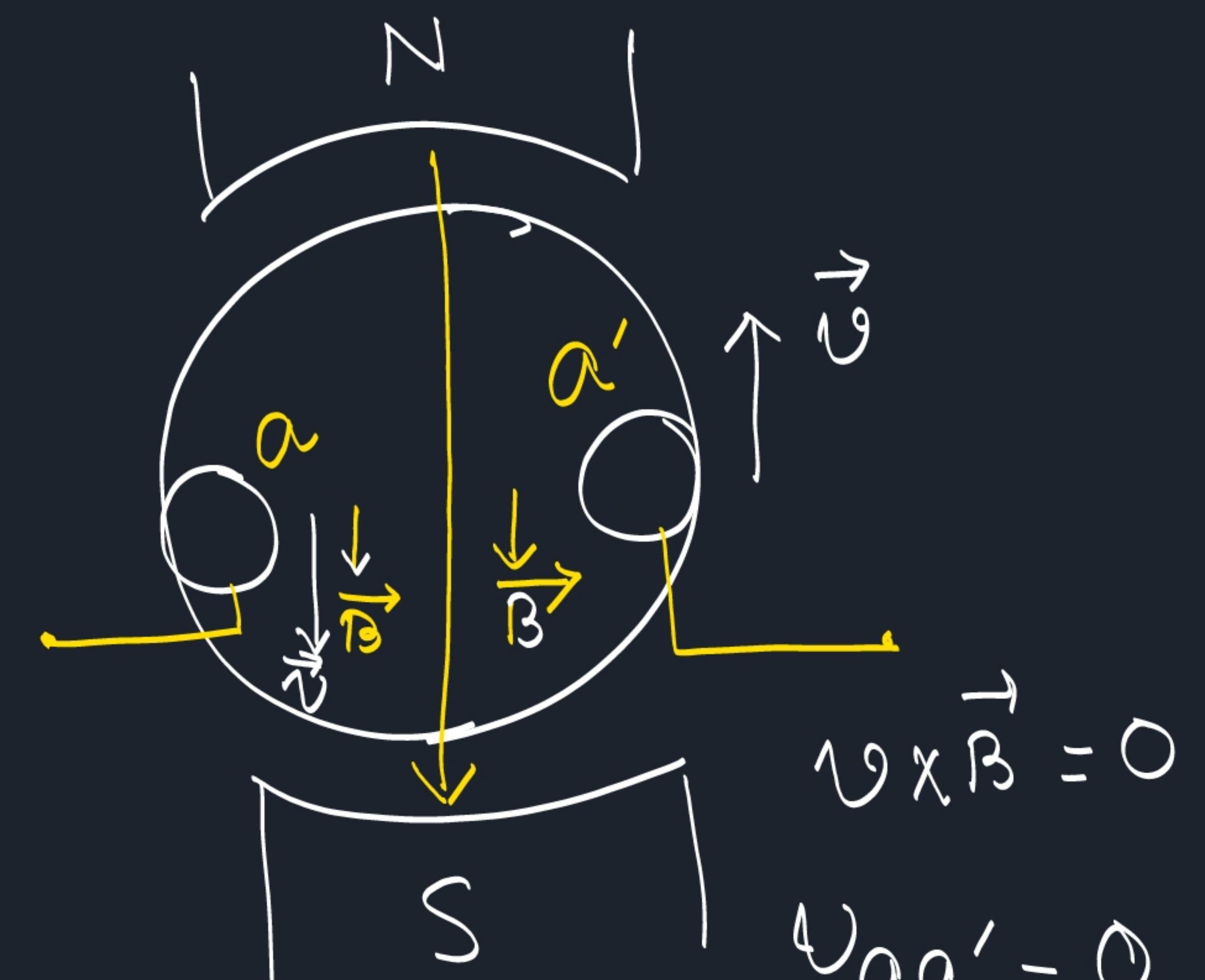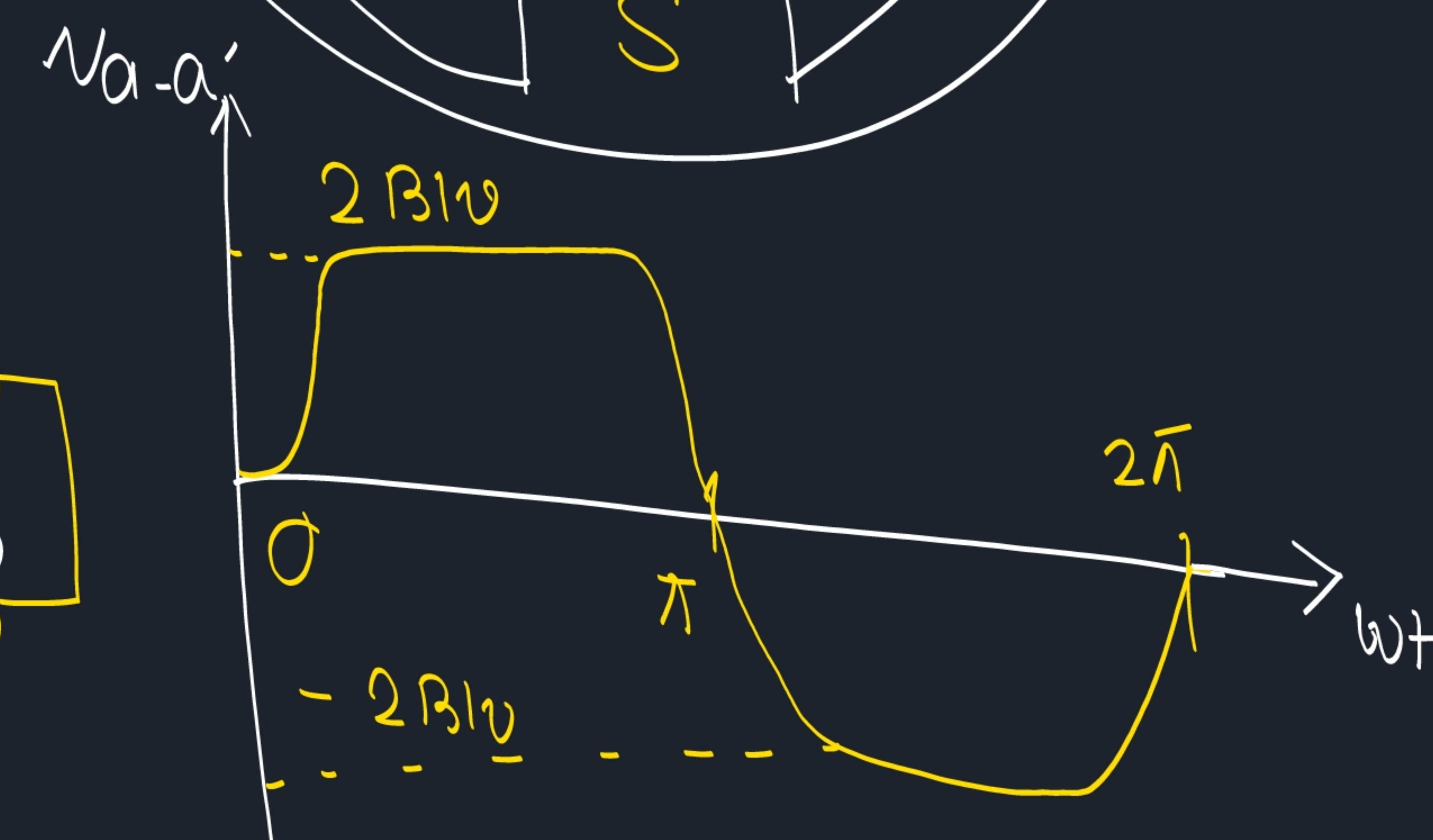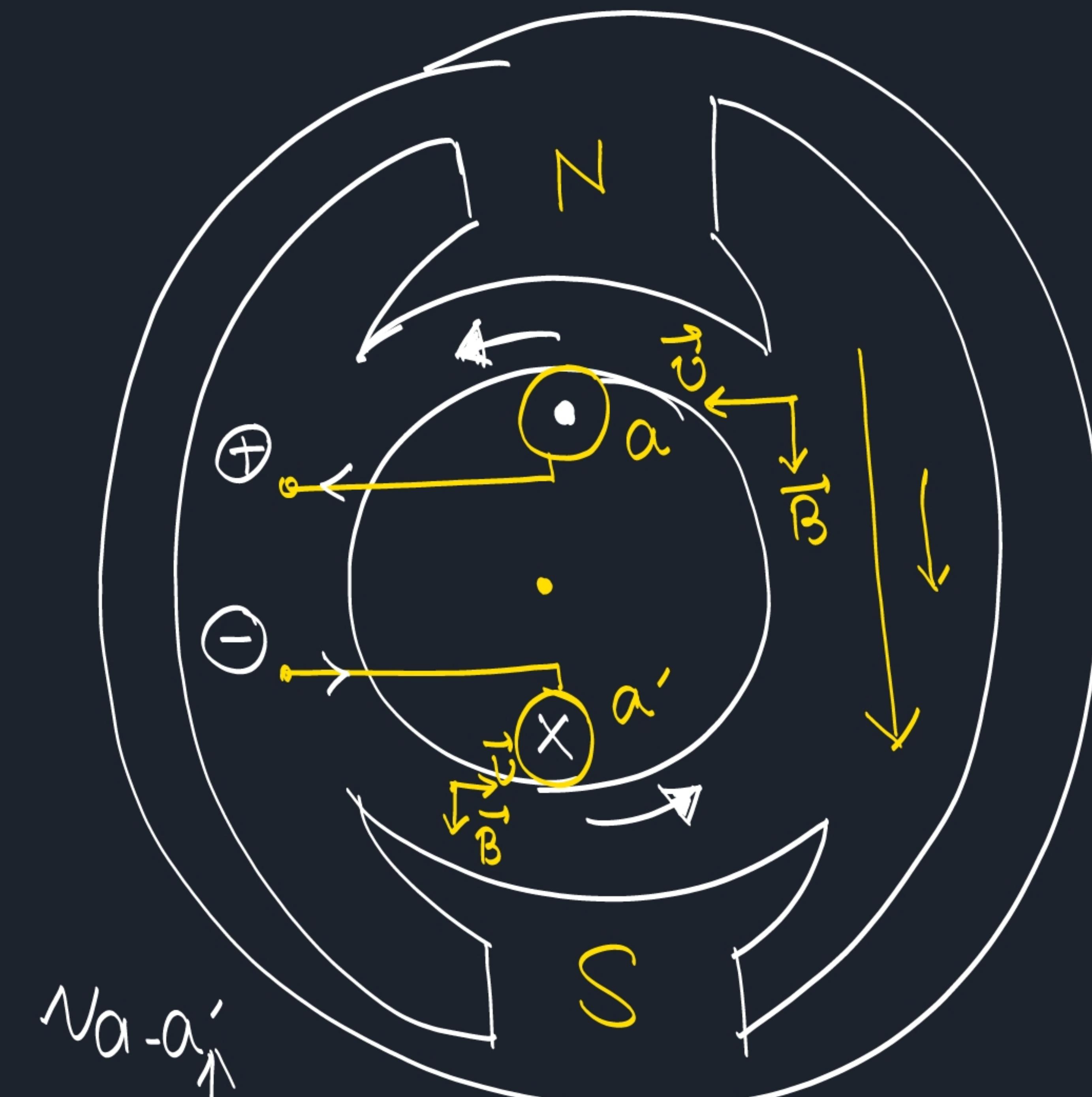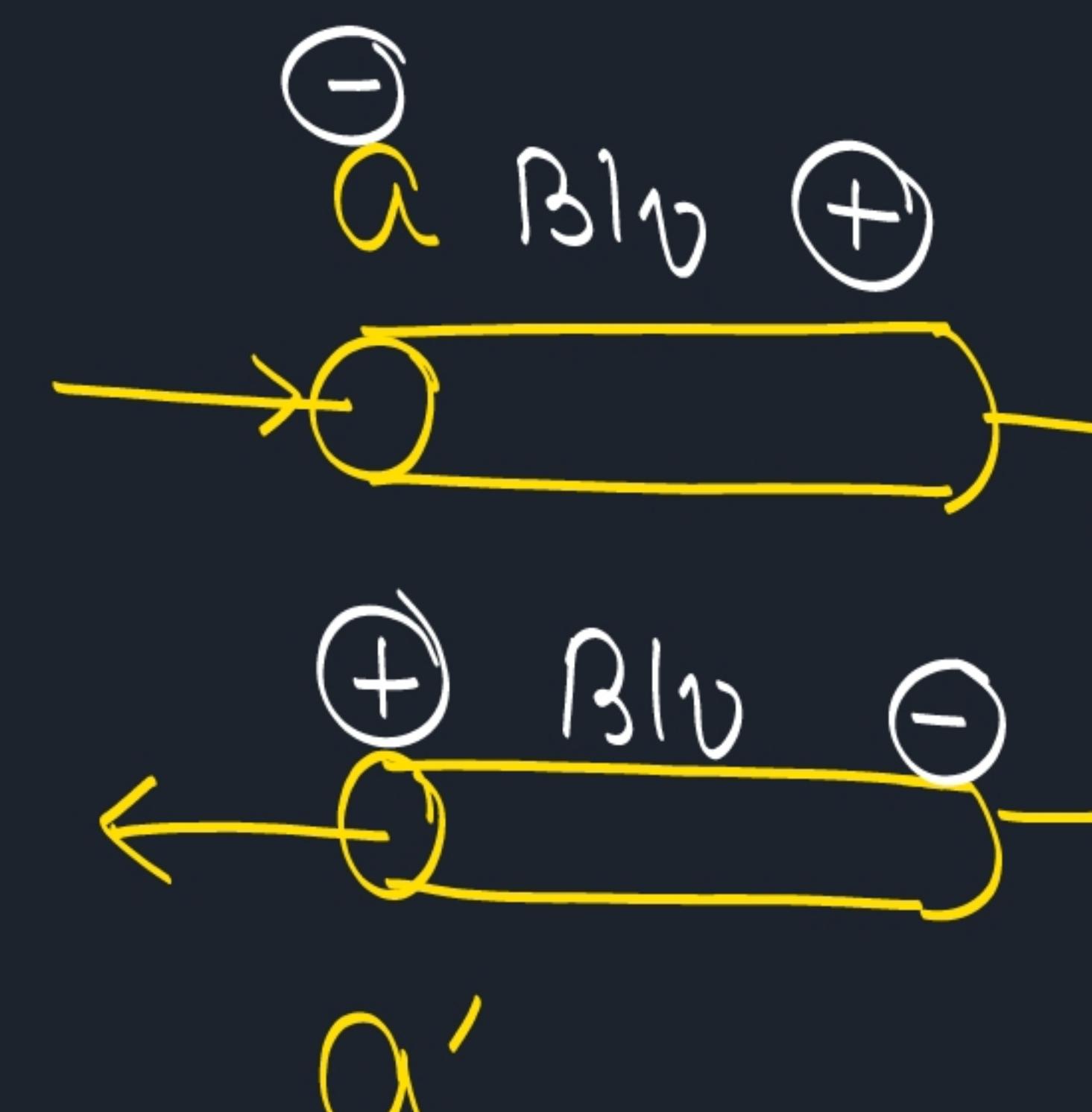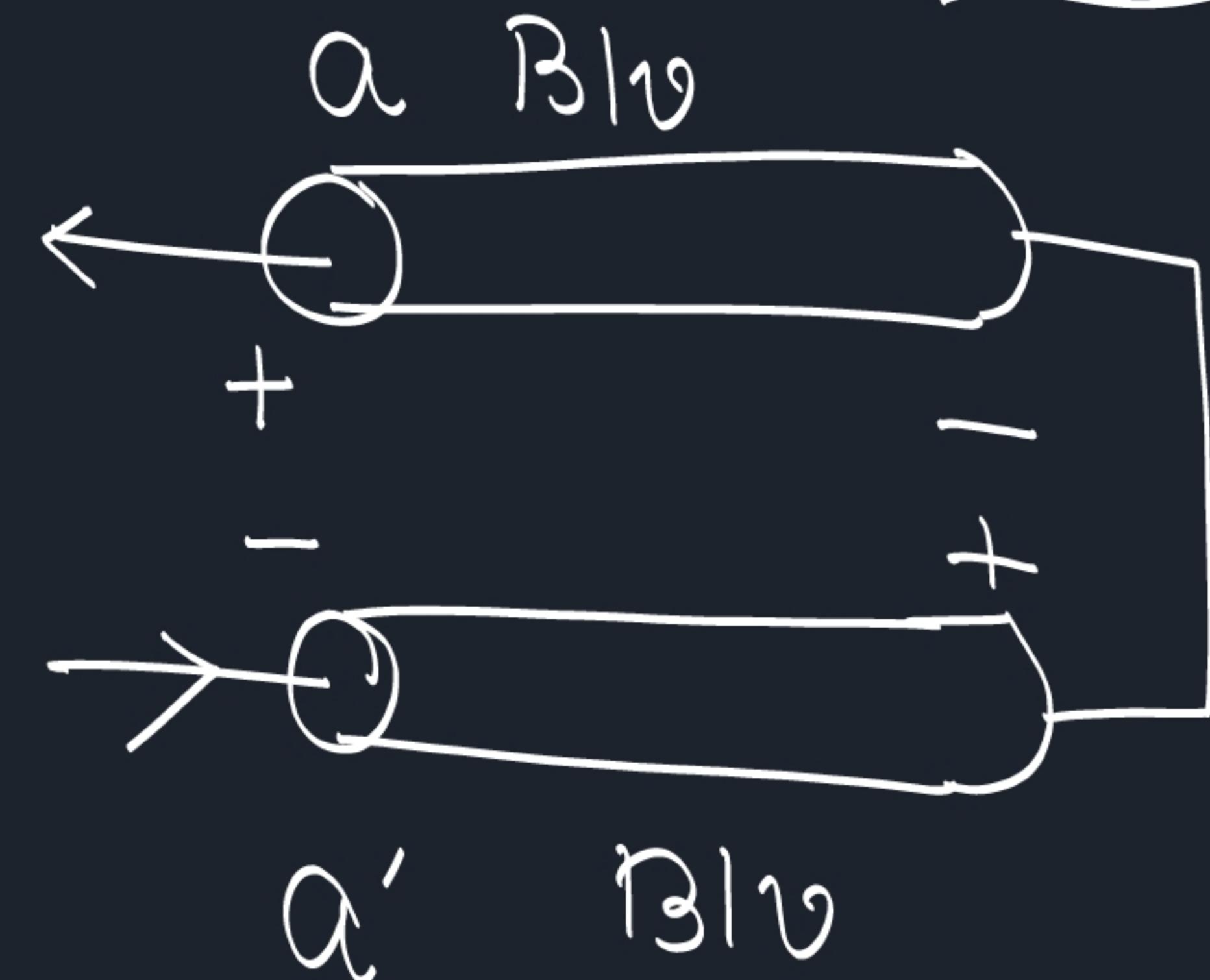
$$v_{a-a'} = \beta l v - (-\beta l v) \\ = 2\beta l v.$$



$$A \otimes B = 0$$

Woo'-o




$$Va - a' = -2B1v$$



Brush + Commutator Arrangement :-


Static  
AC  $\rightarrow$  DC

Rotating

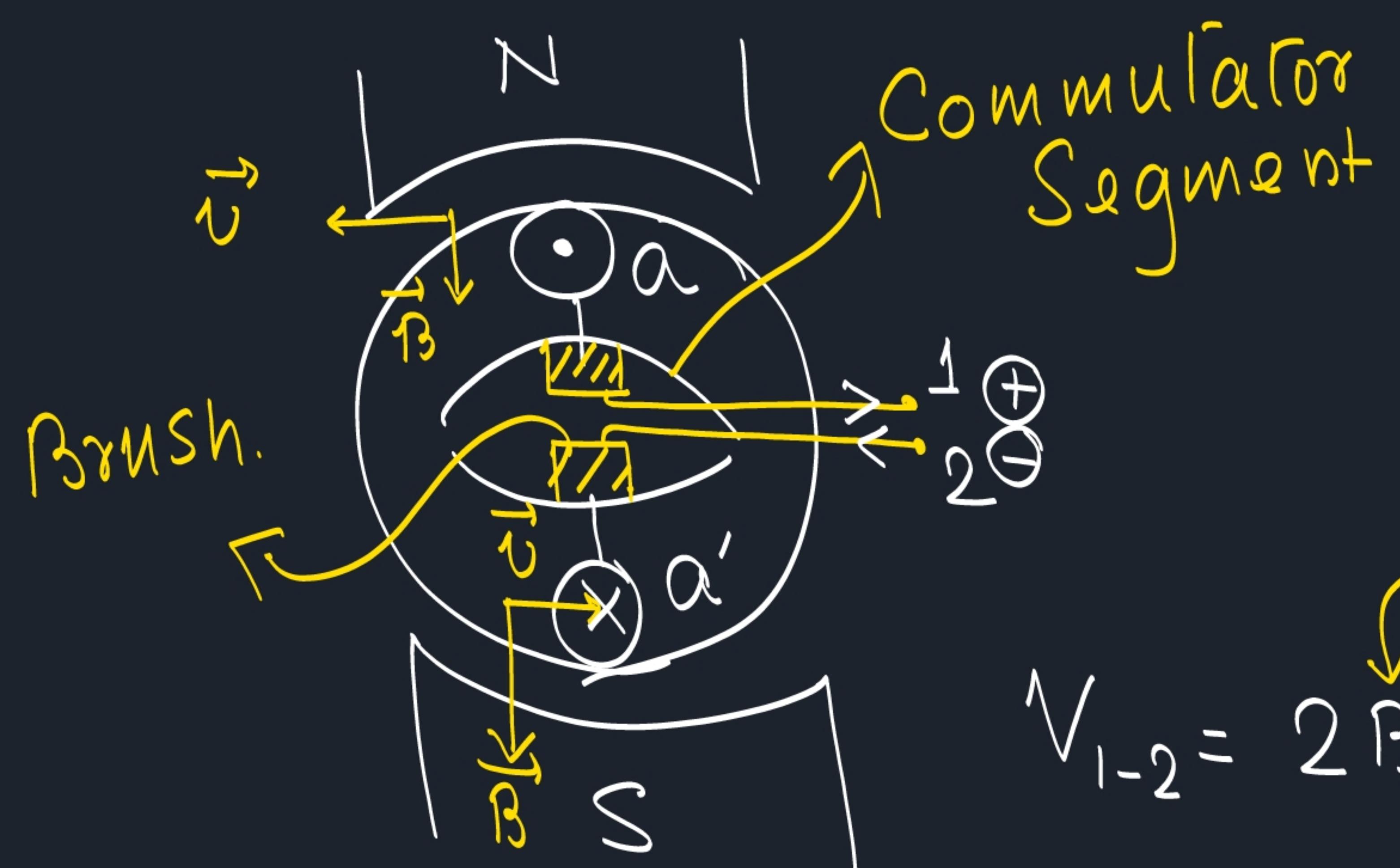

$$V_{1-2} = 2B\omega$$

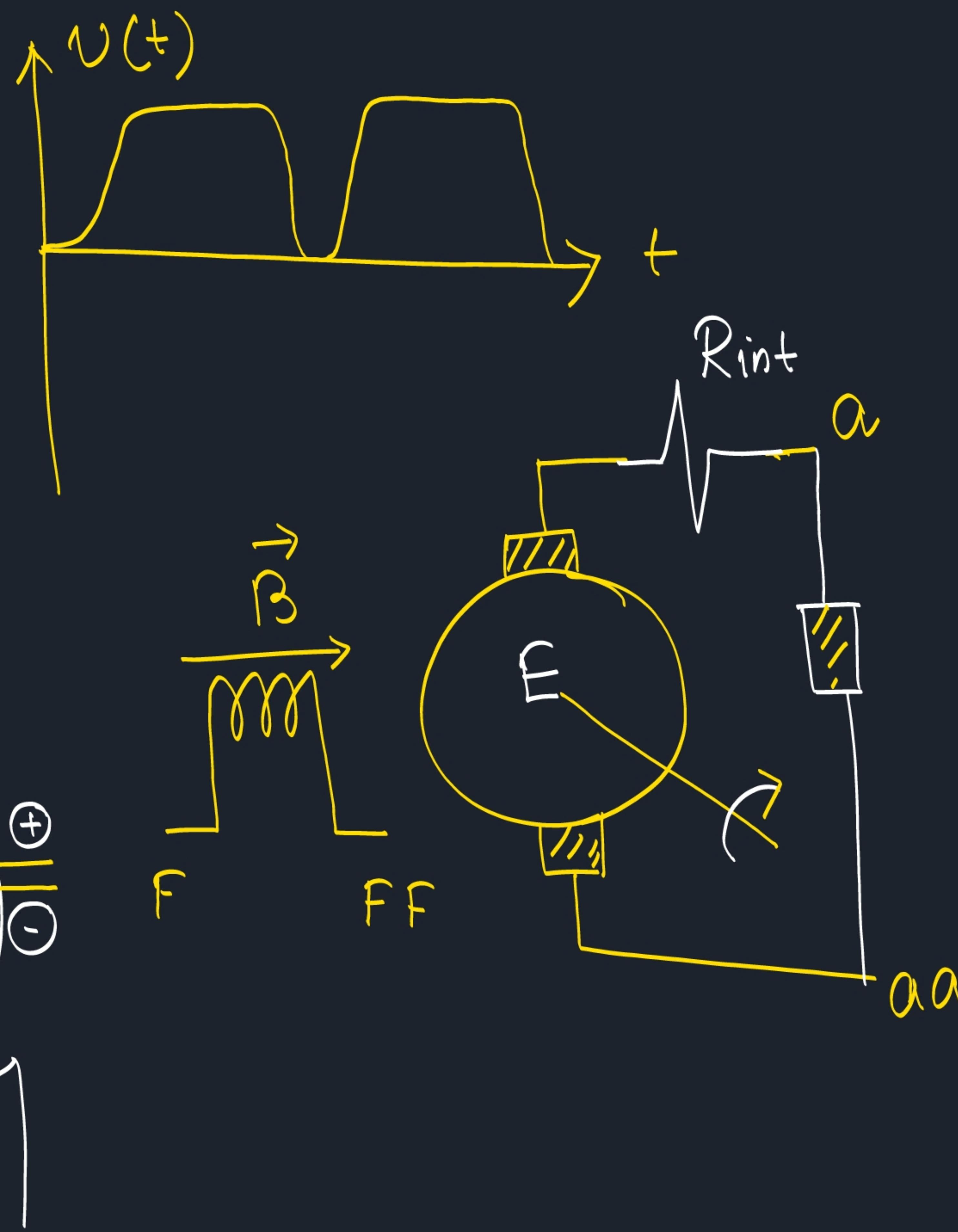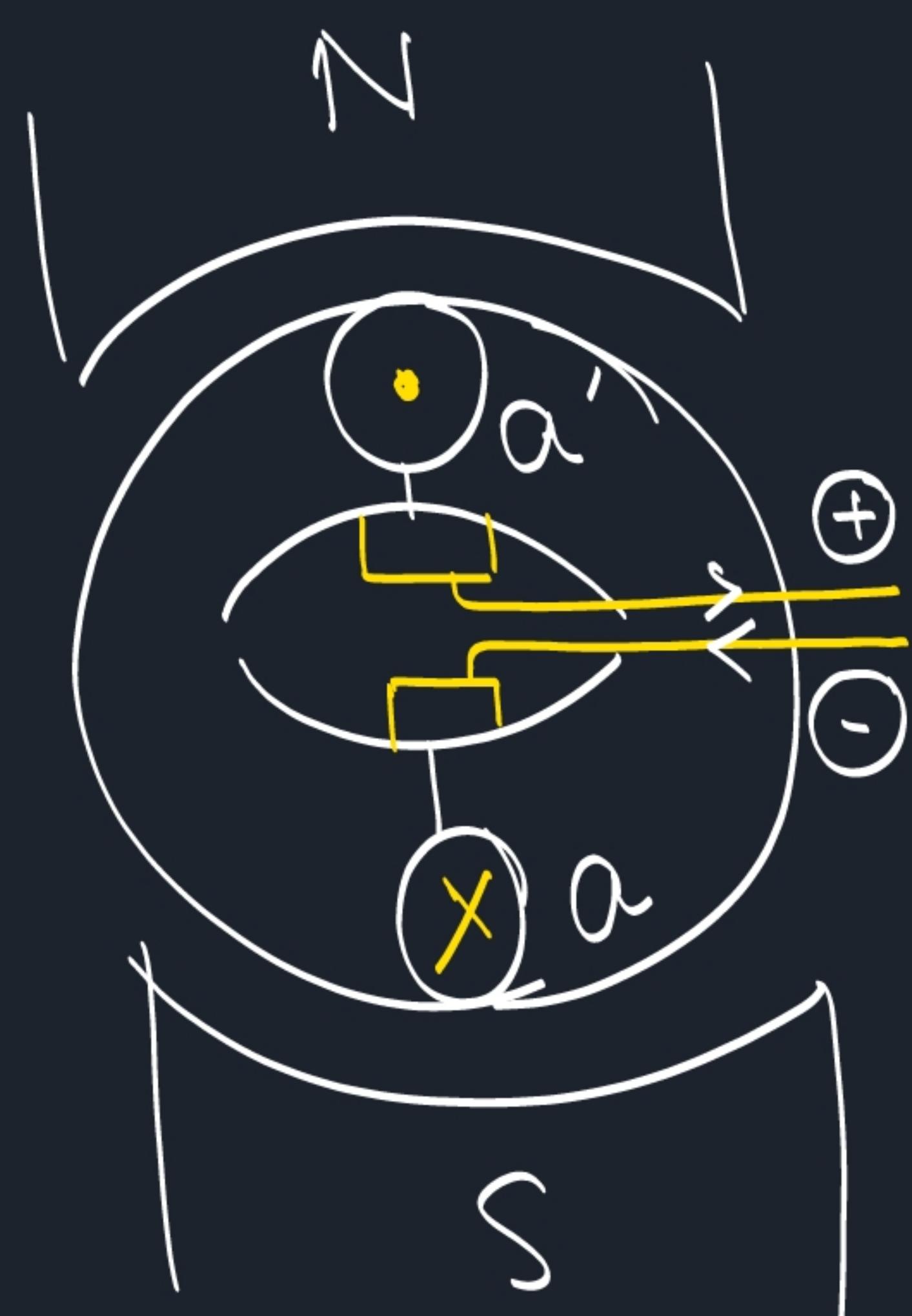

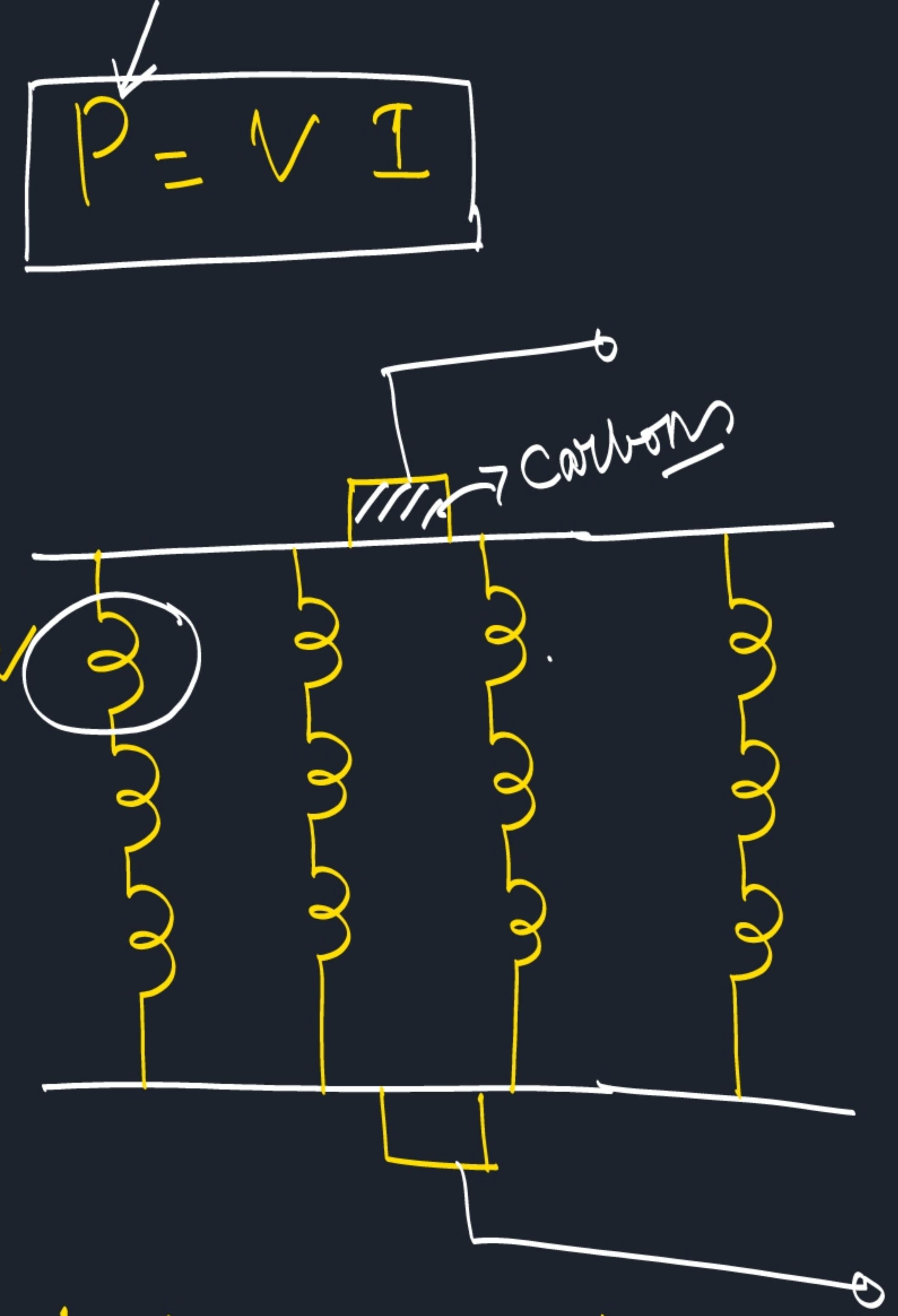

$$|I| = N \frac{d\phi}{dt} = \frac{d\phi}{dt}$$

$$E = \frac{\phi PN}{60} \left( \frac{Z}{A} \right)$$

$Z$  = Total no. of Armature Conductors.


= Total no of Slots  $\times$  Armature conductors per Slot.

$A$  = no of Parallel Path

$\frac{Z}{A}$  = Conductors / Parallel Path.


$P$  = NO of poles.  $\phi$  = flux /  $Pd\theta$ .

$N$  = Rotational Speed. (RPM)

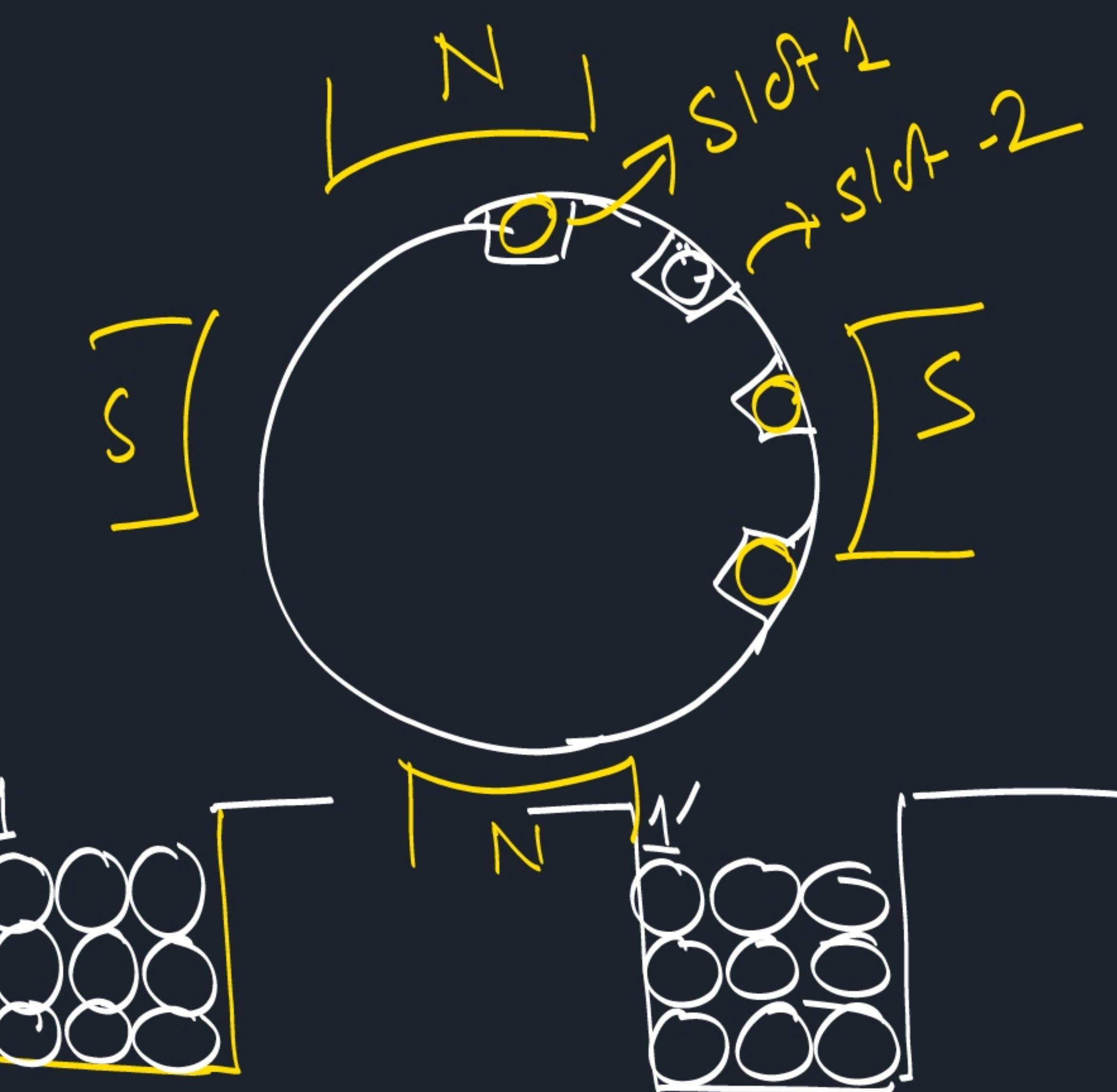


$$\dot{\phi} = P\phi.$$

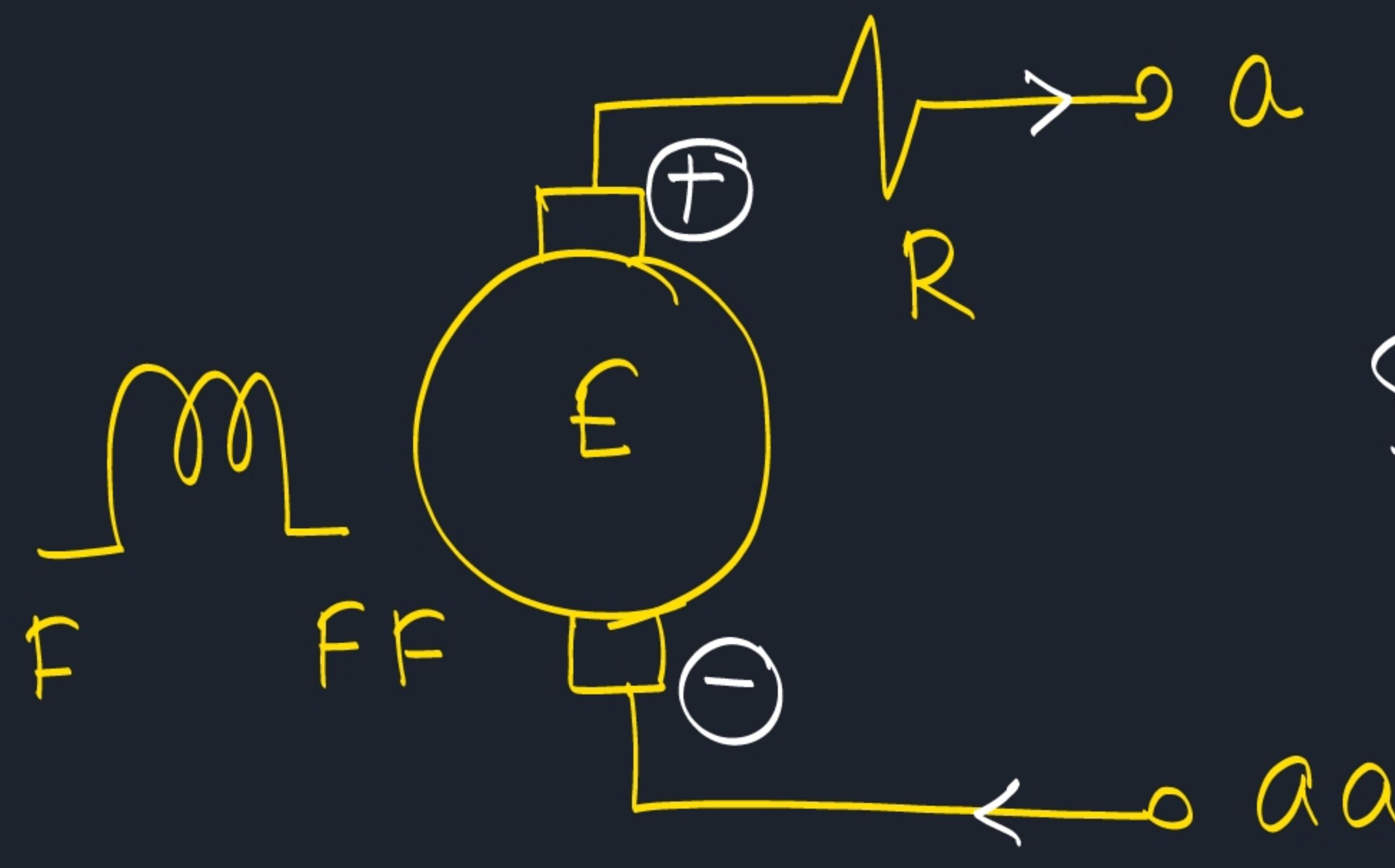
$$\frac{P\phi}{60/N} = \frac{\phi PN}{60}$$




Separately  
excited  
DC Gen.

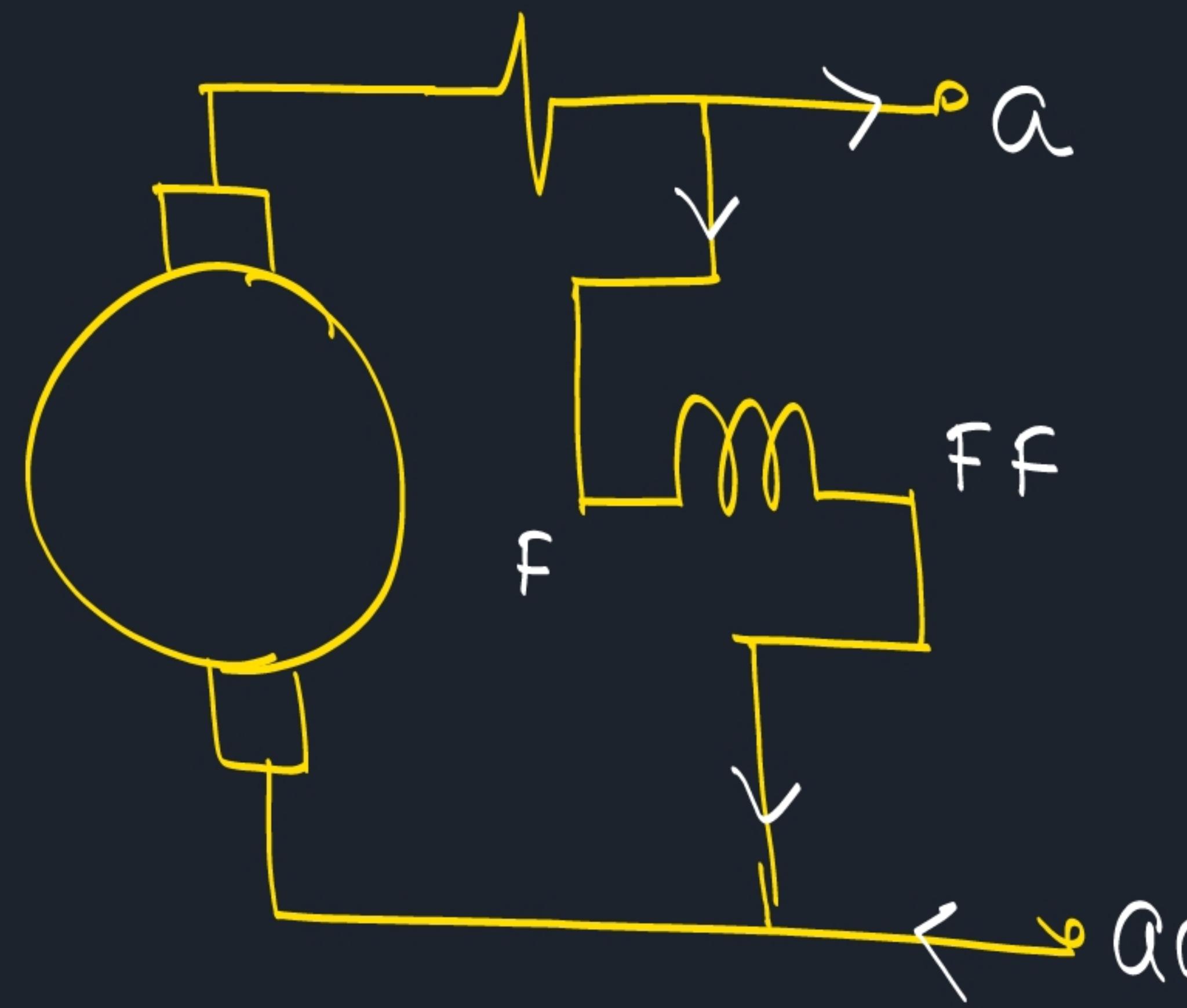

Shunt  
excited  
DC Gen.

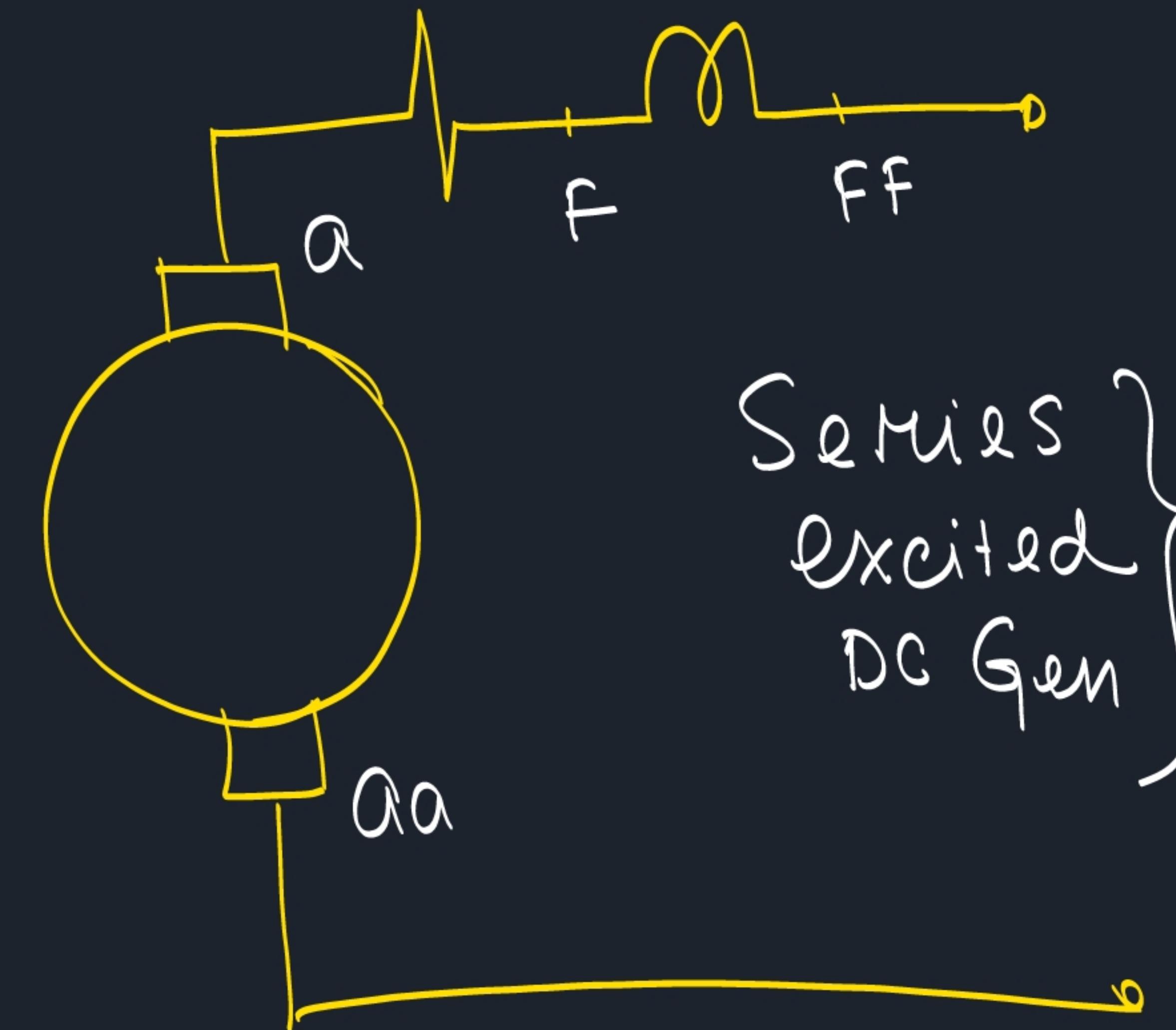

Series  
excited  
DC Gen

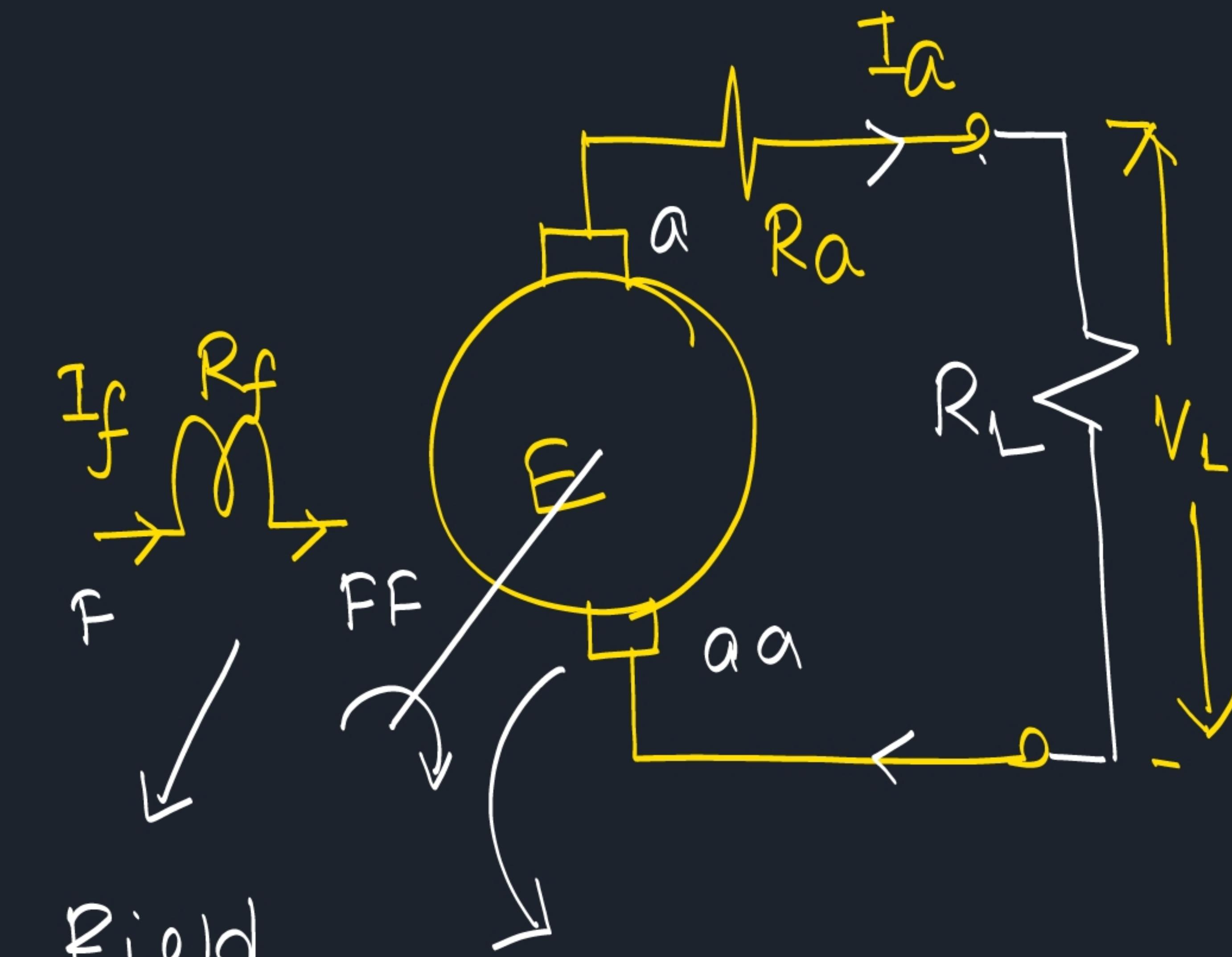

Field winding  
Armature winding.


$$\eta = \frac{P_{out}}{P_{in}} \times 100$$

$$= \frac{P_{load}}{P_{mech.}} \times 100$$


$$= \frac{P_{load}}{P_{load} + V_b I_a + I_a^2 R_a + I_f^2 R_f + P_{fw}}$$

$$E = \left( \frac{\Phi Z N}{60} \cdot \frac{P}{A} \right)$$

$$V_L = E_g - I_a R_a - V_b$$

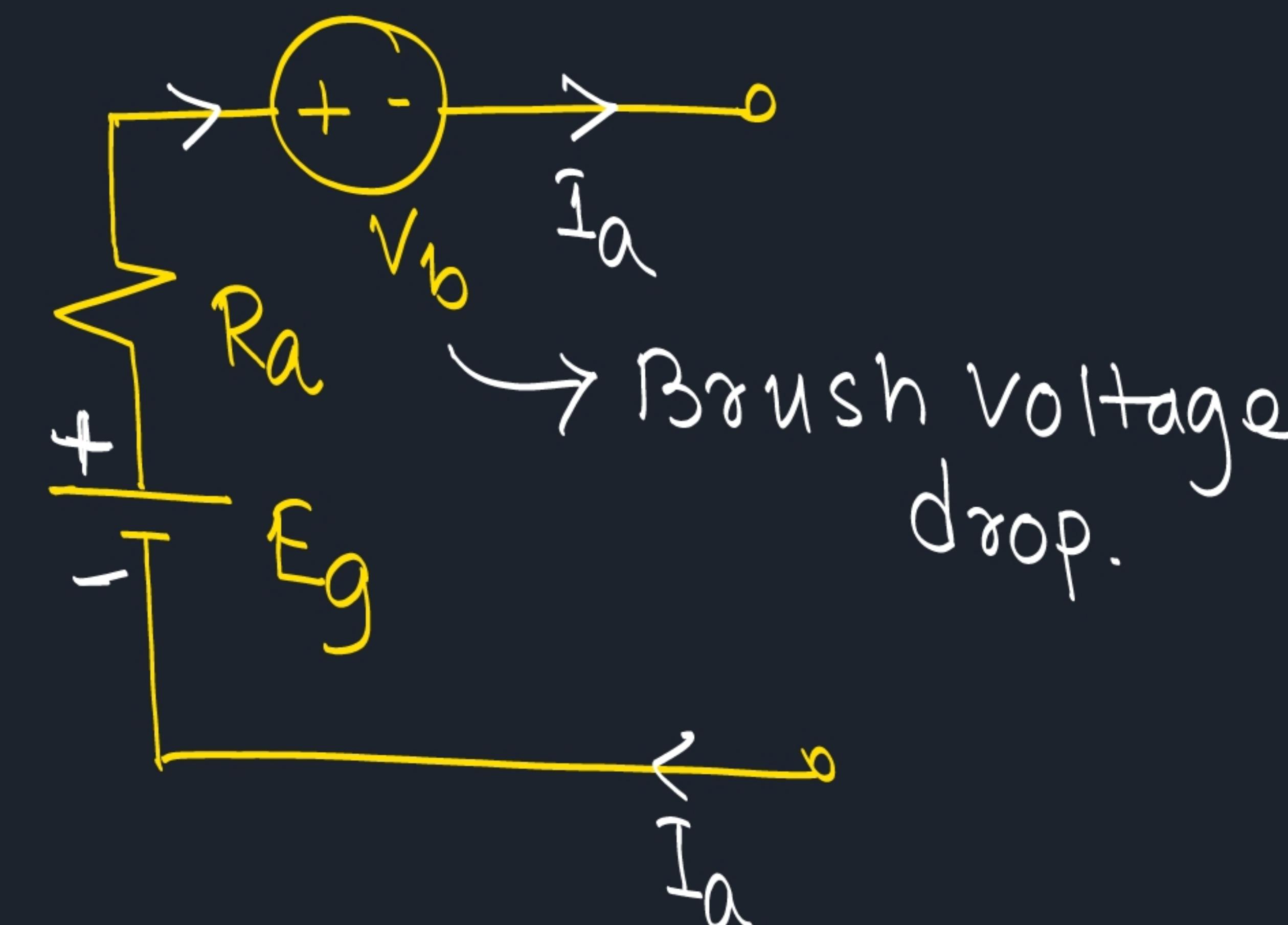

Brush voltage drop.

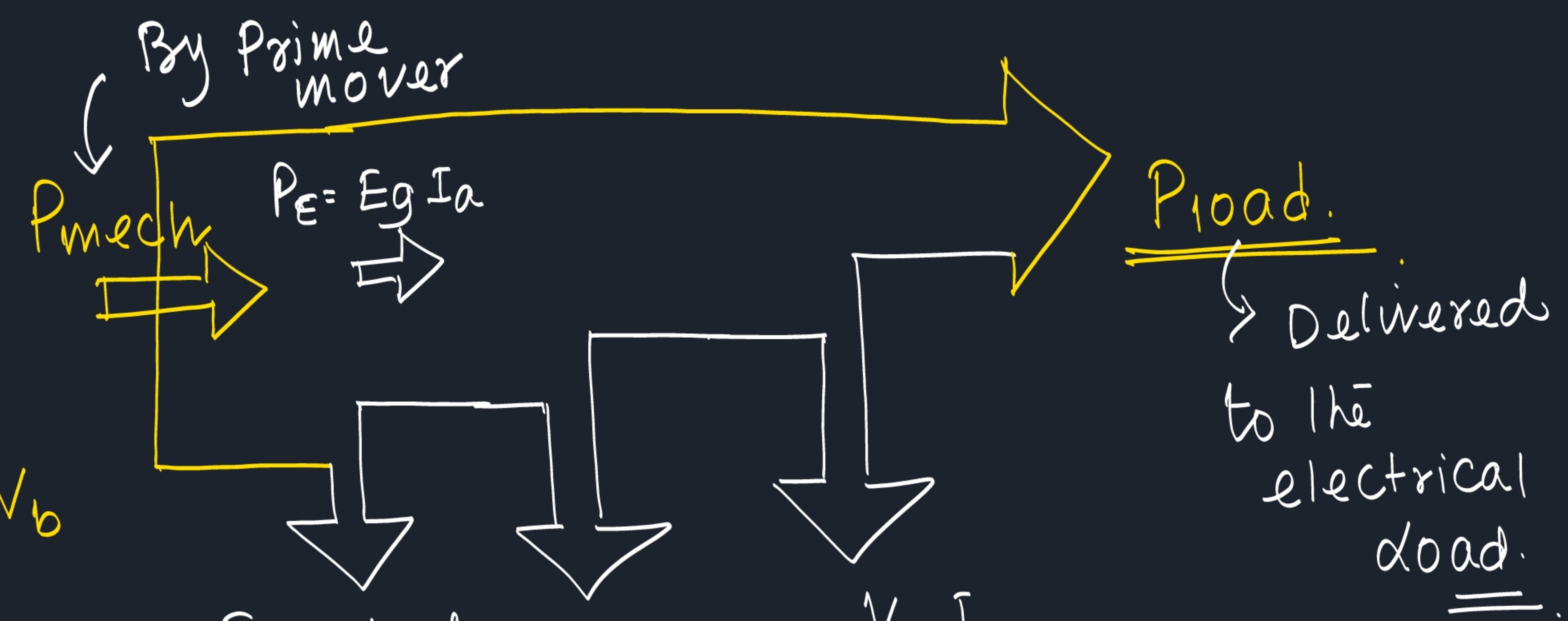


$$\frac{I_a^2 R_a + I_f^2 R_f}{P_{fw}} + \text{Armature Cu loss}$$


$$+ \text{Field Cu loss}$$

$$+ \text{Brush loss}$$

## Shunt Excited Gen:-

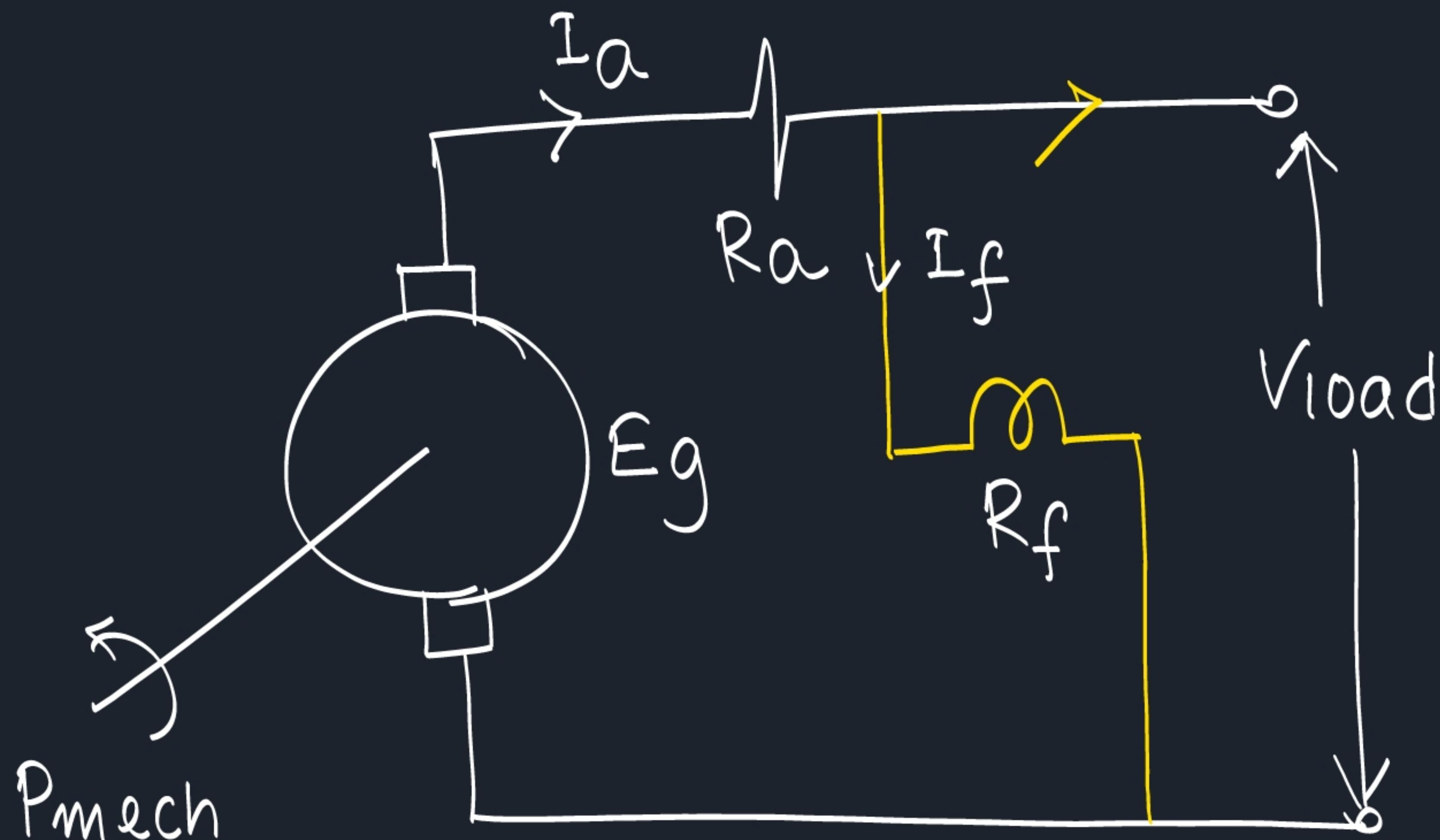
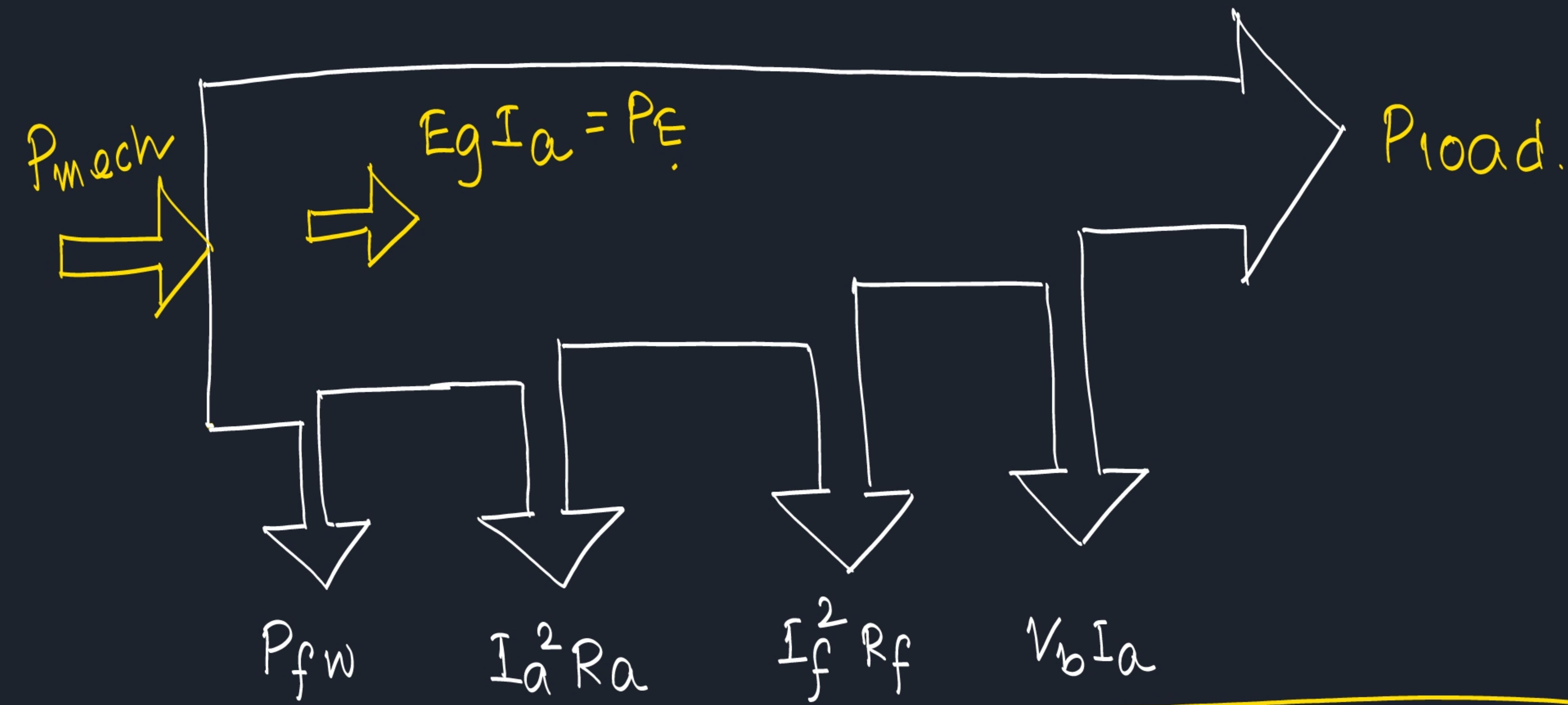
$$\begin{aligned} \text{eff} &= \frac{P_{\text{out}}}{P_{\text{in}}} \\ &= \frac{P_{\text{load}} \times 100}{P_{\text{fw}} + I_a^2 R_a + I_f^2 R_f + V_b I_a + P_{\text{load}}} \end{aligned}$$



$$V_{\text{load}} = E_g - I_a R_a$$

$$P_{\text{load}} = V_{\text{load}} \cdot (I_a - I_f)$$

$$I_f = \frac{E_g - I_a R_a}{R_f} = \frac{V_{\text{load}}}{R_f}$$

$$P_{\text{mech}} = P_E + P_{\text{fw}}$$

$$E_g = \frac{\Phi Z N}{60} \left( \frac{P}{A} \right)$$

$$E_g = \frac{\Phi Z N}{60} \cdot \left( \frac{P}{A} \right)$$

1. Lap winding  $(A = \text{No. of Poles})$   $A = P$

2. Wave winding  $(A = 2)$

↳ For both motor & Gen.

Prob:-


DC Shunt Gen  
Delivers 450 Amp  
@ 230 V

$$R_f = 50 \Omega, R_a = 0.3 \Omega$$

$$P_{fw} = 2 \text{ kW.}$$

Find out  $\eta$  (in %)
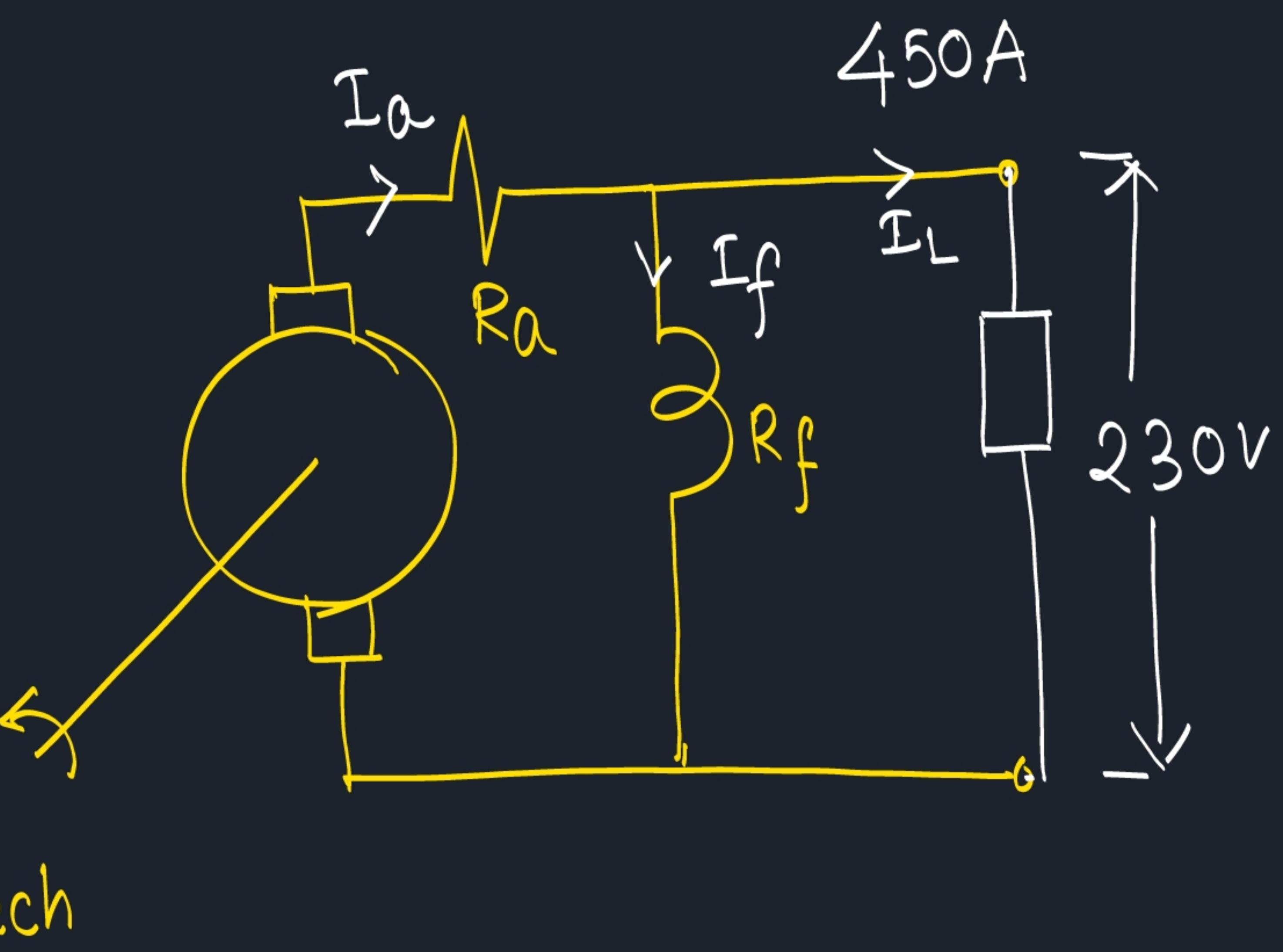
$$\begin{aligned}\eta \% &= \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{mech}} \times 100 \\ &= \frac{450 \times 230 \times 100}{366.38 \times 454.6 + 2000} \\ &= 61.4 \%\end{aligned}$$



$$P_{out} = (450 \times 230) \text{ W}$$

$$\begin{aligned}P_{mech} &= P_{in} = P_E + P_{fw} \\ &= E_g I_a + P_{fw}\end{aligned}$$

$$E_g = V_{load} + I_a R_a$$

$$\begin{aligned}I_a &= I_L + I_f \\ &= 450 + \frac{230}{50} = 454.6 \text{ A.}\end{aligned}$$

$$\begin{aligned}E_g &= 230 + (454.6) \times 0.3 = \\ &= 366.38 \text{ V}\end{aligned}$$

 Prob:-

Sep. Ex. DC Gen.

Delivers 150A @ 400V  
and 1000 rpm.


The load is a constant resistive load.

Current to the load is reduced to 100A

Determine the Speed.

$$R_a = 0.12 \Omega$$

Brush voltage drop = 2volt.

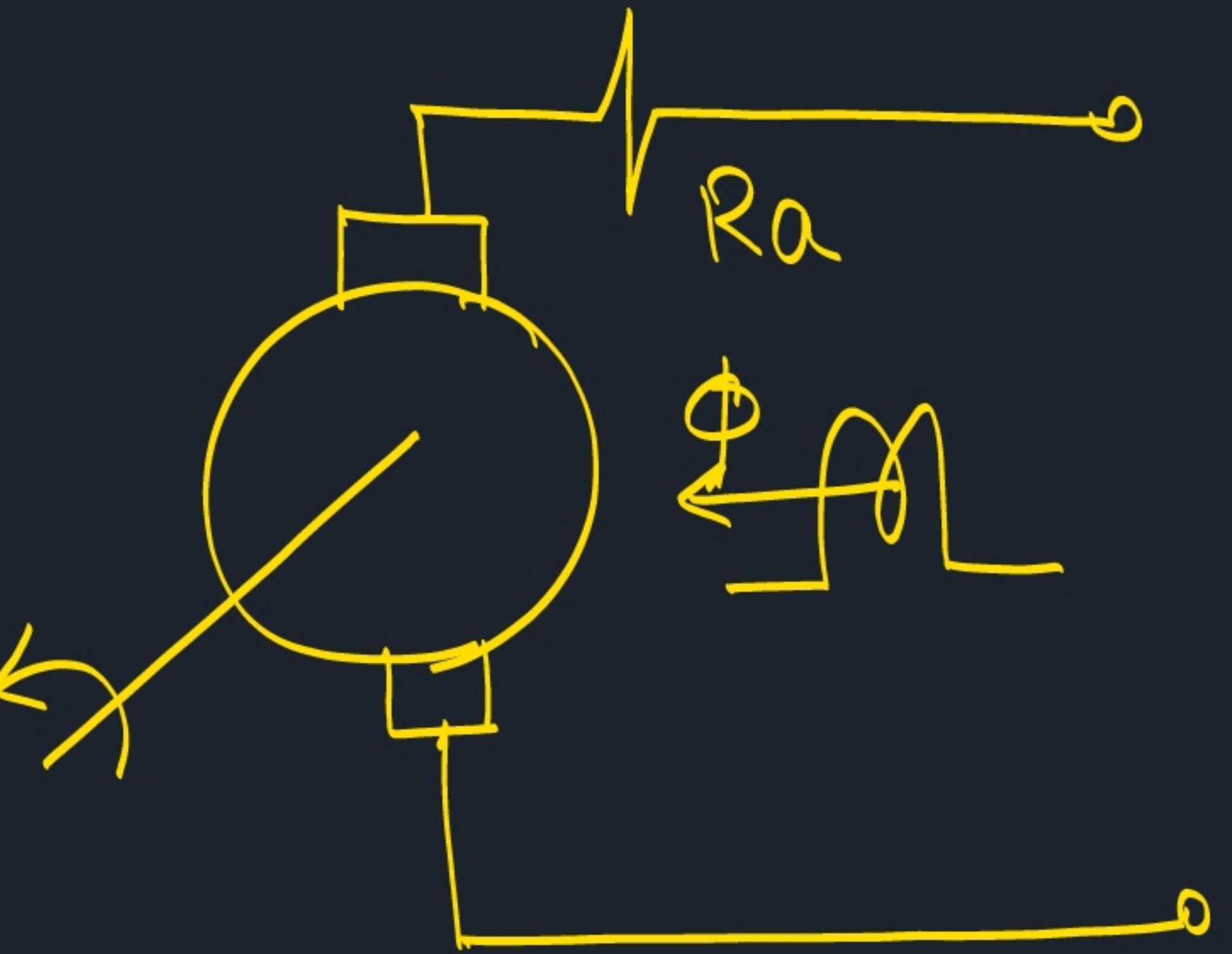

$$E_g = \frac{\Phi Z N}{60} \cdot \left( \frac{P}{A} \right)$$

$$\frac{Eg_1}{Eg_2} = \frac{N_1}{N_2} = \frac{1000}{N_2}$$

$$N_2 = 668.26 \\ \approx \underline{\underline{669}} \text{ rpm}$$

\* Eg<sub>1</sub> :-


$$V_{load_1} = 400V$$

$$\begin{aligned} Eg_1 &= 400 + 150 \times 0.12 \\ &\quad + 2 \\ &= 420 \text{ Volt.} \end{aligned}$$

$$V_{load_2} = ?$$


$$\begin{aligned} &= \left( \frac{400 \times 100}{150} \right) \text{ Volt.} = \\ &= 266.67 \text{ volt.} \end{aligned}$$
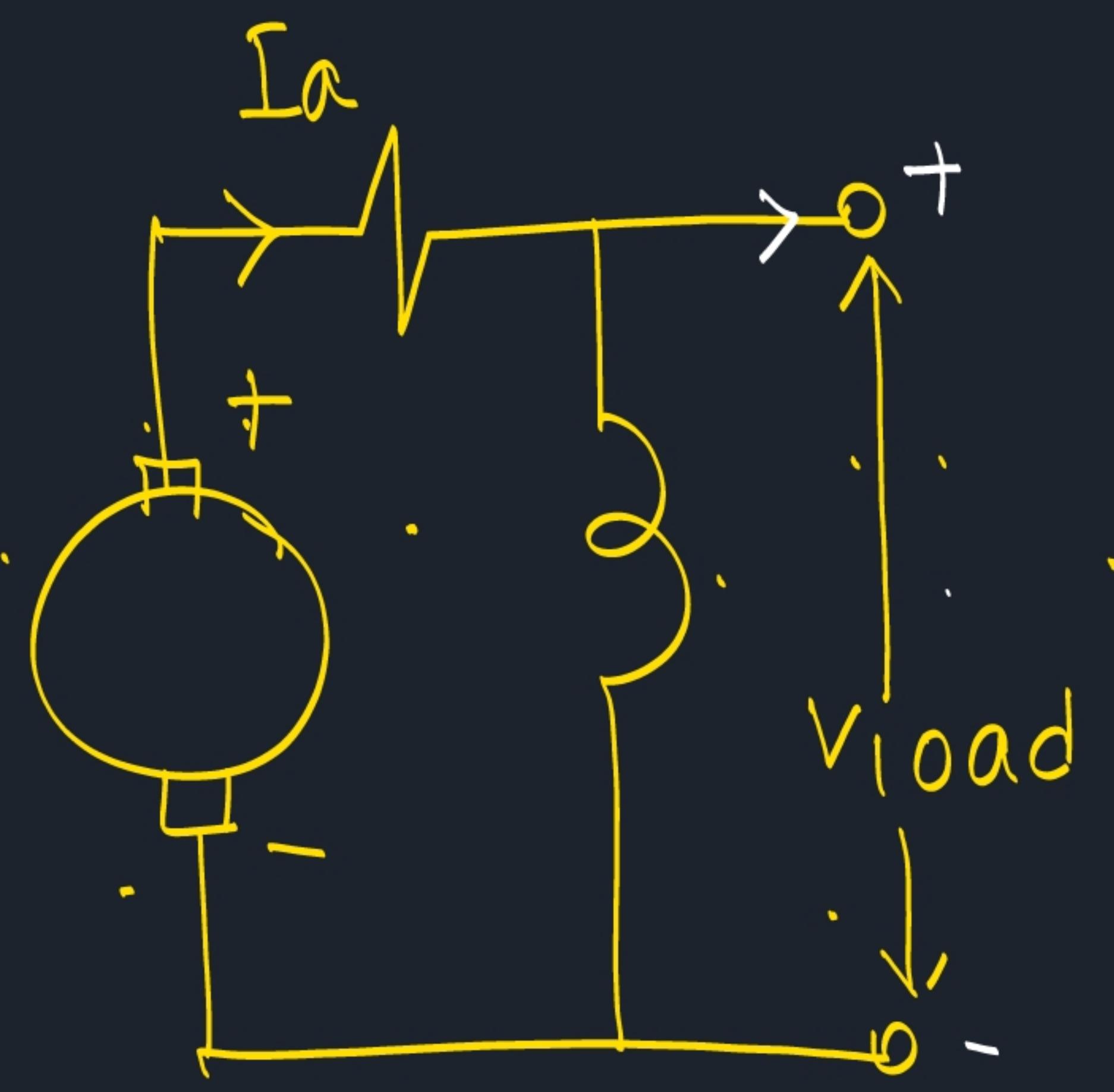
$$\begin{aligned} Eg_2 &= 266.67 + 100 \times 0.12 + 2 \\ &= 280.67 \text{ V} \end{aligned}$$




$$\vec{F} = (\vec{I} \vec{l} \times \vec{B})$$

$$E = (\vec{V} \times \vec{B})$$

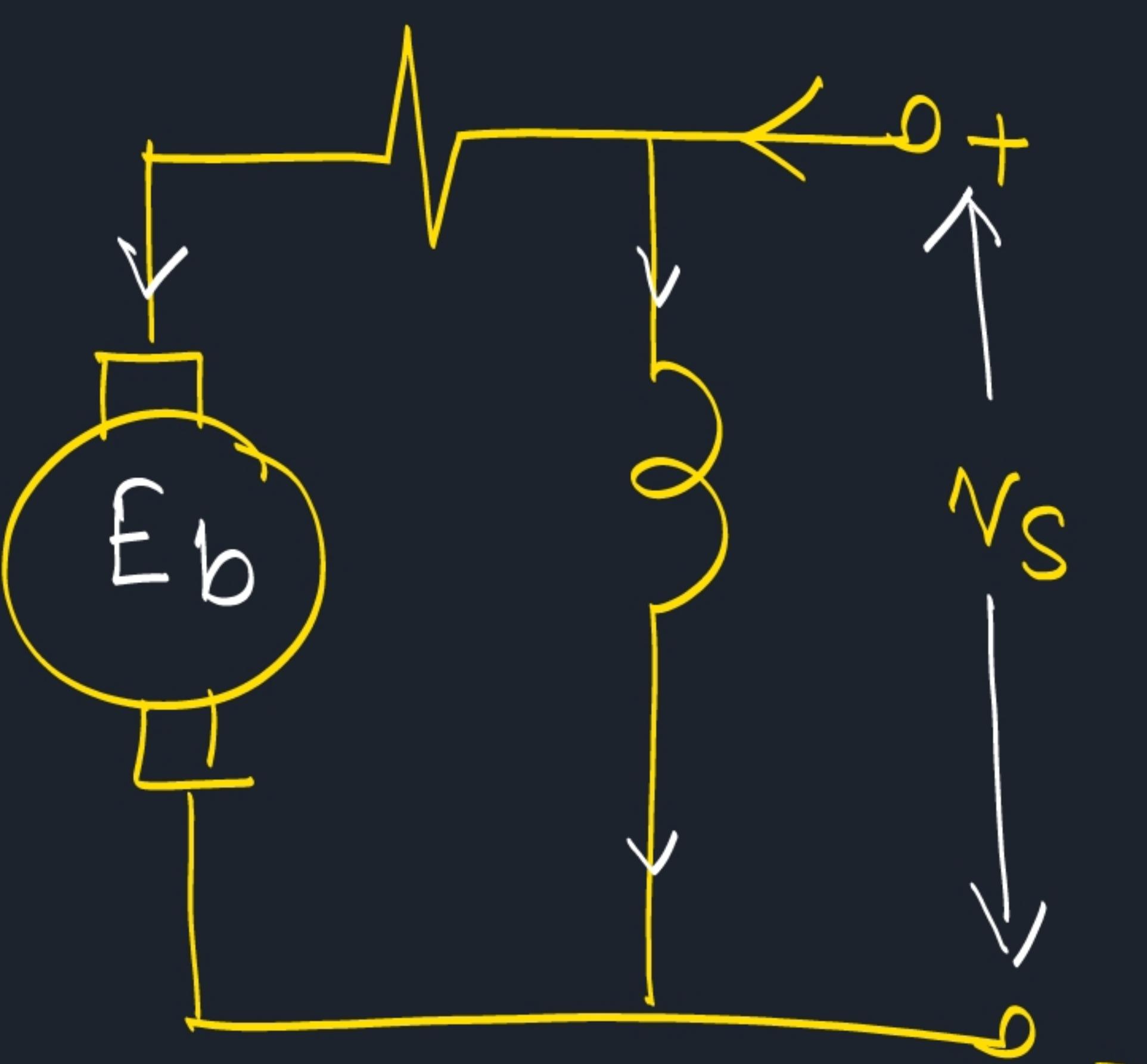

$\left. \begin{array}{l} \text{I/P is electrical power} \\ \text{O/P is mechanical power.} \end{array} \right\}$

## II) Sep. Ex. DC Motor:-

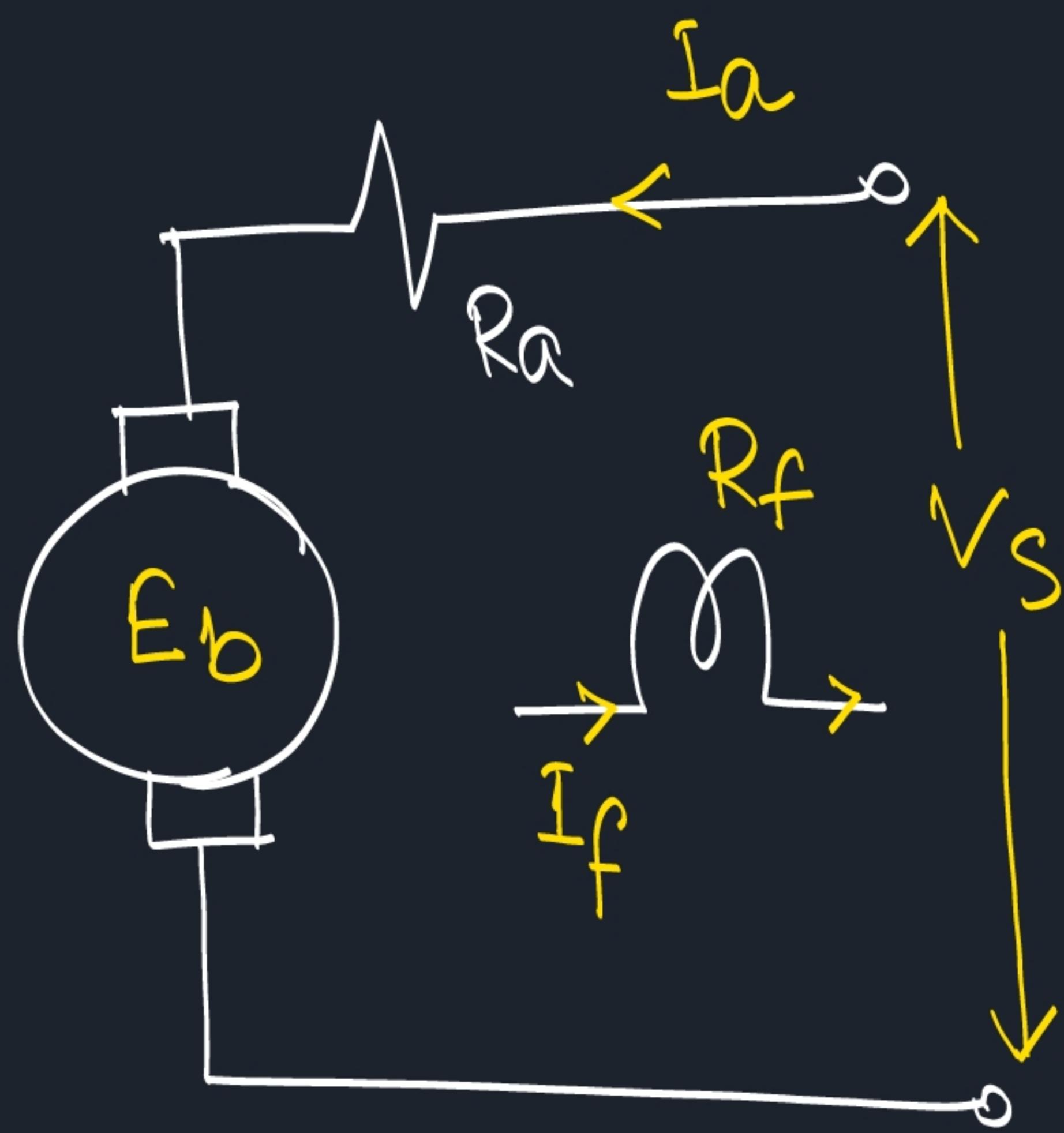

$$E_b = V_s - I_a R_a - V_o$$

$$P = T \cdot \omega$$

$$\Rightarrow E_b I_a = \tau_{gross} \omega$$


$$\tau_{gross} = \frac{E_b I_a}{\omega}$$

$$= \frac{E_b I_a}{\left( \frac{2\pi N}{60} \right)}$$

INPUT = Electrical Power  
OUTPUT = Mechanical Power.

$$P_{shaft} = E_b I_a - P_{fw}$$

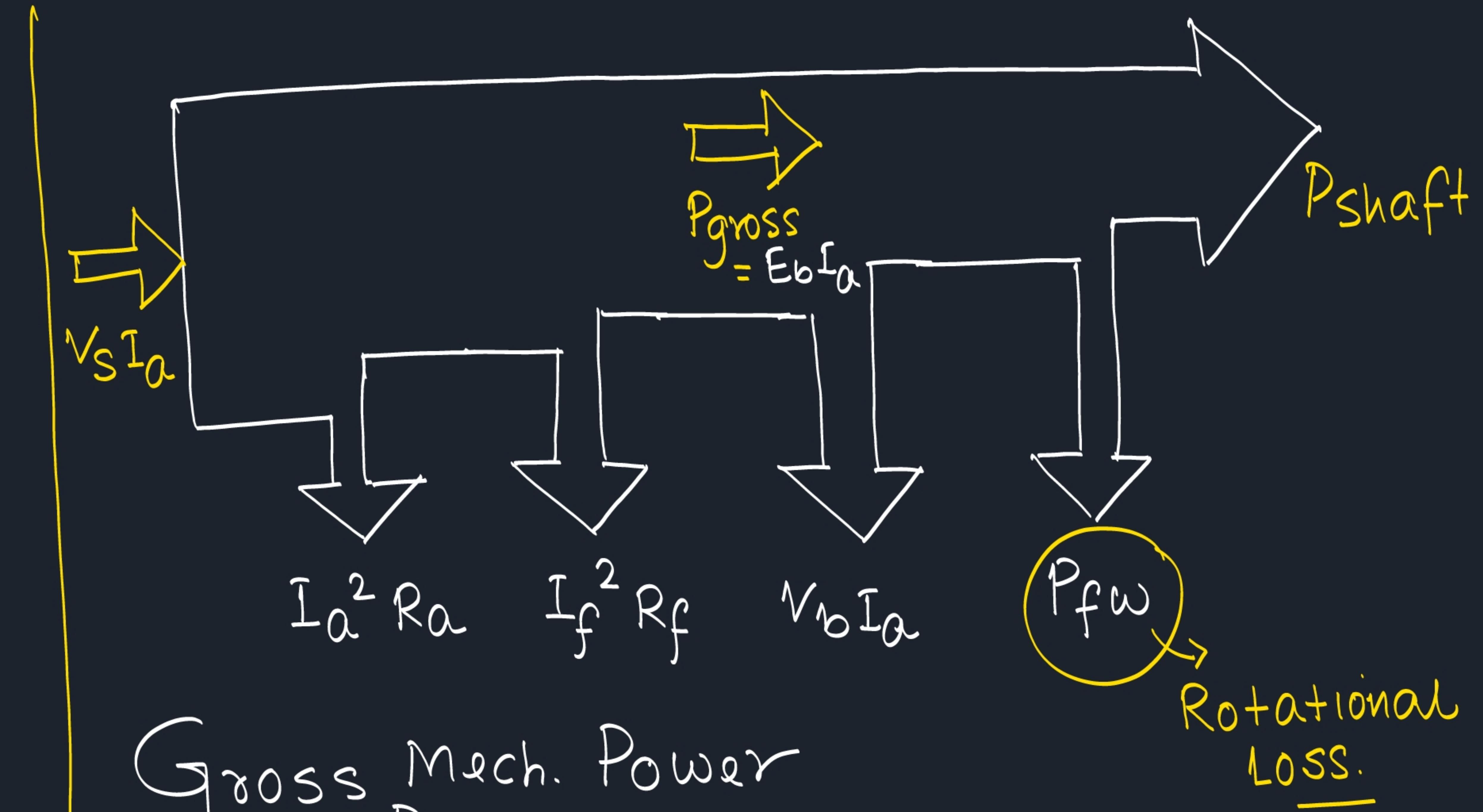
$$\tau_{shaft} = \frac{E_b I_a - P_{fw}}{\left( \frac{2\pi N}{60} \right)}$$



Gross Mech. Power  
Developed =  $E_b I_a$

Shaft power developed  
in the motor =  $P_{shaft}$ .

## Shunt DC Motor :-

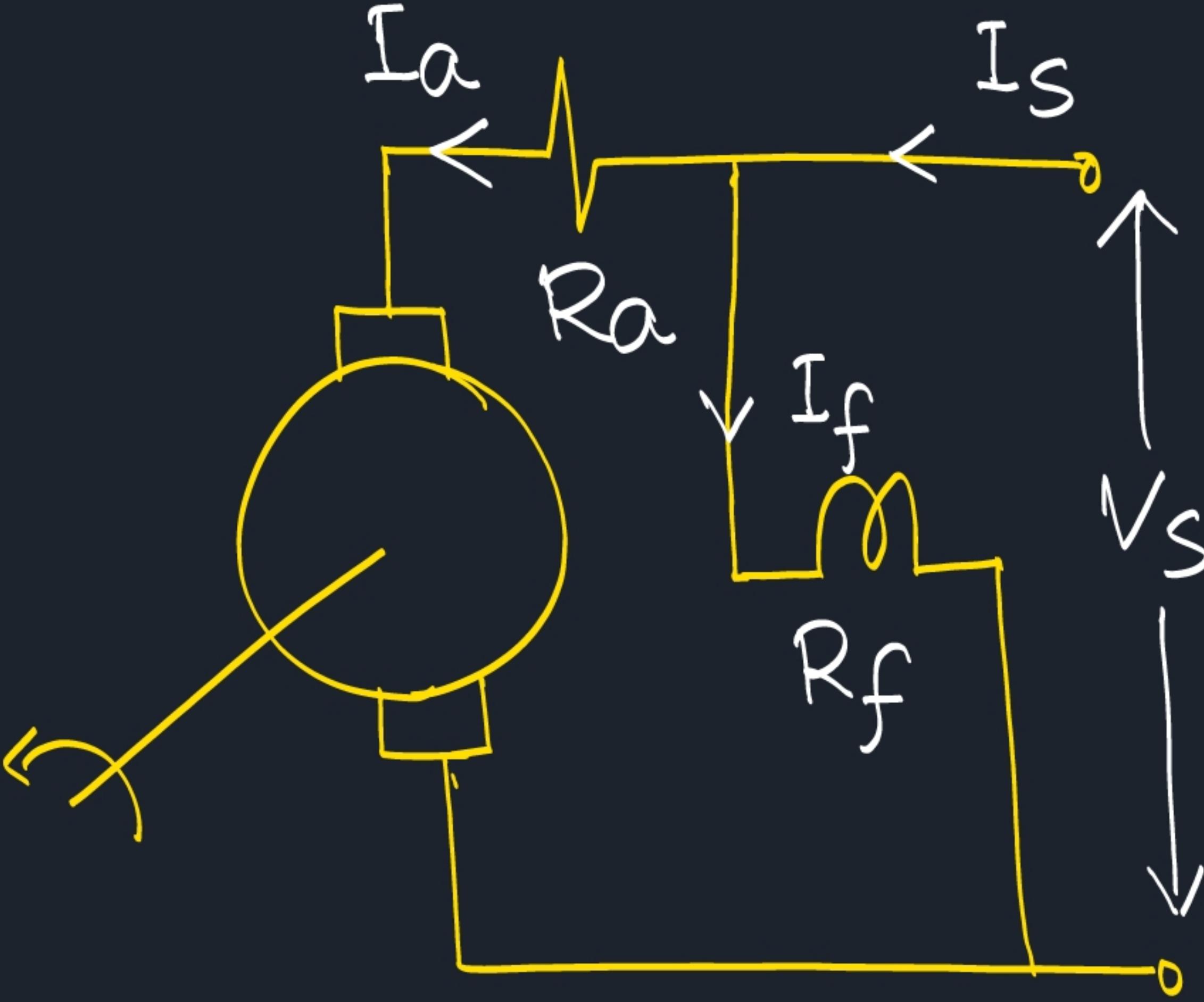

$$E_b = V_s - I_a R_a - V_b$$

$$I_f = \frac{V_s}{R_f}$$

$$I_a = I_s - I_f$$



$$P_{gross} = E_b I_a = \underbrace{\tau_{gross} \cdot \omega}_{\text{Gross Electromagnetic Torque developed.}}$$

$P_{fw}$ : Rotational Loss

$$P_{shaft} = E_b I_a - P_{fw}$$

$$\tau_{shaft} = \frac{E_b I_a - P_{fw}}{\left(\frac{2\pi N}{60}\right)}$$

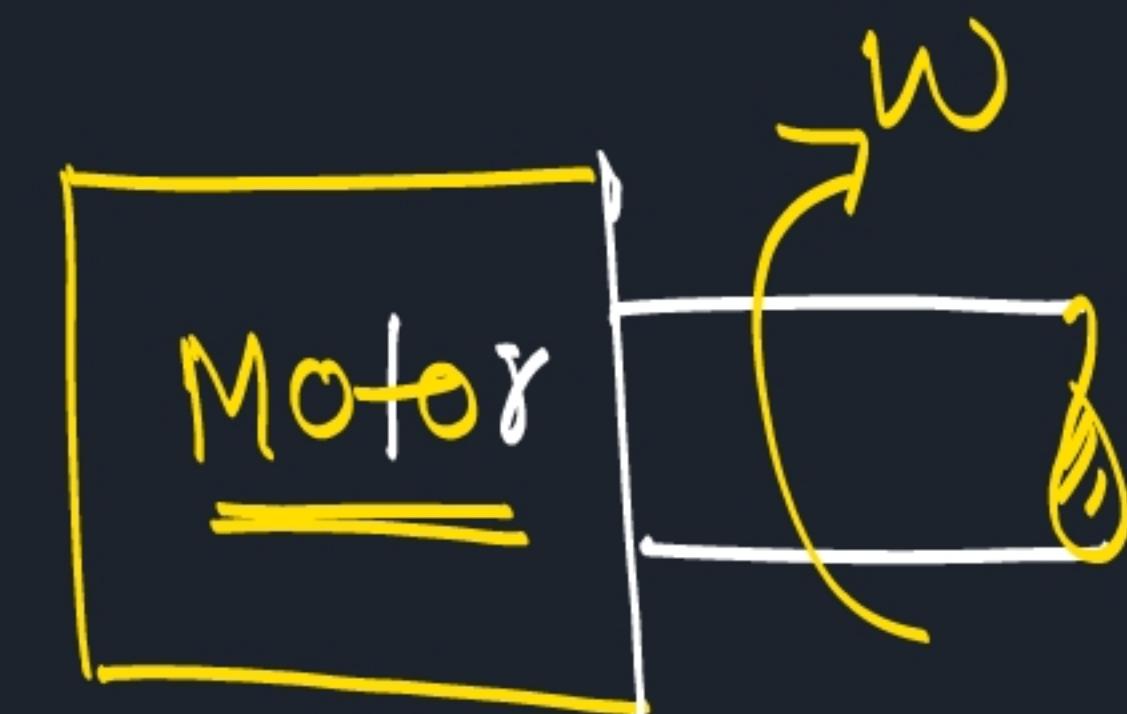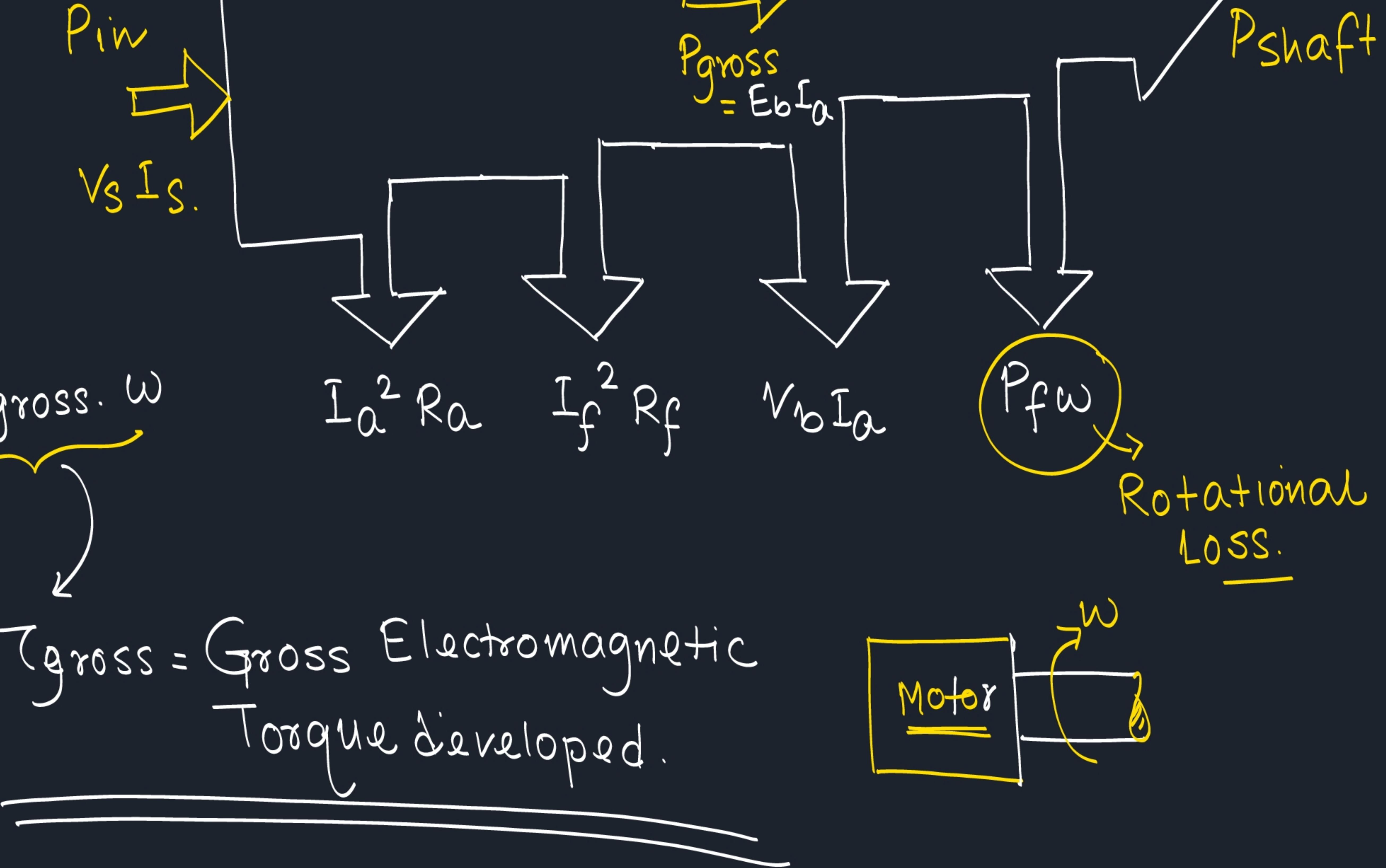Mechanical Torque available in  
motor shaft.



$$\boxed{\tau_e \cdot \omega = E_b I_a}$$

$$E_b = \frac{\Phi Z N}{60} \cdot \left( \frac{P}{A} \right) = \frac{\Phi Z}{60} \cdot \cancel{\frac{60}{2\pi}} \omega \cdot \left( \frac{P}{A} \right)$$

$$\omega = \frac{2\pi N}{60}$$

$$\begin{aligned}\tau_e \cdot \omega &= E_b I_a \\ &= K \phi \omega I_a\end{aligned}$$

$$= (\phi \omega) \cdot \left( \frac{Z P}{2\pi A} \right) \xrightarrow{K}$$

$$\boxed{\tau_e = K \phi I_a}$$

$$\boxed{N = \frac{60}{2\pi} \cdot \omega}$$

rpm

$$\boxed{E_b = K \phi \omega}$$

rad/sec.

Q/ Prob:-

4 pole, 220V dc Shunt Motor

It has 540 Lap wound conductors.

Motor Rating  $\Rightarrow$  5.595 kW


$$I_f = 1 \text{ A}$$

$$I_a = 32 \text{ A}$$

$$R_a = 0.09 \Omega$$

$$\Phi = 30 \text{ mwb.}$$

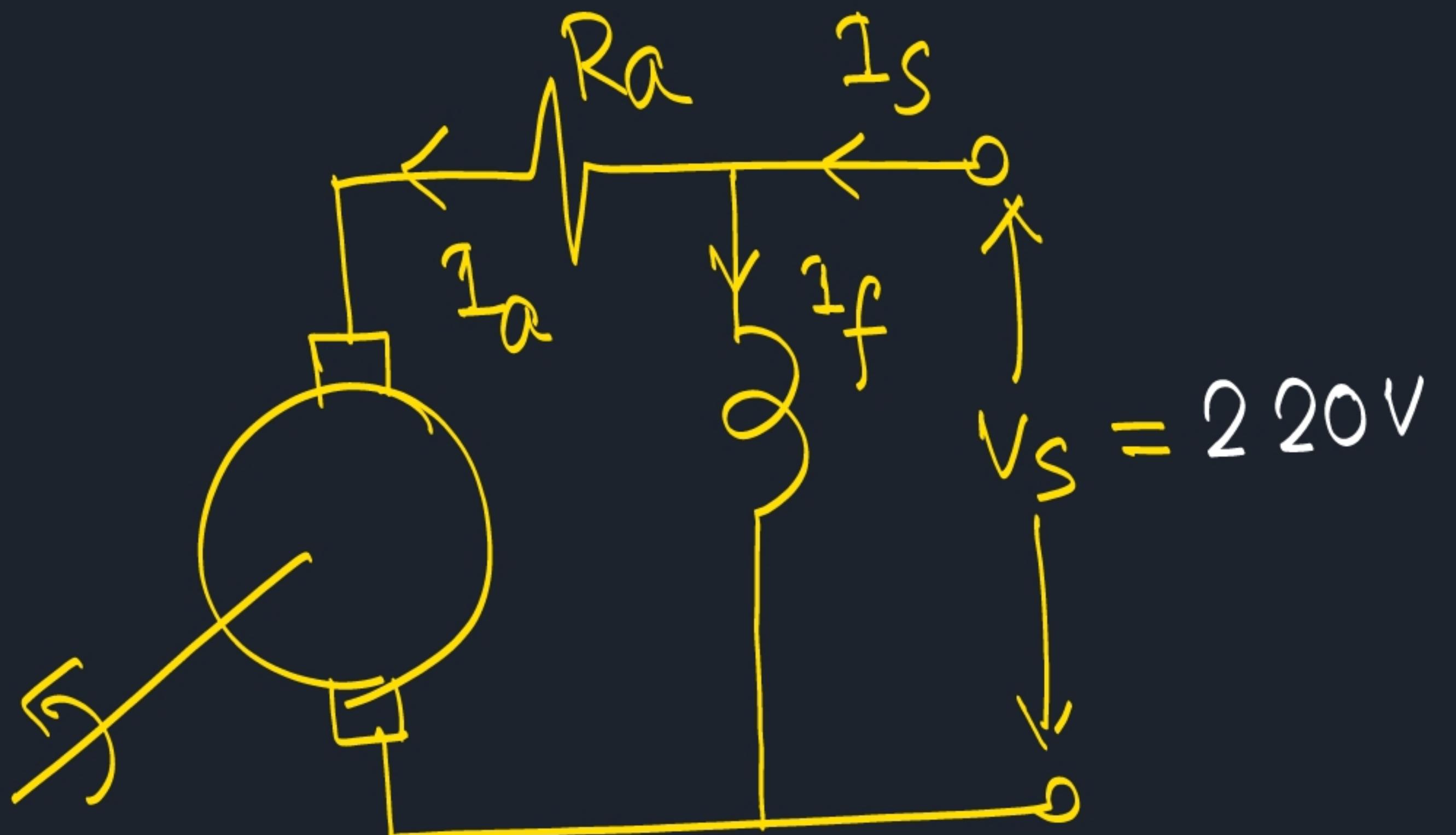- i) Speed.
- ii) Shaft torque developed.
- iii)  $P_{fw}$



$$E_b = ? \quad E_b = V_s - I_a R_a - V_o$$

$$E_b = 220 - (32 \times 0.09)$$

$$= 217.12 \text{ Volt}$$

$$E_b = \frac{\Phi Z N}{60} \left( \frac{P}{A} \right)$$

$$P_{fw} = E_b I_a - P_{shaft}$$

$$= \left\{ (217.12 \times 32) - 5595 \right\} \text{W}$$

$$= 1352.84 \text{ W}$$

Supply voltage = 220V

$P_{shaft} = 5.595 \text{ kW.}$  = Rating of the motor.

Lap wound  $A = P.$

$$217.12 = \frac{30 \times 10^{-3} \times 540 \times N}{60} \left( \frac{4}{4} \right)$$

$$N = 804.15 \text{ RPM.}$$

$$P_{shaft} = T_{shaft} \left( \frac{2\pi N}{60} \right)$$

$$T_{shaft} = \frac{5595 \times 60}{2\pi \times 804.15} \text{ N-m.}$$

$$= 66.44 \text{ N-m}$$

111


Prob:-

A 500 V DC Shunt Motor  
It takes a current of  
5A at no load.

$$R_a = 0.22 \Omega$$

$$R_f = 250 \Omega$$

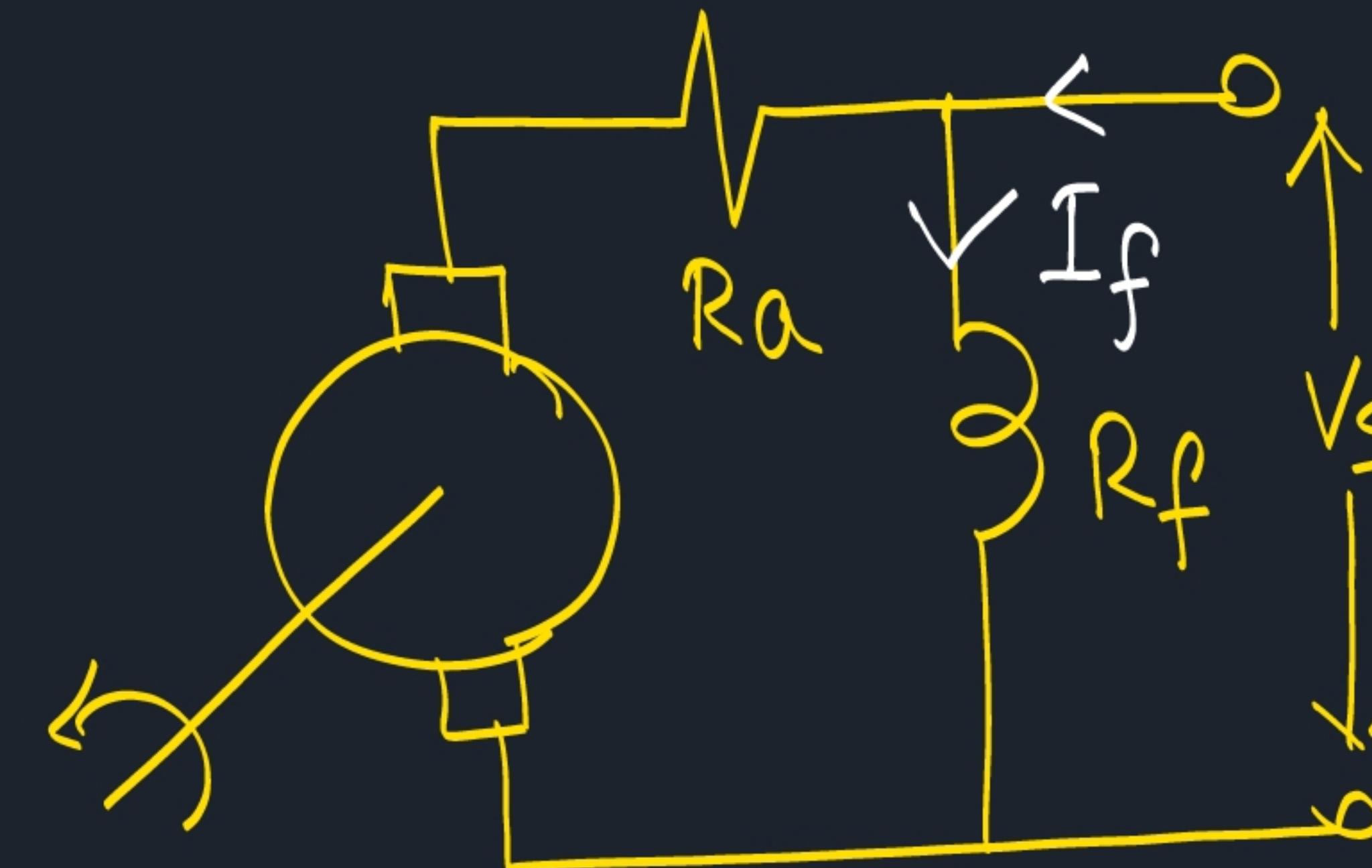Find  $\eta$  when the motor  
is taking a current of  
100 A.



Case-1 (No load) :-

$$E_b I_a = P_{\text{shaft}} + P_{fW}$$

$$E_b = 500 - (100 - 2) \times 0.22$$

$$\begin{aligned} P_{fW} &= E_b \cdot I_a \\ &= 1498.02 \text{ W} \end{aligned}$$

$$V_s = 500 \text{ V}$$

$$I_f = \frac{V_s}{R_f} = \frac{500}{250} = 2 \text{ A}$$

Case-2 (Load cond) :-

$$E_b = 500 - (100 - 2) \times 0.22$$

$$P_{\text{gross}} = E_b I_a$$

$$\begin{aligned} P_{\text{shaft}} &= E_b I_a - 1498.02 \\ &= 45389.5 \text{ W} \end{aligned}$$

$$\begin{aligned} \eta &= \frac{P_{\text{out}}}{P_{\text{in}}} \times 100 \\ &= \frac{45389.5 \times 100}{100 \times 500} \end{aligned} = ?$$


Prob :-

Shunt  
220V DC Motor  
Runs @ 500 rpm  
Armature current = 50A

$$R_a = 0.2 \Omega$$

Calculate the speed if  
torque is doubled.

$$\Phi \propto I_f$$

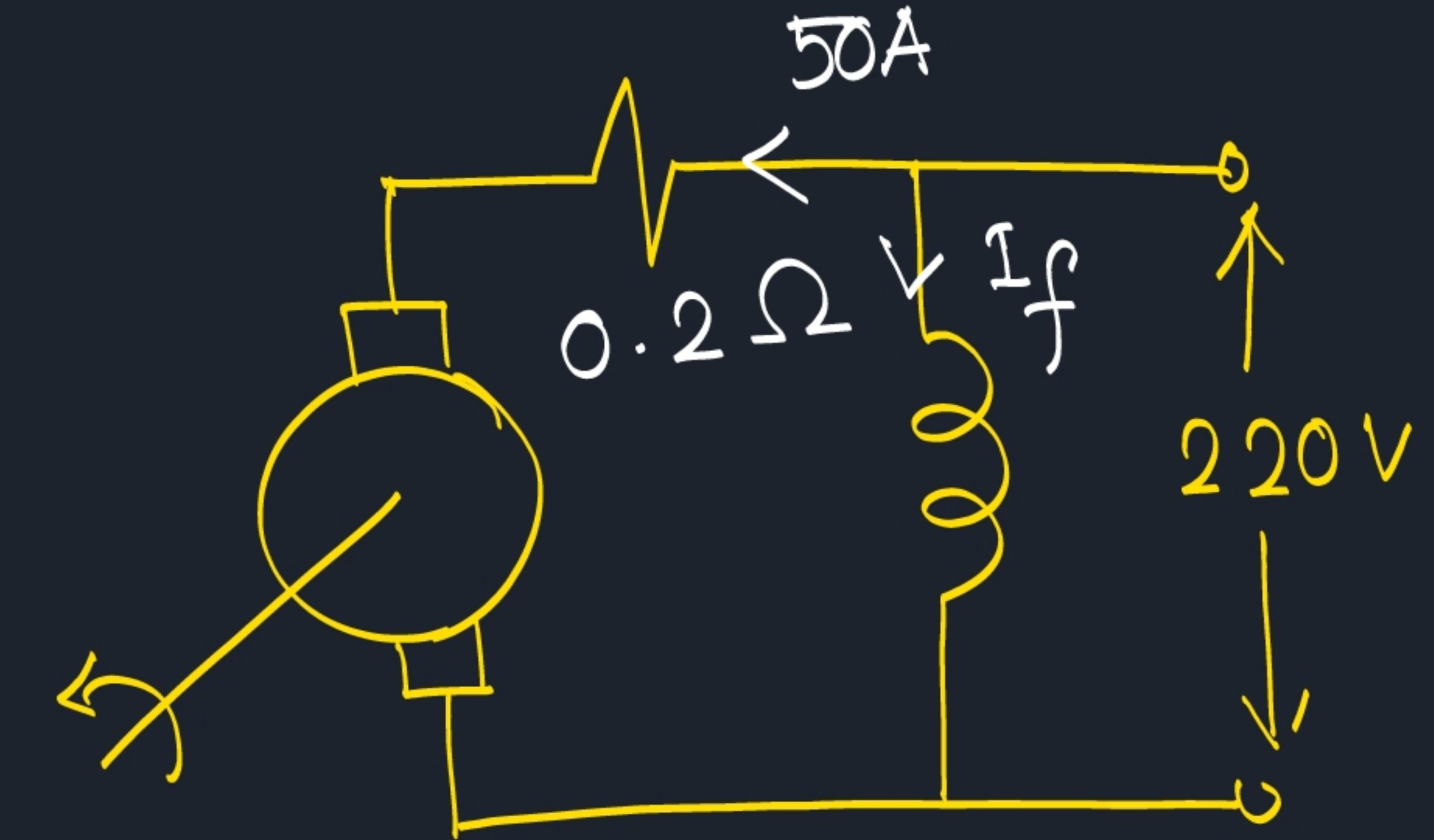

flux is fixed

$$\begin{aligned} T &\propto \Phi I_a \\ E_b &\propto \Phi \omega \\ E_b &\propto \Phi N \end{aligned}$$

$$\Phi_1 = \Phi_2$$

$$\begin{aligned} T_1 &= T, I_{a1} = 50A \\ T_2 &= 2T, I_{a2} = ? \end{aligned}$$

$$E_b = V_t - I_{a1} R_a$$

$$\frac{T_1}{T_2} = \frac{\Phi_1 I_{a1}}{\Phi_2 I_{a2}}$$

$$\frac{T_1}{T_2} = \frac{I_{a1}}{I_{a2}}$$

$$\frac{T}{2T} = \frac{50}{I_{a2}}$$

$$I_{a2} = 50 \times 2 = 100 \text{ Amps.}$$

$$\frac{V_t - I_{a1} R_a}{V_t - I_{a2} R_a} = \frac{500}{N_2}$$

$$\frac{E_{b1}}{E_{b2}} = \frac{\Phi_1 N_1}{\Phi_2 N_2} = \frac{N_1}{N_2}$$

$$\Rightarrow \frac{220 - 50 \times 0.2}{220 - 100 \times 0.2} = \frac{500}{N_2}$$

$$N_2 = 476 \text{ rpm}$$


Prob :-

500 V DC shunt motor  
draws a line current of 5A  
@ no load.

$$R_a = 0.15 \Omega$$

$$R_f = 200 \Omega$$

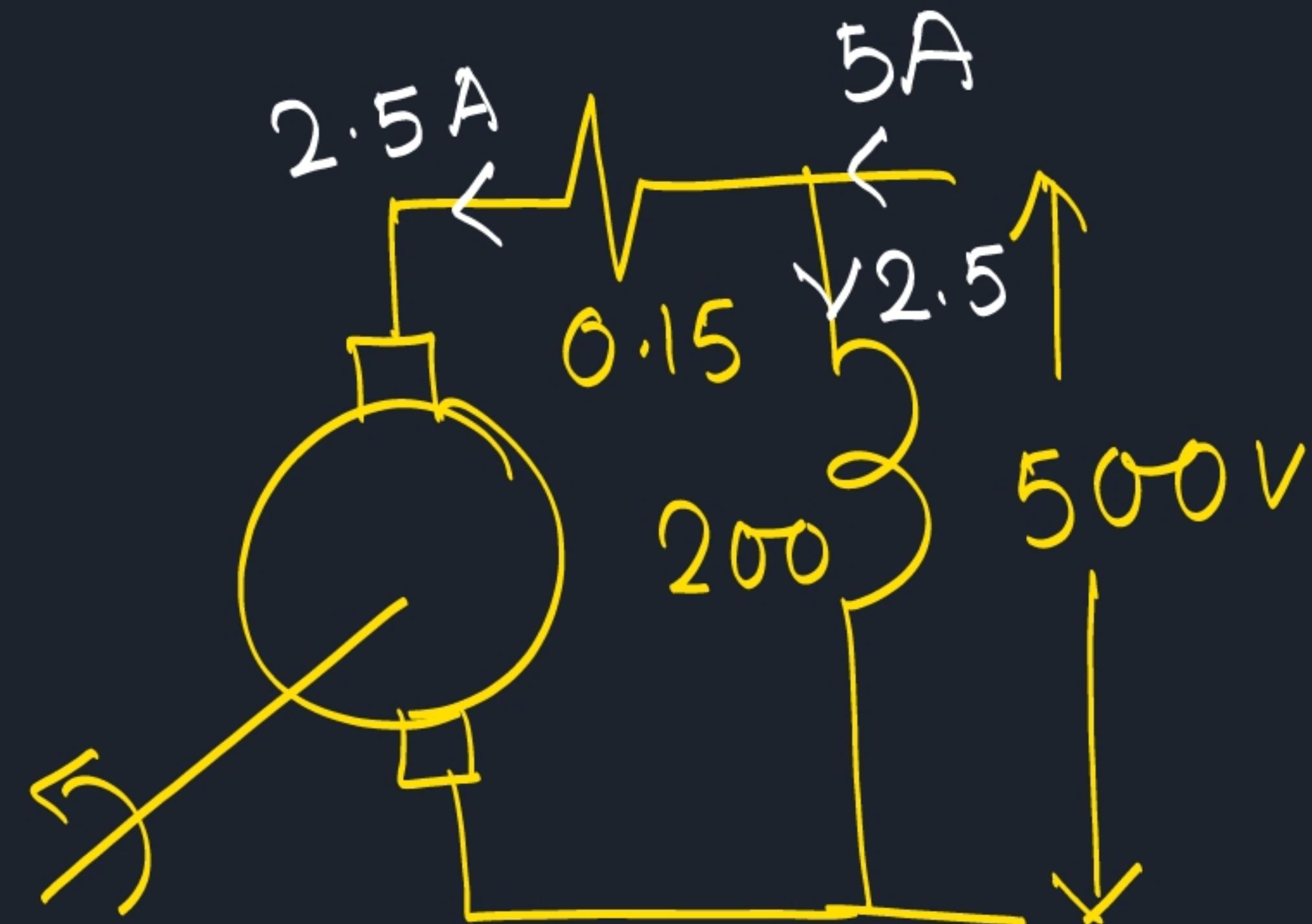
Determine  $\eta$  of the m/c  
running as DC shunt gen  
delivering a load current of  
40 Amps.



$$E_b I_a = P_{shunt} + P_{fw}$$

$$E_b = V_t - I_a R_a \\ = (500 - 2.5 \times 0.15)$$
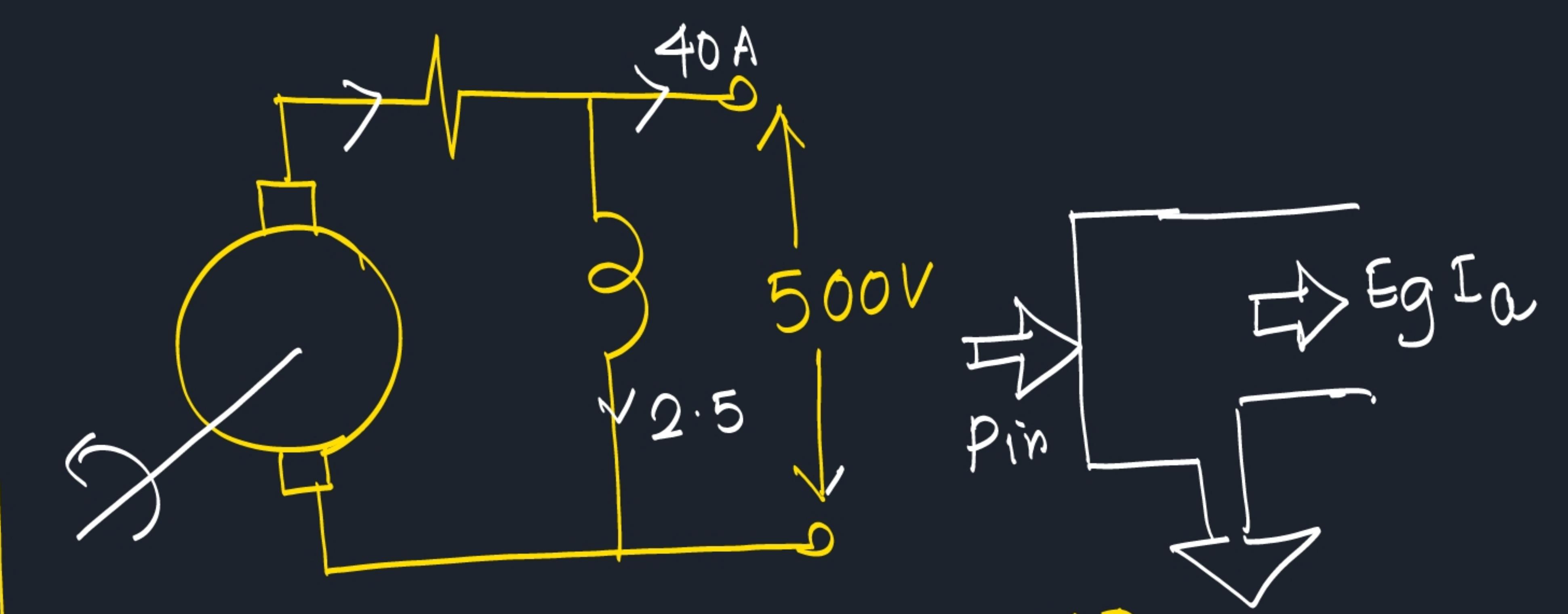
$$P_{fw} = E_b \times 2.5 \\ = 1249.06 \text{ W}$$



$$P_{out} = (40 \times 500) \text{ W} = 20,000 \text{ W}$$

$$E_g = V_t + I_a R_a \\ = 500 + (40 + 2.5) \times 0.15$$

$$E_g I_a = ?$$

$$P_{in} = E_g I_a + P_{fw} = 22770 \text{ W}$$

$$\eta = \frac{20,000 \times 100}{22770} = 87.8\%$$

## Prob:-

230 V DC Shunt motor

$$R_a = 0.5 \Omega$$

$$R_f = 115 \Omega$$

@ no load Speed = 1200 rpm  
4 armature current  
= 2.5 A

\* When rated load applied to  
the motor speed drops to 1120 rpm

Determine Armature Current @  
rated load.

$$\begin{aligned} T &\propto \Phi I_a \checkmark \\ E_b &\propto \Phi \omega \checkmark \\ \Rightarrow N_t - I_a R_a \end{aligned}$$

$$\frac{V_t - I_{a_1} R_a}{V_t - I_{a_2} R_a} = \frac{N_1}{N_2}$$

$$\Rightarrow \frac{230 - 2.5 \times 0.5}{230 - I_{a_2} \times 0.5} = \frac{1200}{1120}$$

$$\Rightarrow I_{a_2} = \underline{\underline{33 \text{ Amps.}}}$$