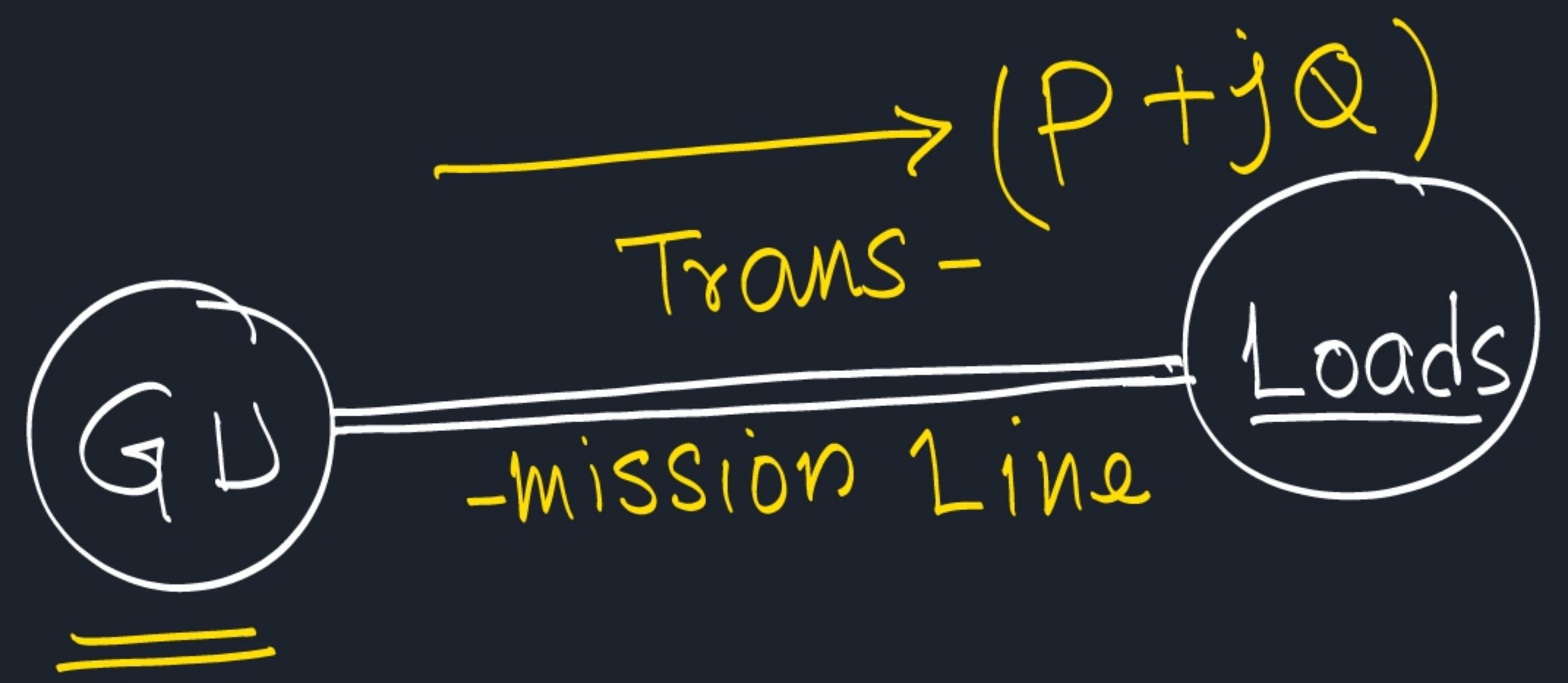


Transformer :-




$$P_{3\phi} = 3 V_{ph} I_{ph} \cos \theta$$


$$I_{ph} = \frac{P_{3\phi}}{3 V_{ph} \cos \theta}$$

$$\begin{aligned} P_{loss} &= 3 (I_{ph})^2 \cdot R_{ph} \\ &= 3 \cdot \frac{P_{3\phi}^2}{9 V_{ph}^2 \cos^2 \theta} \cdot R_{ph} \end{aligned}$$

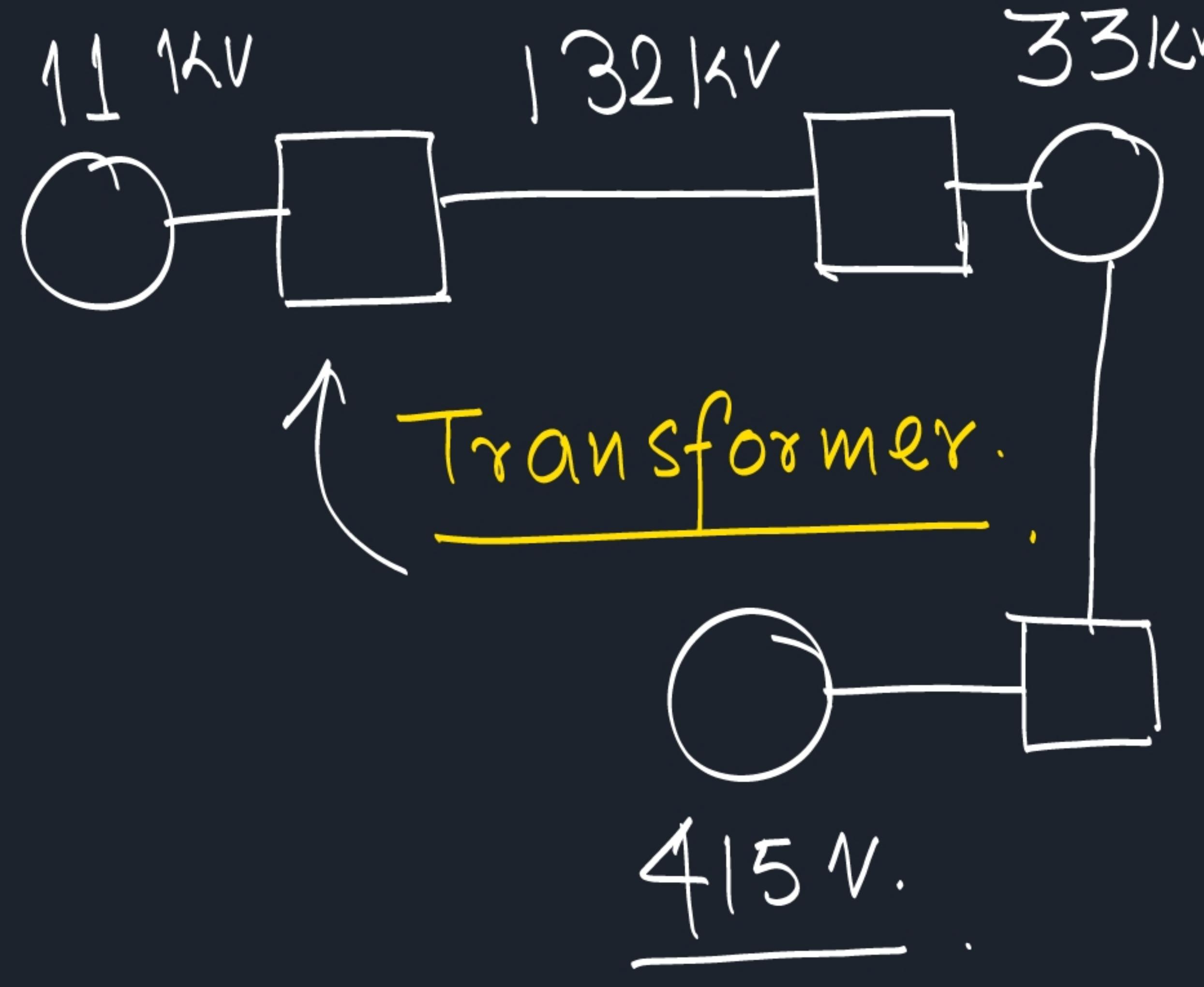$P_{loss} \propto \frac{1}{V_{ph}^2}$ (if $P_{3\phi}, \cos \theta$ Constant)




1. Step Up ↗
2. Step Down ↘

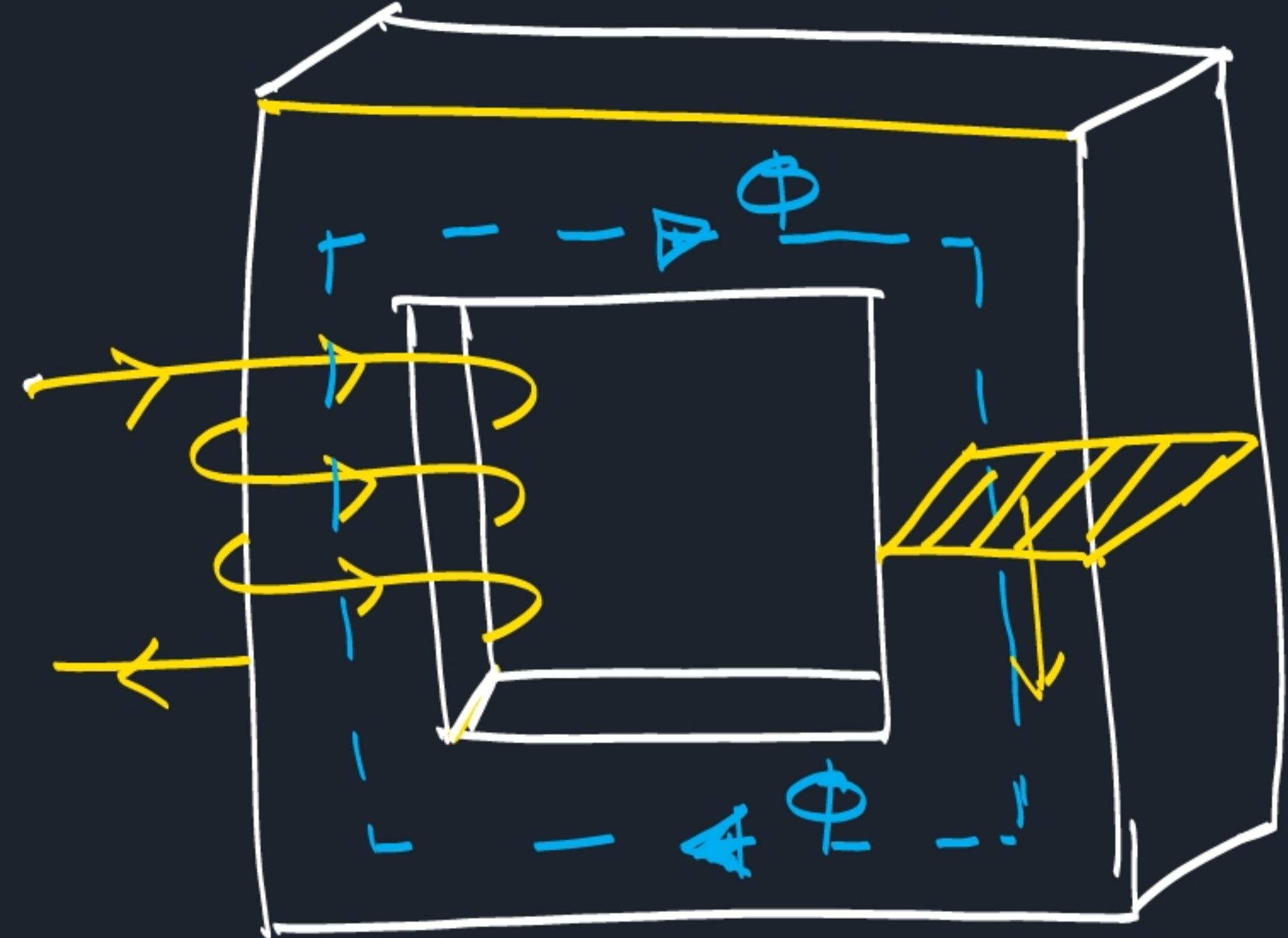

$$\Phi = \vec{B} \cdot \vec{A} = BA \cos \theta$$

$$\boxed{\Phi = BA} \quad \boxed{B = \mu H}$$
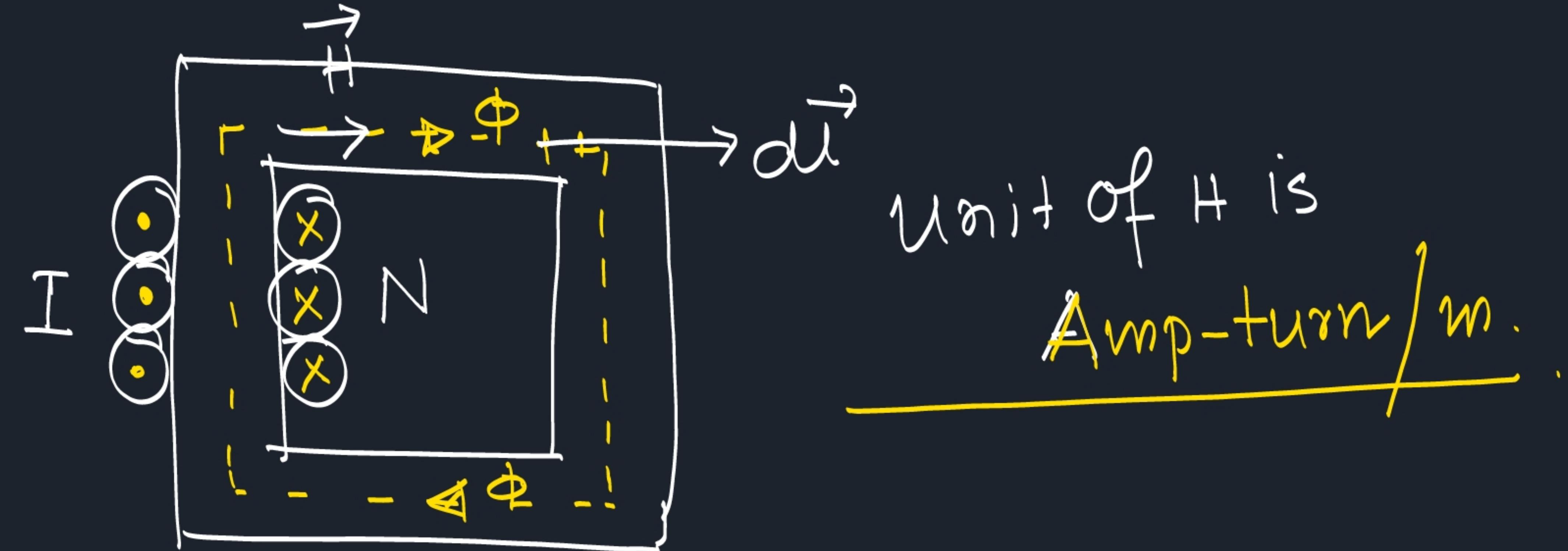
$$\boxed{\mu = \mu_0 \mu_r} \quad 4\pi \times 10^{-7}$$



Ampere's Circuital Law.

$$\oint \vec{H} \cdot d\vec{l} = NI$$


$$H \cdot l = NI$$

$$\Rightarrow H = \frac{NI}{l}$$

$$\Rightarrow B = \frac{NI}{l/\mu}$$

$$\boxed{\Phi = \frac{NI}{R}}$$

$$\boxed{i = \frac{V}{R}}$$

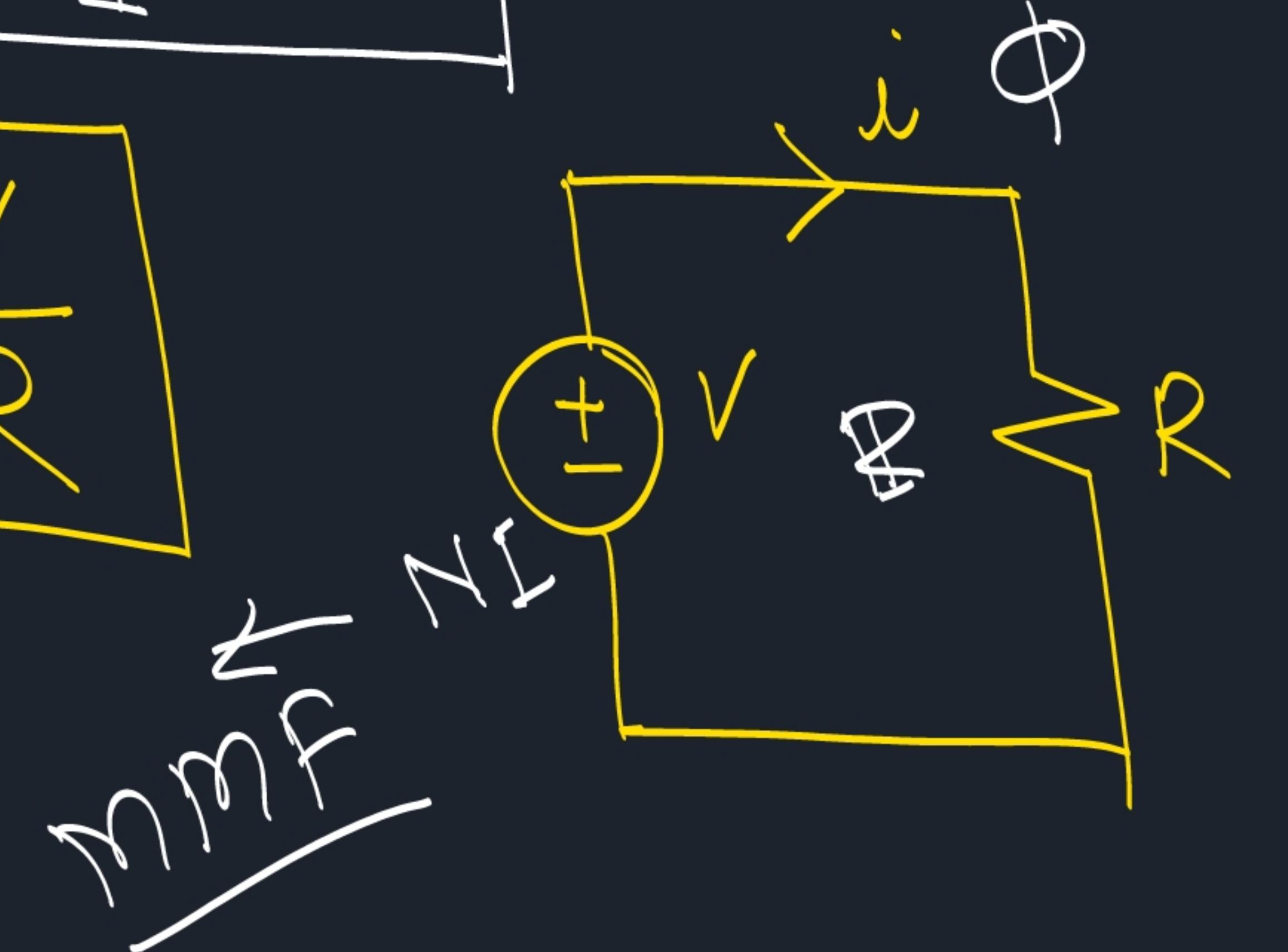

$$\boxed{R = \frac{l}{A \mu_0 \mu_r}}$$


$$\Phi = BA = \frac{NI}{R}$$

$$\frac{l}{\mu A}$$

Reluctance

R

Φ

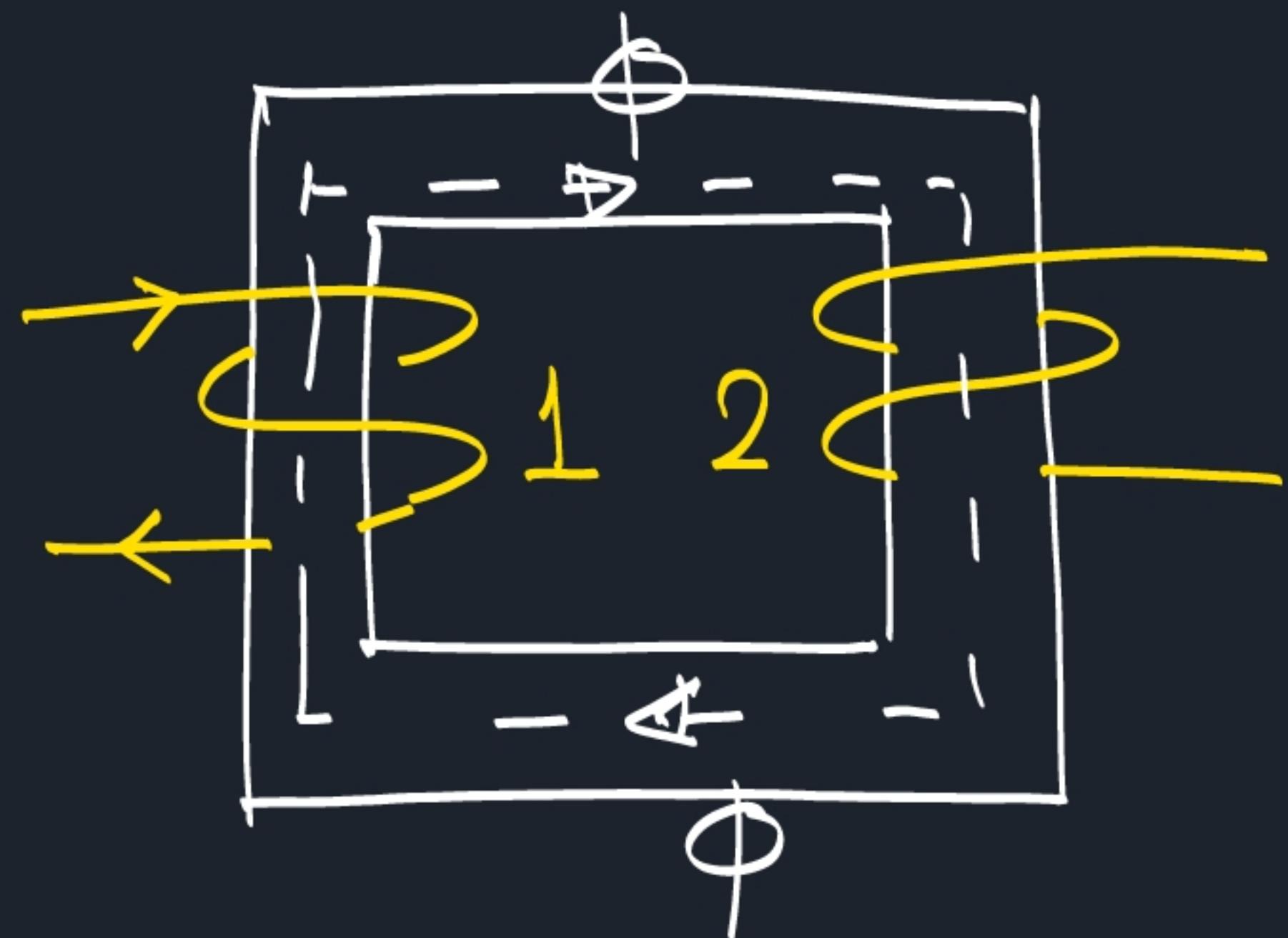

$$\ell_1(t) = -N_1 \frac{d\phi}{dt}$$

$$\frac{\ell_1}{N_1} = - \frac{d\phi}{dt}$$

$$\frac{\ell_1}{N_1} = \frac{\ell_2}{N_2}$$


$$\boxed{\frac{\ell_1}{\ell_2} = \frac{N_1}{N_2}}$$

$$N_1 < N_2$$

$\ell_1 < \ell_2 \Rightarrow \text{Step up } T/F.$

$$N_1 > N_2$$

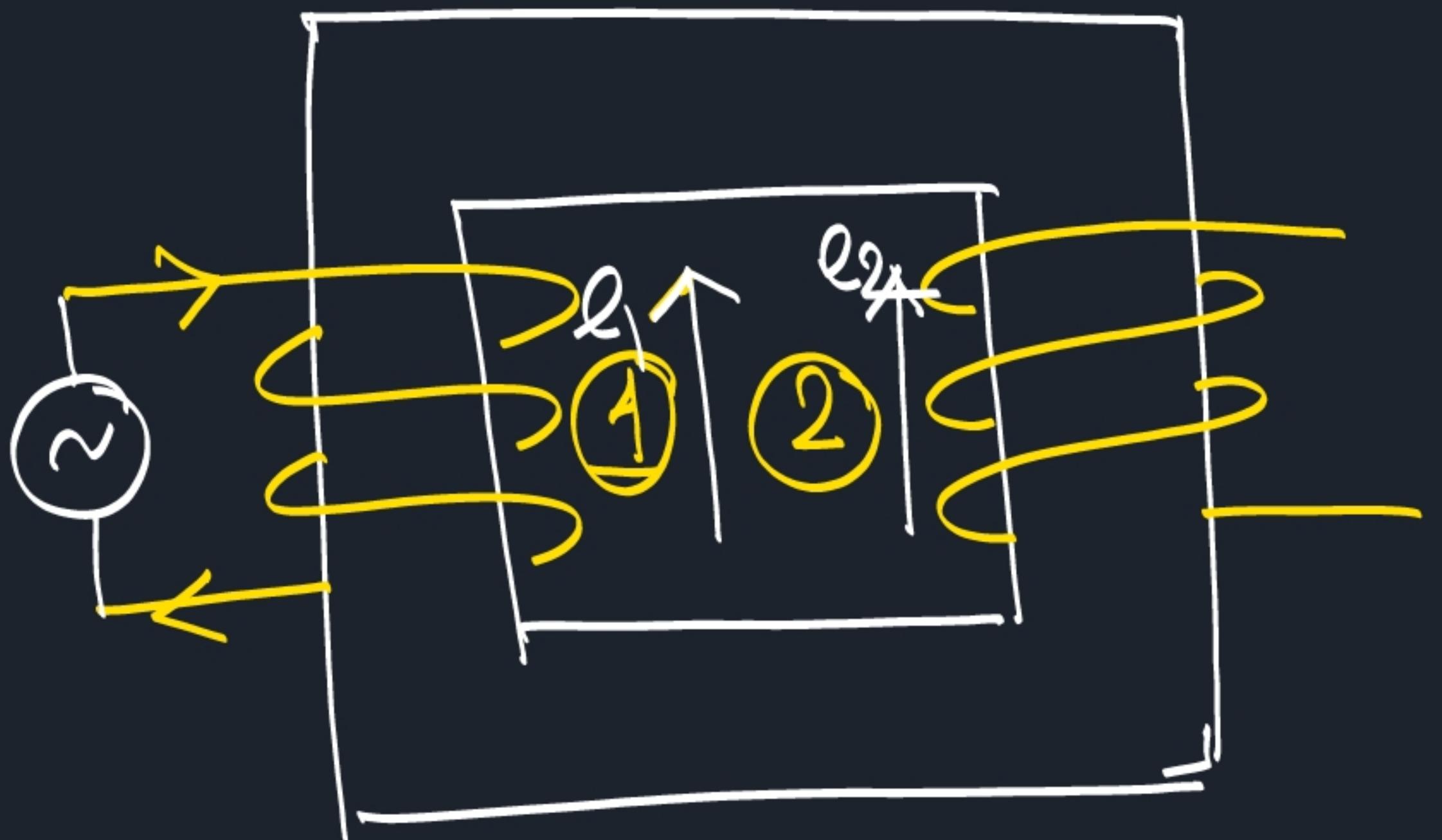$\ell_1 > \ell_2 \Rightarrow \text{Step down } T/F.$



$$e_1 = ? \quad e_2 = ?$$

$$e_1(t) = -N_1 \frac{d\phi(t)}{dt}$$

$$\underline{\phi = BA}$$

$$= B_m \sin \omega t \cdot A$$

$$= \Phi_m \sin \omega t$$

① → Primary

② → Secondary

$$e_1(t) = N_1 \frac{d\phi(t)}{dt}$$

$$e_1(t) = N_1 \Phi_m \omega \cos \omega t \\ = N_1 \Phi_m \omega \sin(\omega t + \pi/2)$$

$$E_1 = \frac{N_1 \Phi_m \omega}{\sqrt{2}}$$

$$= \frac{N_1 \Phi_m 2\pi f}{\sqrt{2}} \cdot$$

$$= \frac{2\pi}{\sqrt{2}} \Phi_m f N_1$$

$$E_1 = 4.44 f \Phi_m N_1$$

$$E_2 = 4.44 f \Phi_m N_2$$


$$f = 50 \text{ Hz}$$

→ Peak Flux.

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\Phi_m \propto E_1$$

T/F → constant flux $\frac{m}{c}$.

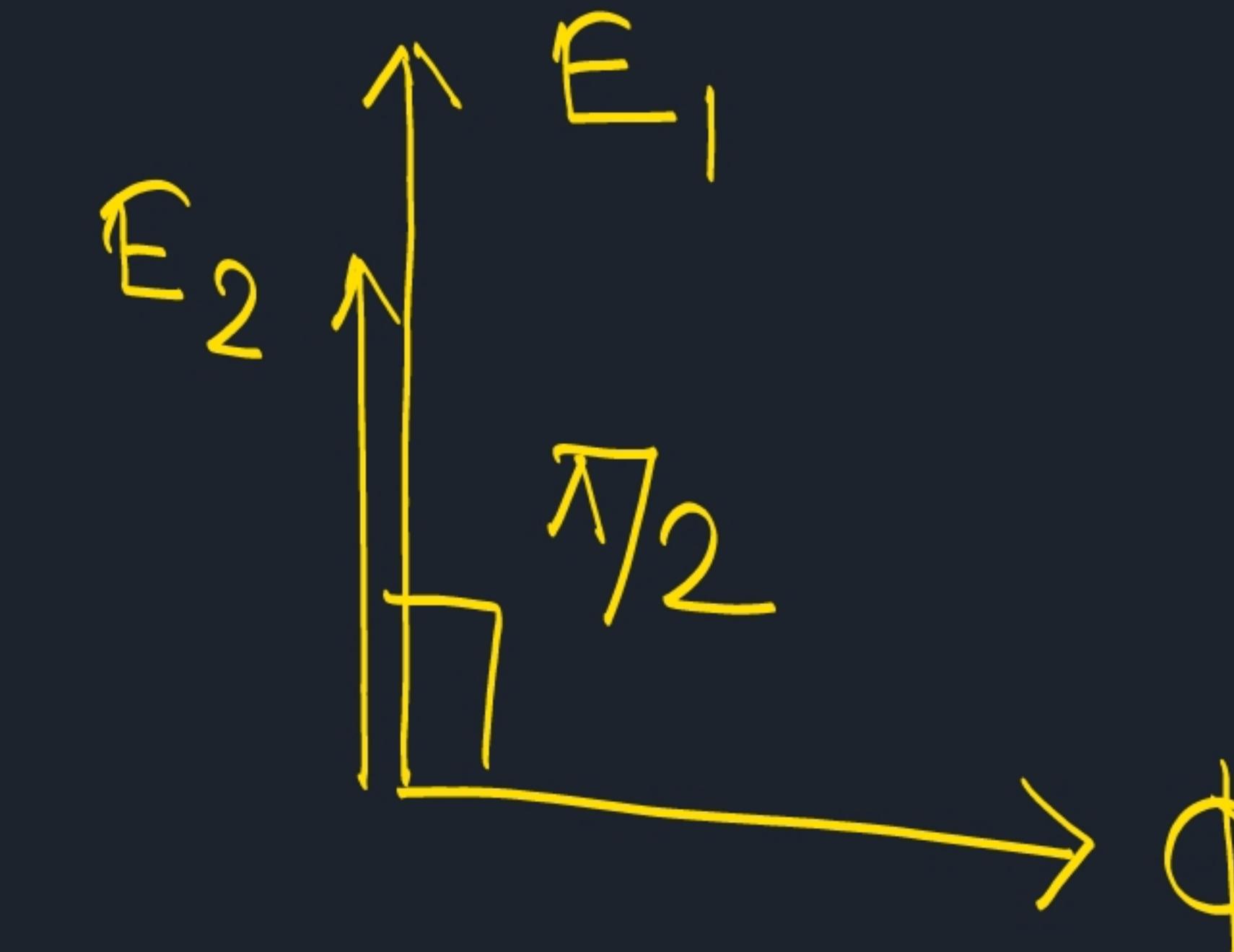

$$\Phi = \frac{NI}{R}$$





$$R = \frac{l}{A \mu_0 \mu_s}$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \dots (i)$$

$$I_1 N_1 = I_2 N_2 \dots (ii)$$

3003

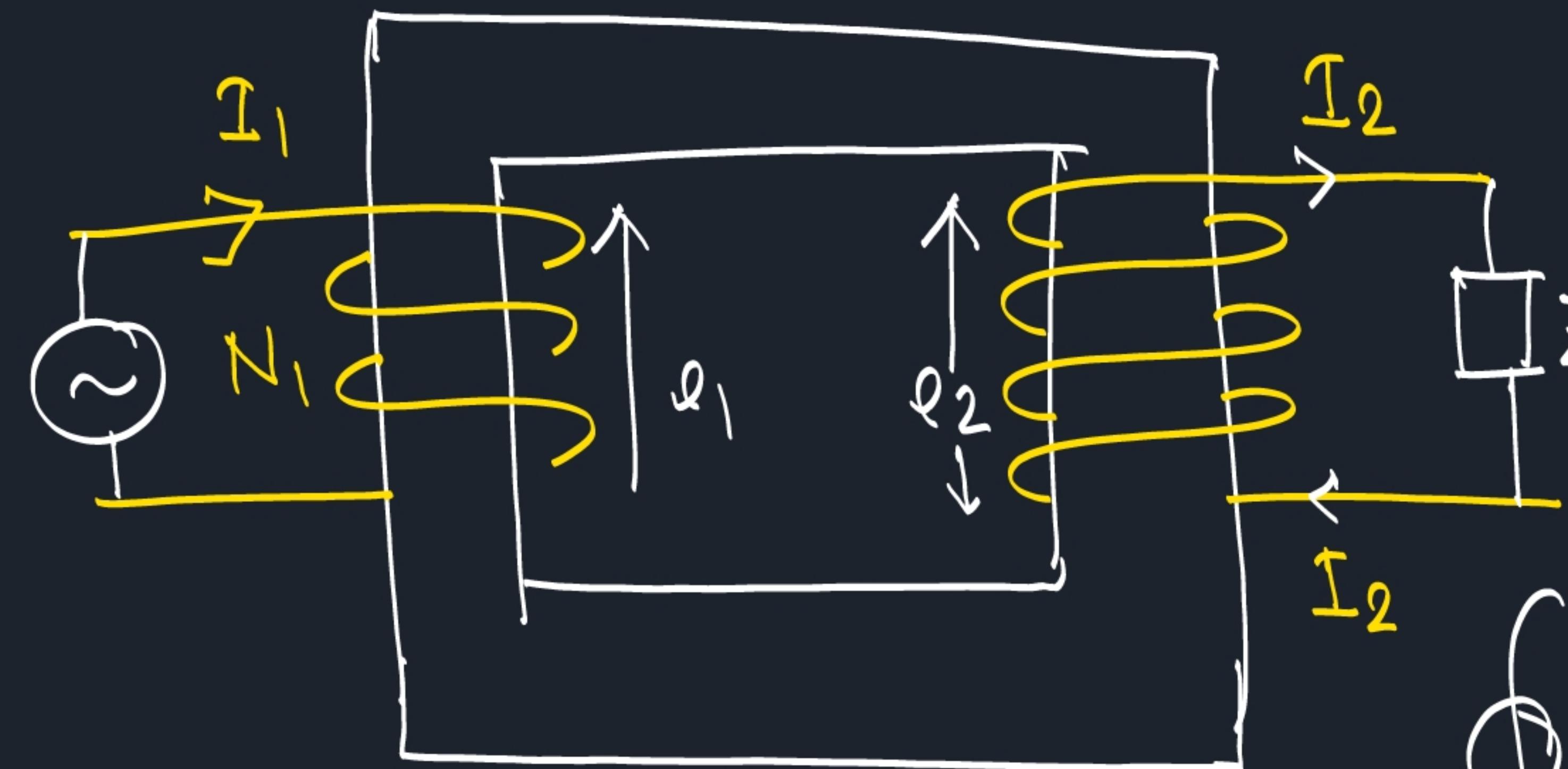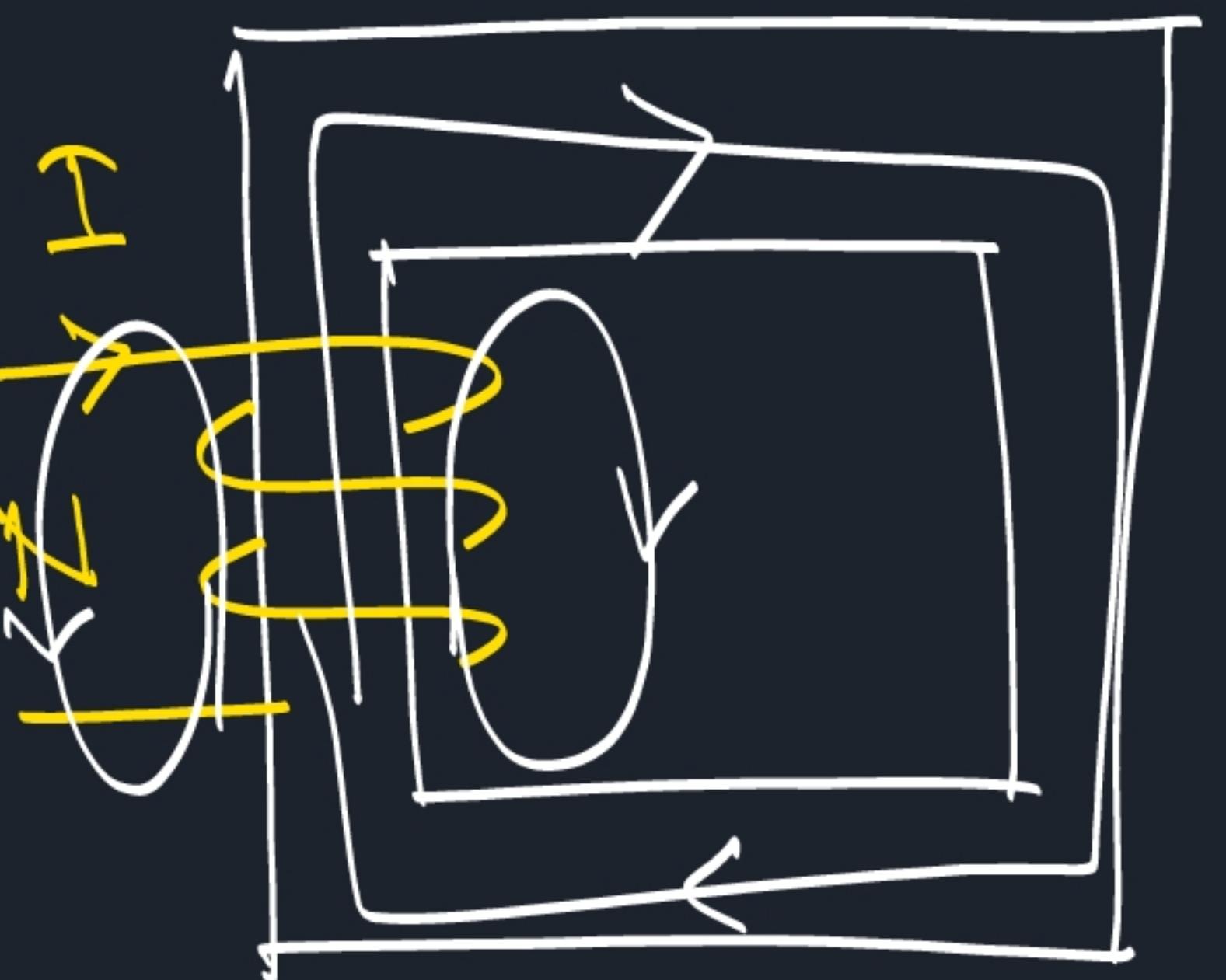

$$I_2 = \frac{E_2}{Z}$$



Ideal Case


$$R \rightarrow 0$$

$$\mu_s \rightarrow \infty$$

$$H = \frac{NI}{l}$$

$$\eta_{T/F} \rightarrow 100\%$$

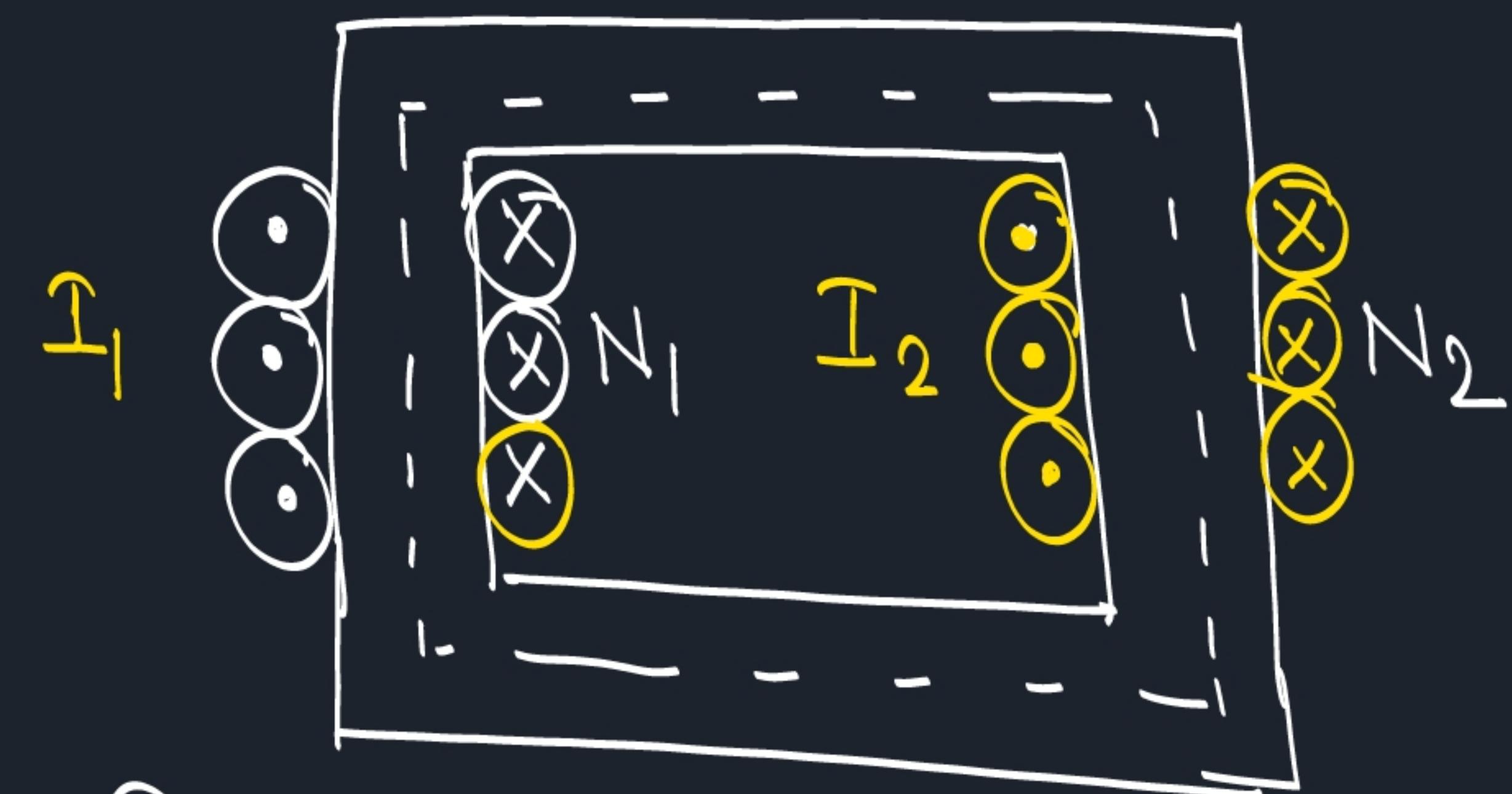
$$V_1 I_1 = V_2 I_2 \Rightarrow \text{VA Rating}$$



$$\oint \vec{H} \cdot d\vec{u} = N_1 I_1 - N_2 I_2 = 0$$

$$N_1 I_1 = N_2 I_2$$

mmf Balance.

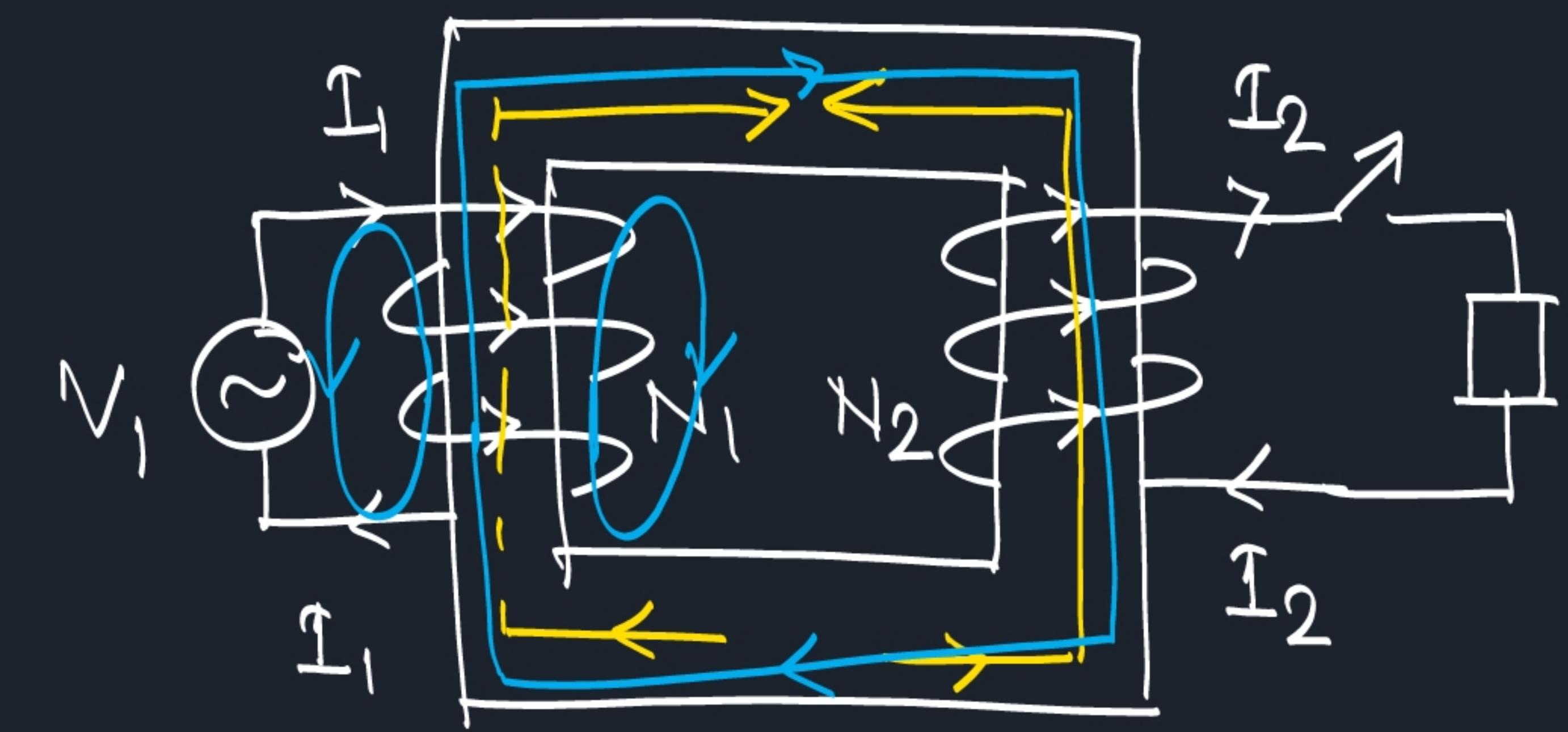

$$\Phi_{\text{total}} = \Phi_m + \Phi_{e1}$$

$$\Phi_m = \frac{N_1 I_m - N_2 I_2 + N_1 I_1'}{R}$$

$$\Phi_m = \frac{N_1 I_m}{R}$$

$$\Phi_m' = \frac{N_1 I_m - I_2 N_2}{R}$$

$$N_1 I_1' = N_2 I_2$$


$$I_1 = I_m + I_1'$$



$$V_1 = E_1 + I_1 R_1 + j I_1 X_{e1}$$

$$\begin{aligned} E_1^{\text{total}} &= 4.44 f \Phi_{\text{total}} N_1 \\ &= 4.44 f (\Phi_m + \Phi_{e1}) N_1 \\ E_1^{\text{total}} &= \underbrace{4.44 f \Phi_m N_1}_{\text{Magnetic Energy}} + \underbrace{4.44 f \Phi_{e1} N_1}_{\text{Electromagnetic Energy}} \end{aligned}$$


$$V_1 - I_1 R_1 = E_1^{\text{total}} = \underbrace{4.44 f \Phi_m N_1}_{\text{Magnetic Energy}} + E_{e1} \\ = E_1 + E_{e1}$$

$$V_1 - E_1 = I_1 R_1 + E_{e1}$$

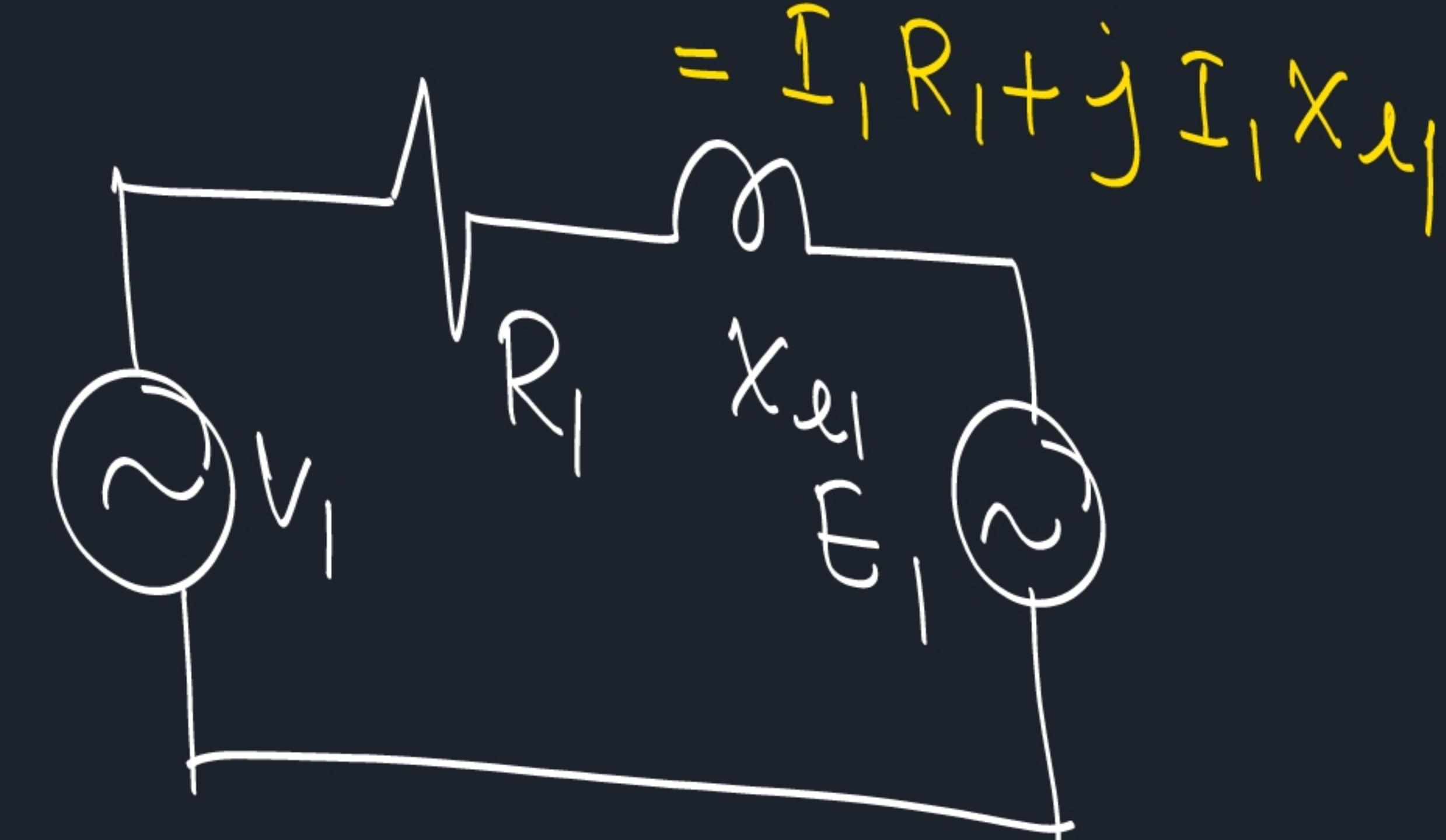

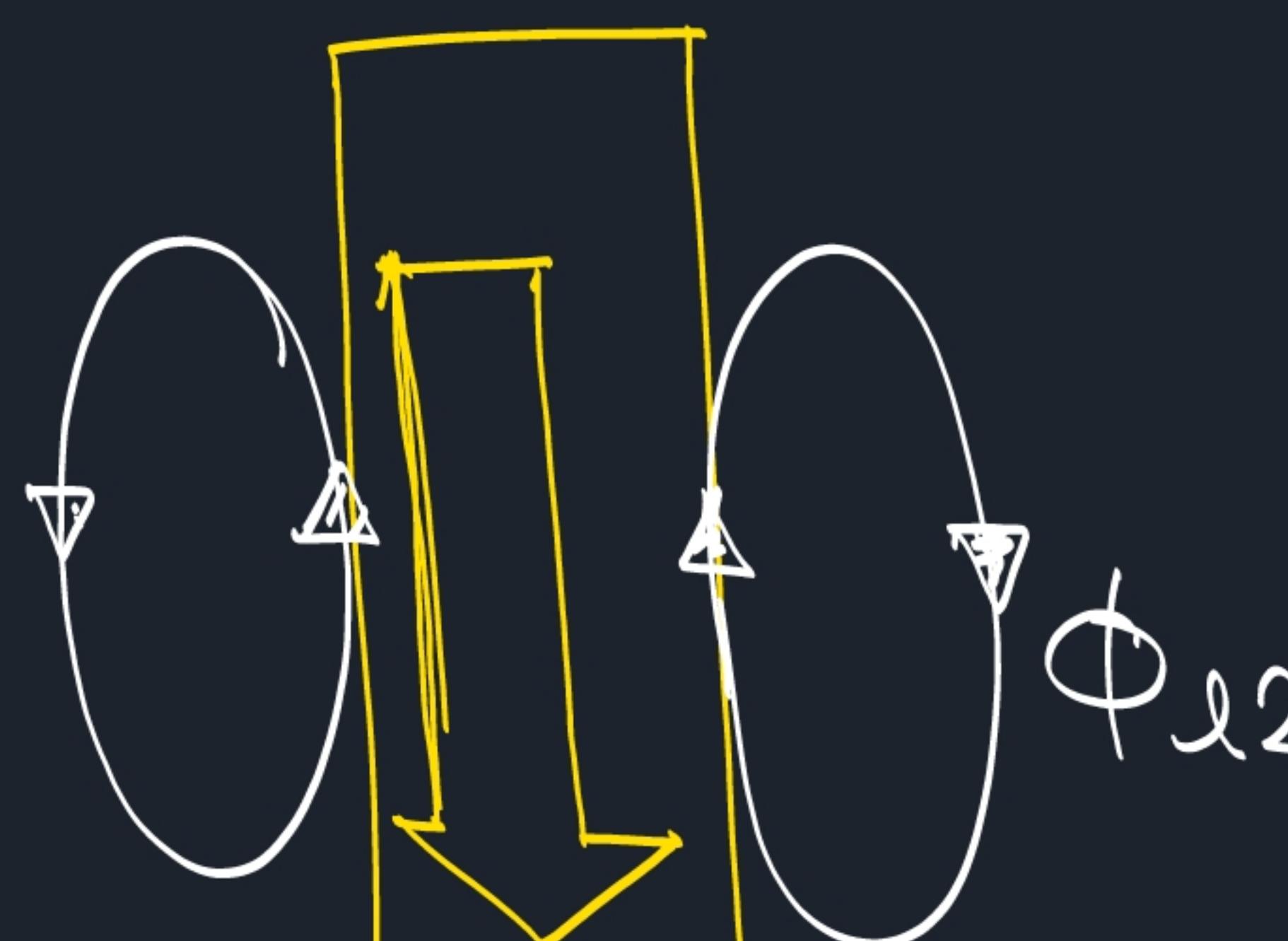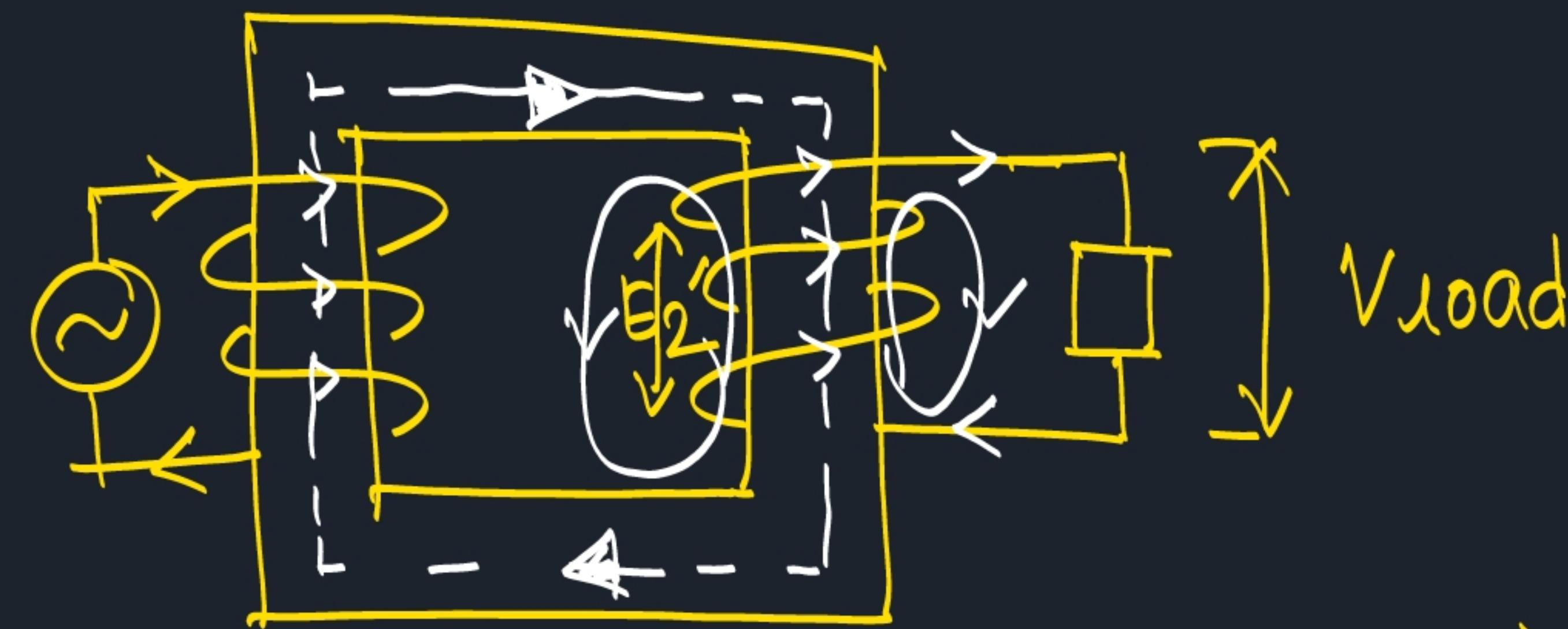


$$\Phi_m \gg \Phi_{l2}$$

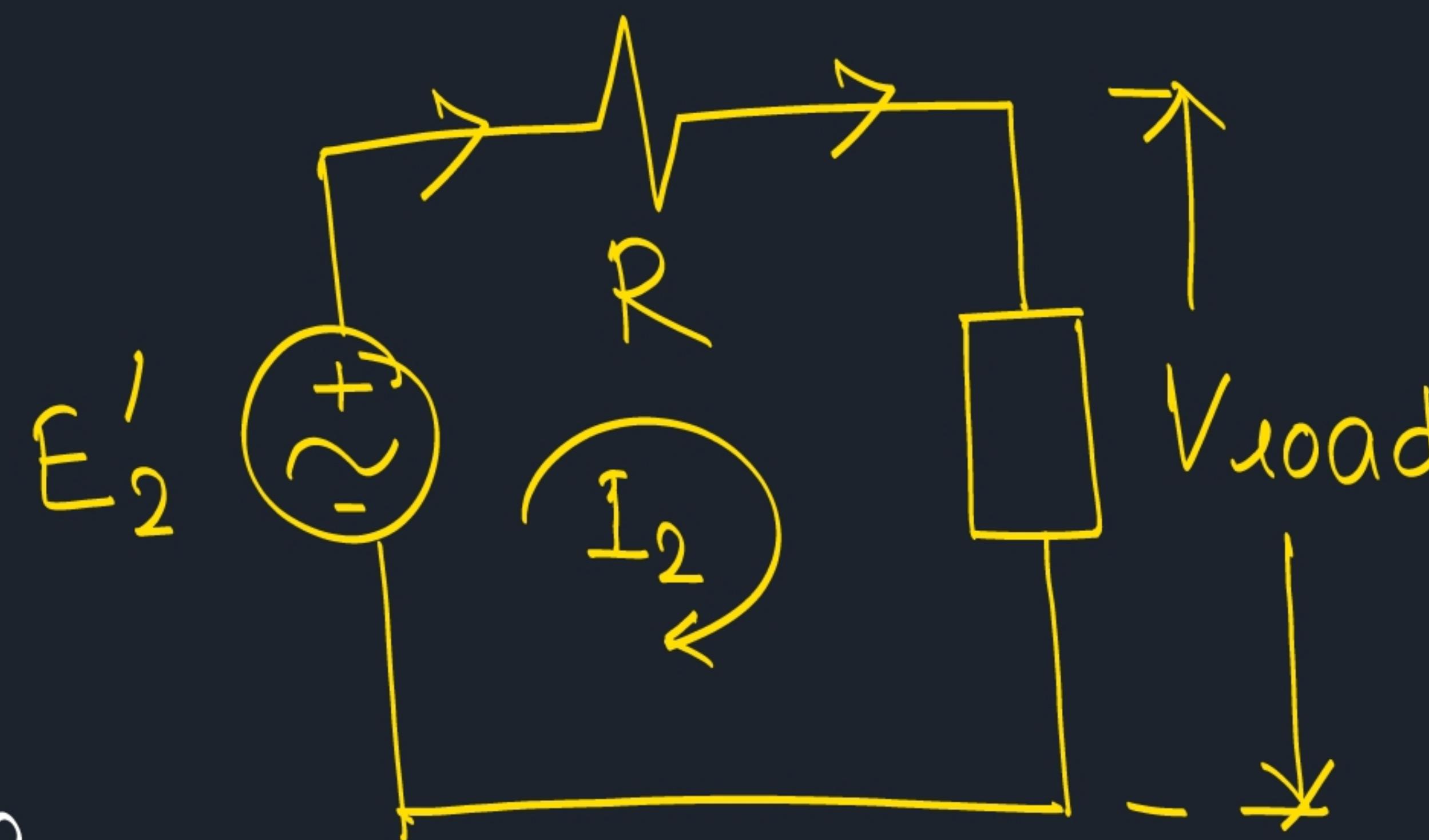


$$\begin{aligned}
 E'_2 &= V_{load} + I_2 R_2 \Rightarrow E_2 - E_{l2} = V_{load} + I_2 R_2 \\
 E_2 &= V_{load} + I_2 R_2 + E_{l2} \\
 &= V_{load} + I_2 R_2 + (I_2 \times \\
 &\quad j\omega L_2) \\
 E'_2 &= 4.44 f \Phi N_2 \\
 &= 4.44 f (\Phi_m - \Phi_{l2}) N_2 \\
 &= \underbrace{4.44 f \Phi_m N_2}_{E_2} - \underbrace{4.44 f \Phi_{l2} N_2}_{E_{l2}} \\
 &= E_2 - E_{l2}
 \end{aligned}$$

$$E_2 = V_{load} + I_2 R_2 + j I_2 X_{l2}$$
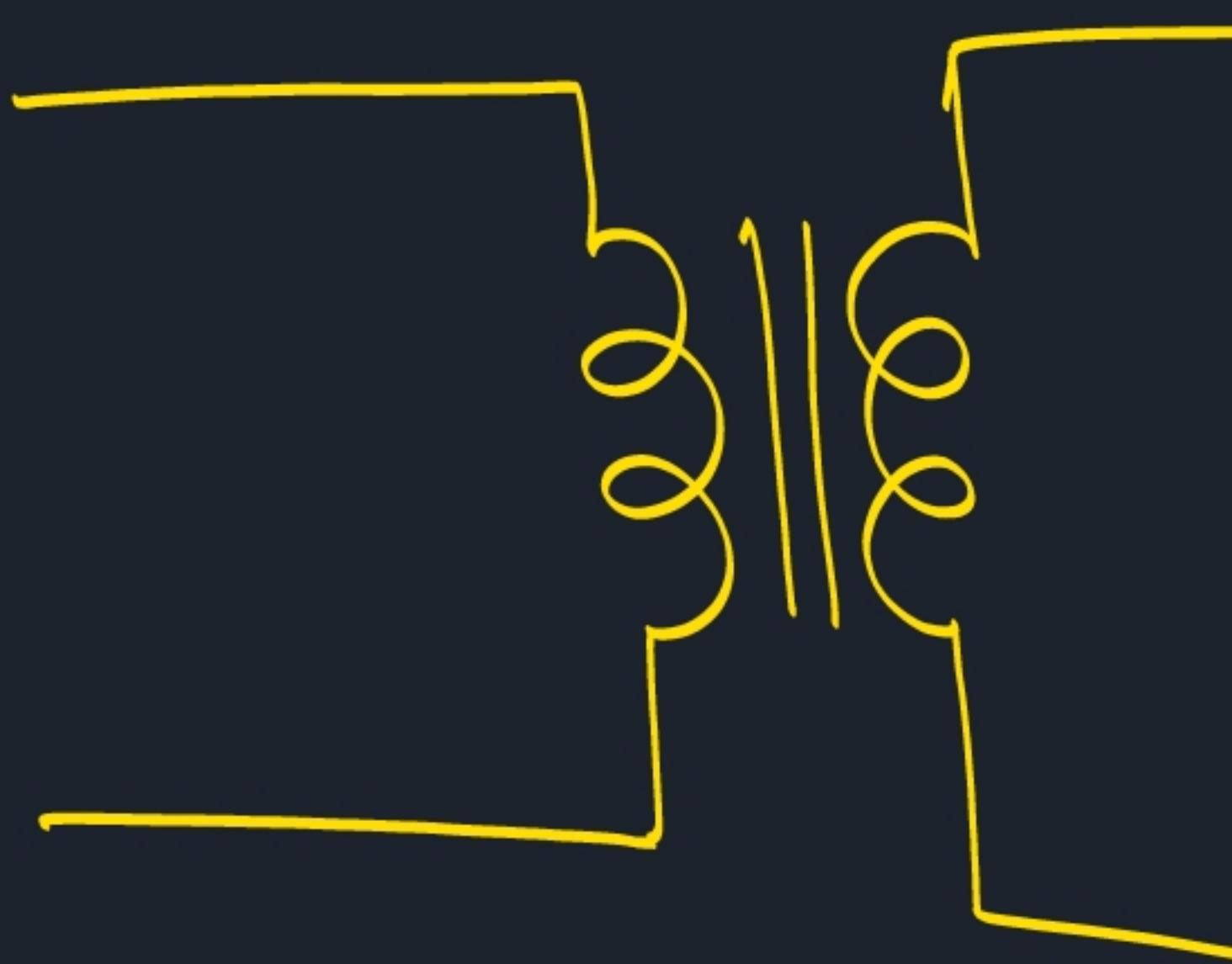
$$\left. \begin{array}{l} V_1 = E_1 + I_1 R_1 + j I_1 X_{L1} \dots \dots \text{(i)} \\ E_2 = V_{\text{load}} + I_2 R_2 + j I_2 X_{L2} \dots \dots \text{(ii)} \\ I_1 = I_m + I'_1 \dots \dots \text{(iii)} \\ I'_1 N_1 = I_2 N_2 \dots \dots \text{(iv)} \end{array} \right\}$$





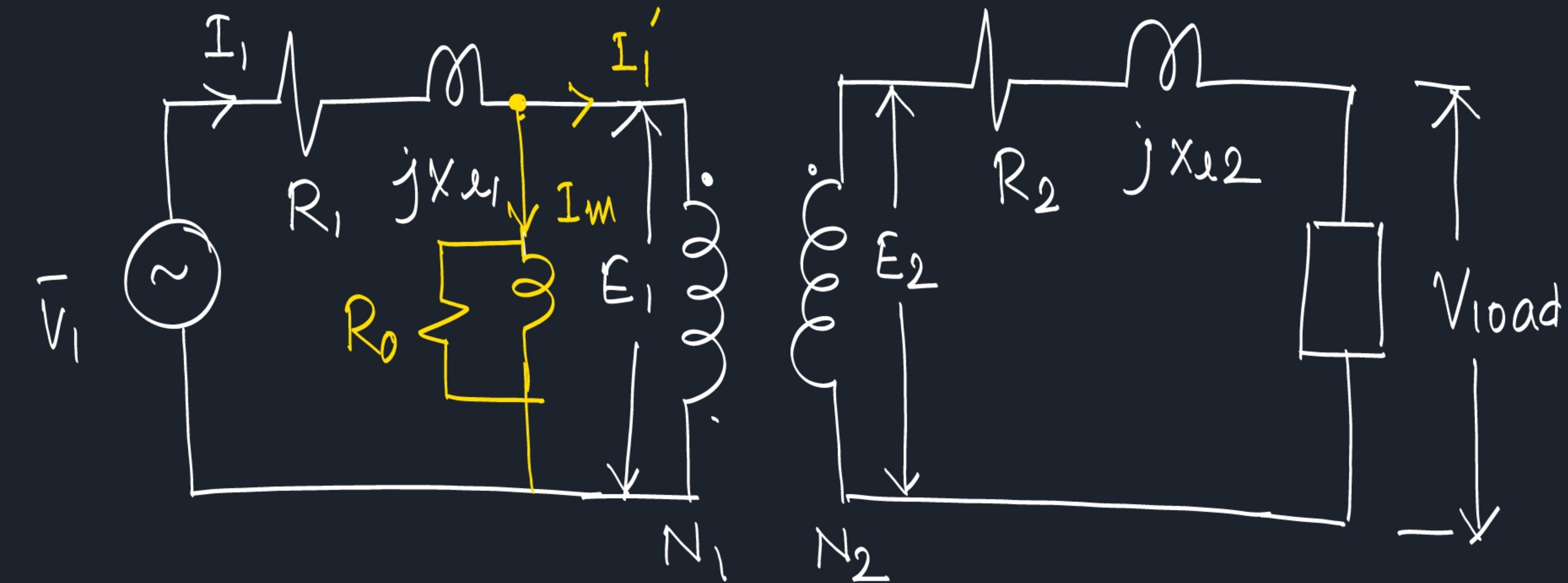I_m creates Φ_m .
i.e. An inductor
Should be associated to Φ_m .



$R_o \Rightarrow$ represents
inter loss of
T/F.
 \rightarrow Hysteresis + Eddy Current.

3874.

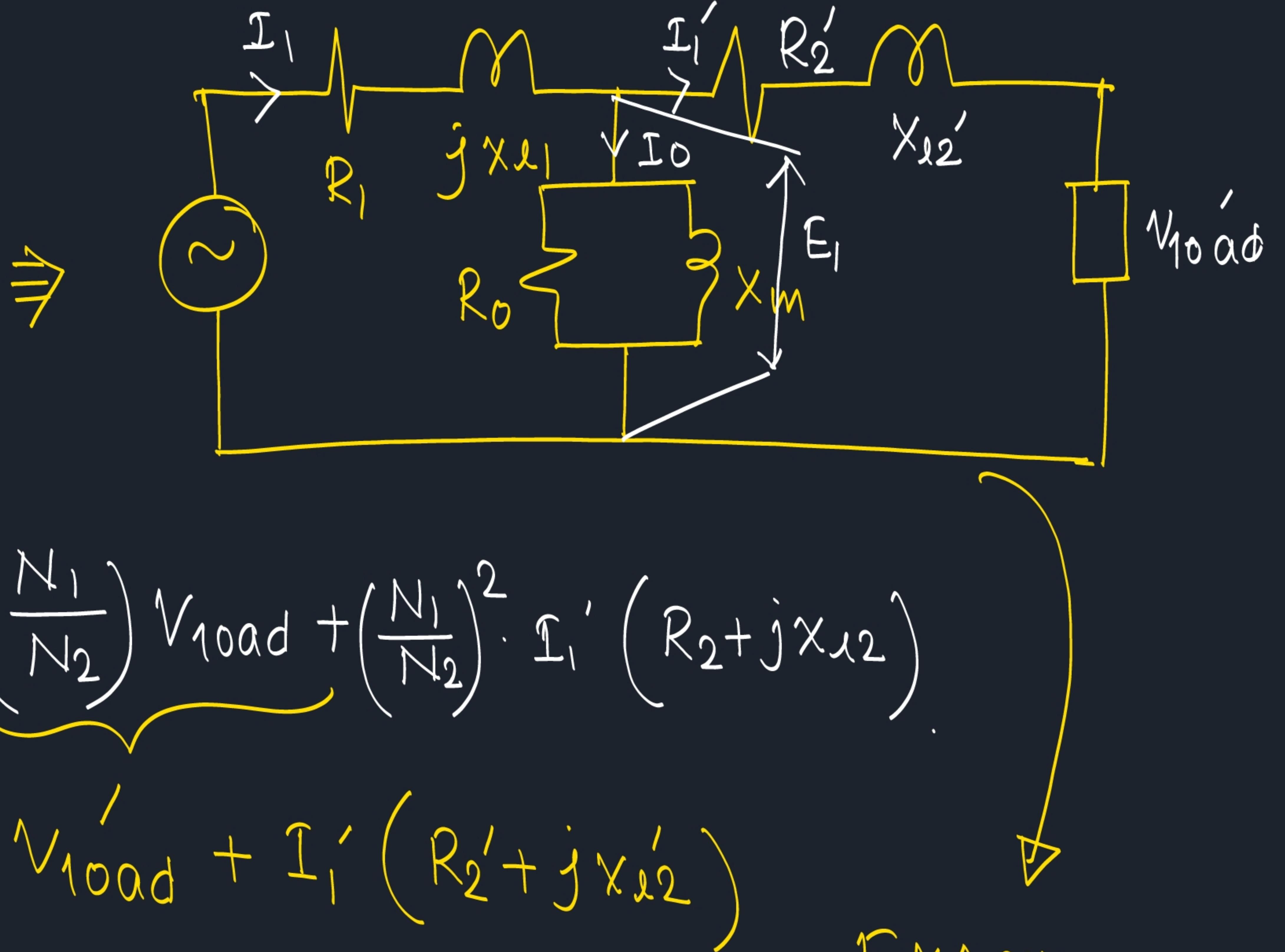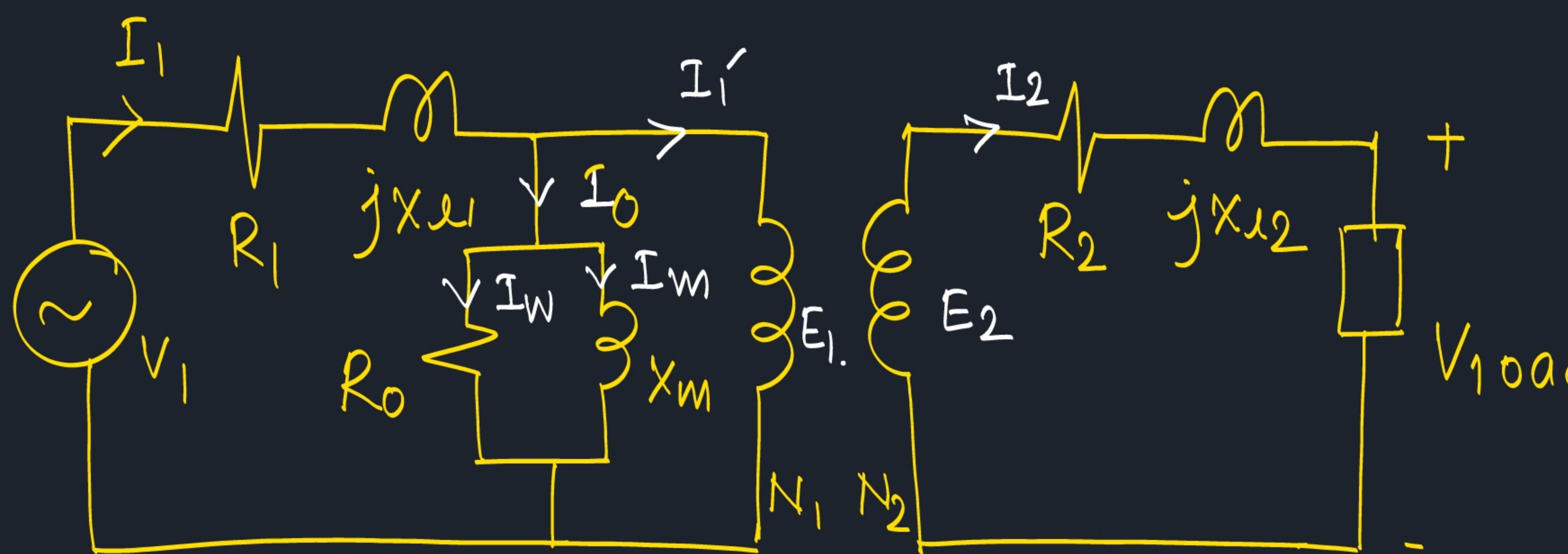

$$E_2 = V_{\text{load}} + I_2(R_2 + jX_{e2})$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$I'_1 N_1 = I_2 N_2$$

$$I_2 = I'_1 \left(\frac{N_1}{N_2} \right)$$



$$\Rightarrow E_1 \cdot \frac{N_2}{N_1} = V_{\text{load}} + I_2(R_2 + jX_{e2})$$

$$\Rightarrow E_1 = \left(\frac{N_1}{N_2} \right) \cdot V_{\text{load}} + \left(\frac{N_1}{N_2} \right) I_2(R_2 + jX_{e2})$$

$$\begin{aligned} E_1 &= \underbrace{\left(\frac{N_1}{N_2} \right)}_{= V'_{\text{load}}} V_{\text{load}} + \left(\frac{N_1}{N_2} \right)^2 \cdot I'_1 (R_2 + jX_{e2}) \\ &= V'_{\text{load}} + I'_1 (R'_2 + jX'_{e2}) \end{aligned}$$

$$\begin{aligned} R'_2 &= \left(\frac{N_1}{N_2} \right)^2 R_2 \Rightarrow \text{Secondary} \\ X'_{e2} &= \left(\frac{N_1}{N_2} \right)^2 X_{e2} \quad \text{Referred to} \\ &\quad \cdot \text{The Primary} \end{aligned}$$

EXACT
Equivalent Ckt
Of 1st/F.

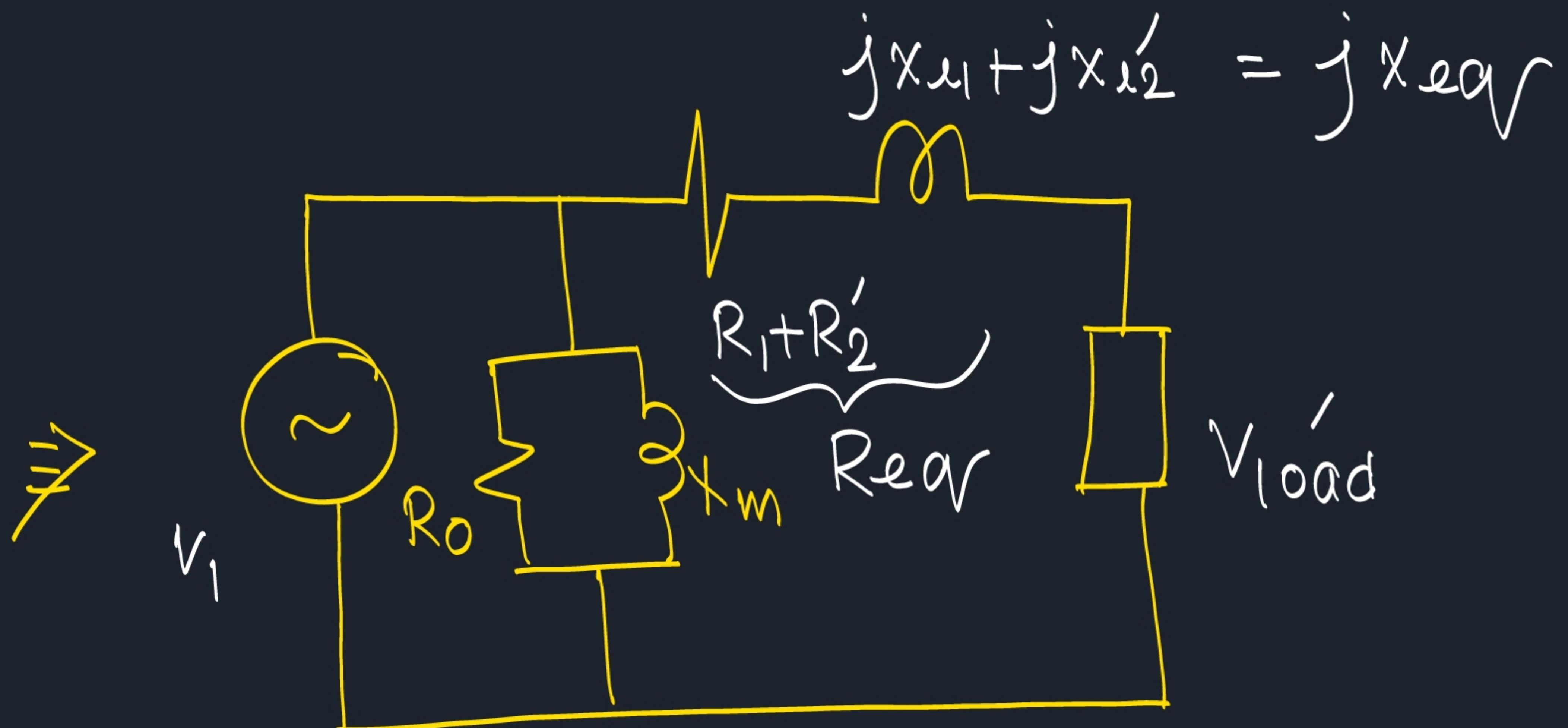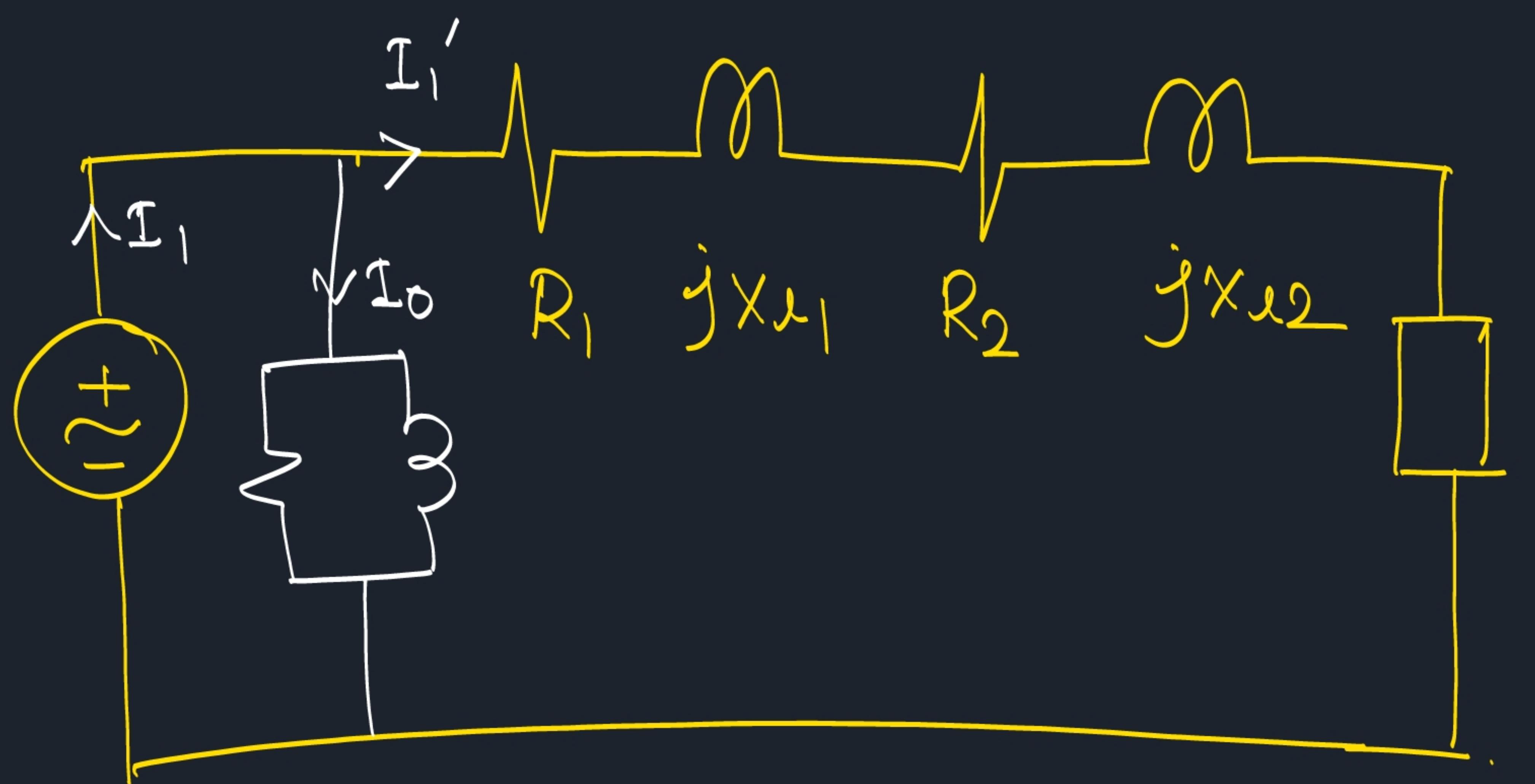

$$\underline{\underline{I_0 \ll \ll I_1 \text{ & } I_1'}}$$

Approx. (2-5%)

$R_0, X_m \Rightarrow$ Shunt Branch parameters

$R_{eq}, X_{eq} \Rightarrow$ Series Branch Parameters.

Approximated
Equivalent circuit of the
T/F.

$$jXu_1 + jXu_2' = jX_{eq}$$

Two tests.



To find out the
parameters of T/F.

i) Open Circuit Test
(OCTest)

ii) Short Circuit Test
(SC Test)


i) Voltmeter
ii) Ammeter
iii) Wattmeter.


$\uparrow V_0, I_0, W_0 \uparrow$

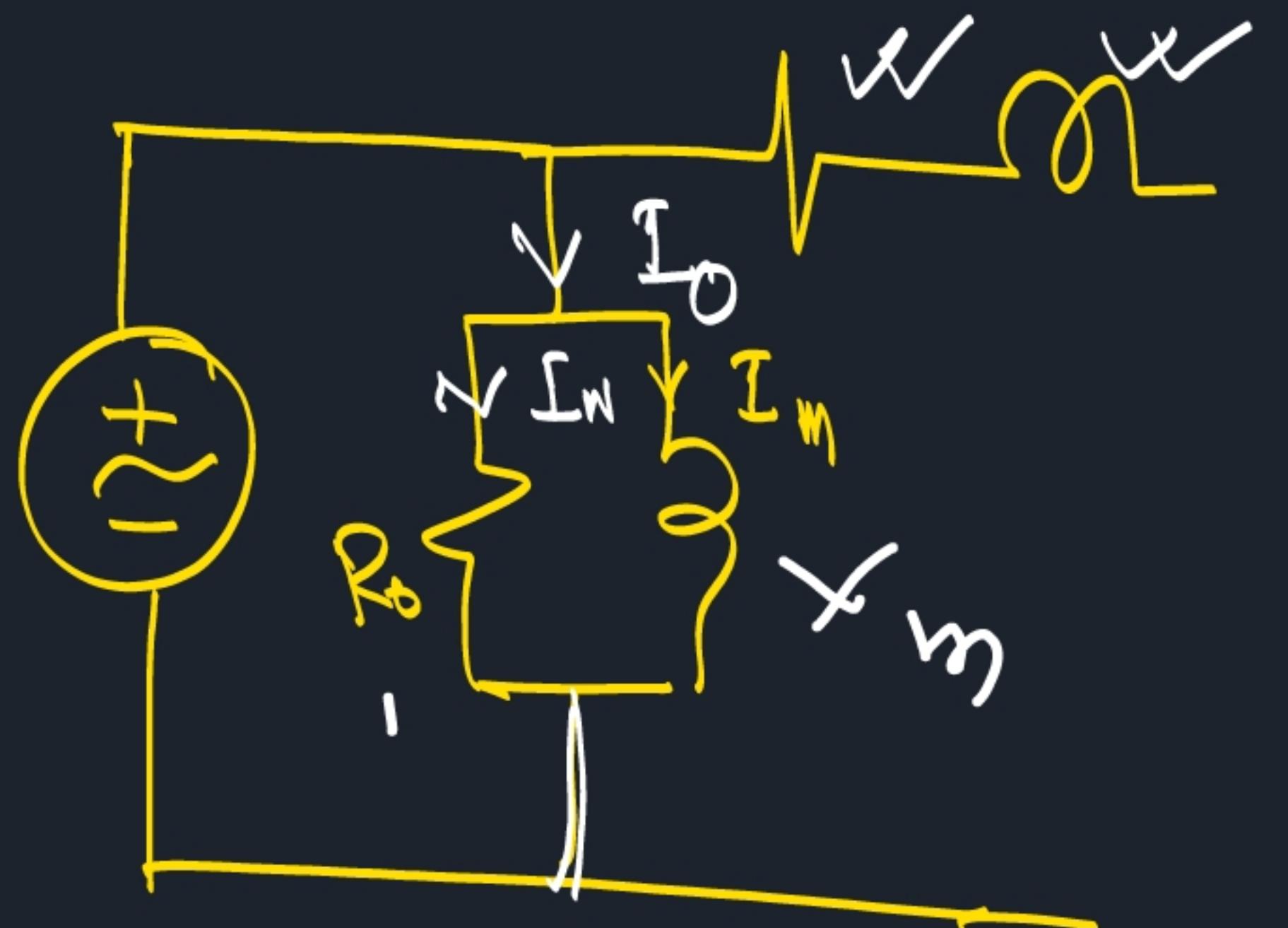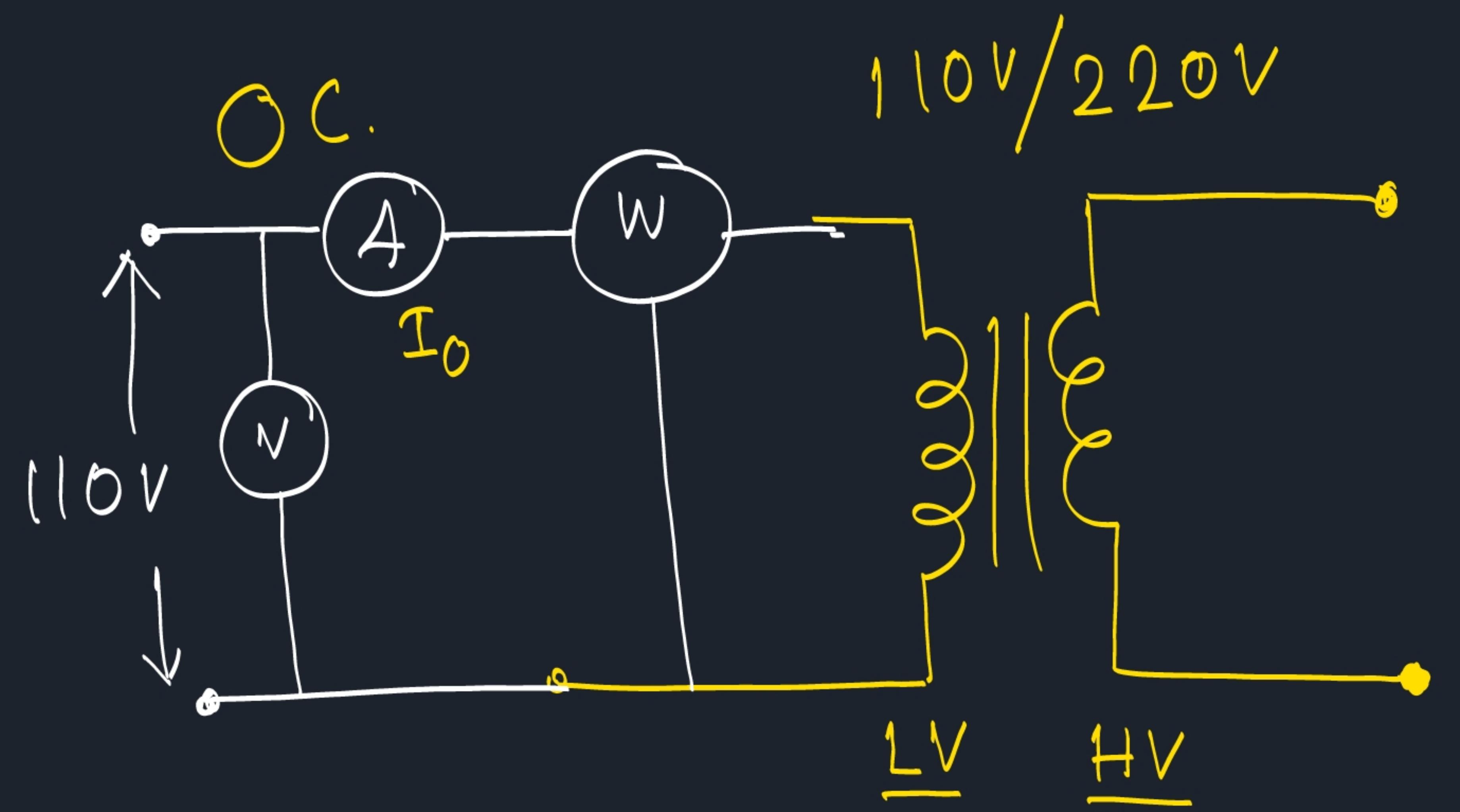

$$W = (I_n^2 \times R_o)$$

V = Rated
Voltage.

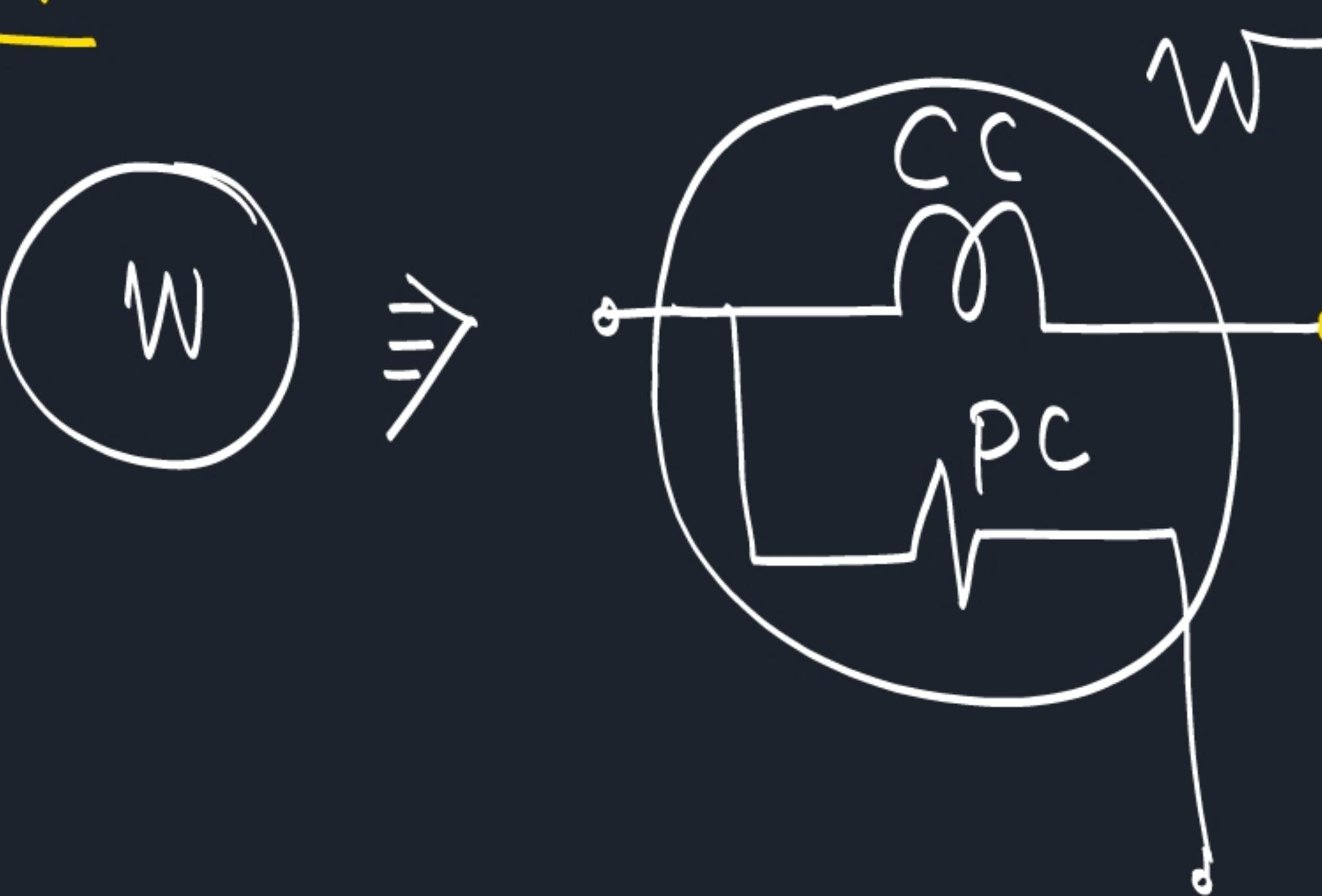

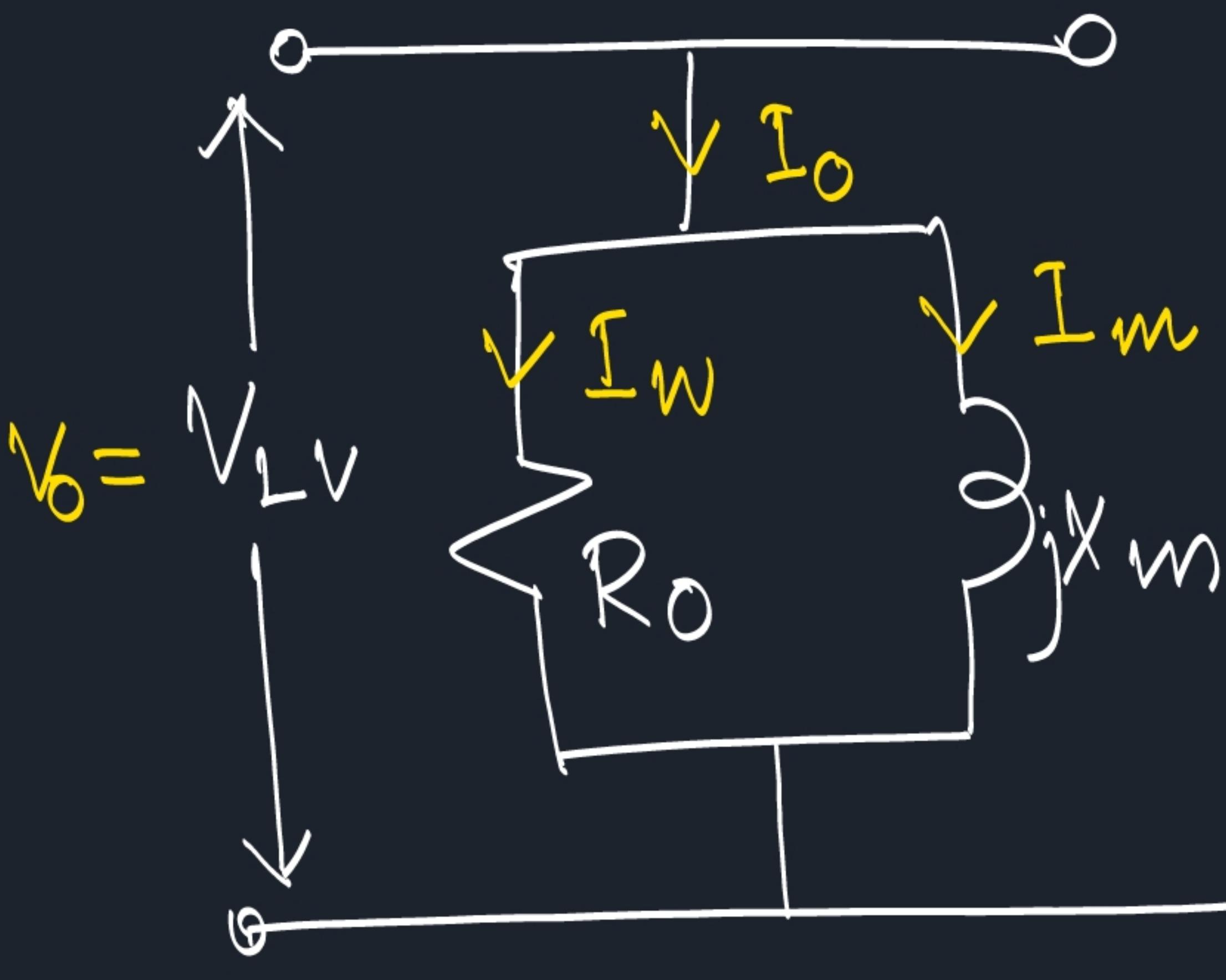

$$V_o, W_o, I_o$$

$$\tilde{I}_o = |I_o| \angle \theta_o$$

Measured
By Ammeter.

$$\left. \begin{aligned} R_o &= \frac{V_o}{I_w} \\ jX_m &= \frac{V_o}{I_m} \\ W_o &= I_w^2 R_o \end{aligned} \right\}$$

$$W_o = V I_w = V_o I_o \cos \theta_o$$

$$\theta_o = \cos^{-1} \left(\frac{W_o}{V_o I_o} \right)$$

$$I_w = |I_o| \cos \theta_o$$

$$I_m = |I_o| \sin \theta_o$$

$$R_o = \frac{V_o}{|I_o| \cos \theta_o}$$

$$X_m = \frac{V_o}{|I_o| \sin \theta_o}$$

SC Test :-

1φ T/F




$$\left. \begin{array}{l} V_{LV} I_{LV} = 1000 \\ V_{HV} I_{HV} = 1000 \end{array} \right\}$$

1 KVA Rating

$$V_1 I_1 = V_2 I_2 = 1000$$


$$\left. \begin{array}{l} |I_{LV}| = \frac{1000}{110} \text{ Amp} \\ |I_{HV}| = \frac{1000}{220} \text{ Amp.} \end{array} \right\}$$

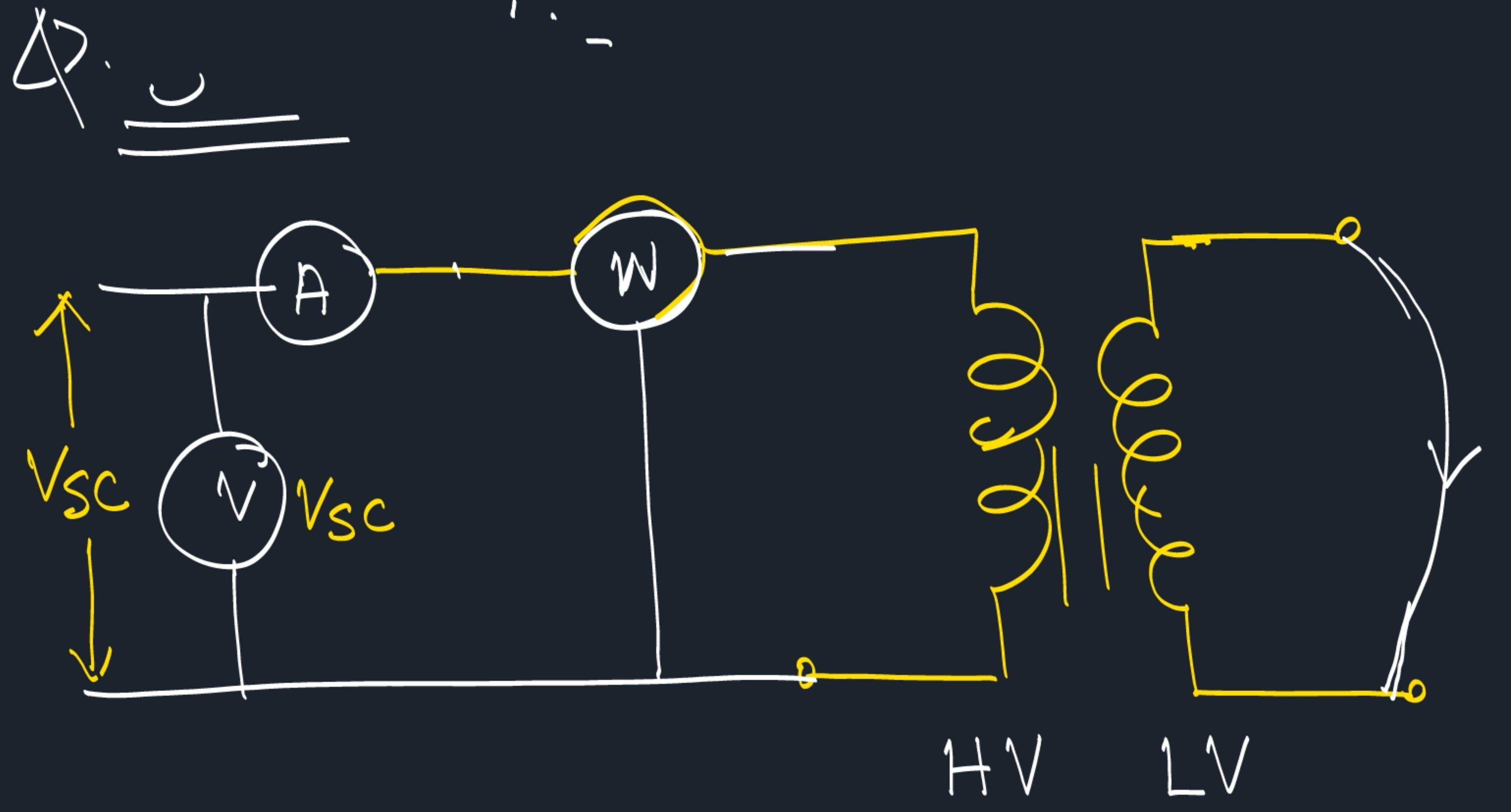

$$\frac{1000}{220} \text{ Amps.}$$

$\underline{\underline{V_{sc}, I_{sc}, W_{sc}}}$

$$|Z_{eq}| = \frac{V_{sc}}{I_{sc}}$$

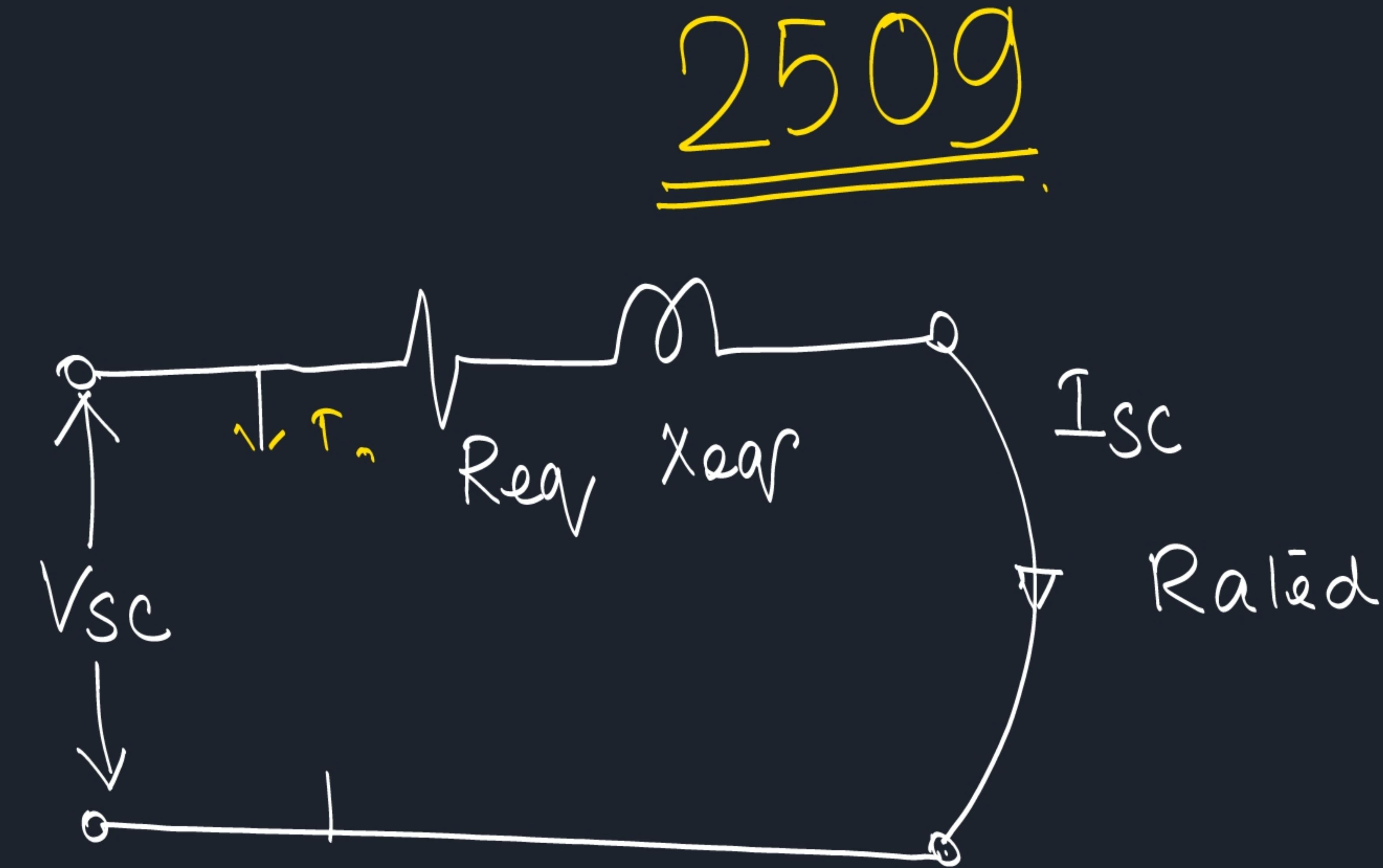

$I_0 \lll I_{sc}$

$$W_{sc} = I_{sc}^2 Req$$

$$Req = \frac{W_{sc}}{I_{sc}^2}$$

$$X_{eq} = \sqrt{Z_{eq}^2 - Req^2}$$

Problem:-

1 Φ T/F

$N_1 = 250$ (pri)

$N_2 = 500$ (Sec)

$A_{core} = 60 \text{ cm}^2$

$f = 50 \text{ Hz}$

$V = 230 \text{ V}$ (Primary)

Peak flux density B_m

$$V_1 = E_1 = 4.44 f \Phi_m N_1$$

$$\Phi_m = \frac{230}{4.44 \times 50 \times 250} \text{ Wb.} = ?$$

$$B_m = \frac{\Phi_m}{A} = \frac{\Phi_m}{60 \times 10^{-4}} \text{ Wb/m}^2 = ?$$

Problem :-

T/F : 5 kVA
200/1000 V

$$(i) \quad \left. \begin{array}{l} V_{LV} = 200 \text{ V} \\ V_{HV} = 1000 \text{ V} \end{array} \right\} \quad V_{HV} I_{HV} = V_{LV} I_{LV} = 5000$$

$$I_{HV} = 5 \text{ Amps.} \quad I_{LV} = \frac{5000}{200} = 25 \text{ Amps}$$

OC. Test : 200 V, 1.2 A, 90 W

(ii) LV Side is chosen for OC Test

$$V_0 = 200 \text{ V}, \quad I_0 = 1.2 \text{ A}, \quad W_0 = 90 \text{ W}$$

Estimate The transformer parameters.

(iii) HV Side is chosen for SC Test

$$V_{SC} = 50 \text{ V}, \quad I_{SC} = 5 \text{ A}, \quad W_{SC} = 110 \text{ W}$$

OC Test :-

Step-1

$$\cos \theta_0 = \frac{w_0}{V_0 I_0}$$

$$= \frac{90}{200 \times 1.2}$$

$$\theta_0 = ? \quad 67.9756^\circ$$

Step-2

$$R_0^{\text{LV}} = \frac{V_0}{I_0 \cos \theta_0} = 444.44 \Omega$$

Step-3

$$X_w^{\text{LV}} = \frac{V_0}{I_0 \sin \theta_0}$$

$$= 179.7866 \Omega$$

SC Test :-

Step-1

$$R_{\text{eqV}}^{\text{HV}} = \frac{w_{\text{SC}}}{I_{\text{SC}}^2}$$

$$= \frac{110}{(5)^2} = 4.4 \Omega$$

Step-2

$$|Z_{\text{eqV}}|^{\text{HV}} = \frac{V_{\text{SC}}}{I_{\text{SC}}}$$


$$= \frac{50}{5} = 10 \Omega$$

Step-3

$$X_{\text{eqV}}^{\text{HV}} = \sqrt{|Z_{\text{eqV}}|^2 - R_{\text{eqV}}^2}$$


$$= \sqrt{10^2 - (4.4)^2}$$

$$= 8.97 \Omega$$

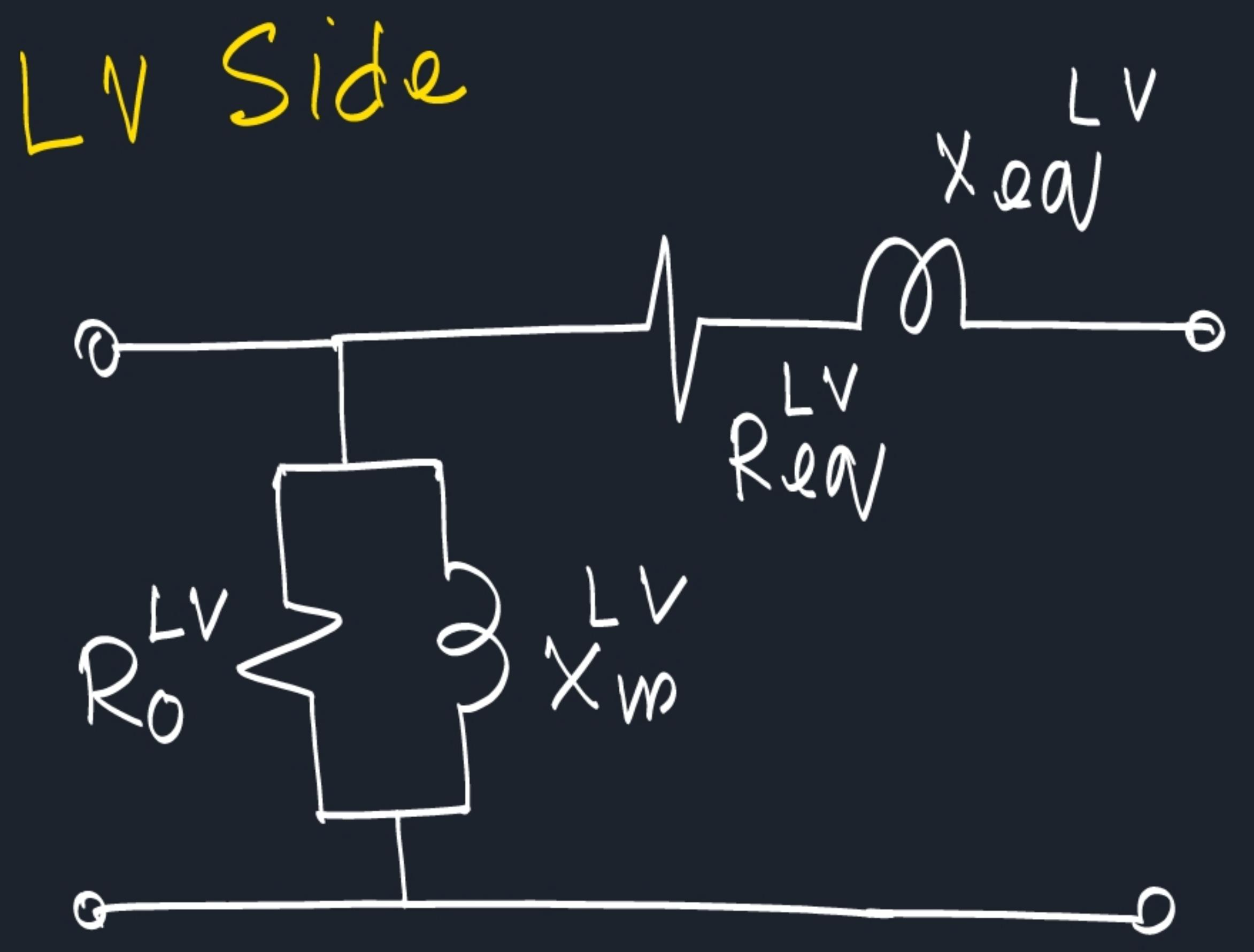


$$\frac{R_{eq}^{LV}}{R_{eq}^{HV}} = \left(\frac{N_{LV}}{N_{HV}} \right)^2 = \left(\frac{V_{LV}}{V_{HV}} \right)^2 = \left(\frac{200}{1000} \right)^2$$
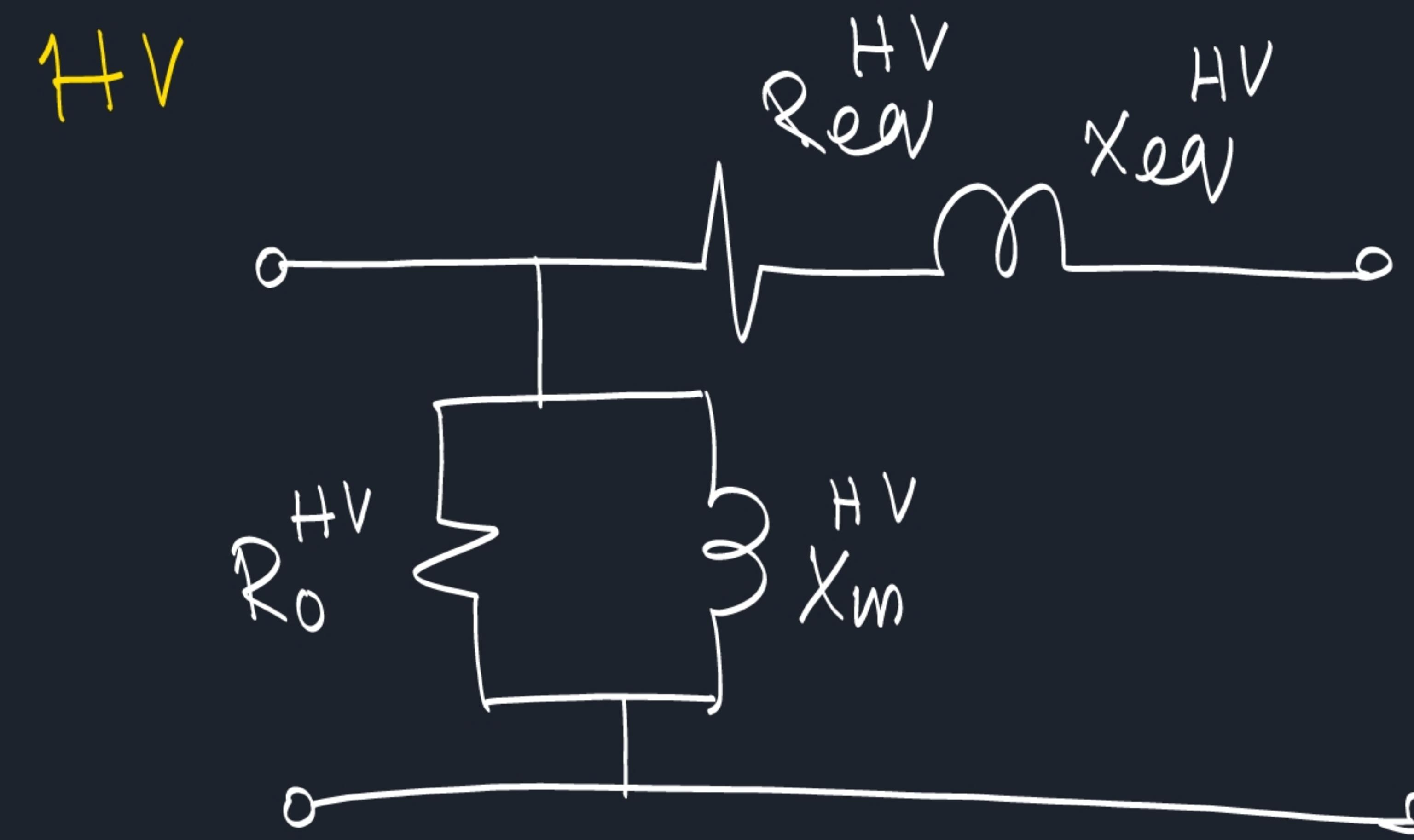
$$\frac{X_{eq}^{LV}}{X_{eq}^{HV}} = \left(\frac{V_{LV}}{V_{HV}} \right)^2$$




$$Y = w\chi$$

$$I = G \cdot V$$

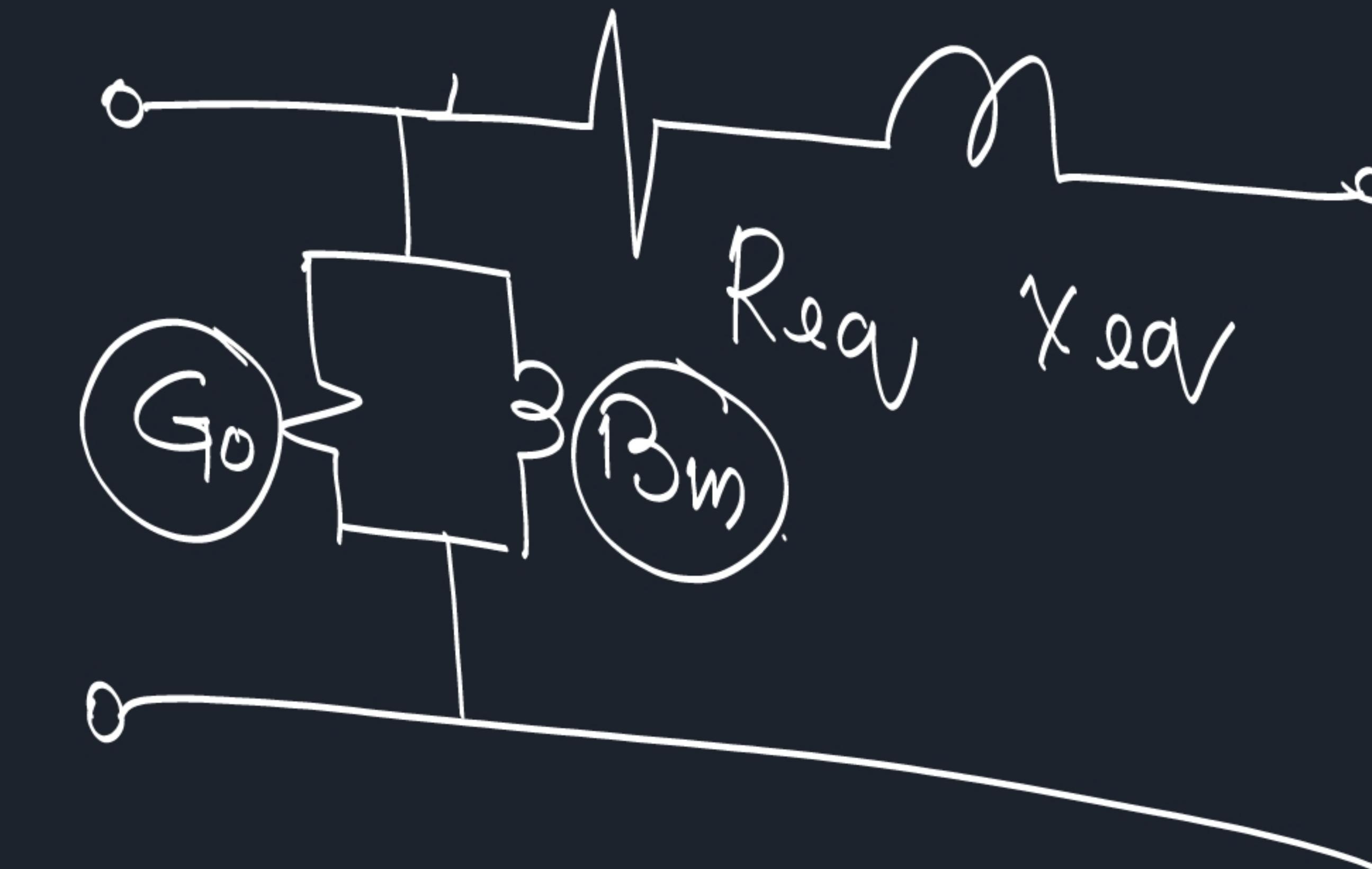


$$G_0 = \frac{1}{R_0}$$

$$B_m = \frac{1}{X_m}$$

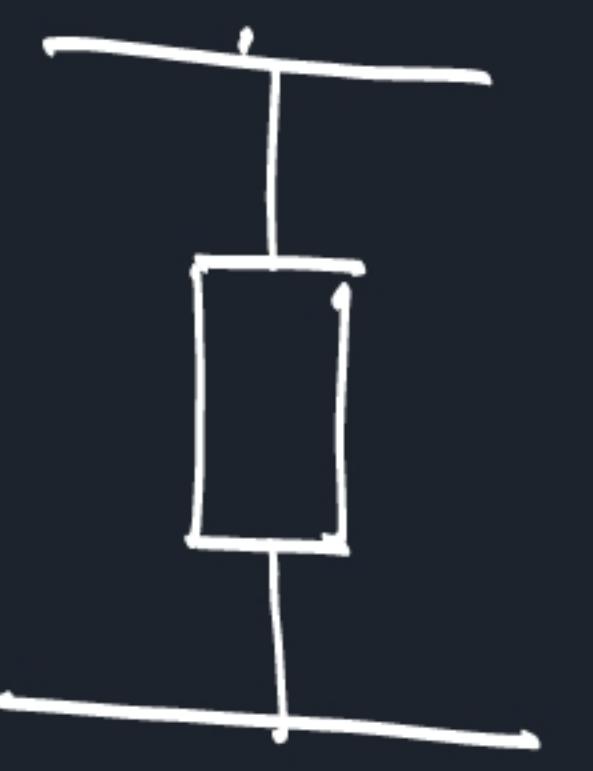

III) Analyzing T/F with Load :-

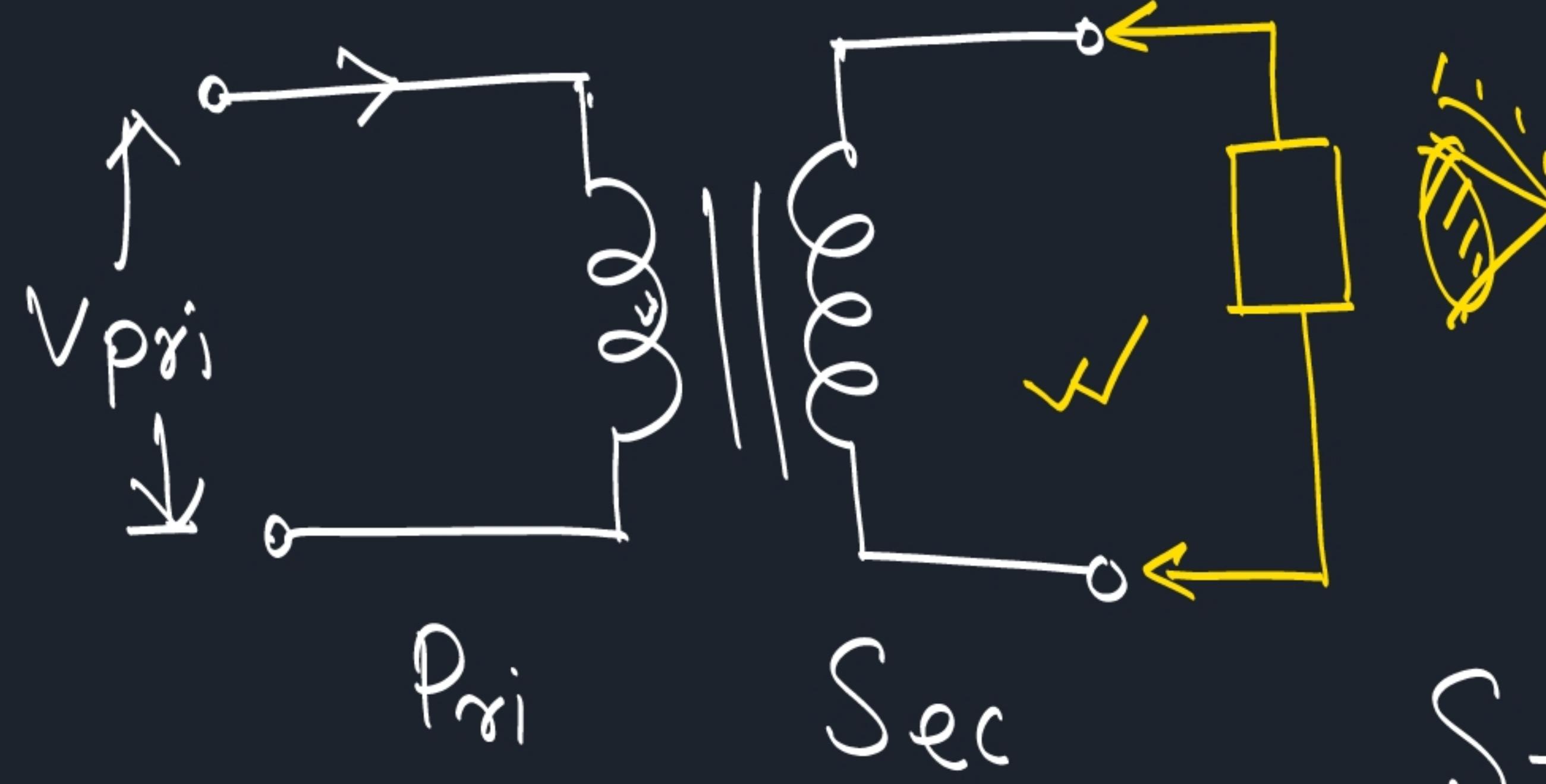


$$220/110\text{V}$$

$$\begin{aligned} S &= VI^* \\ S^* &= V^* I \end{aligned}$$

$R_1, R_2 \Rightarrow$ Winding Resistances
 $R_0 \Rightarrow$ Shunt branch Resistance.

\nwarrow Cu loss
 \nwarrow Core loss

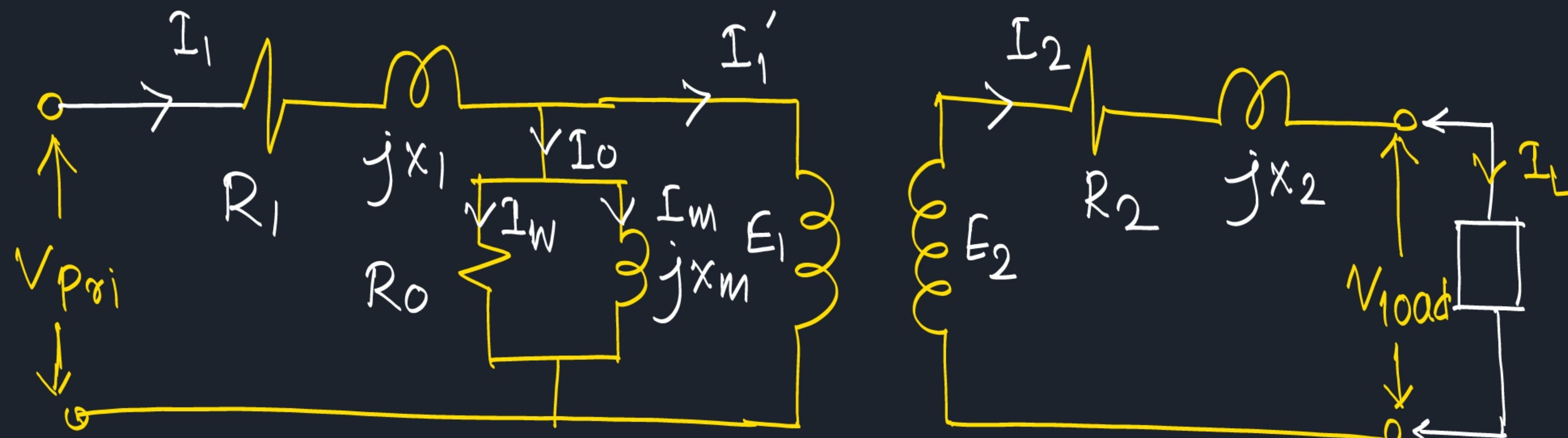

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\begin{aligned} \text{Load} &\rightarrow P_L + jQ_L \\ &\quad (\text{R-L}) \\ P_L - jQ_L &\quad (\text{R-C}) \end{aligned}$$

$$V_{load} = |V_{load}| \angle \theta$$

Let us assume the load is of R-L type. $S = P_L + jQ_L$

$$\begin{aligned} S^* &= V^* I \\ I &= \frac{(P+jQ)^*}{V^*} = \frac{P-jQ}{V_{load} \angle \theta} \end{aligned}$$

$$\tilde{I} = \frac{P - jQ}{\sqrt{V_{load}} Z_0}$$

$$\tilde{I}_1 = \underline{\underline{I}}_1' + \underline{I}_0$$

$$N_1 \underline{I}_1' = N_2 \underline{I}_2$$

$$\underline{I}_2 = \underline{I}$$

$$\begin{aligned}\underline{I}_1' &= \frac{N_2}{N_1} \underline{I} \\ &= \left(\frac{N_2}{N_1}\right) \cdot \underline{I}\end{aligned}$$

$$\tilde{E}_2 = \tilde{V}_{load} + \tilde{I} (R_2 + jX_2)$$

$$\frac{E_1}{E_2} = \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$\tilde{E}_1 = \tilde{E}_2 \cdot \left(\frac{N_1}{N_2} \right)$$

$$\underline{\underline{I}}_0 = \frac{\underline{E}_1}{R_0} + \frac{\underline{E}_1}{jX_m}$$

$$\boxed{V_{pri} = \tilde{E}_1 + \underline{I}_1 (R_1 + jX_1)}$$

8929

Problem :-

1Φ T/F.

150 kVA, 2400/240 V

$R_1 = 0.2 \Omega$

$X_1 = 0.45 \Omega$

$R_0 = 10 \text{ k}\Omega$

$R_2 = 2 \text{ m}\Omega$

$X_2 = 4.5 \text{ m}\Omega$

$X_m = 1.55 \text{ k}$

The load :- Rated current @ rated
Voltage at 0.8 pf (lag)
at LV side.

(Exact ckt)

Soln:-

Rated current = ?

$$|I| = \frac{150 \times 10^3}{240} = 625 \text{ A}$$

$$\tilde{I} = 625 \angle -\cos^{-1}(0.8)$$

$$\begin{aligned} \tilde{E}_2 &= 240 \angle 0 + \tilde{I} \times (2 + j4.5) \times 10^{-3} \\ &= 242.692 \angle 0.354 \text{ V} \end{aligned}$$

$$\frac{\tilde{E}_1}{\tilde{E}_2} = \frac{N_1}{N_2} = \frac{V_1}{V_2} = 10$$

$$\tilde{E}_1 = 2426.92 \angle 0.354 \text{ V}$$

$$I'_1 N_1 = I_2 N_2$$

$$I'_1 = \frac{N_2}{N_1} \cdot I_2$$

$$= \left(\frac{V_2}{V_1} \right) \cdot I_2$$

$$= \left(\frac{240}{2400} \right) \cdot 625 \angle -\cos^{-1}(0.8)$$

$$= 62.5 \angle -\cos^{-1}(0.8)$$

$$\tilde{I}_0 = \frac{E_1}{R_0} + \frac{E_1}{jX_m}$$

$$I_W = 2426.92 \angle 0.354$$

$$\left(\frac{1}{10 \times 10^3} + \frac{1}{j1.55 \times 10^3} \right)$$

$$= 1.5845 \angle -80.835 \text{ Amp.}$$

$$\tilde{I}_1 = \tilde{I}'_0 + \tilde{I}'_1$$

$$= 1.5845 \angle -80.835 + 62.5 \angle -36.869$$

$$= 63.649 \angle -34.86$$

$$\text{Core loss} = |I_W|^2 R_0$$

$$I_W = 0.2427 \angle 0.354$$

$$P_{\text{core}} = \left\{ (0.2427)^2 \times 10 \times 10^3 \right\} = 589 \text{ Watt.}$$

$$V_{\text{pri}} = E_1 + I_1 (R_1 + jX_1)$$

$$= 2426.92 \angle 0.354 +$$

$$(63.649 \angle -34.86) \times (0.2 + j0.45)$$

$$= 2454.68 \angle 0.695 \text{ Volt.}$$

$\circlearrowleft P_{\text{cu}}$


$$P_{\text{cu}} = |I_2|^2 R_2 + |I_1'|^2 R_1$$

$$= (625)^2 \times 2 \times 10^{-3} + (63.649)^2 \times 0.2 \text{ Watt.}$$

$$= \underline{1591.489 \text{ W}}$$

Phasor Diagram :-

Exact Equivalent Ckt.

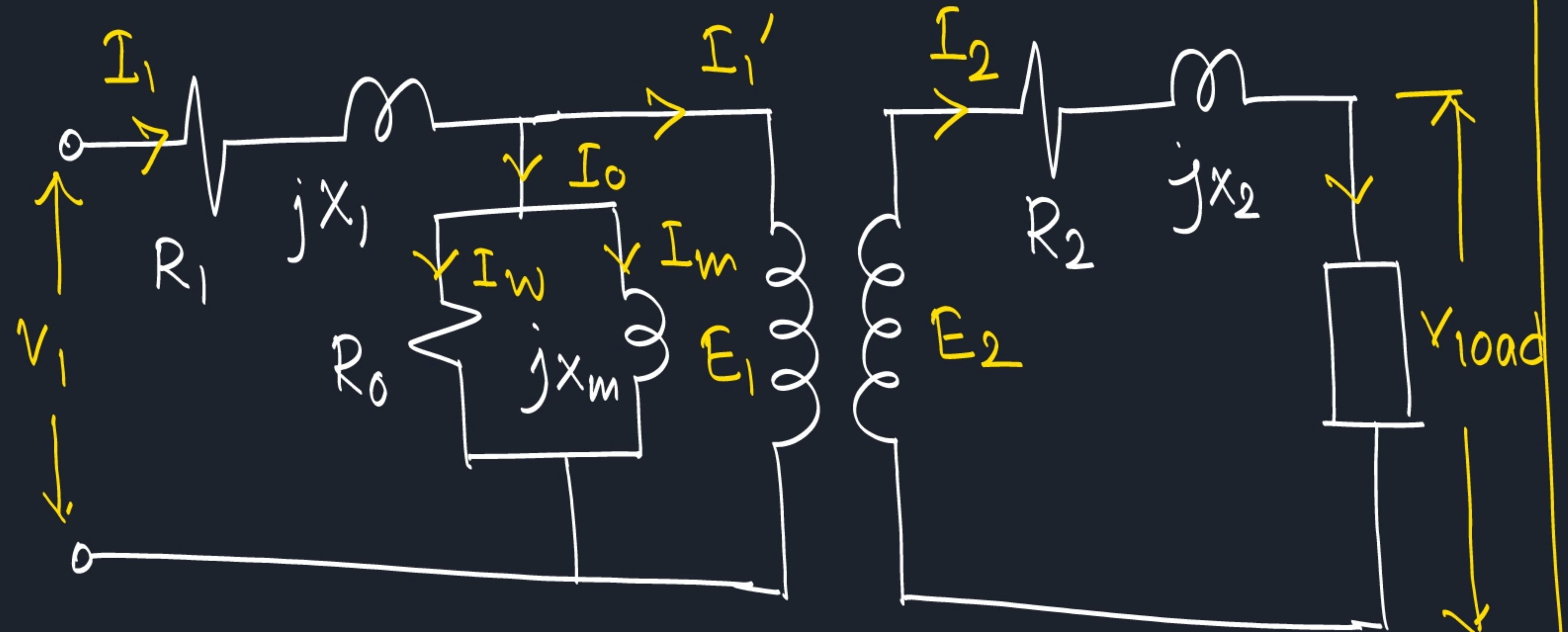

Consider


V_1 / V_2	$\underline{V_1 > V_2}$
$V_{\text{load}} = V_2 \angle 0$	\rightarrow Ref. Phasor.
$I_2 = I_{\text{load}}$	

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} > 1$$



$$E_1 > E_2 \quad I_1' < I_2$$

$$I_0 = \frac{E_1}{R_0} + \frac{E_1}{jX_m} = \frac{E_1}{R_0} - j \frac{E_1}{X_m}$$

$$I_1 = I_1' + I_0$$

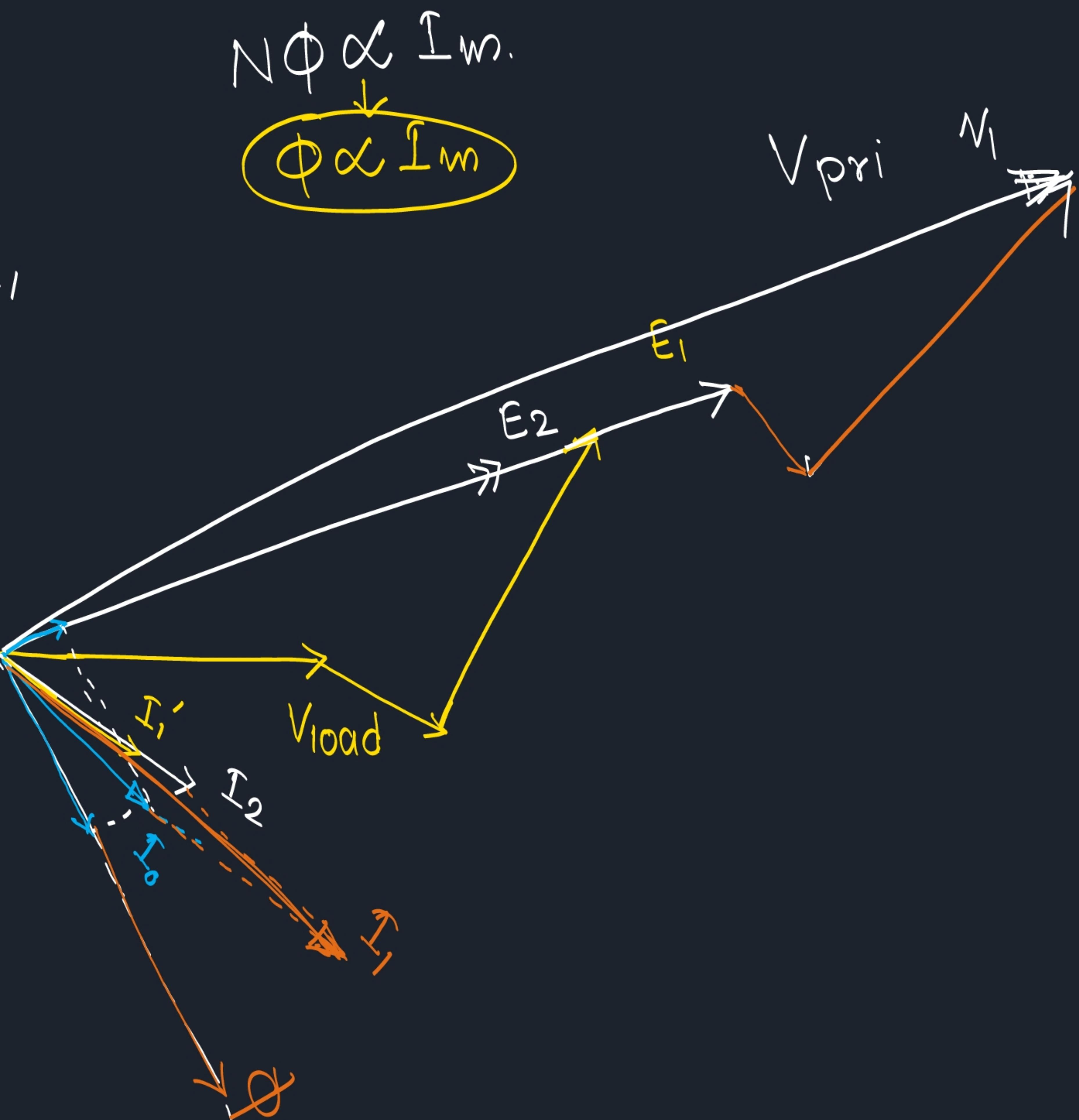

Voltage Regulation:-

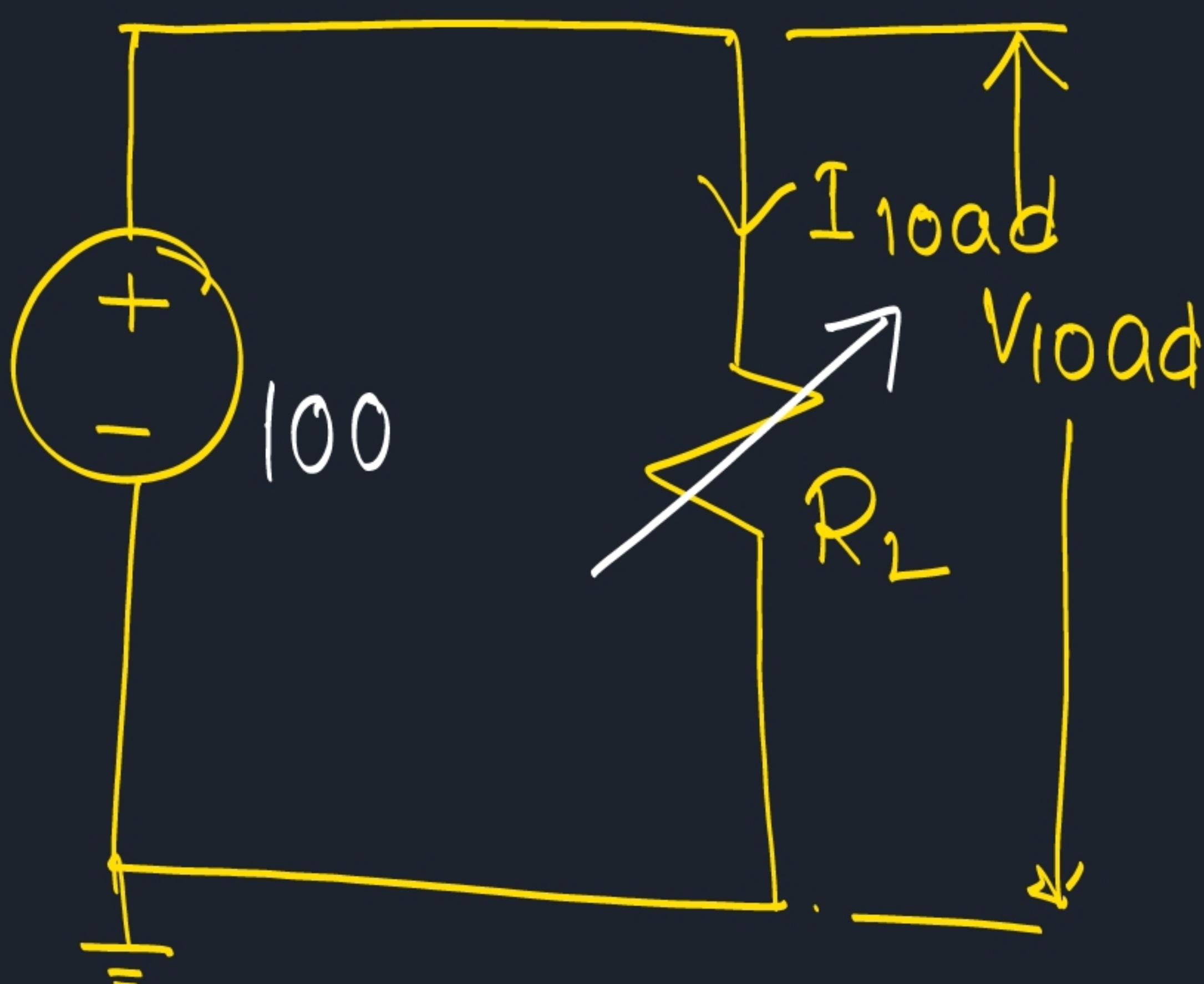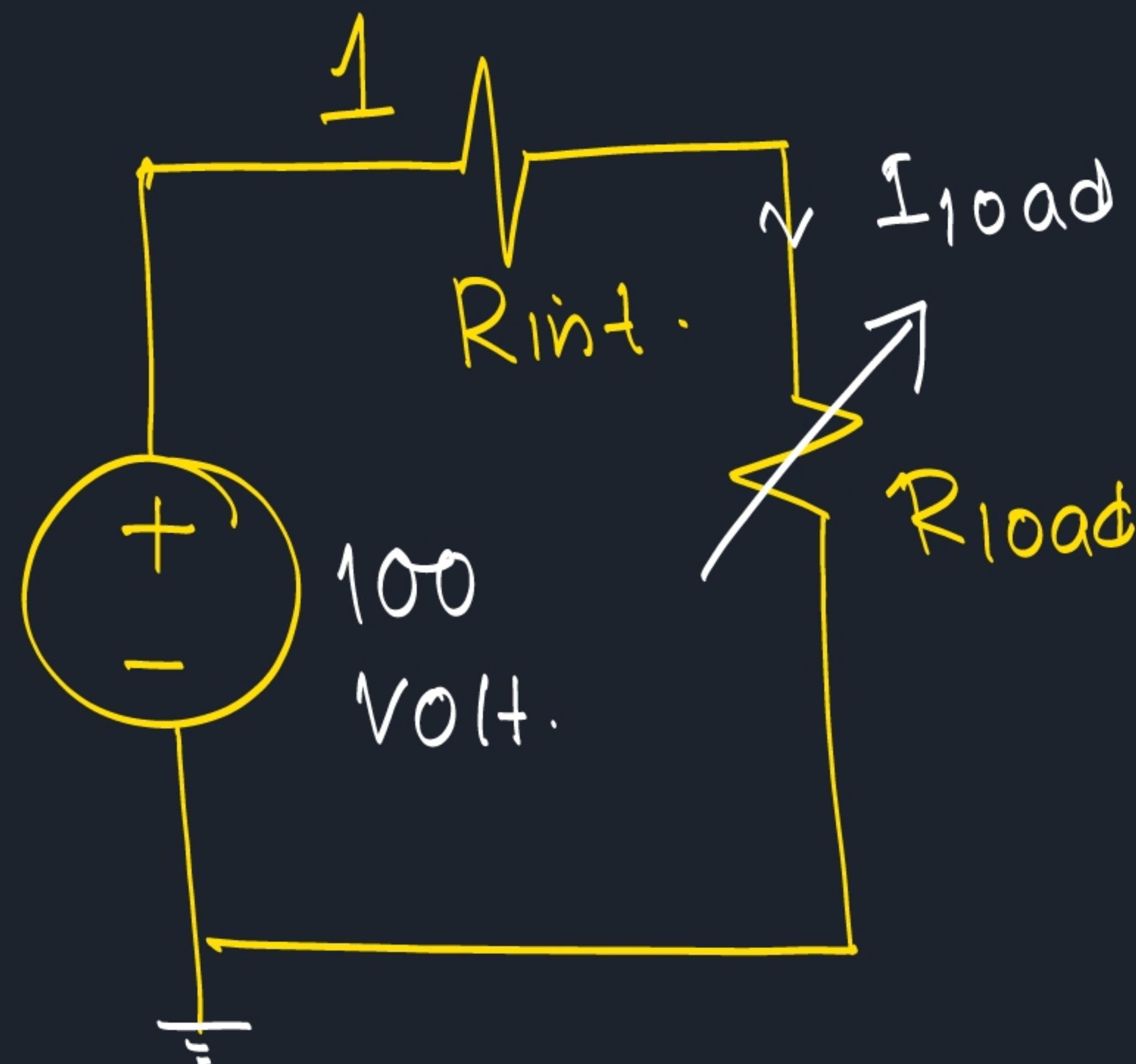


$$V_{load} = 100 - R_{int} \cdot I_{load}$$

$$= 100 - R_{int} \cdot \frac{100}{R_{int} + R_{load}} = \frac{20}{80} \times 100 \\ = 25\%$$

R_{load}	I_{load}	V_{load}
4	20	80
19	5	$19 \times 5 =$
49	2	$49 \times 2 =$
99	1	$99 \times 1 = 99$

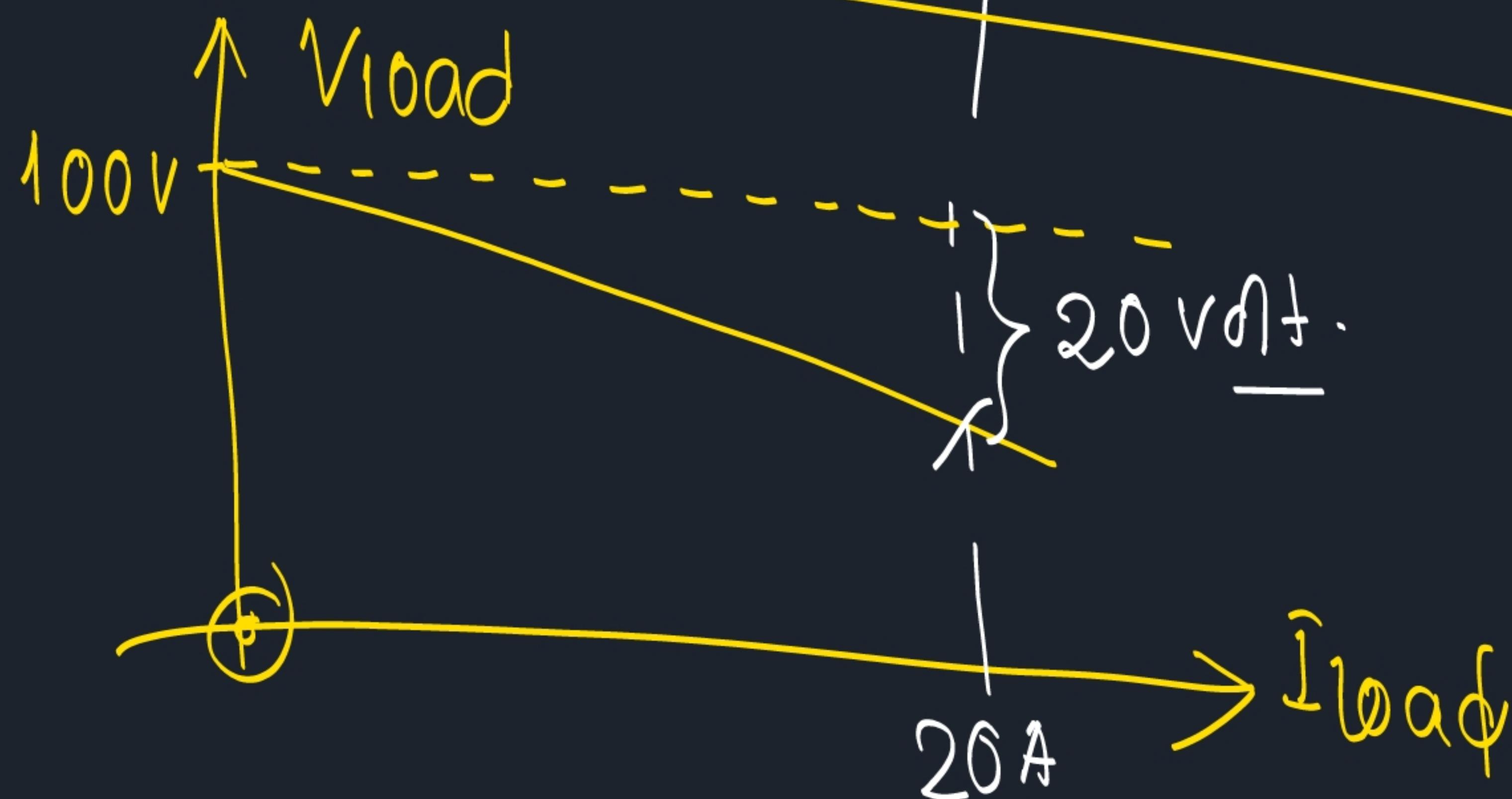$\left(\frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 \right)$
 \therefore Voltage Regulation.




$$2454.68 \text{ V}$$

$$\% \text{ Reg} = \frac{|V_{NL}| - |V_{FL}|}{|V_{FL}|} \times 100.$$

Terminal / Load voltage $\rightarrow 240 \text{ V}$


No load rating $2400 / 240$

$$\left[\frac{N_1}{N_2} = 10 \right]$$

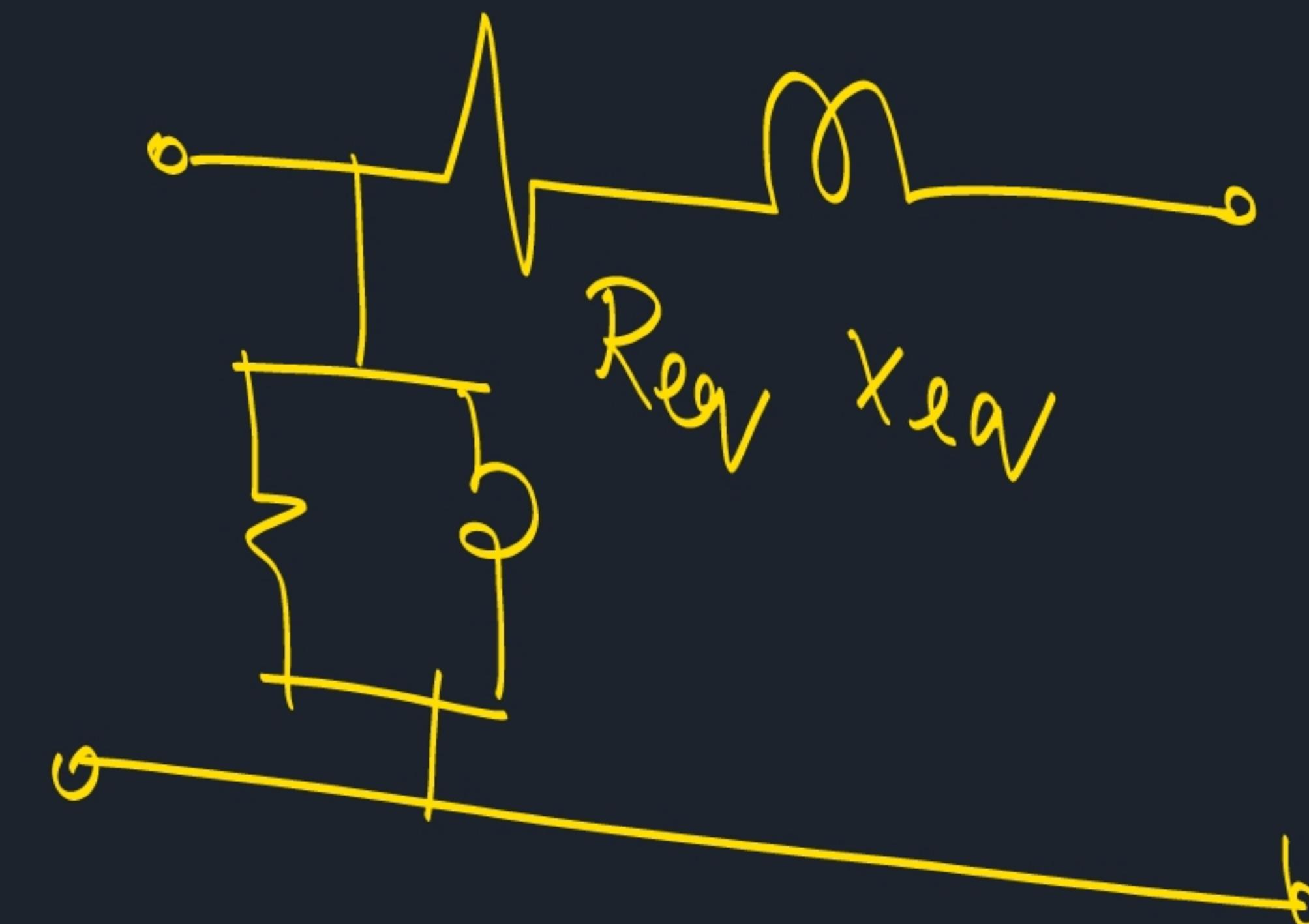

$$\% \text{ Reg.} = \left\{ \frac{245.468 - 240}{240} \times 100 \right\}$$

$$I_0 \ll I_1$$

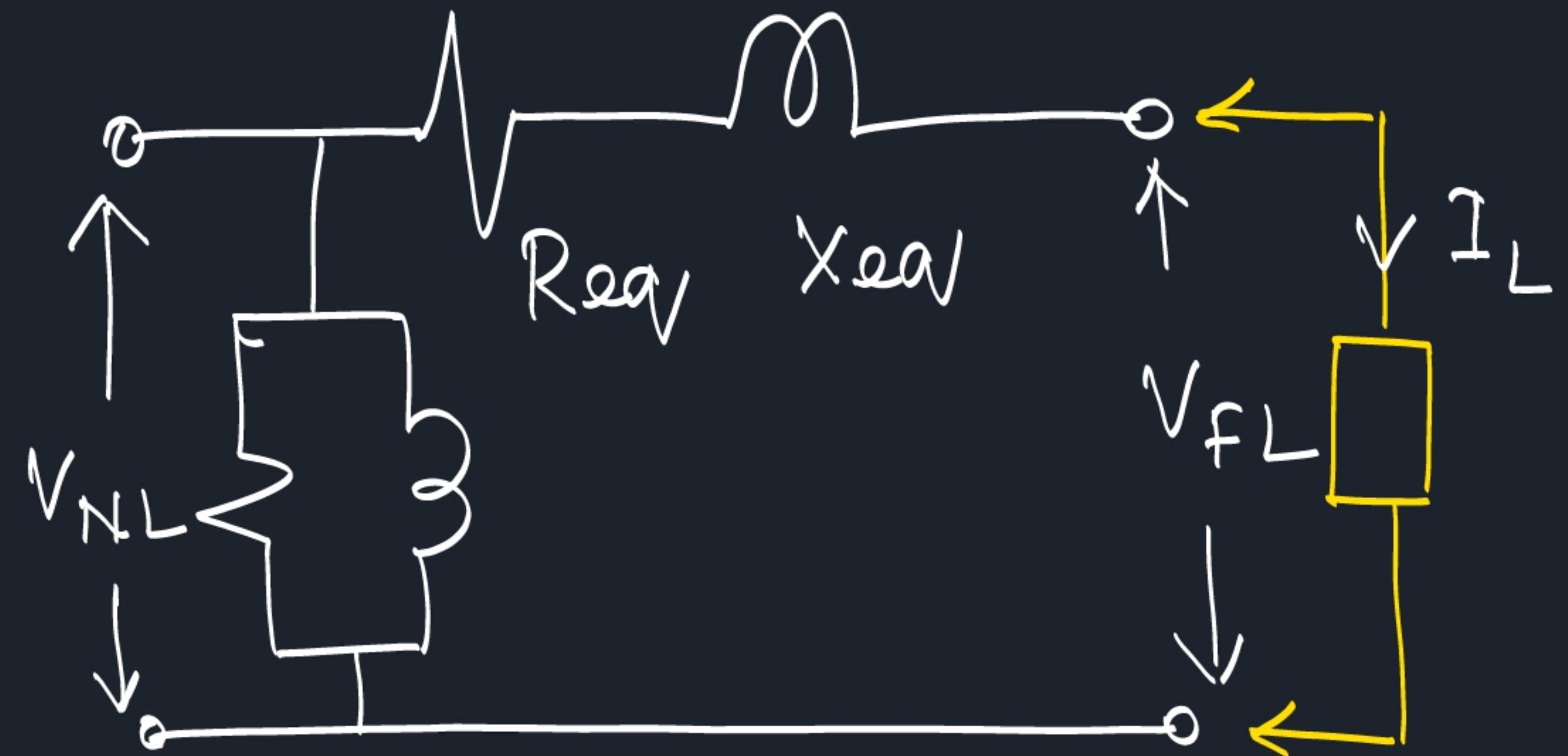

$$V_{NL} = V_{FL} + I_L(R_{req} + jX_{req})$$

$\oplus \Rightarrow$ lagging δ

$\ominus \Rightarrow$ leading δ .

$$\gamma \cdot Reg = \frac{|V_{NL}| - |V_{FL}|}{|V_{FL}|}$$

$$= \left\{ \frac{|I_L|(R_{req} \cos \theta \pm X_{req} \sin \theta)}{|V_{FL}|} \times 100 \right\}$$

$$OC = OB \cos \delta$$



$$OC \approx OB.$$

$$OC = OA + AD + DC$$


$$= OA + AD + EF$$

$$V_{NL} = V_{FL} + AEC \cos \theta + EBS \sin \theta$$
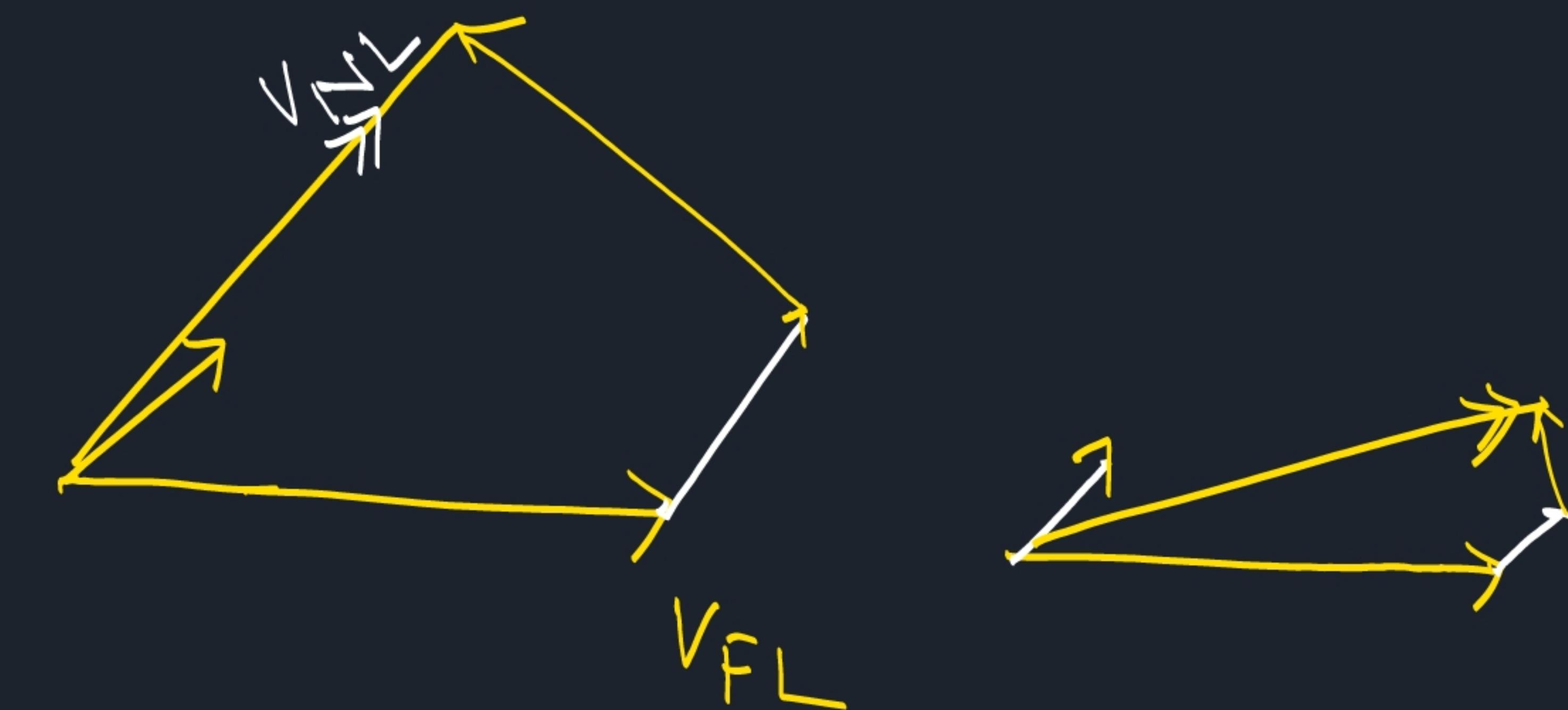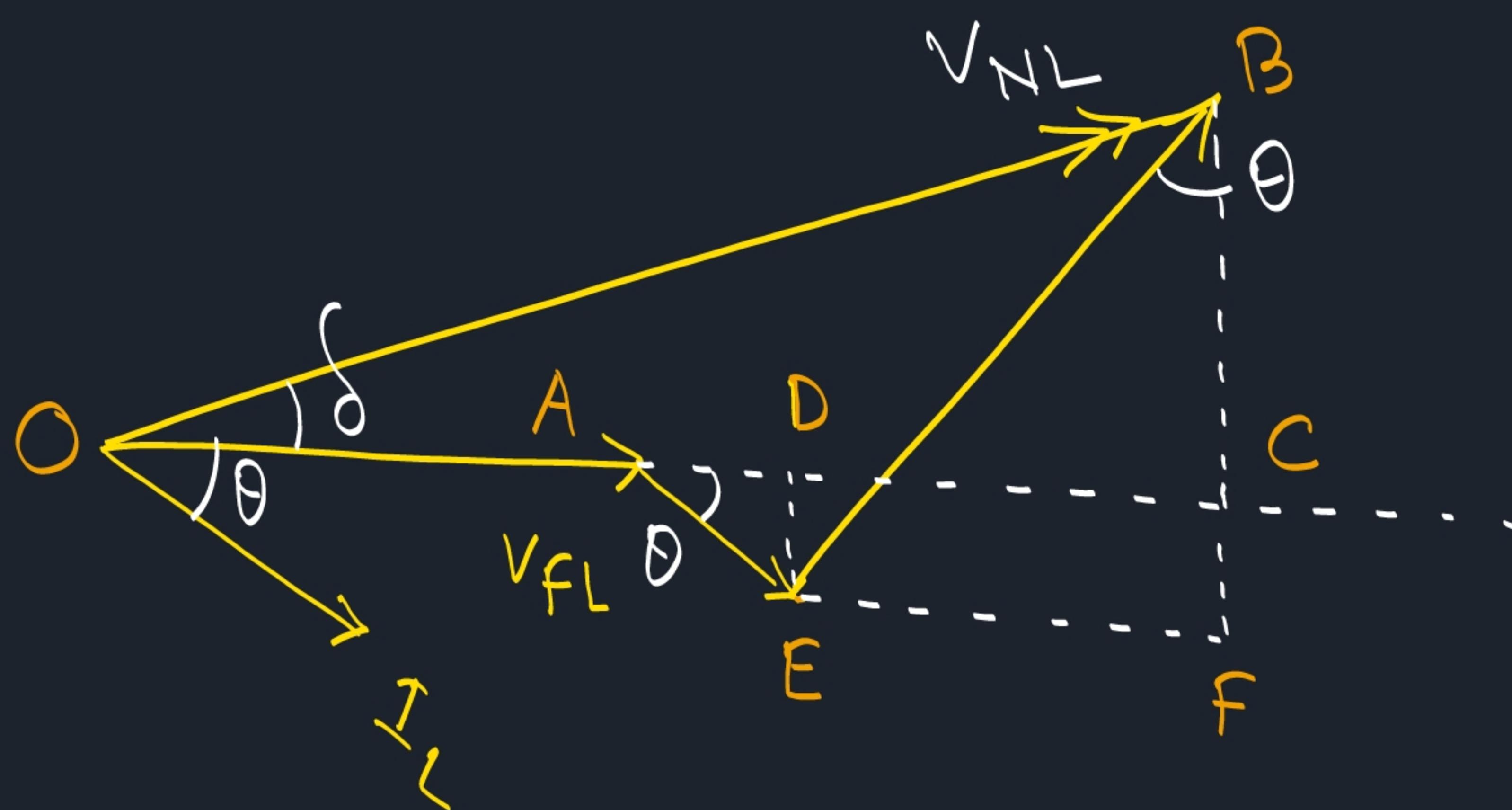
$$= V_{FL} + I_L R_{req} \cos \theta + I_L X_{req} \sin \theta$$



$$\therefore R_{eq} = \frac{|I_L| (R_{eq} \cos \theta \pm X_{eq} \sin \theta)}{|V_{FL}|}$$

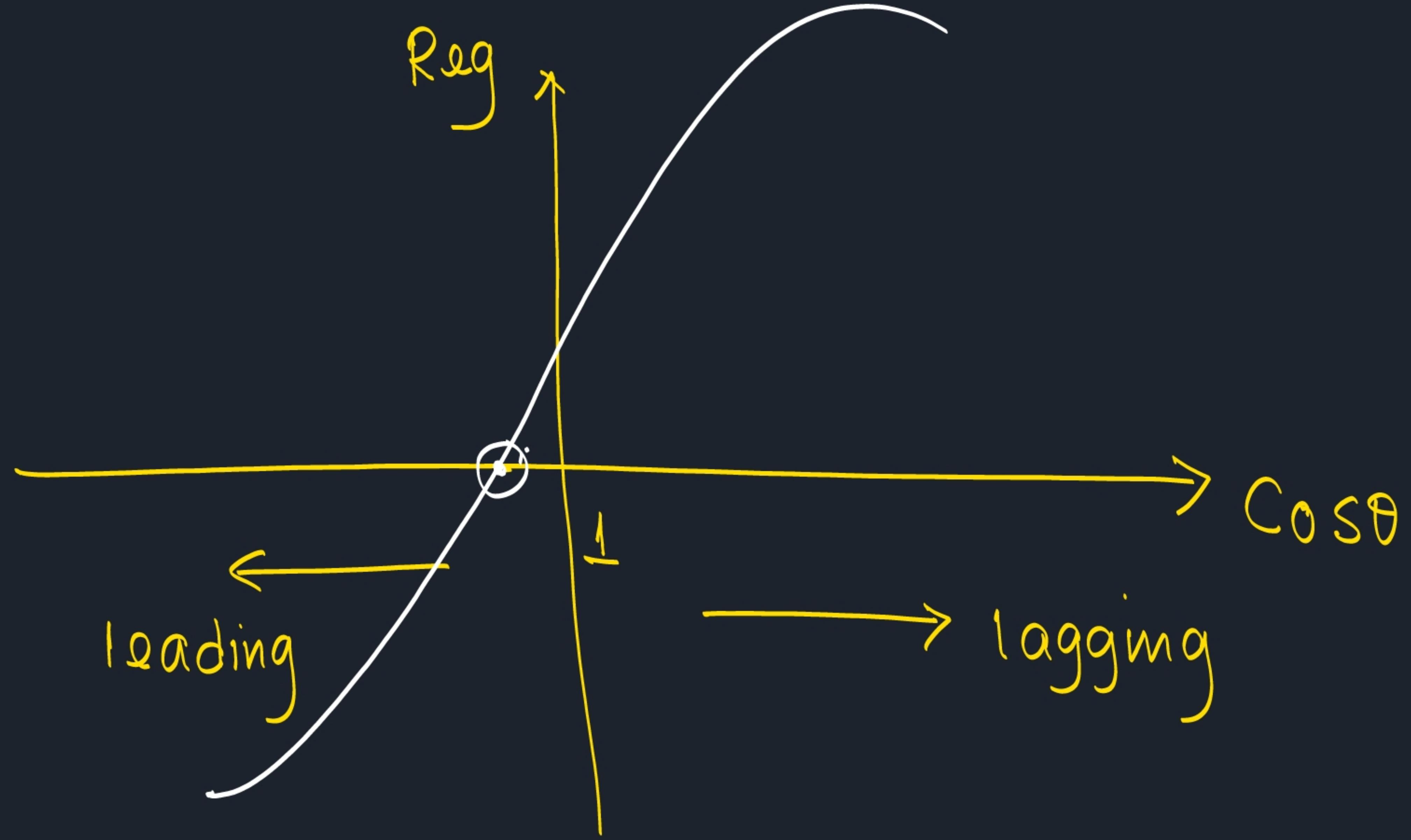

$$\underline{\underline{\text{Max } VR}} \\ R = k \cdot (R_{eq} \cos \theta + X_{eq} \sin \theta)$$

$$\frac{dR}{d\theta} = k (R_{eq} \sin \theta + X_{eq} \cos \theta) = 0$$

$$R_{eq} \sin \theta = X_{eq} \cos \theta$$

$$\tan \theta = \frac{X_{eq}}{R_{eq}} \quad \theta = \tan^{-1} \left(\frac{X_{eq}}{R_{eq}} \right)$$

$$\underline{\underline{\text{Zero VR}}}$$

$$R = k (R_{eq} \cos \theta - X_{eq} \sin \theta) = 0$$

$$\tan \theta = \frac{R_{eq}}{X_{eq}} \quad \theta = \tan^{-1} \left(\frac{R_{eq}}{X_{eq}} \right)$$

efficiency :-


$$\text{Eff} = \frac{\text{O/P Power}}{\text{I/P Power}} \times 100.$$

$$= \frac{\text{O/P Power}}{\text{O/P Power} + \text{losses}}$$

Core loss
(P_{core})

Cu loss.
(P_{cu})

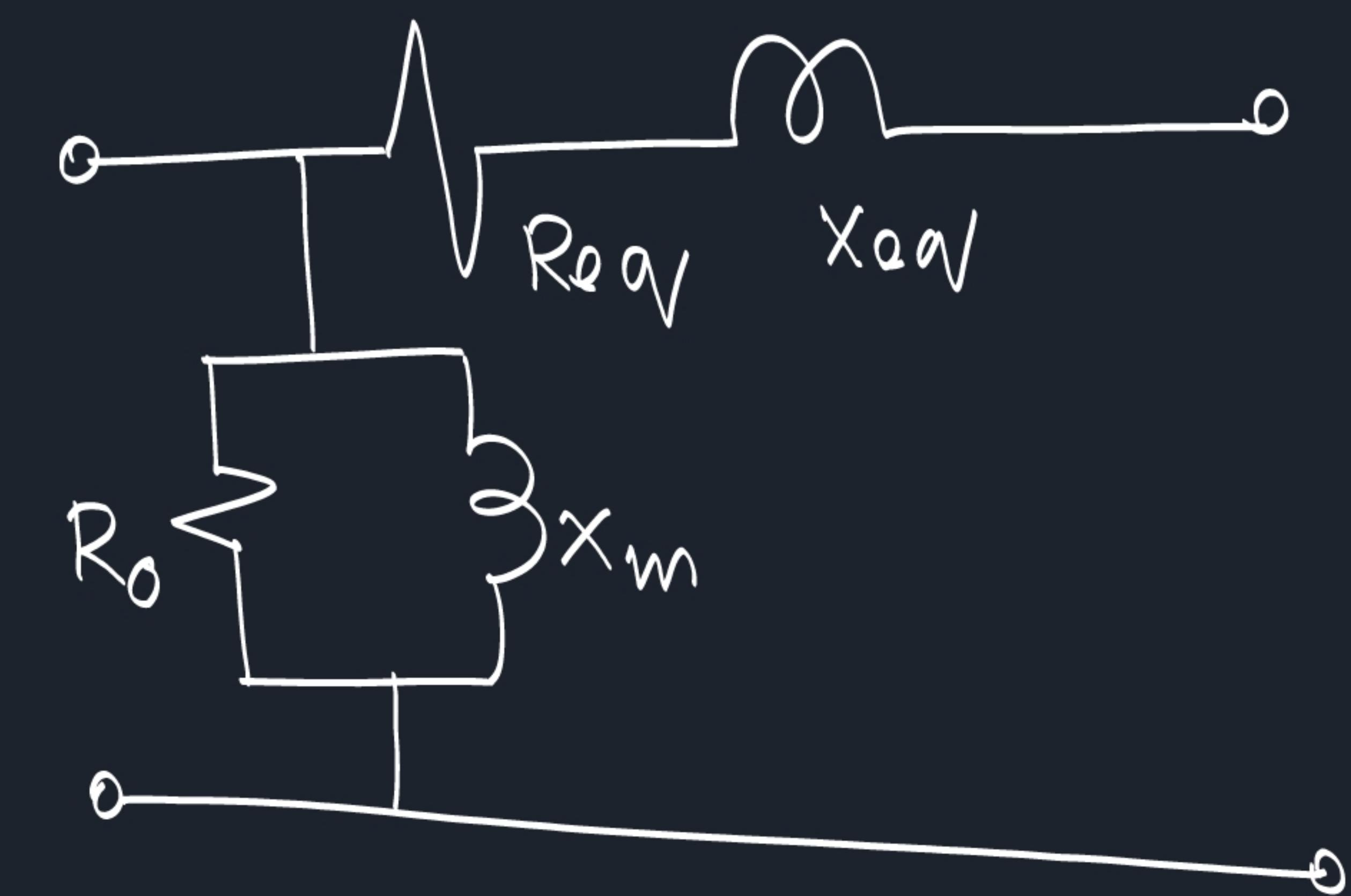Wattmeter Reading (OC Test) → Rated Power
,, „ (SC Test) → Rated Power



$$\text{eff} = \frac{\text{O/P Power}}{\text{O/P Power} + P_{core} + P_{cu}}$$

$$K = \frac{\text{Actual Current}}{\text{Rated Current}}$$

$$(P_{cu})_{\text{any load}} = \kappa^2 \cdot (P_{cu})$$

$$\eta_{eff} = \frac{P_{out}}{P_{out} + P_{core} + K^2 P_{cu}} = \frac{K S \cos\theta}{K S \cos\theta + P_{core} + K^2 P_{cu}}$$

$$\frac{d(\eta_{eff})}{dK} = 0$$

find the value of K

For a T/F

I know the VA rating

$VI \cos\theta$

$$= S \cos\theta$$



VARating of T/F

$$\eta_{eff} = f(K, \cos\theta)$$

Case-1 \Rightarrow when K changes & $\cos\theta$ fixed.


Case-2 \Rightarrow when $\cos\theta$ changes & K is fixed.

$$K = \sqrt{\frac{P_{core}}{P_{cu}}}$$

$$-\frac{P_{core}}{K^2} + P_{cu} = 0$$

$$K^2 = \frac{P_{core}}{P_{cu}}$$
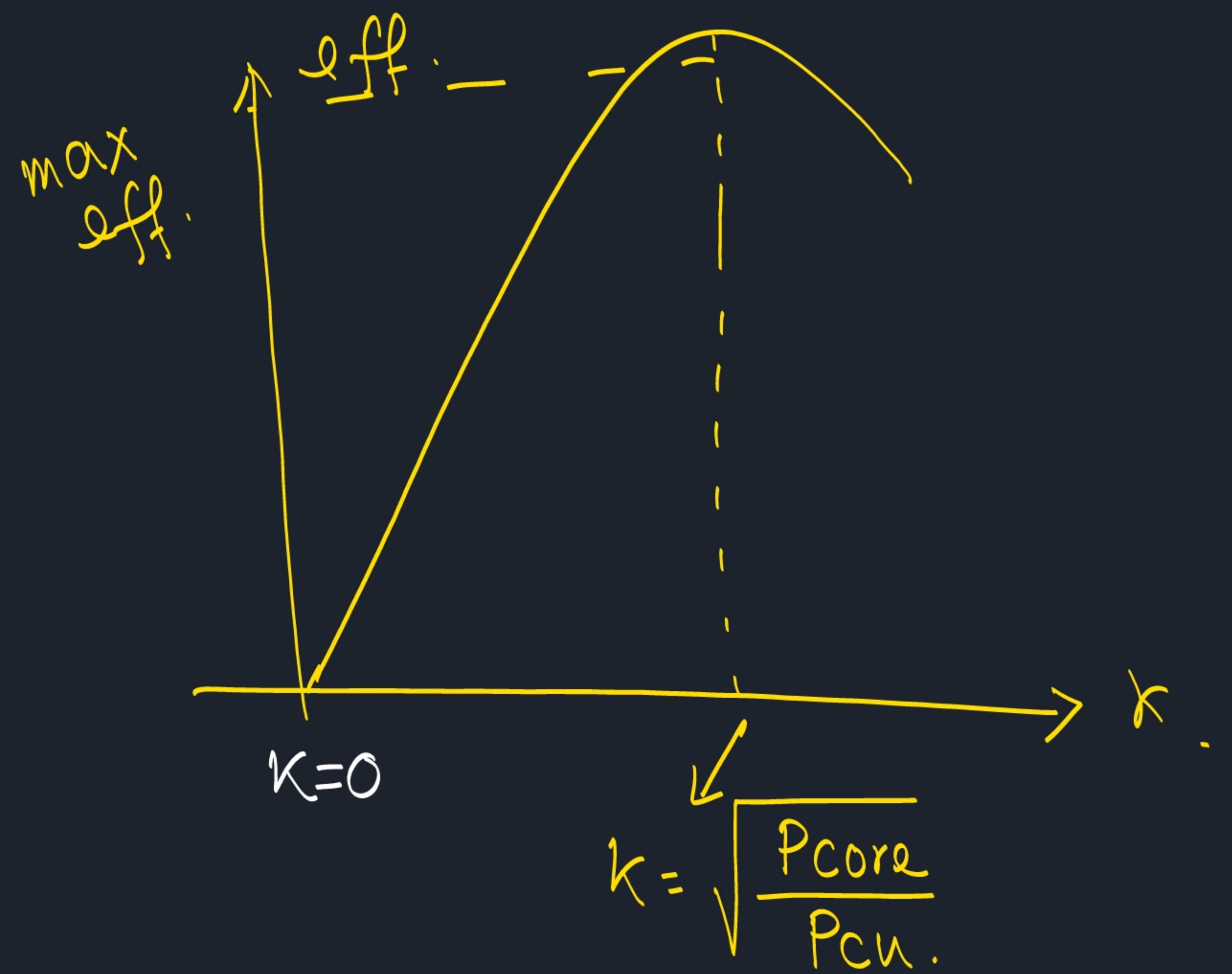
$$= \frac{S \cos\theta}{S \cos\theta + \frac{P_{core}}{K} + K P_{cu}}$$



$$K = \sqrt{\frac{P_{core}}{P_{cu}}}.$$