

Total emf induced in the DC M/c is

$$e = \frac{P \Phi N}{60} \times \frac{Z}{A}$$

There are two type of winding

i) Lap winding $\Rightarrow A = \text{no. of parallel paths}$
 $= P \text{ (poles)}$

ii) wave winding $\Rightarrow A = 2 \text{ (always)}$

⊙ PROBLEM:-

4 Pole DC Generator

Wave Winding

51 slots & each slot contains 20 conductors

Flux per pole is 7.0 mwb

Generator is driven at 1500 rpm.

Ans:-

$$E_g = \frac{\phi Z N}{60} \cdot \left(\frac{P}{A}\right)$$

$$Z = ?$$

$$\phi = 07.0 \text{ mwb}$$


$$A = ?$$

$$E_g = ?$$


$$P = 4$$

$$N = 1500 \text{ RPM}$$


Different types of Dc Generators :-

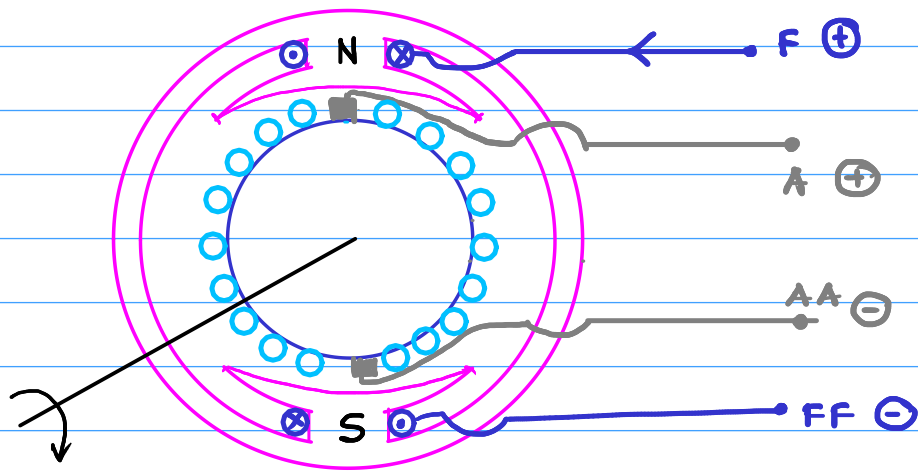

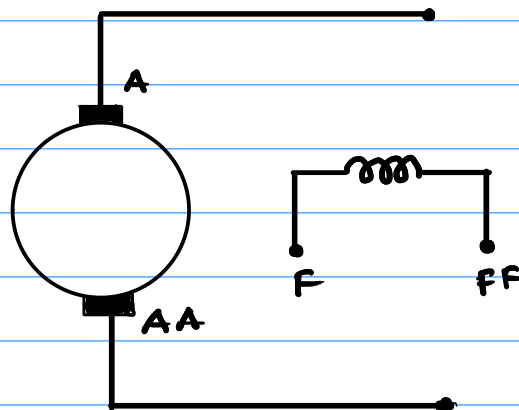Symbolically the generator can be represented by



⇓

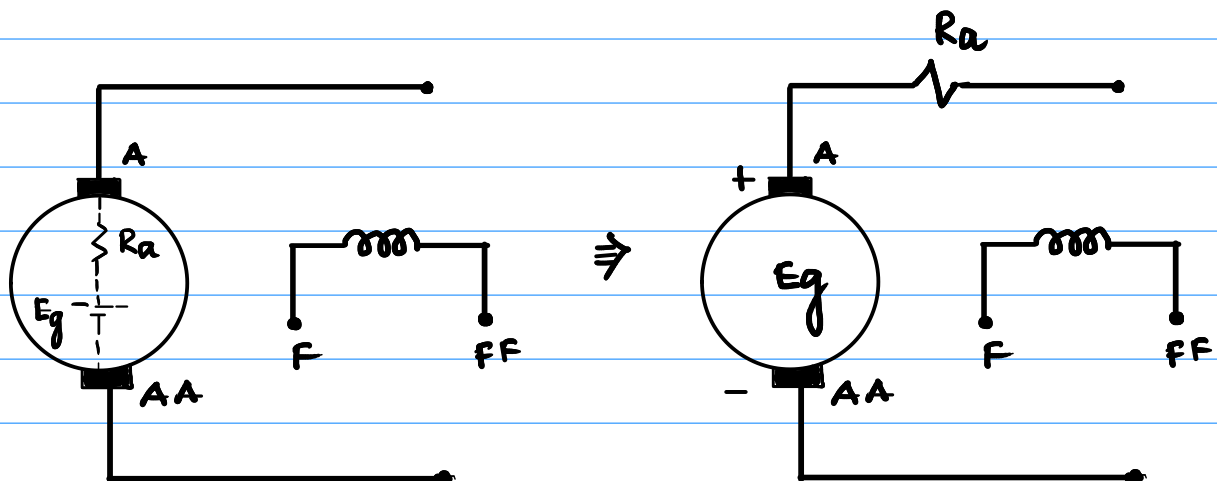

Depending on the Connection of the field coil to the armature different DC generators are possible

- i) Separately excited DC generator
- ii) Shunt excited DC generator
- iii) Series excited DC generator.


● Separately excited DC Gen :-

$$V_f = I_f R_f$$

$$V_t = E_g - I_a R_a - 2V_{\text{brush}}$$

$$E_g = \frac{\Phi Z N}{60} \left(\frac{P}{A} \right)$$

$$I_a = I_L$$

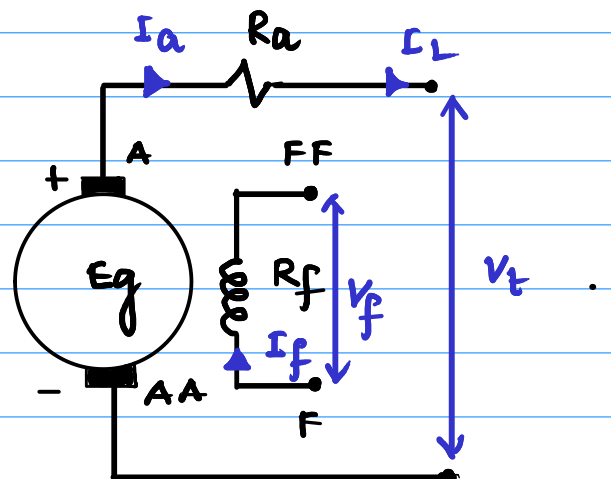

Electrical power generated $P_g = E_g I_a$

$$(P_{cu})_a = I_a^2 R_a = I_L^2 R_a$$


$$(P_{cu})_f = I_f^2 R_f = \frac{V_f^2}{R_f}$$

$$\omega = \frac{2\pi N}{60} \text{ rad/sec}$$

$$N = \text{Speed in RPM}$$

$$(P_{\text{loss}})_b = 2V_{\text{brush}} I_a$$

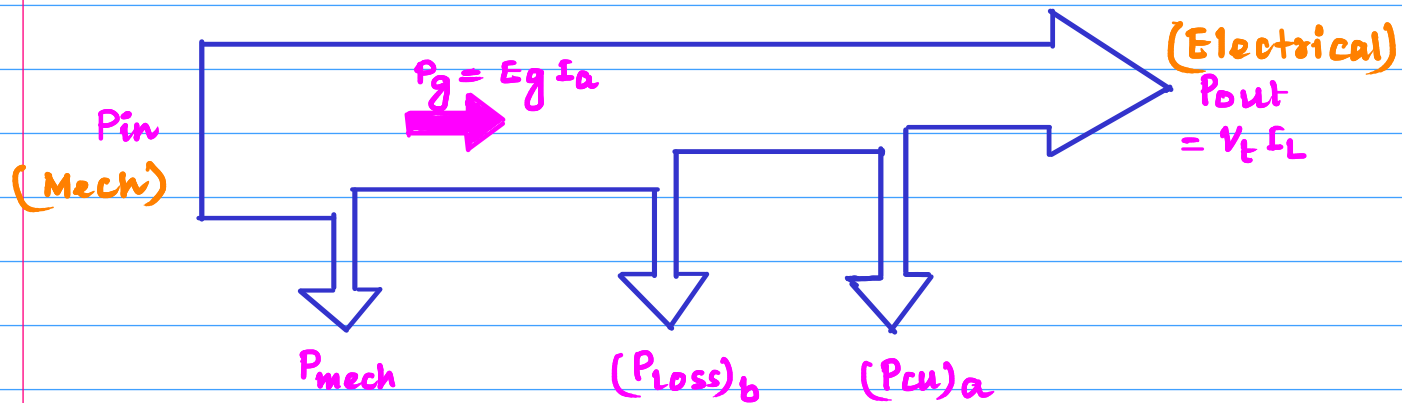$P_{\text{mech}} = \text{Friction and windage loss}$



Power flow diagram of separately excited DC Generator.

Efficiency for DC generator

$$= \frac{P_{out}}{P_{in}} \times 100$$


$$= \frac{P_{out}}{P_{out} + (P_{cu})_a + (P_{loss})_b + P_{mech}} \times 100 \%$$

Shunt Excited DC Generator:-

$$V_t = E_g - I_a R_a - 2V_{brush}$$

$$E_g = \frac{\Phi Z N (P)}{60 (A)}$$

$$I_a = I_f + I_L$$

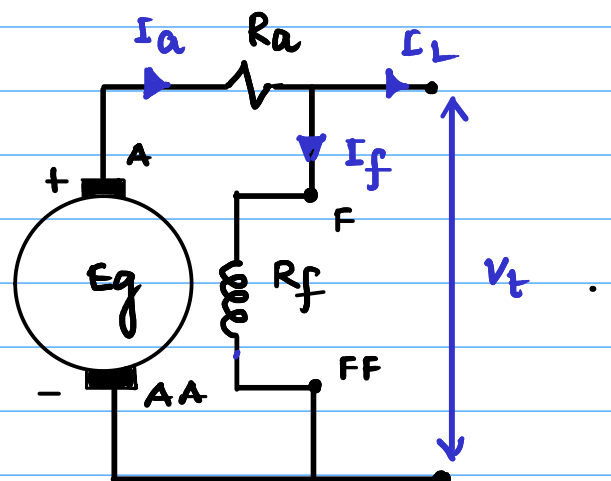

$$\text{Electric Power Generated} = P_g = E_g I_a$$

$$(P_{cu})_a = I_a^2 R_a$$


$$(P_{cu})_f = I_f^2 R_f = \frac{V_t^2}{R_f}$$

$$\omega = \frac{2\pi N}{60} \text{ rad/sec}$$

$N = \text{Speed in RPM}$

$$(P_{loss})_b = 2V_{brush} I_a$$

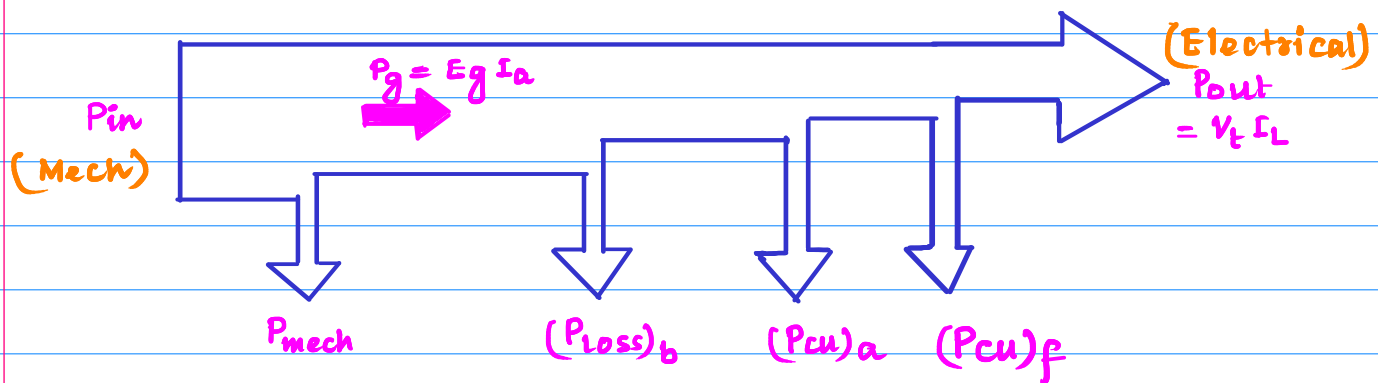$P_{mech} = \text{Friction and windage loss}$




Power flow diagram of Shunt excited DC Generator.

Efficiency for DC generator

$$= \frac{P_{out}}{P_{in}} \times 100$$

$$= \frac{P_{out} \times 100}{P_{out} + (P_{cu})_a + (P_{loss})_b + P_{mech} + (P_{cu})_f} \%$$

● Series Excited DC Generator:-

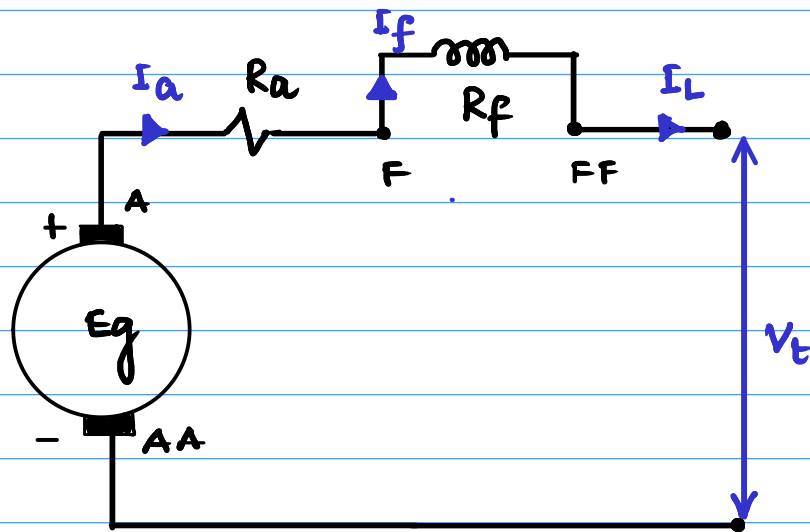

$$V_t = E_g - I_a (R_a + R_f) - 2V_{\text{brush}}$$

$$E_g = \frac{\Phi Z N}{60} \left(\frac{P}{A} \right)$$

$$I_a = I_f = I_L$$

$$\text{Electric Power Generated} = P_g = E_g I_a$$

$$(P_{cu})_a = I_a^2 R_a$$


$$(P_{cu})_f = I_f^2 R_f = I_a^2 R_f$$

$$(P_{\text{loss}})_b = 2V_{\text{brush}} I_a$$

$$P_{\text{mech}} = \text{Friction and windage loss}$$

$$\omega = \frac{2\pi N}{60} \text{ rad/sec}$$

$$N = \text{Speed in RPM}$$

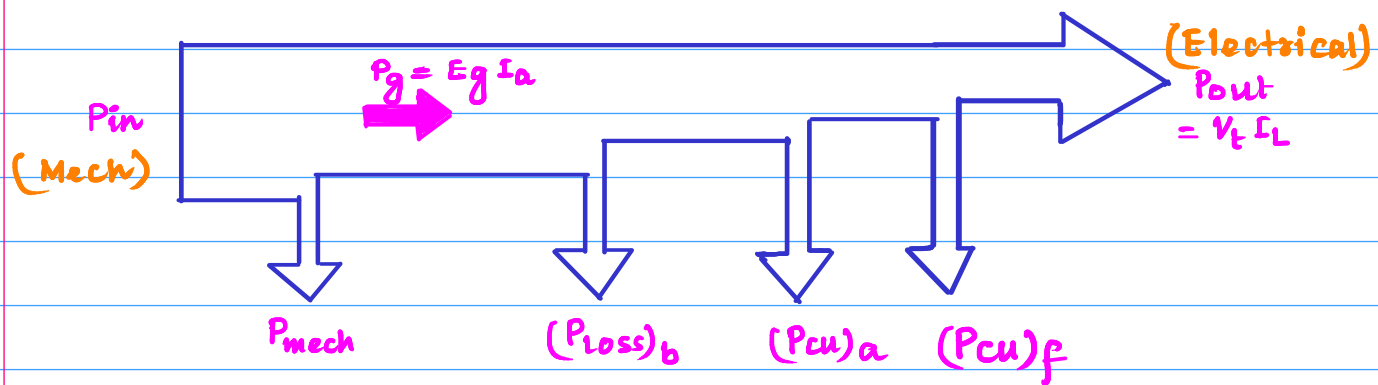

Power flow diagram of Series excited
DC Generator.

Efficiency for DC generator

$$= \frac{P_{out}}{P_{in}} \times 100$$

$$= \frac{P_{out} \times 100}{P_{out} + (P_{cu})_a + (P_{loss})_b + P_{mech} + (P_{cu})_f} \%$$

PROBLEM:-

A shunt generator delivers 450 A at 230 V

$$R_f = 50 \Omega \quad R_a = 0.3 \Omega$$

$$P_{\text{mech}} = 2000 \text{ watt}$$

Soln

$$V_t = ?$$

$$I_L = ?$$

$$I_f = ?$$

$$I_a = I_L + I_f = ?$$


$$E_g = V_t + I_a R_a = ?$$

$$P_g = E_b I_a = ?$$

$$P_{\text{in}} = P_g + P_{\text{mech}} = ?$$

$$P_{\text{out}} = ?$$
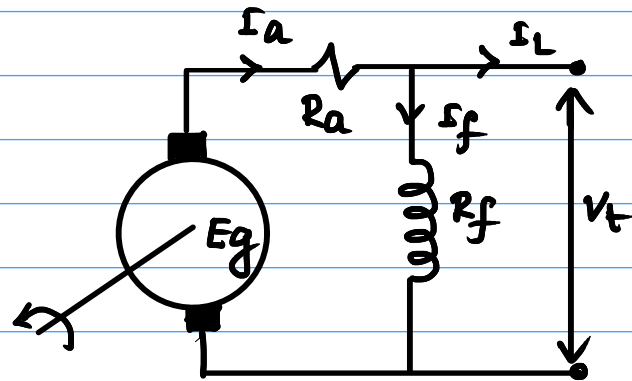
$$\text{efficiency } \eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100 = ?$$



$$(P_{\text{cu}})_f = ?$$

$$(P_{\text{cu}})_a = ?$$

Problem :-

Separately excited DC generator delivers 150 A to a const. resistive load at 400 V and 1000 rpm.

$$R_a = 0.12 \Omega$$

Current reduced to 100 A.

Determine Speed.

$$[\text{Total Brush contact Drop} = 2 \text{ V}]$$

Soln

$$E_g = V_t + I_a R_a = ?$$

Load Resistance is constant

$$R_L = ?$$

$$V_t' = R_L \times I_L' = ?$$

$$E_g' = V_t' + I_a' R_a = ?$$

$$\frac{E_g}{E_g'} = \frac{N_1}{N_2} = \frac{1000}{N_2}$$

$$N_2 = ?$$


● Separately excited Dc Motor:-

$$V_f = I_f R_f$$

$$V_S = E_b + I_a R_a + 2V_{brush}$$

$$E_b = \frac{\Phi Z N}{60} \left(\frac{P}{A} \right)$$

$$I_a = I_S$$

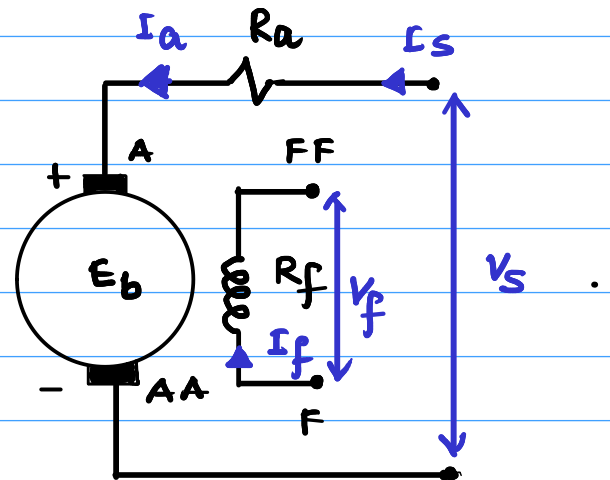

$$\text{Gross mechanical power developed} = P_{gross} = E_b I_a$$

$$(P_{cu})_a = I_a^2 R_a = I_L^2 R_a$$

$$(P_{cu})_f = I_f^2 R_f = \frac{V_f^2}{R_f}$$

$$(P_{loss})_b = 2V_{brush} I_a$$

$$\omega = \frac{2\pi N}{60} \text{ rad/sec}$$

$$N = \text{Speed in RPM}$$


$$P_{mech} = \text{Friction and windage loss}$$

$$\text{Shaft power developed} \Rightarrow P_{shaft} = P_{gross} - P_{mech}$$

$$\tau_{gross} = \frac{P_{gross}}{\omega}$$

$$\tau_{shaft} = \frac{P_{shaft}}{\omega}$$
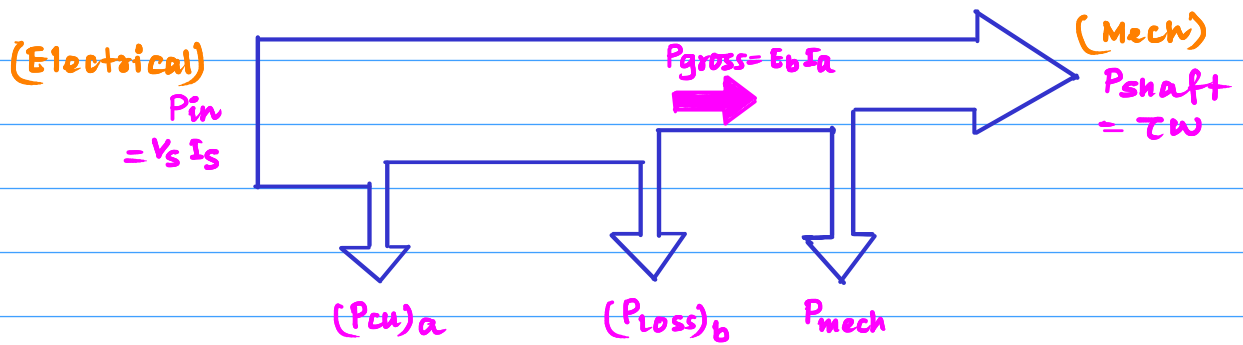
$$\omega = \frac{2\pi N}{60} \text{ rad/sec.}$$



Power flow diagram of separately excited DC Motor

Efficiency for DC Motor

$$= \frac{P_{out}}{P_{in}} \times 100$$


$$= \frac{P_{out}}{P_{out} + (P_{cu})_a + (P_{loss})_b + P_{mech}} \times 100 \%$$

Shunt DC Motor :-

$$V_s = E_b + I_a R_a + 2V_{brush}$$

$$E_b = \frac{\Phi Z N (P)}{60 (A)}$$

$$I_s = I_f + I_a$$

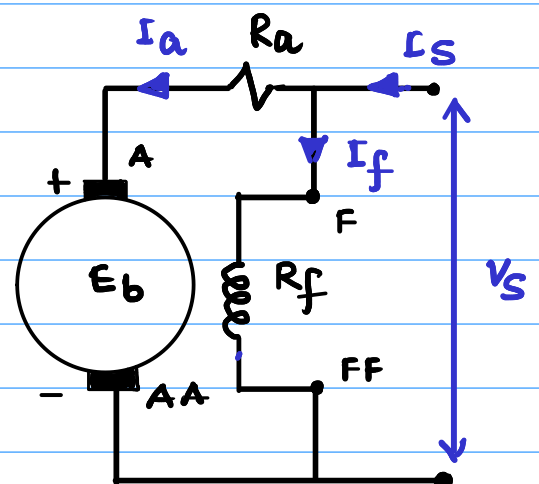


Gross Mechanical Power Developed $\Rightarrow P_{gross} = E_b I_a$

Shaft power developed $\Rightarrow P_{\text{shaft}} = P_{\text{gross}} - P_{\text{mech}}$

$$\tau_{\text{gross}} = \frac{P_{\text{gross}}}{\omega}$$

$$\tau_{\text{shaft}} = \frac{P_{\text{shaft}}}{\omega}$$
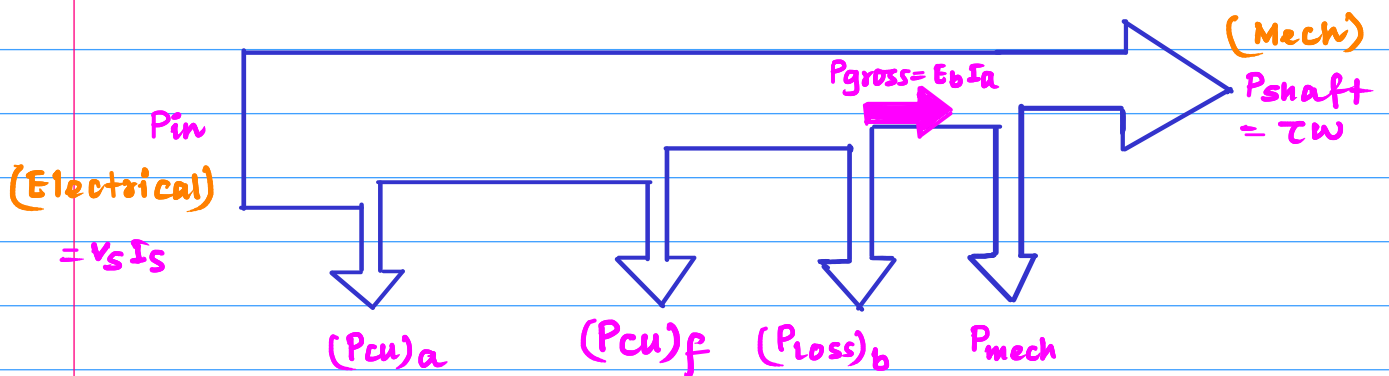
$$\omega = \frac{2\pi N}{60} \text{ rad/sec.}$$



Power flow diagram of DC shunt motor

Efficiency for DC Motor

$$= \frac{P_{\text{out}}}{P_{\text{in}}} \times 100$$

$$= \frac{P_{\text{out}}}{P_{\text{out}} + (P_{\text{cu}})_a + (P_{\text{loss}})_b + (P_{\text{cu}})_f + P_{\text{mech}}} \times 100 \%$$